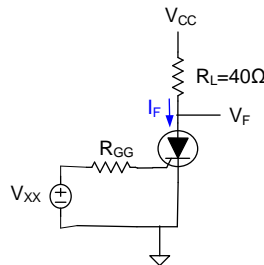


All problems are weighted equally. Characteristics for an SCR and for a Triac are appended at the end of this assignment. Use these characteristics when solving the problems involving Thyristors. Unless specified to the contrary, assume all n-channel MOS transistors have model parameters  $\mu_n C_{OX} = 350 \mu\text{A}/\text{V}^2$ ,  $V_{Tn} = 0.5\text{V}$ , and  $\lambda=0$ , all p-channel transistors have model parameters  $\mu_p C_{OX} = 70 \mu\text{A}/\text{V}^2$ ,  $V_{Tp} = -0.5\text{V}$ , and  $\lambda=0$ , and all JFET devices are from a process with  $I_{DSSn0} = 100 \mu\text{A}$ ,  $I_{DSSp0} = 30 \mu\text{A}$ ,  $V_{Pp} = 1\text{V}$ ,  $V_{Pn} = -1\text{V}$ , and  $\lambda=0$ .


**Problem 1** A circuit using an SCR that is rated at current levels of 10A is shown below. Relevant parameters from the datasheet for this device are appended at the end of this assignment. Assume the voltage  $V_{CC}$  is fixed at 50V and that the SCR is initially off.

- If  $V_{XX}$  is increased to 12V to turn on the SCR, what is the maximum value of  $R_{GG}$  that can be used if the SCR must turn on for  $0\text{C} < T < 80\text{C}$ .
- What will be the static power dissipation in the Anode when it is ON?
- What will be the static power dissipation in the Gate if the gate signal  $V_{XX}$  remains at 12V and the value determined in part a) is used for  $R_{GG}$ ?




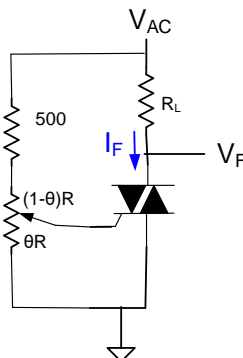**Problem 2** Assume the potentiometer in the following circuit has a full range value of  $R=500\Omega$ , that  $R_L=20\Omega$  and  $V_{AC}=60\sin(2\pi 60t)$ . Assume the device is operating at a temperature of 25C and that it is characterized by the parameters given at the end of this assignment.


- Determine  $V_F(t)$  if  $\theta=0.1$
- Determine the average power dissipation in the Triac for the value of  $\theta$  given in part a)
- Which quadrant or quadrants are used to trigger the triac in this circuit?



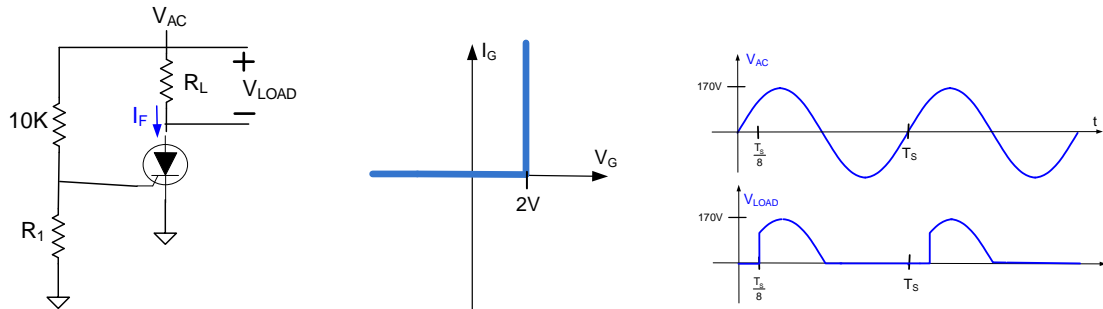**Problem 3** Consider the following circuit. The waveforms  $V_{AC}$  is the 60Hz line voltage. Assume the SCR has a gate trigger voltage of 2V and that the relationship between the gate current and the gate voltage of the SCR is as shown on the  $I_G:V_G$  plot on the right. Size the resistor  $R_1$  so that the SCR turns on at  $T_S/8$ ,  $T_S + T_S/8$ ,  $2T_S + T_S/8$ , ... as shown below for two periods of the  $V_{LOAD}$  waveform. The time  $T_S$  is the period of the 60 Hz AC line voltage.




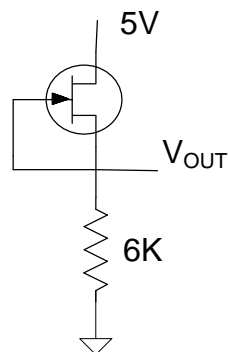**Problem 4** Assume the JFET in the following circuit has parameters  $I_{DSS}=100\mu A$  and  $V_P=-1V$ . Determine the output voltage.




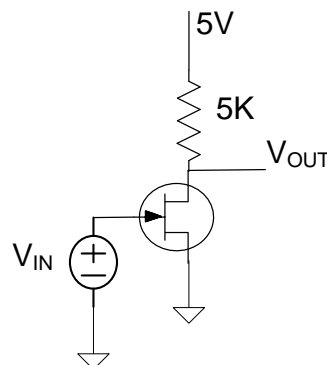**Problem 5** Assume the JFET in the following circuit has parameters  $I_{DSS}=100\mu A$  and  $V_P=-1V$ .

- If the input voltage is a 1KHz square wave that varies between +25mV and -25mV, obtain the output waveform
- What is the maximum value of  $V_{IN}$  that can be applied to this circuit if the JFET is to operate normally (that is, the pn-junctions do not conduct significant current)



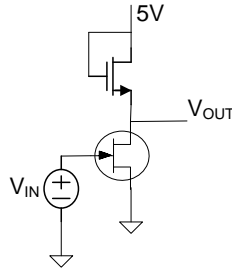**Problem 6** Assume the JFET in the following circuit has parameters  $I_{DSS}=100\mu A$  and  $V_P=-1V$  and the MOSFET is in a process that was characterized in the introduction to this HW assignment. If the length of the MOSFET is  $8\mu$ , determine the width of the MOSFET so that the output voltage of the following circuit is  $3V$  when  $V_{IN}=-0.5V$ .



**Problem 7** Assume the drain current of a p-channel JFET is given by the expression


$$I_D = \begin{cases} 0 & V_{GS} > V_P \\ -\frac{2I_{DSSp0}W}{V_P^2L} \left( V_{GS} - V_P - \frac{V_{DS}}{2} \right) V_{DS} & -0.3 < V_{GS} < V_P \quad V_{GS} + 0.3 > V_{DS} > V_{GS} - V_P \\ -\frac{I_{DSSp0}W}{L} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 (1 - \lambda V_{DS}) & -0.3 < V_{GS} < V_P \quad V_{DS} < V_{GS} - V_P \end{cases}$$

where the parameter  $I_{DSSp0}$  is related to the parameter  $I_{DSSp}$  that is often given in the model for a JFET by the expression

$$I_{DSSp} = \frac{W}{L} I_{DSSp0}$$

Develop a small-signal model of the JFET when operating in the saturation region.

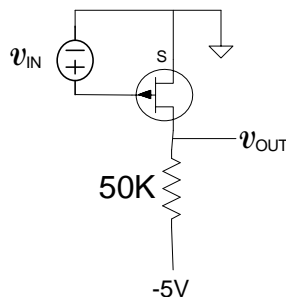**Problem 8** Using the small-signal model of the JFET developed in the previous problem and the model parameters given at the top of this assignment, determine the operating point and small-signal voltage gain of the following circuit if  $W=10\mu m$  and  $L=15\mu m$ .



**Problem 9** Design a light dimmer circuit that will control a  $100W$   $120V_{AC}$  incandescent lamp where the lamp is completely on when a dc control voltage is  $5V$ , completely off when the dc control voltage is  $0V$ , and that continuously varies in intensity from completely off to completely on as the control voltage is varied between  $0V$  and  $5V$ . You may assume Thyristors with the specifications given below are available for your design.

## SCR Specifications:

$I_{DRM}$  and  $I_{RRM}$  — Peak off-state current at  $V_{DRM}$  and  $V_{RRM}$

$I_{GT}$  — DC gate trigger current  $V_D = 6\text{ V dc}$ ;  $R_L = 100\ \Omega$

$I_{GM}$  — Peak gate current

$I_H$  — DC holding current; initial on-state current = 20 mA

$I_T$  — Maximum on-state current

$V_{DRM}$  and  $V_{RRM}$  — Repetitive peak off-state forward and reverse voltage


$V_{GRM}$  — Peak reverse gate voltage

$V_{GT}$  — DC gate trigger voltage;  $V_D = 6\text{ V dc}$ ;  $R_L = 100\ \Omega$

$V_{TM}$  — Peak on-state voltage

$I_T$		$V_{DRM}$ & $V_{RRM}$	$I_{GT}$	$I_{DRM}$ & $I_{RRM}$		$V_{TM}$
Amps		Volts	$\mu\text{Amps}$	$\mu\text{Amps}$		Volts
$I_{T(RMS)}$	$I_{T(AV)}$			$T_C = 25\ ^\circ\text{C}$	$T_C = 110\ ^\circ\text{C}$	
MAX	MAX			MAX	MAX	
10	6.4	400	200	5	250	1.6

V <sub>GT</sub>			I <sub>H</sub>	I <sub>GM</sub>	V <sub>GRM</sub>	P <sub>GM</sub>
Volts			mAmps	Amps	Volts	Watts
T <sub>C</sub> = -40 °C	T <sub>C</sub> = 25 °C	T <sub>C</sub> = 110 °C				
MAX						
1	0.8	0.25	6	1	6	1

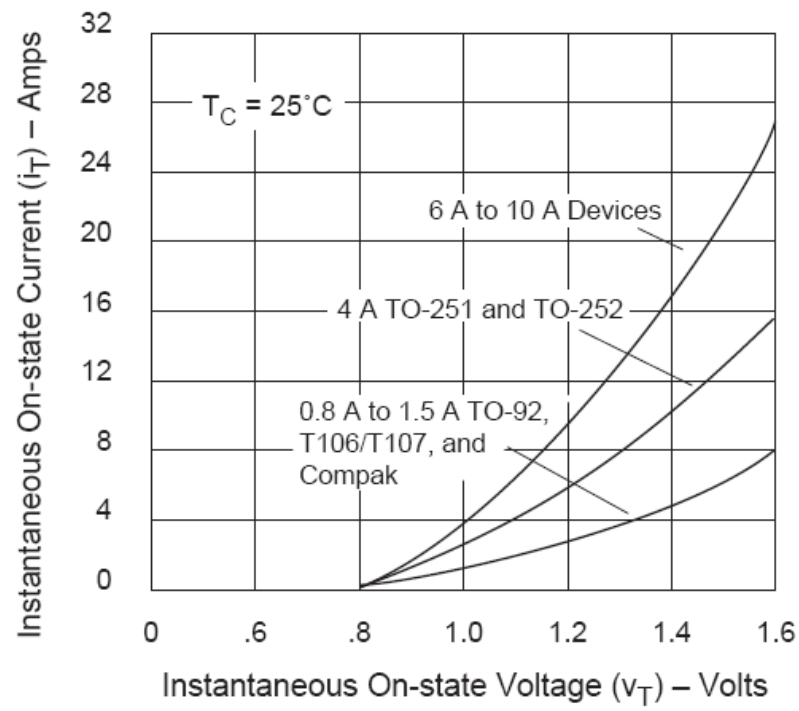

## TRIAC Specifications

$V_{DRM}$	$I_{GT}$					$I_{DRM}$		
	mAmps					mAmps		
Volts	QI	QII	QIII	QIV	QIV	$T_C = 25\text{ }^{\circ}\text{C}$	$T_C = 100\text{ }^{\circ}\text{C}$	$T_C = 125\text{ }^{\circ}\text{C}$
MIN	MAX				TYP	MAX		
400	50	50	50			0.05	0.5	2

$V_{TM}$	$V_{GT}$	$I_H$	$I_{GTM}$	$P_{GM}$	$P_{G(AV)}$
Volts	Volts				
$T_C = 25\text{ }^{\circ}\text{C}$	$T_C = 25\text{ }^{\circ}\text{C}$	mAmps	Amps	Watts	Watts
1.6	2.5	70	2	20	0.5

