

Report: **Second-order filters**

Lab work done by _____ Tejas Agarwal _____

and _____ Sean Gordon _____

Lab work date:

Report submission date:

Lab Section: E

Graded by _____


Score _____

Introduction

This lab focuses on second order filters of various types, proposing several designs for experimentation to reinforce the relationship between frequency and output. The lab goes over several types of active and inactive filters, requiring graphs of the output.

A. Active low-pass filters

Figure 1. (a) First-order low-pass. (b) Second-order low-pass.

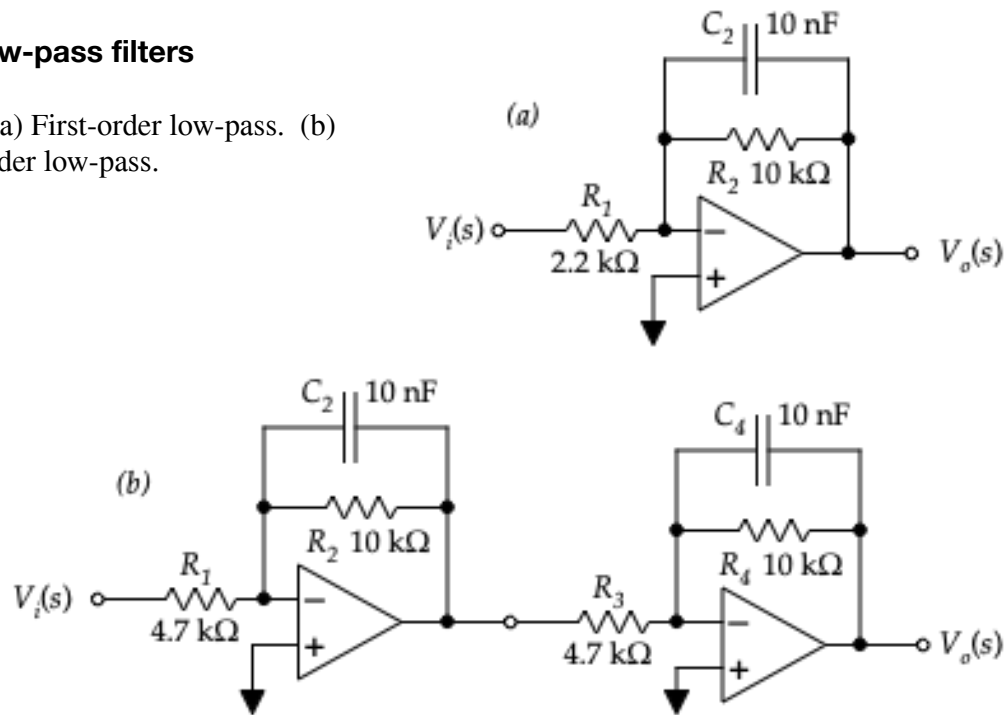



Include the calculations for expected f_c and G_o for the first-order circuit and f_o , Q_p , and G_o for the second-order circuit. Comment on how well the calculations and measurements matched.

$$f_c = 1591.6 \text{ Hz} \quad G_o = -4.54$$

$$f_o = 1591.6 \text{ Hz} \quad G_o = 20.66 \quad Q_p = .5$$

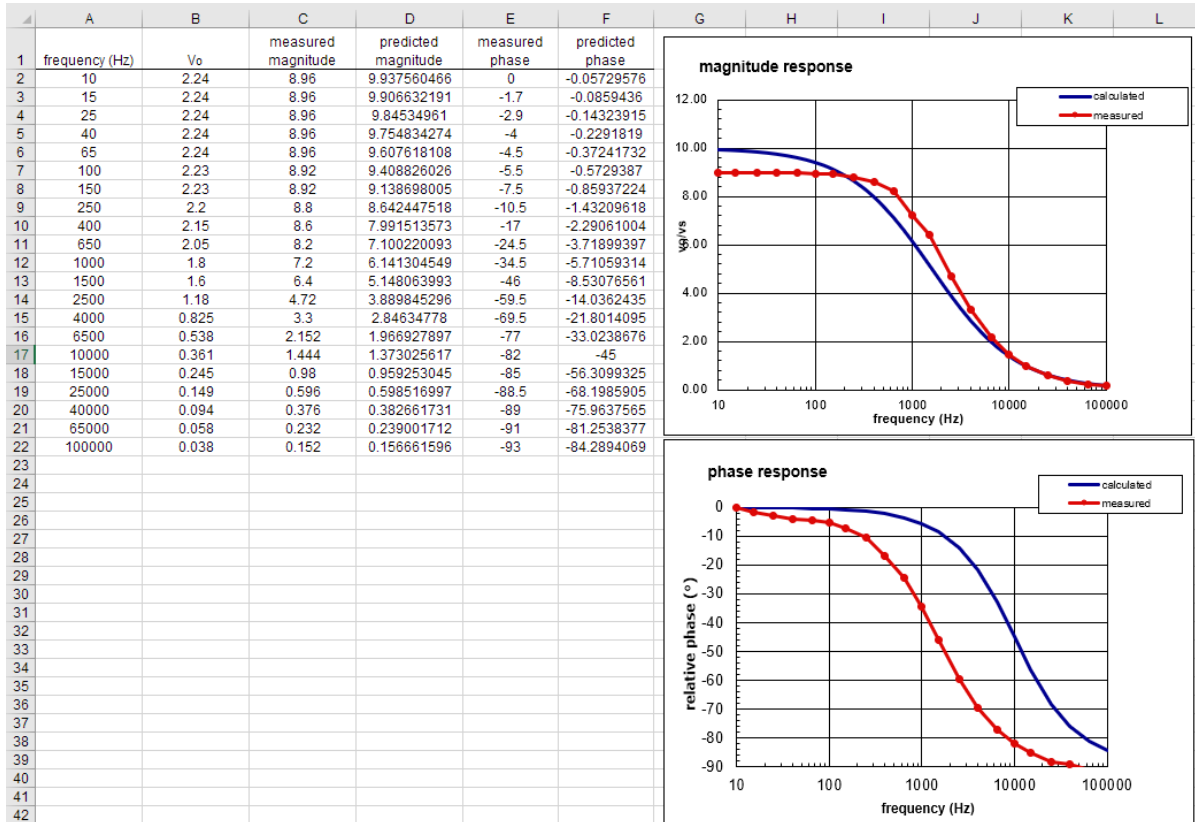Figures: Insert plots of the magnitudes versus frequency (both curves in one Bode plot) and phase angle versus frequency (also both curves on one set of axes).



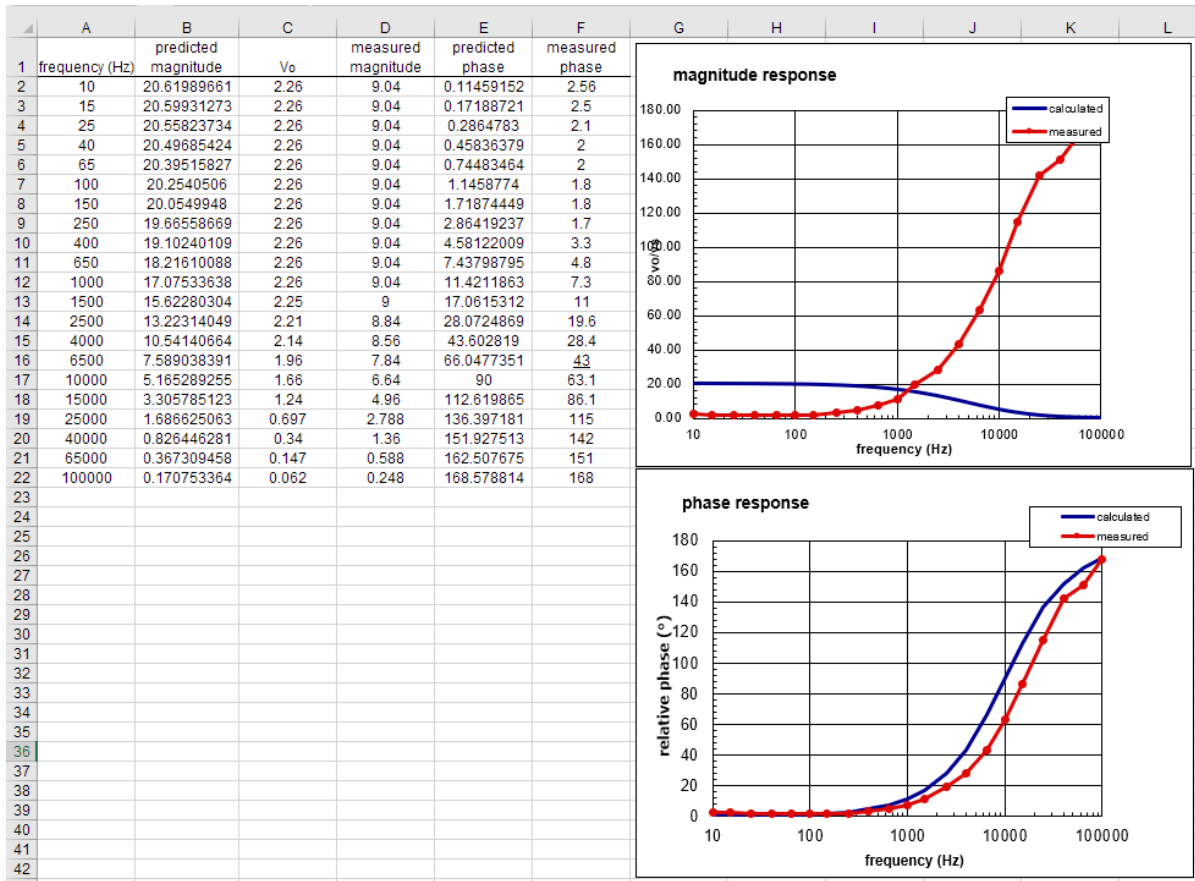

B. RLC 2nd-order filters

Include the calculations for f_o , Q_p , and G_o for the circuits. *Comment on how well the calculations and measurements matched.*

Figure 2. Low-pass.

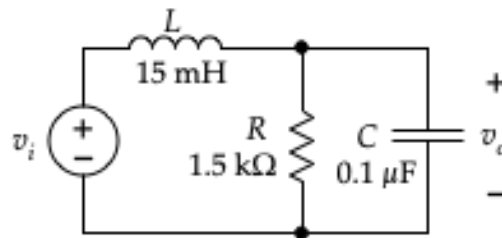


Figure 3. High-pass


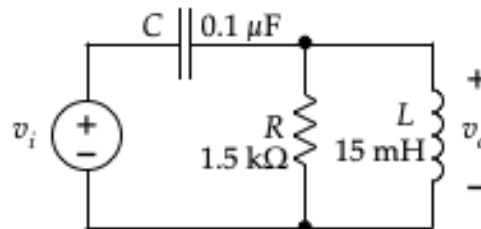


Figure 4. Band-pass

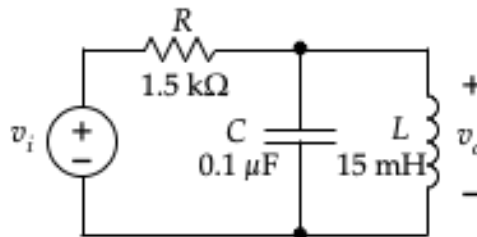


For all Circuits:

$$f_o = 4109 \text{ Hz}$$

$$Q_p = 3.87$$

$$G = 1$$

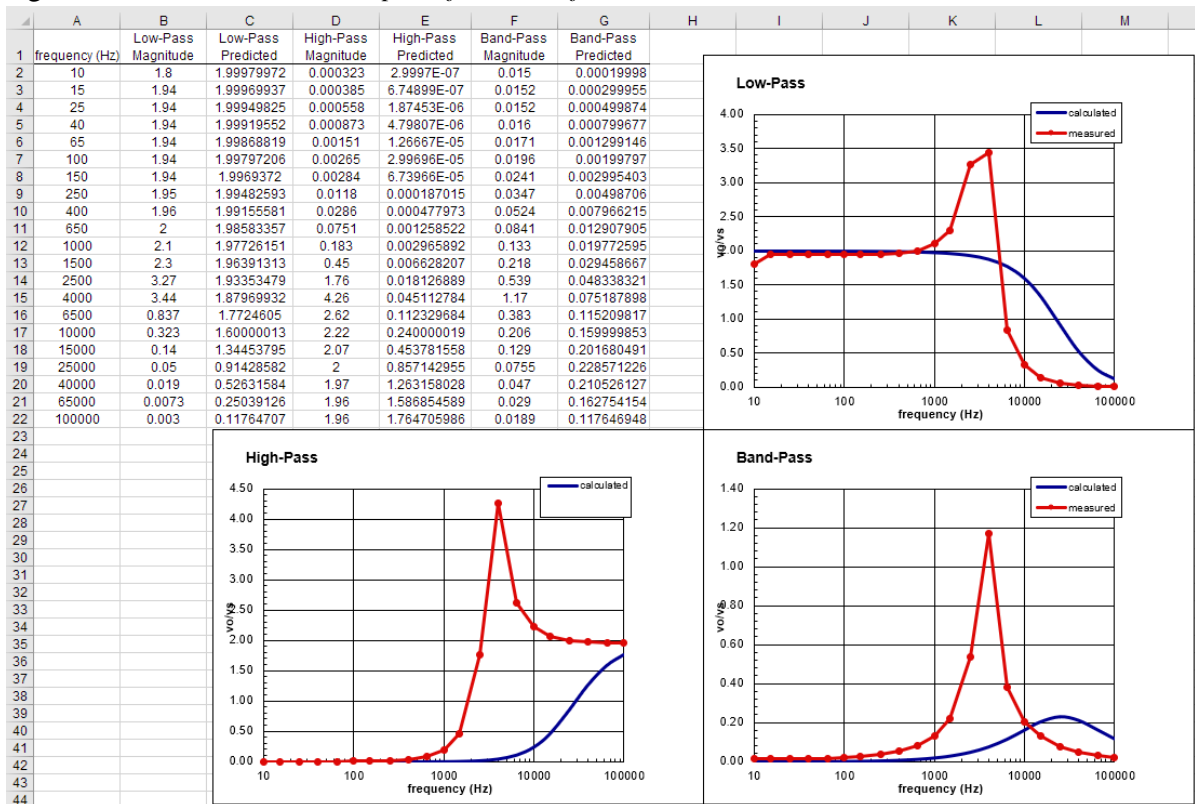Figures. Insert measured Bode plots for each of the three circuits.



C. Active Bi-quads

Include the calculations for f_o , Q_p , and G_o for each circuit. Comment on how well the calculations and measurements matched.

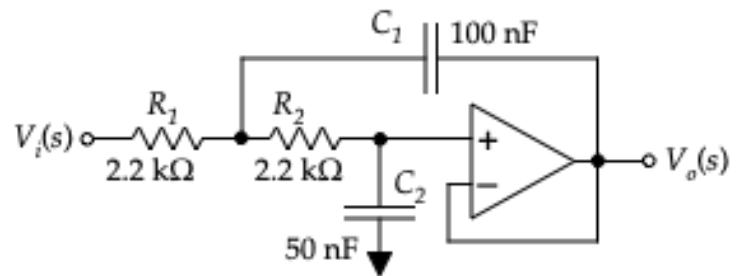


Figure 5. Sallen-Key low-pass.

Note that you can make a 50 nF capacitor using two 100-nF caps in series.

$$f_o = 723.4 \text{ Hz}$$

$$Q_p = .5$$

$$G = 1$$

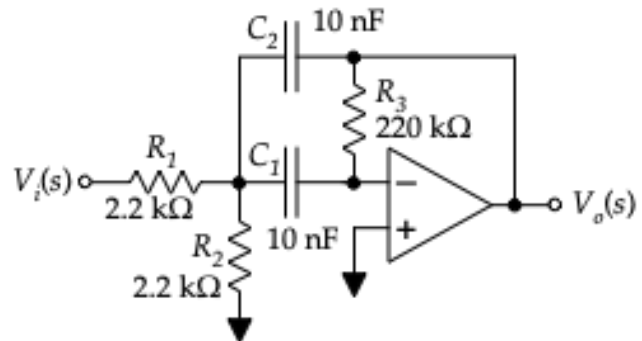


Figure 6. Delyiannis-Friend band-pass.


$$f_o = 102.3 \text{ Hz}$$

$$Q_p = .07$$


$$G = .5$$

Figures. Insert the measured Bode plots for each circuit.

Sallen-Key:

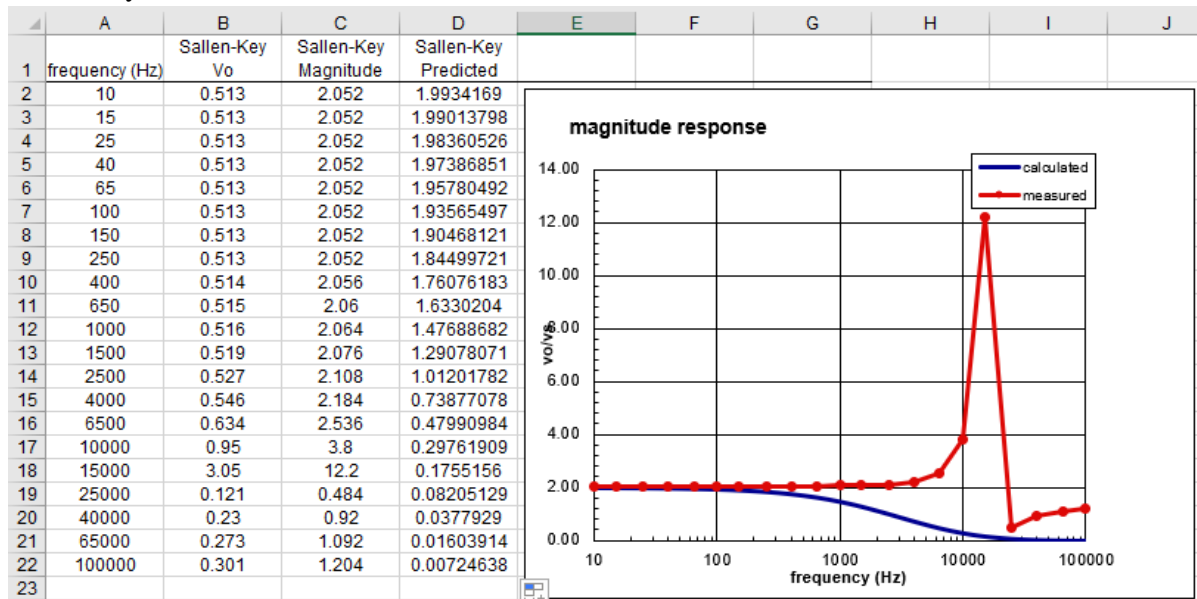

Deliyannis-Friend:

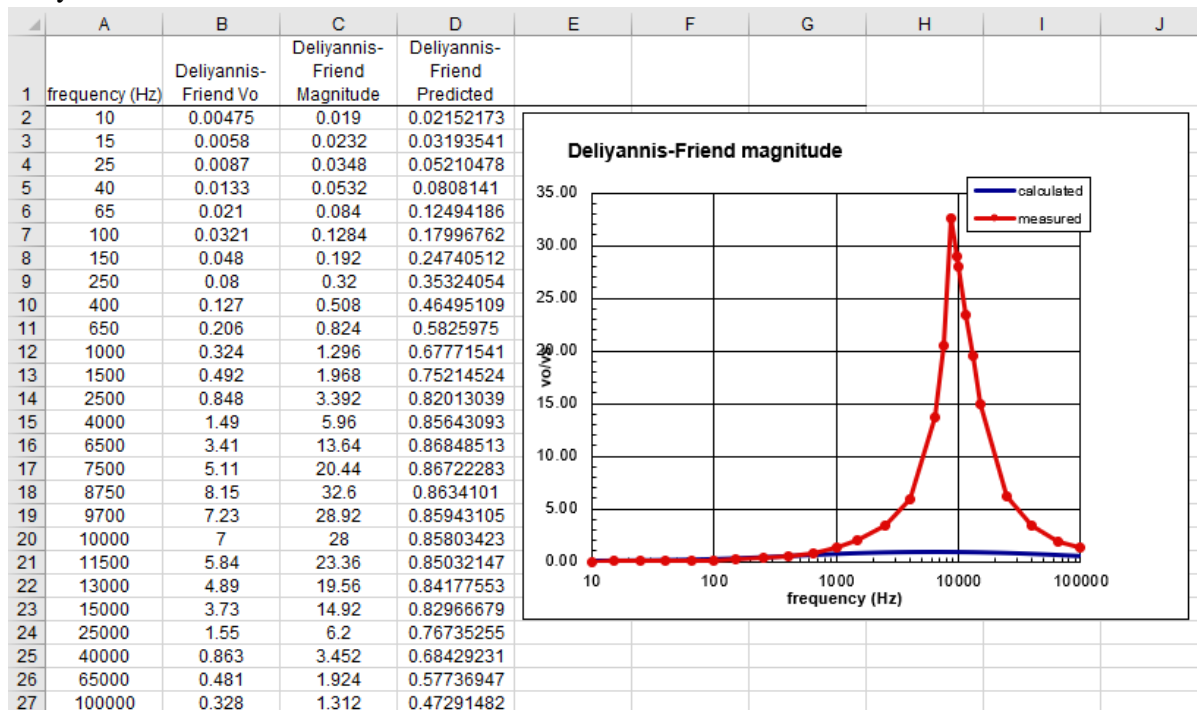

D. Psuedo-inductor circuit


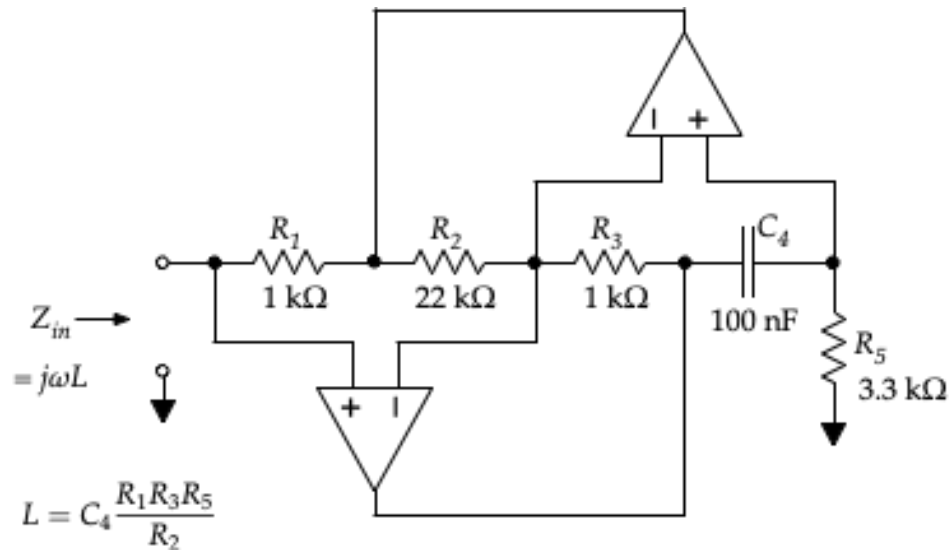


Figure 7. Inductor simulation circuit.

Include the calculation for expected inductance.

$$L = \frac{R_1 R_3 R_5 C}{R_2} = .015 \text{ H}$$

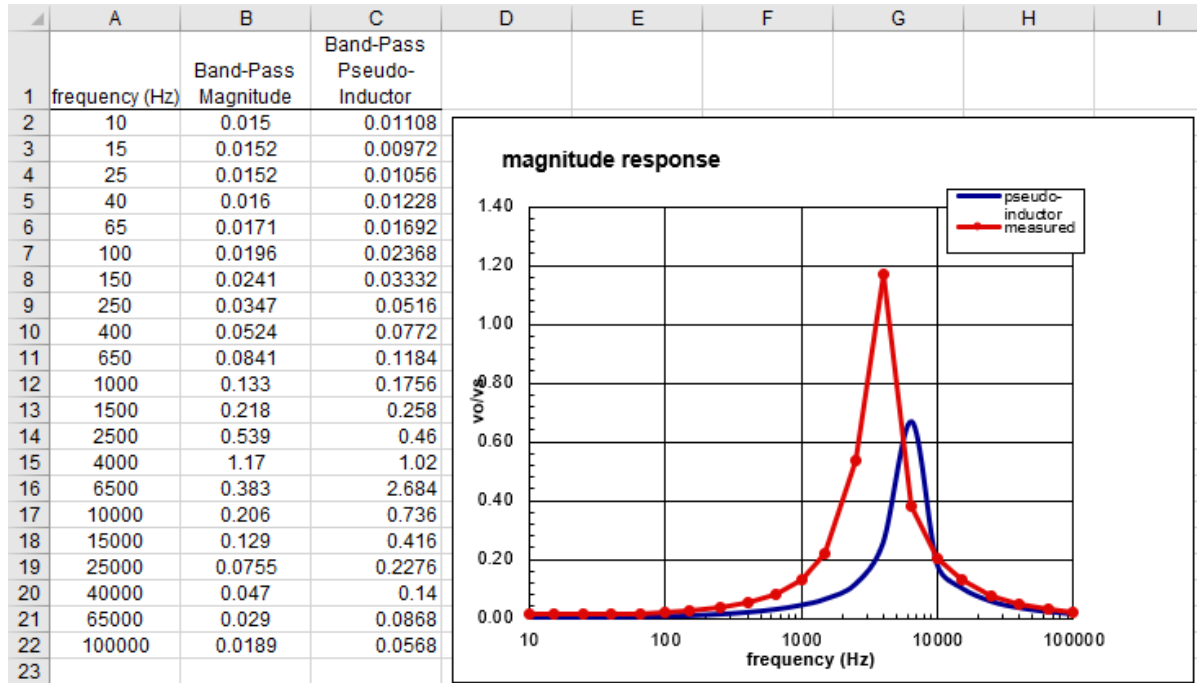Figures. Insert Bode plots of the the RLC bandpass circuit (measured in part B) and the bandpass circuit using the psuedo-inductor measured here. Put both curves on one set of axes.



Conclusion

This lab focused on the relationship between frequency and output for several different types of filters. The lab went over several specific filter designs, as well as just general passive and active second order filters.