 


Due 9/7/2012

I Problem 1.6 of WH

b) $Y = (AB + C) \cdot D$


logic level

3 logic levels
14 transistors

Transistor level


$$Y_{PUN} = \bar{Y} = (AB + C) \cdot D$$
 
$$Y_{PUN} = Y_{PON}' = (A+B) \cdot C + D$$



8 transistors

c) $Y = A \cdot B + C \cdot (A + B)$

 
logic level

3 logic levels
20 transistors

Transistor level

$$Y_{PUN} = \bar{Y} = A \cdot B + C \cdot (A + B)$$
 
$$Y_{PUN} = Y_{PON}' = (A+B) \cdot (C + A \cdot B)$$




10 transistors

2 Problem 1.7 of WH

 c) $Y = \bar{A} \cdot \bar{B} + A \cdot B$


$$\begin{aligned} &= \overline{\overline{\bar{A} \cdot \bar{B}} + \overline{A \cdot B}} \\ &= \overline{A + B + \bar{A} + \bar{B}} \\ &= \overline{(A + B) \cdot (\bar{A} + \bar{B})} \end{aligned}$$



 d) $Y = A \cdot B + B \cdot C + A \cdot C$

$$= \overline{\overline{A \cdot B} + \overline{B \cdot C} + \overline{A \cdot C}}$$

$$= \overline{(A \cdot B) \cdot (B \cdot C) \cdot (A \cdot C)}$$




3 Problem 1.16 of WH


a) $F = \overline{(A+B) \cdot C}$

$$F_{PDN} = \bar{F} = (A+B) \cdot C$$

$$P_{PUN} = F_{PDN}' = A \cdot B + C$$

 

b)

 


4

$$Y_{PDN} = A + B$$

$$Y_{PUN} = A \cdot B$$


logic

 

$$Y = \overline{A + B}$$


transistor

2 input NOR gate

 


5

Original w/ errors

 

5 errors


Corrected design

 

6

2 input NOR + inverter

$$C = A \cdot B$$

 


7

$$Y = (A + \bar{B}) \cdot C$$

$$= \overline{\overline{(A + \bar{B}) \cdot C}}$$
 
$$Y = \overline{(A + \bar{B}) + \bar{C}}$$




3 logic level
12 transistors

$$Y_{PDN} = \bar{Y} = \overline{(A + \bar{B}) + \bar{C}}$$

$$= \bar{A} \cdot B + \bar{C}$$

+ transistor
 
$$Y_{PUN} = Y_{PDN}' = (\bar{A} + B) \cdot \bar{C}$$



2 logic levels
10 transistors

8

for the ON 0.5 μ process

$$C_{GS} = 1.5 \text{ fF}$$

$$C_L = (1.5 \text{ fF}) * (2) * (8) = 24 \text{ fF}$$

$$R_{sw} = 2 \text{ k}\Omega \quad \text{n-channel}$$

$$= 6 \text{ k}\Omega \quad \text{p-channel}$$

$$t_{HL} = (R_{sw_n}) * (C_L) = 24 \text{ fF} \cdot 2 \text{ k}\Omega$$

$$t_{HL} = 48 \text{ ps}$$

9

attached

A) With if-else statement

```

1 module SecurityCamera_A(SWITCH, JEWELS, ARTIFACTS, look_at);
2   input SWITCH, JEWELS, ARTIFACTS;
3   output reg look_at;
4
5   always @(SWITCH or JEWELS or ARTIFACTS)
6     if(SWITCH)
7       look_at = JEWELS;
8     else
9       look_at = ARTIFACTS;
10
11 endmodule

```

B) Without if-else statement

```
1 module SecurityCamera_B(SWITCH, JEWELS, ARTIFACTS, look_at);
2   input SWITCH, JEWELS, ARTIFACTS;
3   output look_at;
4
5   assign look_at = JEWELS & SWITCH | ARTIFACTS & ~SWITCH;
6
7 endmodule
```

Testbench

```

1 `timescale 1ns / 1ps
2
3 module SecurityCamera_tb();
4     reg SWITCH_t, JEWELS_t, ARTIFACTS_t;
5     wire look_at_t, look_at_2_t;
6
7     //Security Camera A -> using if-else statements
8     SecurityCamera_A SecCam_A_1(SWITCH_t, JEWELS_t, ARTIFACTS_t, look_at_t);
9
10    //Security Camera B -> without using if-else statements
11    SecurityCamera_B SecCam_B_1(SWITCH_t, JEWELS_t, ARTIFACTS_t, look_at_2_t);
12
13    initial
14    begin
15        #0 SWITCH_t<=0; JEWELS_t<=0; ARTIFACTS_t<=0; // case 0
16        #1 SWITCH_t<=0; JEWELS_t<=0; ARTIFACTS_t<=1; // case 1
17        #1 SWITCH_t<=0; JEWELS_t<=1; ARTIFACTS_t<=0; // case 2
18        #1 SWITCH_t<=0; JEWELS_t<=1; ARTIFACTS_t<=1; // case 3
19        #1 SWITCH_t<=1; JEWELS_t<=0; ARTIFACTS_t<=0; // case 4
20        #1 SWITCH_t<=1; JEWELS_t<=0; ARTIFACTS_t<=1; // case 5
21        #1 SWITCH_t<=1; JEWELS_t<=1; ARTIFACTS_t<=0; // case 6
22        #1 SWITCH_t<=1; JEWELS_t<=1; ARTIFACTS_t<=1; // case 7
23    end
24 endmodule

```

Waveform

