

EE330

Homework 8

Fall 2017

Solutions – TA: Joseph Aymond

### Problem 1

Assume BJT works in forward active region


$$I_B = \left( \frac{10 - 0.6}{500k} \right) = 18.8\mu A$$

$$I_C = \beta I_B = 100 * 18.8\mu A = 1.88mA$$

$$V_C = 10 - 4000 * 0.00188 = 2.48V$$

$V_{out} = 0V$  (there is a capacitor creating an open circuit in DC.)

Small signal equivalent circuit:

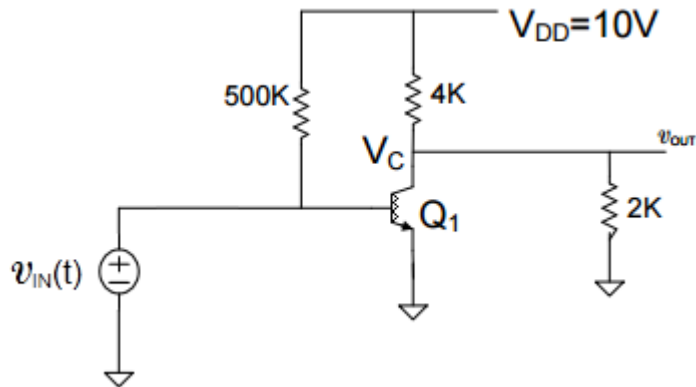

### Problem 2

For the MOSFET to be in saturation  $V_{DS} \geq V_{GS} - V_T$

$$V_{out} + 2 \geq 2 - 0.5 \rightarrow V_{out} \geq -0.5$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2 = \frac{4 - V_{out}}{R_1} \rightarrow V_{out} = 4 - 337.5 * 10^{-6} * R_1 \geq -0.5V$$

$$\rightarrow R_1 \leq 13.3k\Omega$$

### Problem 3

$$\frac{R_1}{2} = 6.666k\Omega$$

$$A_V = \frac{2I_{DQ}R}{V_{SS} + V_T} = \frac{4.5V}{-1.5V} = -3$$

#### Problem 4

Assuming that  $M_1$  and  $M_2$  are in saturation

$$I_{D1} = I_{D2} \rightarrow \frac{\mu_n C_{ox} W_n}{2L_n} (V_{GS} - V_T)^2 = \frac{\mu_p C_{ox} W_p}{2L_p} (V_{GS} - V_T)^2$$
$$\rightarrow \frac{100 * 10^{-6} * 10}{2 * 2} (0 - (-2) - 0.5)^2 = \frac{30 * 10^{-6} * 3}{2 * 1} (V_{out} - 5 - (-0.5))^2$$
$$\rightarrow V_{out} = 0.96447V$$

#### Problem 5

For quiescent values that capacitors act as open circuits, so the voltage is simply,

$$I_B = \frac{32 - V_B}{90K} - \frac{V_B}{10K} = \frac{32 - 10 * V_B}{90K}$$
$$I_E = (\beta + 1)I_B = (101) * \frac{32 - 10 * (V_E + 0.6)}{90K} = \frac{V_E}{1.5K} \rightarrow V_E = 2.454V \rightarrow V_B = 3.054V$$
$$I_C = 101 * 16.222 \mu A \rightarrow V_C = 32 - 3000 * I_C = 27.085V$$
$$V_{out} = 0V$$

#### Problem 6

$$V_{out} = 12 - (12000 * i_{DQ})$$
$$I_{DQ} = 100 * 10^{-6} * \left(\frac{6}{2 * 4}\right) * (0 - (-2) - 1)^2$$
$$I_{DQ} = 75 \mu A$$
$$V_{out} = 11.1V$$

#### Problem 7

a)

$$I_{DQ} = 100 * 10^{-6} * \left(\frac{6}{2 * 3}\right) (2 - 1)^2$$
$$I_{DQ} = 100 \mu A$$
$$V_{outq} = 4 + 100 \mu * 20k = 6V$$

b)

$$\text{When } V_{in} = 0V, V_{out1} = V_{outQ} = 6V$$
$$\text{When } V_{in} = 25mV, V_{out2} = V_{outQ} + \Delta V$$
$$g_m = 100 * 10^{-6} * \left(\frac{6}{3}\right) (1) = 200 \frac{\mu A}{V}$$
$$\Delta V = (g_m * \Delta V_{in}) * 20k = 0.1V$$
$$V_{out2} = 6.1V$$

### Problem 8

$$R_{FET} = \frac{1}{\mu_n C_{OX}} \left( \frac{L}{W} \right) (2 - 1)$$

$$\frac{V_{out} - V_{in}}{R_F} = \frac{V_{in}}{R_{FET}}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_F}{R_{FET}}$$

$$\rightarrow \frac{V_{out}}{V_{in}} = 1 + \mu_n C_{OX} * \left( \frac{W}{L} \right) * R_F = 1 + \frac{R_F}{2500}$$

### Problem 9

$$a) \frac{I_{B1}}{I_{B2}} = \frac{A_{E1}}{A_{E2}} = \frac{1}{4}$$

$$I_B = I_{B1} + I_{B2} = 5 I_{B1}$$

$$I_{IN} = I_{C1} + \beta I_B = \beta I_{B1} + 5 I_{B1}$$

$$I_{B1} = I_{in} \left( \frac{1}{\beta + 5} \right) \rightarrow I_{out} = \beta I_{B2} = \beta * 4 I_{B1} = I_{in} \left( \frac{4}{1 + \frac{5}{\beta}} \right)$$

Assuming that  $\beta$  is large  $\rightarrow I_{out} = 4 * I_{in} = 4 \text{ mA}$

b)

$$\frac{I_{D1}}{I_{D2}} = \frac{\frac{W_1}{L_1}}{\frac{W_2}{L_2}} = \frac{10}{20} = \frac{1}{2}$$

$$I_{out} = 2 I_{in} = 2 \text{ mA}$$

### Problem 10

$$BJT: I_{out} = \frac{A_{E2}}{A_{E1}} I_{in}$$

$$MOSFET: I_{out} = \frac{\frac{W_2}{L_2}}{\frac{W_1}{L_1}} I_{in}$$

### Problem 11

At the basics,  $I_d = \mu C_{ox} \left( \frac{w}{2L} \right) (V_{gs} - V_T)^2$ , and all three have the same total length and width. Because the length/width is the one degree of freedom we have to modify the MOSFET, they should behave the same.

### Problem 12

Yes, this does behave as a rectifier, but it does not work particularly well. It is "Diode Connected" and behaves as a diode, but its I-V curve is not as good as the standard diodes used in class, but may be better than some LEDs.

### Problem 13

As always, we will assume we are operating in saturation region,

$$I_D = \mu_n C_{ox} \left( \frac{W}{2L} \right) (V_{gs} - V_T)^2 = \frac{V_{dd} - V_{out1}}{R_1}$$

$$I_D = \frac{(4 - 3)}{10k} = 0.1mA$$

$$100 * 10^{-6} * \left( \frac{W}{2L} \right) (2 - 1)^2 = 0.0001$$

$$\frac{W}{2L} = 1 \rightarrow W = 2L$$

$$W = 0.6\mu, L = 0.3\mu$$

## Problem 14









Code:

Ln#	
1	
2	module DFF(D, Q, notQ, clk);
3	input D, clk;
4	output Q, notQ;
5	reg Q, notQ;
6	
7	always@(posedge clk) begin
8	Q <= D;
9	notQ <= ~D;
10	end
11	
12	endmodule

Testbench:

Ln#	
1	
2	module DFF(D, Q, notQ, clk);
3	input D, clk;
4	output Q, notQ;
5	reg Q, notQ;
6	
7	always@(posedge clk) begin
8	Q <= D;
9	notQ <= ~D;
10	end
11	
12	endmodule

Output:

	Msgs	
		
 /DFF_tb/D	0	
 /DFF_tb/c	0	
 /DFF_tb/oQ	x	
 /DFF_tb/onotQ	x	