

EE330 Lab 9
Section 5, 8:00 am

Discrete Semiconductor Amplifiers

Sean Gordon
Sgordon4

Part 1: Common-Emitter Amplifier


a) These values were measured using $R_B = 470 \text{ k}\Omega$

I_B was measured to be $24.689 \text{ }\mu\text{A}$

I_C was measured to be $2.390 \text{ mA} = 2390 \text{ }\mu\text{A}$


$I_C = \beta I_B \Rightarrow \beta = I_C / I_B = 2390 \text{ }\mu\text{A} / 24.689 \text{ }\mu\text{A} = \mathbf{96.8}$

b) For I_C to $\approx 1 \text{ mA}$

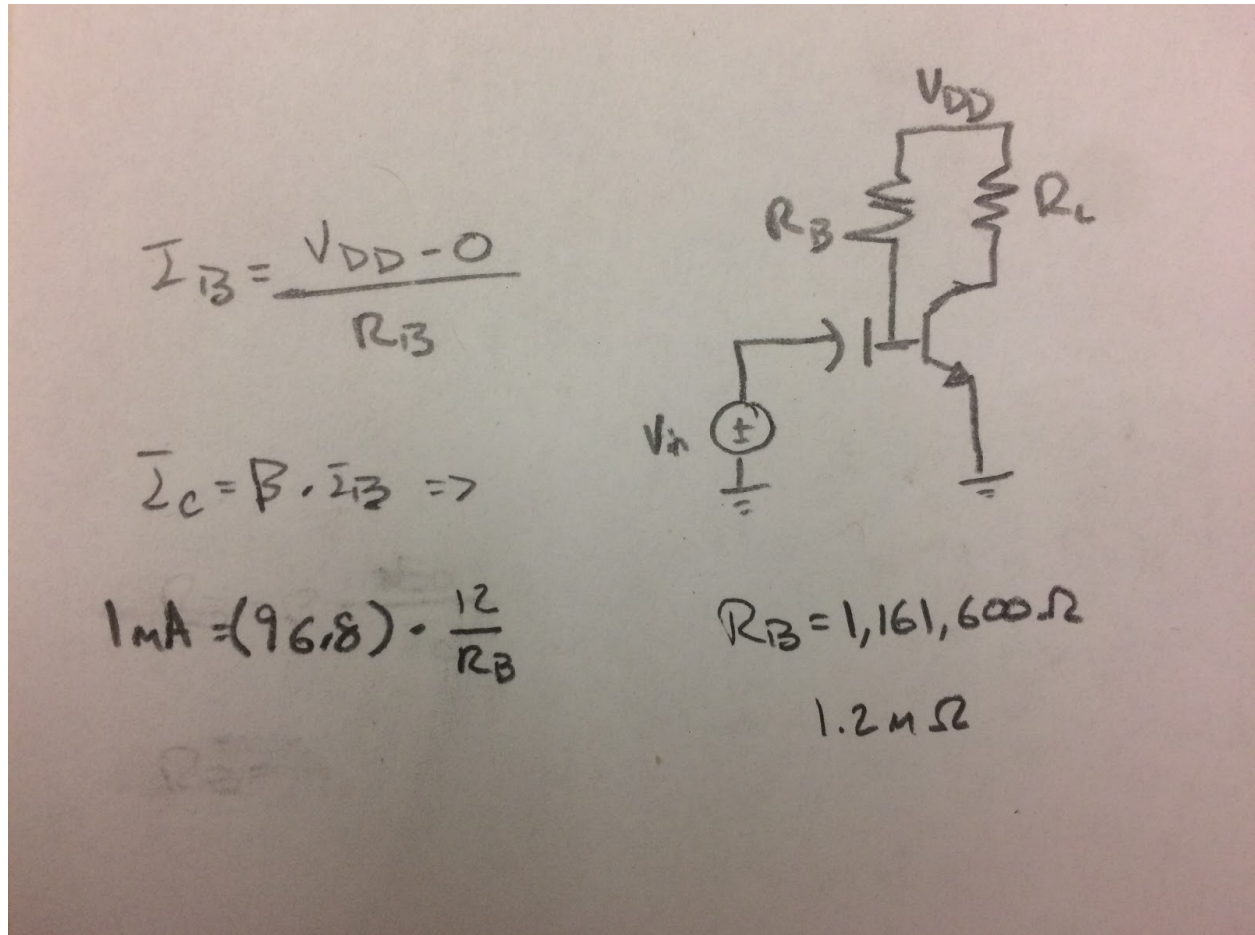

c) I'm getting output voltage $\approx 12.9 \text{ V}$, $.9 \text{ V}$ higher than what I'm putting in ($V_{DD} = 12 \text{ V}$), so clearly I have no idea what I'm doing. However, I also have no time to correct that.

d) Yeah any voltage will do with my mess of a circuit apparently.

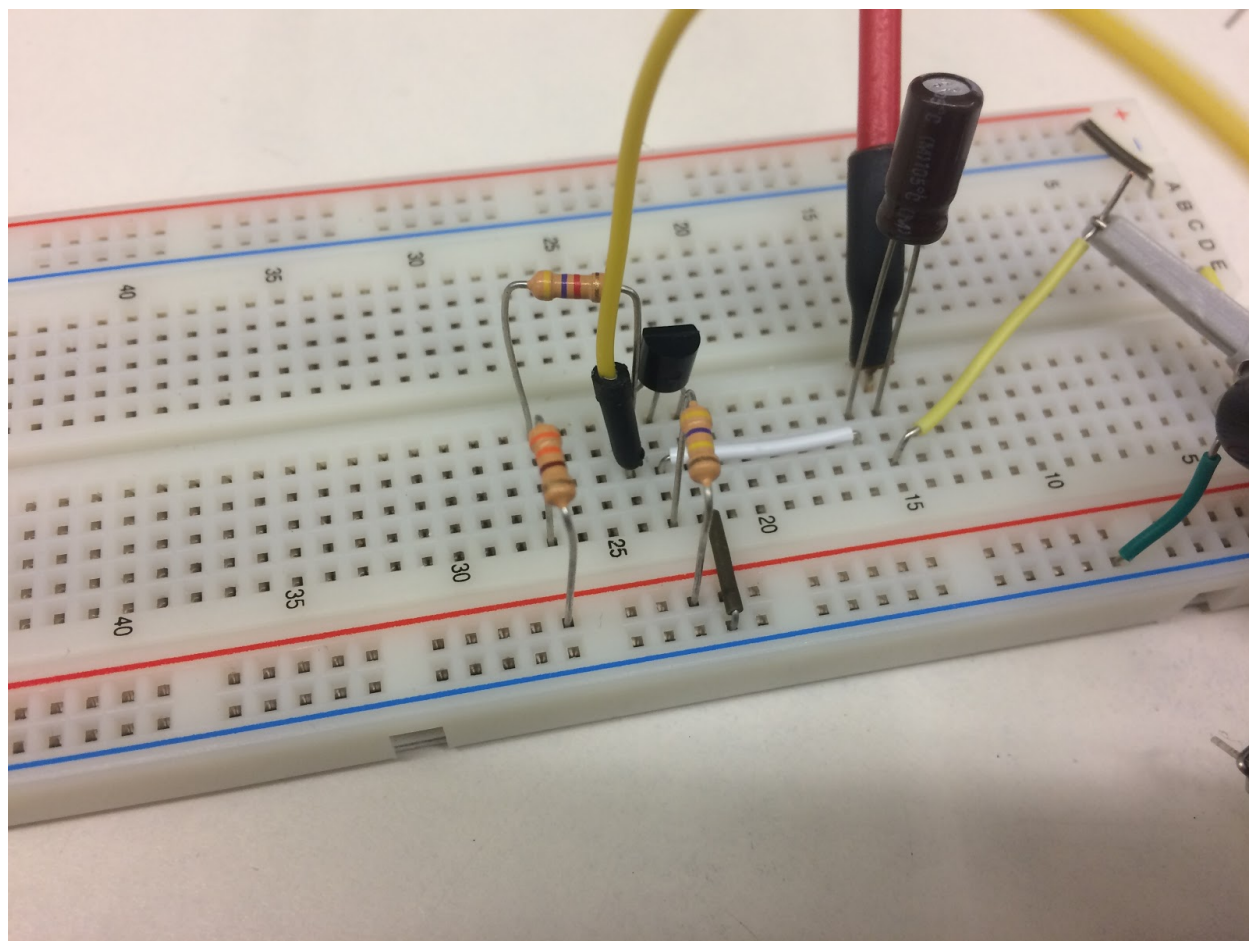

Part 2: Common Source Amplifier

a)

$$A_v = \frac{V_o}{V_{in}} = -g_m \cdot R_L$$

$$g_m = \mu C_{ox} \left(\frac{W}{L} \right) (V_{DD} \cdot \frac{R_{B2}}{R_{B1} + R_{B2}} - V_T)$$

$$A_v = - \left(0.036 \right) \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) - (0.0015) \cdot (5000)$$

$$-10 = -180 \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right) + 7.5 \quad \frac{R_{B2}}{R_{B1} + R_{B2}} = 0.0972$$

b)

$$A_v = \frac{V_o}{V_{in}}$$

$$V_{gs} = V_{in} - V_{ss} \quad V_o = -g_m \cdot V_{gs} \cdot R_L = -g_m \cdot (V_{in} - V_{ss}) \cdot R_L$$

$$g_m = \mu C_{ox} \left(\frac{W}{L} \right) (V_{gs} - V_T) = -1.5 \cdot 10^{-3} \quad R_L = 10k$$

$$V_o = -1.5 \cdot 10^{-3} \cdot 10k \cdot (V_{in} - V_{ss})$$

$$\frac{V_o}{V_{in}} = \frac{+15 \cdot V_{ss}}{V_{in}} \quad \text{Uhhhh...}$$

I seem to not know how to do this, but I don't have time to learn because I have homework to do so this is how it will stay.

Part 3: Amplifier Design

$$A_v = -10 = \frac{-I_C \cdot R_L}{V_T} \Rightarrow$$

$$I_C = \frac{10 \cdot V_T}{R_L} \quad I_C = \beta \cdot I_B$$

$$I_C = \frac{10(0.026)}{5000} = 5.2 \cdot 10^{-6}$$

$$I_B = \frac{I_C}{\beta} = \frac{5.2 \cdot 10^{-6}}{100} = 5.2 \cdot 10^{-7}$$

$$I_B = \frac{V_{DD} - V_{in}}{R_1} \Rightarrow V_{in} = 0 \Rightarrow 5.2 \cdot 10^{-7} = \frac{12}{R_1}$$

$R_1 = 23 \text{ M}\Omega$

When building the circuit, to provide a 5k resistor I used a 330 and a 4.7k in series.