

## **Olouwole Eteka**

### **EE 330 lab 7**

#### **Introduction**


we are measuring the parameters from an actual hardware MOSFET transistor with the help of test equipment mentioned below and the software Signal Express. It is similar to the previous lab but in this one we are using an actual hardware to take our measurements. We will use the function generator and the oscilloscope to measure values and the parameter analyzer for the stimulation.

#### **Part 1. Set up Signal Express**


We will begin by setting up signal express as well as all our test equipment. Then we have to connect our device to the computer and to signal express. After powering them on, we can go ahead and set up the Signal Express. Then we can follow the steps.

- a. IVI Power Supply
- b. IVI DMM Acquire
- c. Sweep

We can see it on the pictures below.

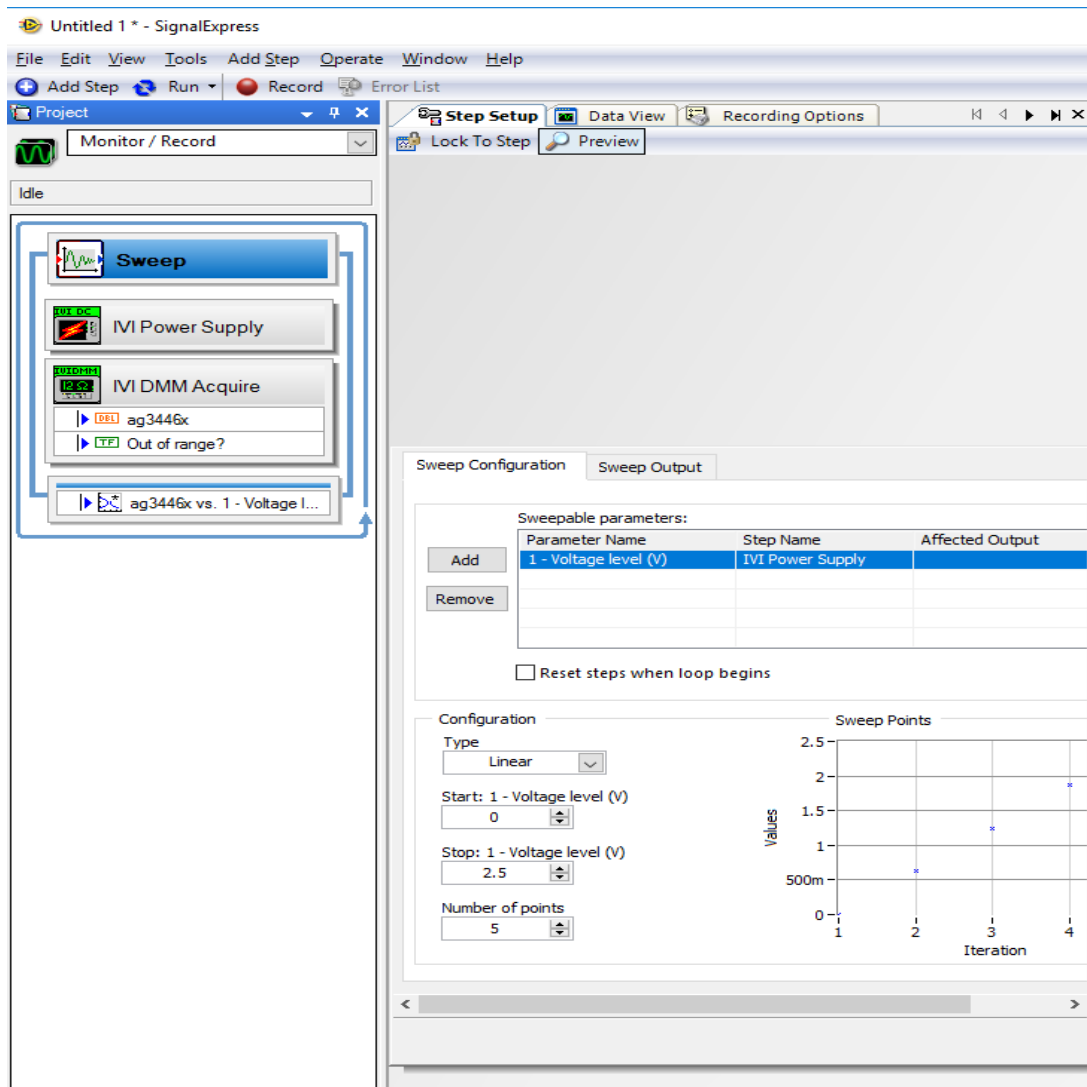


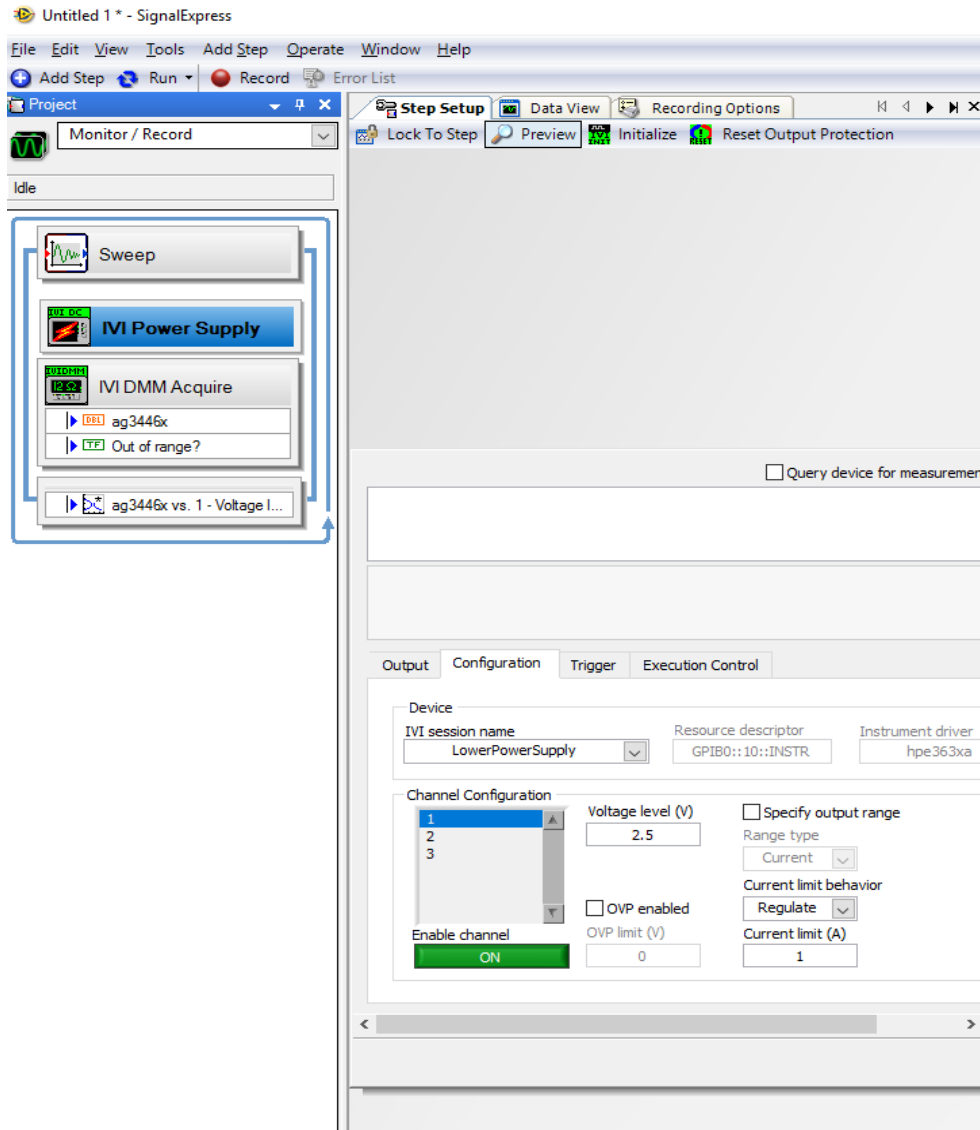In order to set up the power supply, we have to first make sure that we connect to the right power supply device under the drop down box of configuration tab. Then, we have to make sure that all channels 1-3 are turned on. They each represent different voltage terminal of the DC power supply



we can set up the Sweep in the Sweep Configuration tab and proceed to the sweep.

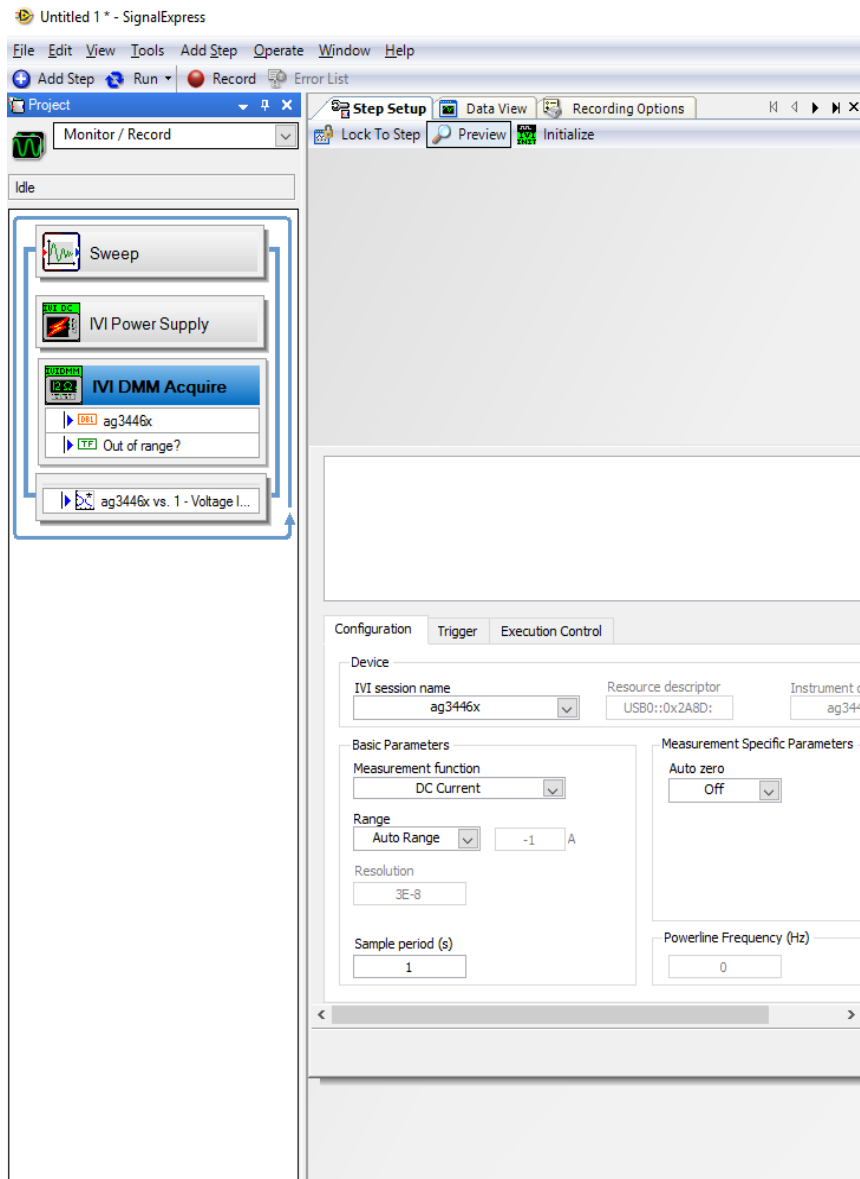Try running it with a different setting and we can run it by using the shortcut key (Ctrl+Shift+R) or click on the Run Once button on toolbar above




## Part 2. Measurement of MOSFET output characteristics Part 2. Measurement of MOSFET output characteristics

We will be setting up the MOS device in this part and look their characteristics. We want to know the relationships between the current  $I_D$  and the voltage variables  $V_{GS}$  and  $V_{DS}$ . Similar to what we did in previous lab, we can do that by sweeping  $V_{DS}$  values and measuring the  $I_D$  with  $V_{GS}$  being

constant, then repeat with different  $V_{GS}$  values but in this case we are using MOSFET. we are allowed to choose any one of the transistors model inside, I've chosen to use NMOS short channel transistor.


Date	#####	Date	#####	Date	#####	Date	#####	Date	#####
Y_Unit_La ag3446x (A)		Y_Unit_Label ag3446x (A)		Y_Unit_La ag3446x (A)		Y_Unit_La ag3446x (A)		Y_Unit_La ag3446x (A)	
X_Dimens1 - Voltage level (V)		X_Dimension1 - Voltage level (V)		X_Dimens1 - Voltage level (V)		X_Dimens1 - Voltage level (V)		X_Dimens1 - Voltage level (V)	
***End_of_Header***		***End_of_Header***		***End_of_Header***		***End_of_Header***		***End_of_Header***	
X_Values	Y_Values	X_Values	Y_Values	X_Values	Y_Values	X_Values	Y_Values	X_Values	Y_Values
0	2.44E-11	0	2.66E-09	0	4.30E-07	0	9.38E-07	0	9.96E-07
0.62	2.09E-10	0.62	1.12E-07	0.62	4.93E-05	0.62	0.000499	0.625	0.00085
1.25	2.49E-10	1.25	1.46E-07	1.25	5.38E-05	1.25	0.000544	1.25	0.000999
1.87	2.74E-10	1.87	1.78E-07	1.87	5.78E-05	1.87	0.000565	1.875	0.001182
2.5	3.09E-10	2.5	2.14E-07	2.5	9.97E-05	2.5	0.000742	2.5	0.001459

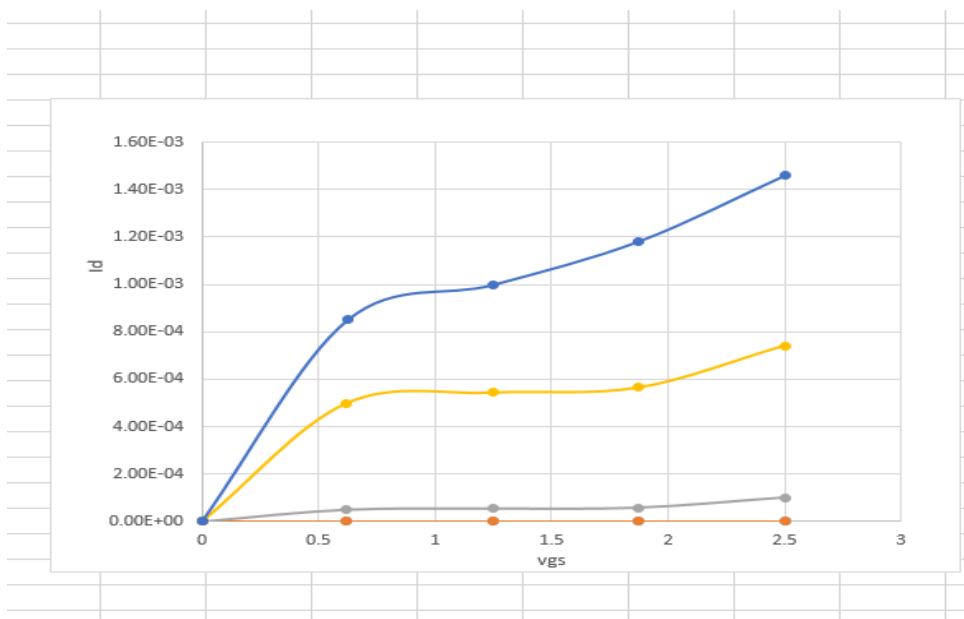we are sweeping the  $V_{DS}$  to create a graph with good accuracy


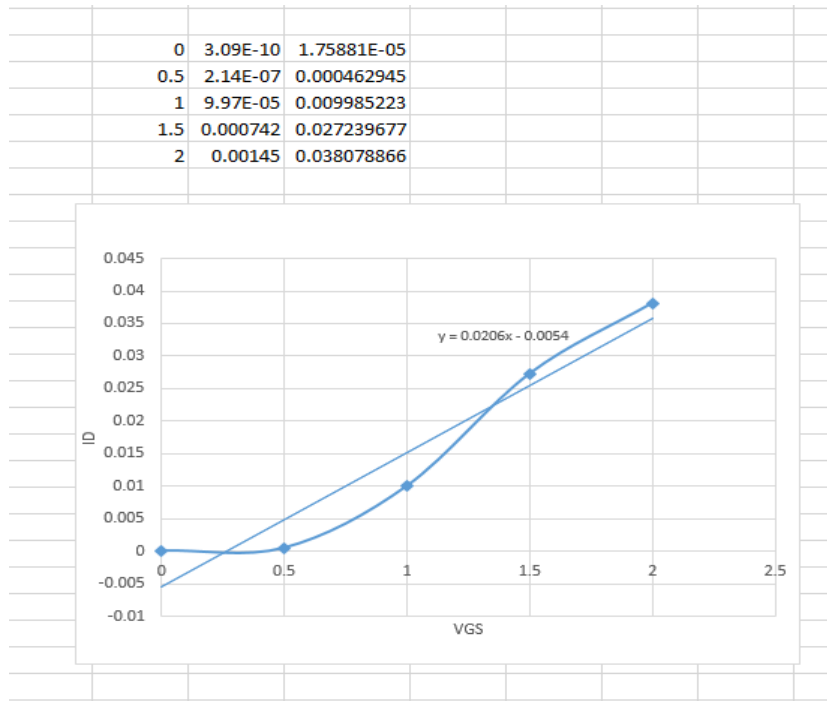
### Part 3. Measurement of MOSFET parameters

We are required to find the parameters  $\mu C_{ox}$ ,  $V_{T0}$ ,  $\lambda$  and  $\gamma$ .



Slope = 0.0206

We can find the  $\mu C_{ox}$  using the equation since we the slope :

$$\mu C_{ox} = 54.3 \mu A/V^2$$

For this part of the lab, we will be getting a plot from 0V to 2.5V for  $V_{DS}$  but instead of using the whole graph, we are only using the graph at the part which it starts to form a linear-like plot and we draw a best fit out of it so that we can apply the equations that we got earlier. As shown above, the slope is 0.0206 and the  $V_{GS}$  axis intercept can be calculated from the linear equation which is about 0.48. From that, we get that  $V_{T0} = 0.479V$ , and  $\mu C_{ox} = 54.3 \mu A/V^2$ .

To extract these parameters, we can do an approach like connecting substrate(bulb) to the source which makes  $V_{BS} = 0$  and we estimate  $\lambda = 0$ . From that, our saturation region equation can be simplified to:

$$I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_{T0})^2$$

When we are connecting the gate to drain ( $V_{GS} = V_{DS}$ ), it's going to force the device into the saturation region (if  $V_{GS} > V_T$ ) and therefore we can use the same method as Part 2 to plot  $I_D$  versus  $V_{GS}$

## b) Extraction of $\gamma$


Voltage (V)	$I_D$ (mA)
-------------	------------

0	0
0.5	0
1	16.79
1.5	0.40
2	0.979

$$V_t = V_{to} + \gamma (\sqrt{\phi - V_b} - \sqrt{\phi})$$

$V_{to}$  = slope of  $X = 0.0206$

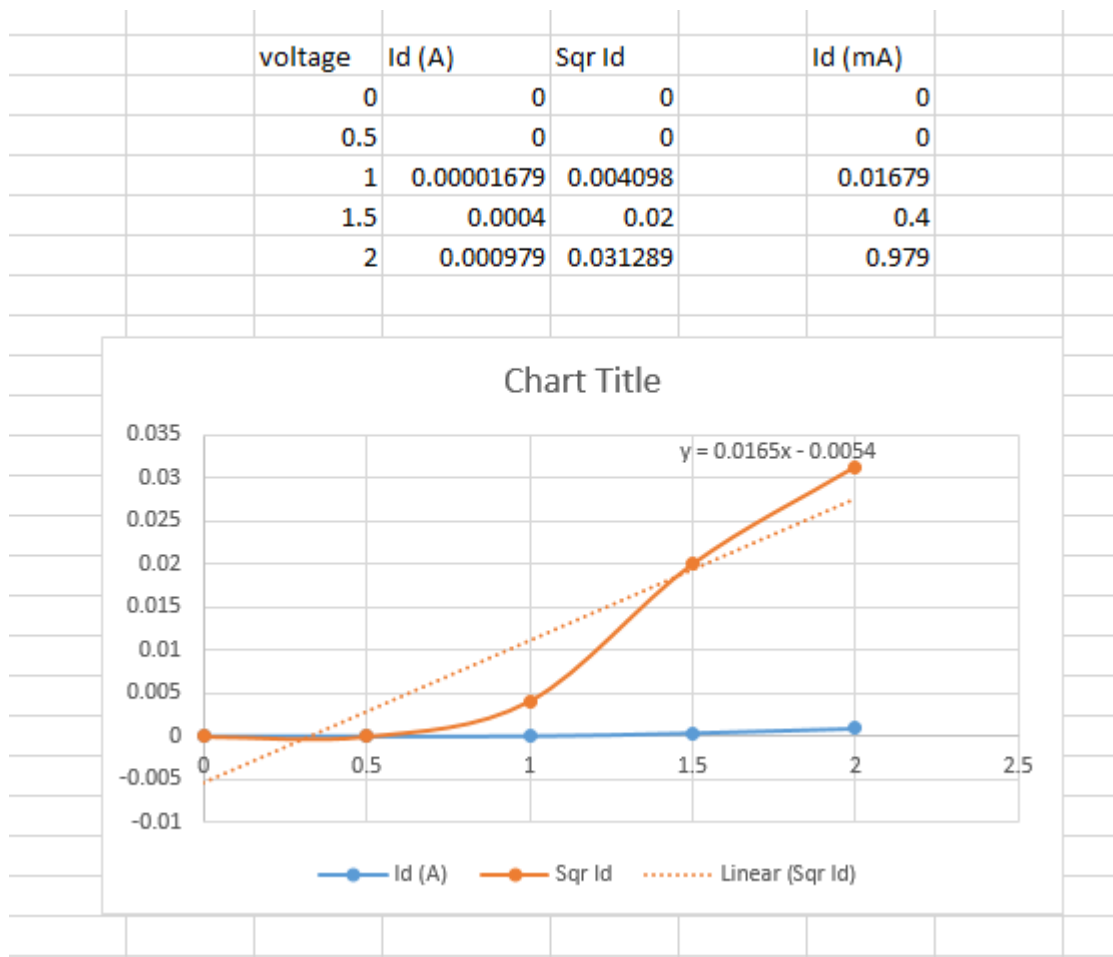From the figure above, we can calculate that the  $V_{GS}$  axis intercept has the value of 0.54, so we know that  $V_T = 0.54V$ . Then, we can use the equation above along with the slop to find the  $\gamma = 0.14$ .



**c) extraction of  $\lambda$**

$$\lambda = \frac{I_{d2} - I_{d1}}{I_{d1} * V_{ds2} - I_{d2} * V_{ds1}}$$

Vds(v)	Id(mA)
Vds1=2	Id1=2.176
Vds2=2.5	Id2=2.695

$$\lambda = ((2.295 \times 10^{-3}) - (2.176 \times 10^{-3})) / ((2.176 \times 10^{-3})(2.5) - (2.295 \times 10^{-3})(2))$$

$$\lambda = \mathbf{0.14}$$

## Part 4. Measurement of parameters using B1500a Parameter Analyzer

We will be finding  $\mu_{Cox}$ ,  $V_{T0}$ ,  $\lambda$  and  $\gamma$  as before But instead of using Signal Express to get the graphs and analyze them like the previous part, we are using the B1500a Parameter Analyzer to do what we did before. The table of data extraction below.

Part 4.txt - Notepad

Index	Vgate	Vsource	Vdrain	Vsubs	Idrain	IdrainPerWg
1	0 V	0 V	0 V	0 V	-5.170 pA	-430.8333333 fA/um
2	0 V	0 V	500.0 mV	0 V	136.460 pA	11.37166667 pA/um
3	0 V	0 V	1.0000 V	0 V	184.320 pA	15.36000000 pA/um
4	0 V	0 V	1.5000 V	0 V	189.620 pA	15.80166667 pA/um
5	0 V	0 V	2.0000 V	0 V	220.480 pA	18.37333333 pA/um
6	0 V	0 V	2.5000 V	0 V	239.400 pA	19.95000000 pA/um
7	500.00 mV	0 V	0 V	0 V	25.750 pA	2.145833333 pA/um
8	500.00 mV	0 V	500.0 mV	0 V	118.030 nA	9.835833333 nA/um
9	500.00 mV	0 V	1.0000 V	0 V	147.970 nA	12.33083333 nA/um
10	500.00 mV	0 V	1.5000 V	0 V	174.270 nA	14.52250000 nA/um
11	500.00 mV	0 V	2.0000 V	0 V	198.140 nA	16.51166667 nA/um
12	500.00 mV	0 V	2.5000 V	0 V	221.950 nA	18.49583333 nA/um
13	1.0000 V	0 V	0 V	0 V	12.9710 nA	1.080916667 nA/um
14	1.0000 V	0 V	500.0 mV	0 V	133.690 uA	11.14083333 uA/um
15	1.0000 V	0 V	1.0000 V	0 V	148.270 uA	12.35583333 uA/um
16	1.0000 V	0 V	1.5000 V	0 V	157.090 uA	13.09083333 uA/um
17	1.0000 V	0 V	2.0000 V	0 V	163.830 uA	13.65250000 uA/um
18	1.0000 V	0 V	2.5000 V	0 V	169.680 uA	14.14000000 uA/um
19	1.5000 V	0 V	0 V	0 V	34.2590 nA	2.854916667 nA/um
20	1.5000 V	0 V	500.0 mV	0 V	598.690 uA	49.89083333 uA/um
21	1.5000 V	0 V	1.0000 V	0 V	706.030 uA	58.83583333 uA/um
22	1.5000 V	0 V	1.5000 V	0 V	734.360 uA	61.19666667 uA/um
23	1.5000 V	0 V	2.0000 V	0 V	751.070 uA	62.58916667 uA/um
24	1.5000 V	0 V	2.5000 V	0 V	763.670 uA	63.63916667 uA/um
25	2.0000 V	0 V	0 V	0 V	41.2620 nA	3.438500000 nA/um
26	2.0000 V	0 V	500.0 mV	0 V	988.670 uA	82.38916667 uA/um
27	2.0000 V	0 V	1.0000 V	0 V	1.37270 mA	114.3916667 uA/um
28	2.0000 V	0 V	1.5000 V	0 V	1.45330 mA	121.1083333 uA/um
29	2.0000 V	0 V	2.0000 V	0 V	1.48370 mA	123.6416667 uA/um
30	2.0000 V	0 V	2.5000 V	0 V	1.50170 mA	125.1416667 uA/um
31	2.5000 V	0 V	0 V	0 V	54.6090 nA	4.550750000 nA/um
32	2.5000 V	0 V	500.0 mV	0 V	1.26930 mA	105.7750000 uA/um
33	2.5000 V	0 V	1.0000 V	0 V	1.97300 mA	164.4166667 uA/um
34	2.5000 V	0 V	1.5000 V	0 V	2.19470 mA	182.8916667 uA/um
35	2.5000 V	0 V	2.0000 V	0 V	2.25700 mA	188.0833333 uA/um
36	2.5000 V	0 V	2.5000 V	0 V	2.28420 mA	190.3500000 uA/um

The amplitude from the function generator to the oscilloscope is off. It was supposed to be 2.5-volt peak to peak but it was given me 2.72v for the first case and 3.20v for the second case. But the transistors are working and inverting correctly.




**In Case 1, M1 will be an NMOS(Short Channel), and M2 will be a PMOS(Short Channel)**

Short Channel Transistors




On the diagram above, the left is the schematic diagram of the short channel NMOS while the right is the schematic diagram of the short channel PMOS.

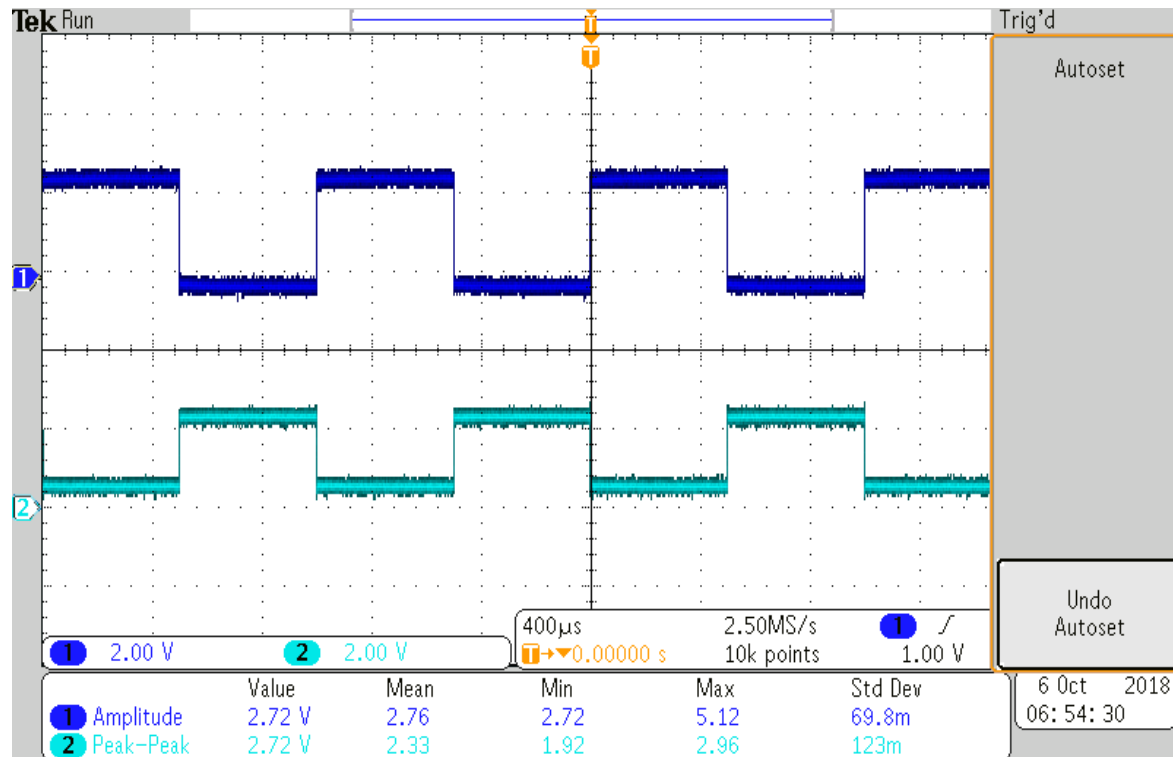$V_{in} = 0V$ ,  $V_{out} = 0V$  and  $V_{in} = 2.5V$ ,  $V_{out} = 2.5V$



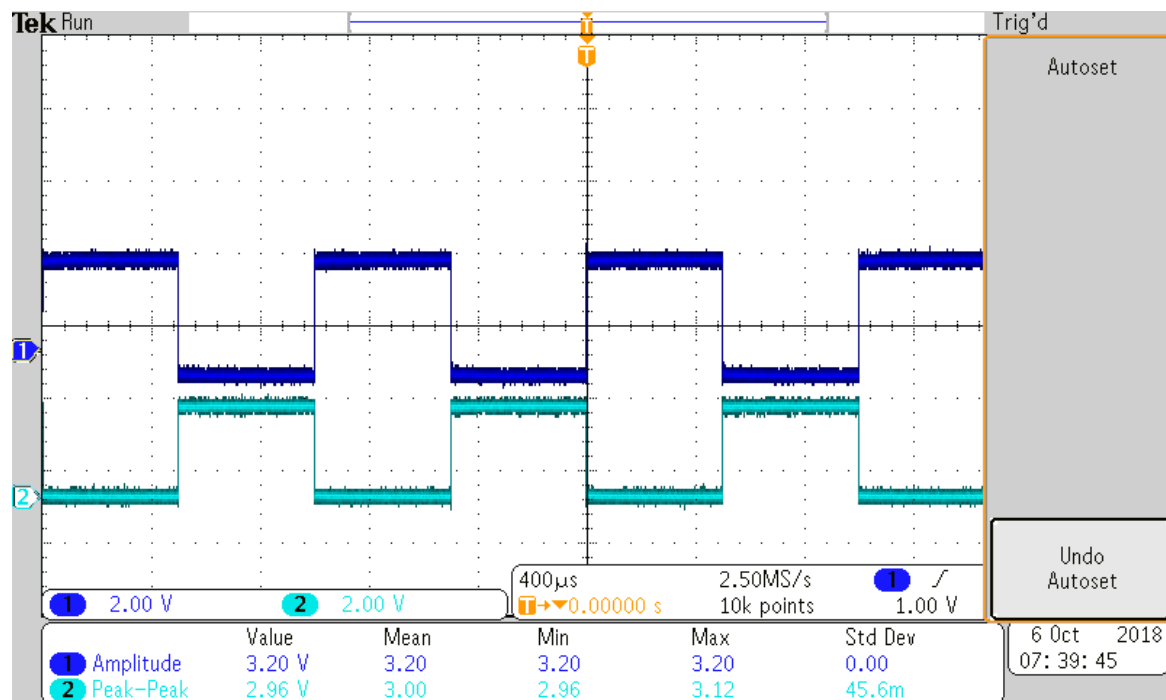**In Case 2, M1 will be an NMOS(Long Channel) , and M2 will be a PMOS(Short Channel)**



As we observe from both of the cases of short and long channels, we can see that they both give about the same graph but only with slight differences in amplitude.

From comparison we can tell that the results we got from method in Part 3 & 4 doesn't have much different except the difference is a little high for  $\lambda$  and  $V_{TO}$ . But regardless of using method in Part 3 or Part 4, we get values that are a lot more different than what it supposed to be except for  $V_{TO}$ . The one in part 3 was close.

## Conclusion

I learned that in reality, the parameters of the transistor might malfunction. we can assume that we get similar results for the parameters when we do different tests such as the method in Part 2 and the other method that was using the Parameter Analyzer but the result can be very different. We also have to check if the transistor is working properly.