

Homework 2 Fall 2017 TA: Joseph Aymond


Problem 1:

In figure 1.4 we can find the count of transistors in the processor increases by about ~10 times per seven years. In 2002 the count was about 0.1 Billion, so we can predict the count in 2020 to be about

$$0.1 \text{ billion} * 10^{(18/7)} = \mathbf{37.28 \text{ billion.}}$$

 Problem 2:

The transistor level schematic for a CMOS 3-input NOR gate can be made like this (other ways are possible)



X1, X2, and X3 are inputs

Y is the output

$$Y = \overline{X1 + X2 + X3}$$

Problem 3:

$$\text{Area of die } A_{\text{die}} = (3.5\text{mm})^2 = 12.25 \text{ mm}^2 = 0.1225 \text{ cm}^2$$

$$\text{Area of wafer } A_{\text{wafer}} = \left(\frac{300}{2}\right)^2 * \pi = 70685 \text{ mm}^2 = 706.85 \text{ cm}^2$$

$$\text{Hard yield of die } Y_H = e^{-A_{\text{die}} * d} = e^{-0.1225 * 1.4} = e^{-0.157} = 0.854$$

$$\text{The total yield } Y = Y_H * Y_S = 0.854 * 1 = 0.854$$

$$\text{The cost per good die } C_{\text{good}} = \frac{C_{\text{wafer}}}{A_{\text{wafer}}/A_{\text{die}}} * \frac{1}{Y} = \frac{\$3200}{\frac{70685}{12.25}} * \frac{1}{0.854} = \mathbf{\$0.649}$$

Problem 4:

$$Y = \frac{x - u}{g} = \frac{3\text{mv} - 0\text{mv}}{1.5 \text{ mv}} = \frac{3}{1.5} = 2$$

$$P_{\text{Soft_Amp}} = \int_2^2 f(x) dx = 2F_N(2) - 1 = 0.9545$$

$$\text{Two Op Amps per chip } P_{\text{Soft_chip}} = 0.9545^2 = \mathbf{0.911}$$

Problem 5:

Since the input offset voltage follow Gaussian distribution we have the soft yield θ :

$$Y_s = P_{soft} = 2F_N(y) - 1 = 0.98 \Rightarrow F_N(y) = 0.990$$

$$\therefore y = 2.33 = \frac{x - u}{g} = \frac{1mv - 0}{\left(\frac{A_{VTO}}{\sqrt{A}}\right)} \Rightarrow A = 2172 \mu m^2$$

Problem 6:

$$\text{The area of a die in new process} = A_{die} = \left(\frac{7}{65}\right)^2 * 0.5cm^2 = 5.7988 * 10^{-3}cm^2$$


$$\text{The hard yield} = Y_H = e^{-A_{die}*d} = e^{-0.00725} = 0.9928$$

$$\text{The yield } Y = Y_H * Y_s = 0.9928$$

$$C_{good} = \frac{C_{wafer}}{(A_{wafer}/A_{die})} * \frac{1}{Y} = \frac{\$8000}{\frac{1590.4}{0.005799}} * \frac{1}{0.9928} = \$0.0294$$

Problem 7:

This switch level model assumes $A=1$ and $\bar{C} = 1$.

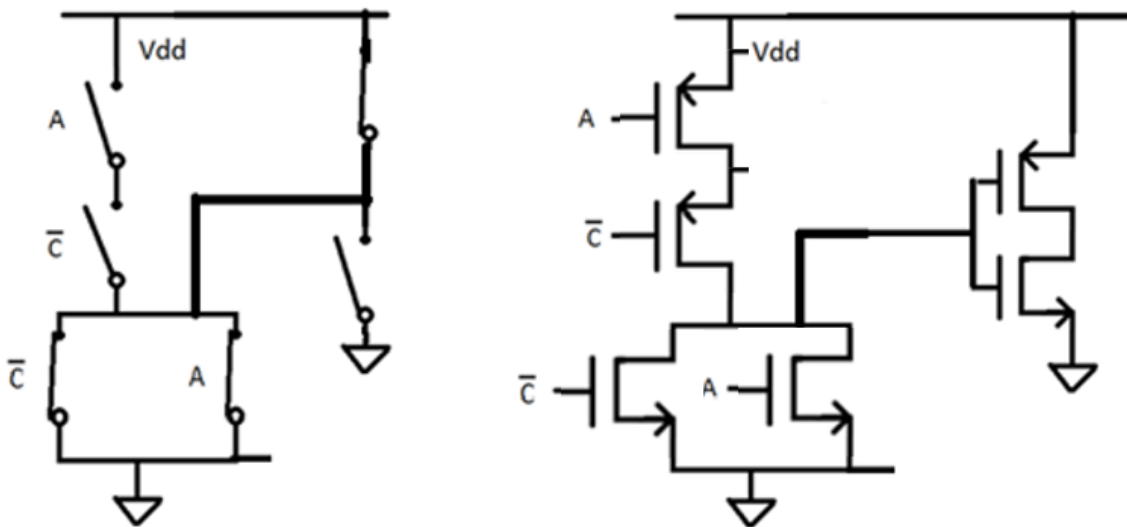

Problem 8:

When both inputs are 0V the output is VDD = 3V

When one input is 0V and the other is 3V the output is VDD = 0V

When both inputs are 3V the output is VSS = 0V

Problem 9:

- a- The master is addressing a slave and requesting data. Data is transferred to the master.
- b- The master is sending data to slave and receiving acknowledgement again just like part a.
- c- Open drain refers to the exposed drain of a transistor typically used as the output.
- d- Logic contention refers to data being driven at any time from several devices. I2C follows a protocol so that the contention doesn't appear.
- e- Due to the I2C open drain protocols the bus remains on a low threshold voltage. Devices can drive past the threshold so that the different logic levels are apparent

Problem 10:

Here is one solution to this problem

Ln#	
1	<code> timescale 1ns/1ps</code>
2	<code>module NOR2 (i_A, i_B, o_F);</code>
3	<code>input i_A, i_B;</code>
4	<code>output o_F;</code>
5	
6	<code>assign o_F = ~(i_A i_B);</code>
7	
8	<code>endmodule</code>
9	

Ln#	
1	<code> </code>
2	<code>timescale 1ns/1ps</code>
3	<code>module OR2 (i_A, i_B, o_F);</code>
4	<code>input i_A, i_B;</code>
5	<code>output o_F;</code>
6	<code>wire A_nor_B;</code>
7	
8	<code>NOR2 nor0(.i_A(i_A), .i_B(i_B), .o_F(A_nor_B));</code>
9	<code>NOR2 nor1(.i_A(A_nor_B), .i_B(A_nor_B), .o_F(o_F));</code>
10	
11	<code>endmodule</code>
12	
13	

Ln#	
1	
2	`timescale 1ns/1ps
3	module AND2 (i_A, i_B, o_F);
4	input i_A, i_B;
5	output o_F;
6	wire A_not, B_not;
7	
8	NOR2 nor0(.i_A(i_A), .i_B(i_A), .o_F(A_not));
9	NOR2 nor1(.i_A(i_B), .i_B(i_B), .o_F(B_not));
10	NOR2 nor2(.i_A(A_not), .i_B(B_not), .o_F(o_F));
11	
12	endmodule

Ln#	
1	module Function_Spring2018(iA, iB, oF);
2	input iA, iB;
3	output oF;
4	wire nA, nB;
5	wire nA_B, A_nB;
6	
7	NOR2 nor0(.i_A(iA), .i_B(iA), .o_F(nA));
8	NOR2 nor1(.i_A(iB), .i_B(iB), .o_F(nB));
9	AND2 and0(.i_A(nA), .i_B(iB), .o_F(nA_B));
10	AND2 and1(.i_A(iA), .i_B(nB), .o_F(A_nB));
11	OR2 or0(.i_A(nA_B), .i_B(A_nB), .o_F(oF));
12	
13	endmodule
14	

```

|
`timescale 1ns/1ps
module Function_Spring2018_tb();
  reg r_A, r_B;
  wire w_F;

  initial
  begin
    r_A = 1'b0;
    r_B = 1'b0;
  end

  always
  #10 r_A=~r_A;
  always
  #20 r_B=~r_B;

  Function_Spring2018 U(.iA(r_A),.iB(r_B),.oF(w_F));

endmodule

```

	/Function_Spring2018_tb/r_A	0				
	/Function_Spring2018_tb/r_B	0				
	/Function_Spring2018_tb/w_F	0				