

Transceiver Block

...

Sean Gordon and Bryan Friestad


The project

- The goal of this device is to more efficiently transmit serial data
- A clock line should not be sent
- Instead, we can recover the clock line from the data using a PLL
- This requires the data to be dense with transitions
- We have designed an encoding/decoding scheme to add additional transitions

Requirements

- a. Devise a 4-bit to 5-bit coding scheme that will guarantee at most 4 consecutive 0s or 1s for any input data sequence.
- b. Design a circuit that will take an 8-bit wide parallel data sequence at 10K bytes/sec and serialize it using the 4-bit to 5-bit coding scheme you devised in part (a). This assumes that a 10KHz clock is present that is synchronous with the input data.
- c. Design a receiver that will take the serial data string, decode it, and recreate an 8-bit wide data sequence at the output.
- d. Design a “comma detect” circuit that will allow for proper framing of the received data. The “comma” should be a 10-bit code that cannot represent any data sequence. The “comma” would be inserted in place of a byte in the transmitted data stream for synchronization and the receiver should frame the received data relative to the detected “comma” whenever a comma is detected. After the “comma” is detected, the received should be in synch with the input data sequence.

High-level diagram

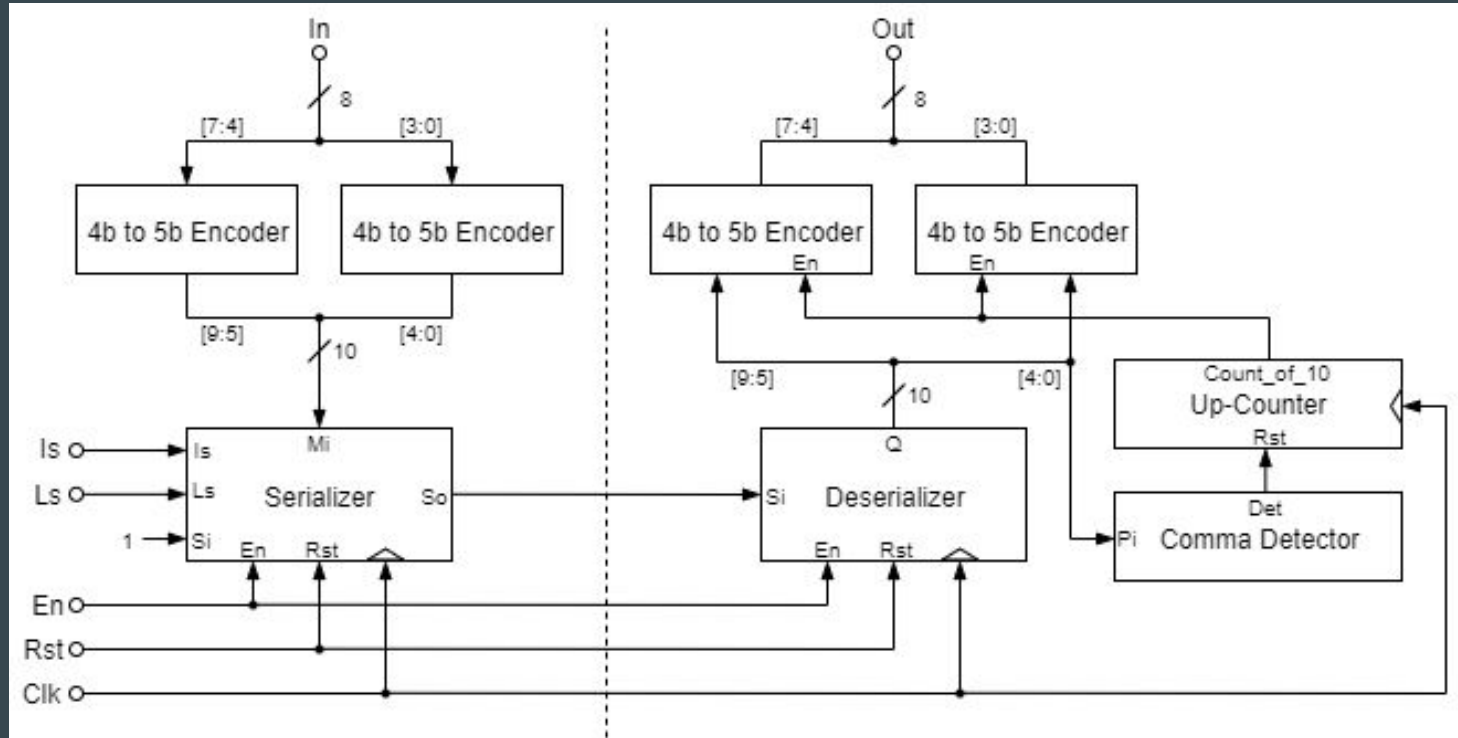

Designing the Encoding/Decoding Scheme

- Needed to devise a 4-bit to 5-bit scheme that guaranteed at most 4 consecutive 0/1s
- Design drawback: Non-equal bit disparity

0000 → 00000

Input: 0000_0000
Conv: 00000_00000



0000 → 00100

Input: 0000_0000
Conv: 00100_00100



Encoding chart

- From 5-bit strings, we selected the most transition heavy
- Each byte is split into a low and a high nibble
- Each nibble is equivalently encoded
- Decoding is just a reverse mapping
- All unmapped 5-bit words output Z

Transcript	
VSIM 8>run 160ns	
# 0000	-> 00100
# 0001	-> 00101
# 0010	-> 00110
# 0011	-> 01001
# 0100	-> 01010
# 0101	-> 01011
# 0110	-> 01100
# 0111	-> 01101
# 1000	-> 10010
# 1001	-> 10011
# 1010	-> 10100
# 1011	-> 10101
# 1100	-> 10110
# 1101	-> 11001
# 1110	-> 11010
# 1111	-> 11011


VSIM 17>restart -f	
VSIM 18>run 320ns	
# 00100	-> 0000
# 00101	-> 0001
# 00110	-> 0010
# 01001	-> 0011
# 01010	-> 0100
# 01011	-> 0101
# 01100	-> 0110
# 01101	-> 0111
# 10010	-> 1000
# 10011	-> 1001
# 10100	-> 1010
# 10101	-> 1011
# 10110	-> 1100
# 11001	-> 1101
# 11010	-> 1110
# 11011	-> 1111
# 11011	-> zzzz
# 11111	-> zzzz

Encoder/Decoder Testbenches


+ /encoder_4b_5b_...	-No Data-	0	1	2	3	4	5	6	7	8	9	a	b	c	d	e	f
+ /encoder_4b_5b_...	-No Data-	04	05	06	09	0a	0b	0c	0d	12	13	14	15	16	19	1a	1b

Wave - Default		Msgs							
+ /decoder_10b_8b/in	-No Data-	1011000100	0110101001	0100010001	1101000000				
+ /decoder_10b_8b/out	-No Data-	11000000	01110011	01110011	1110zzzz				
+ /decoder_10b_8b/en	-No Data-								

Serializer Block Diagram

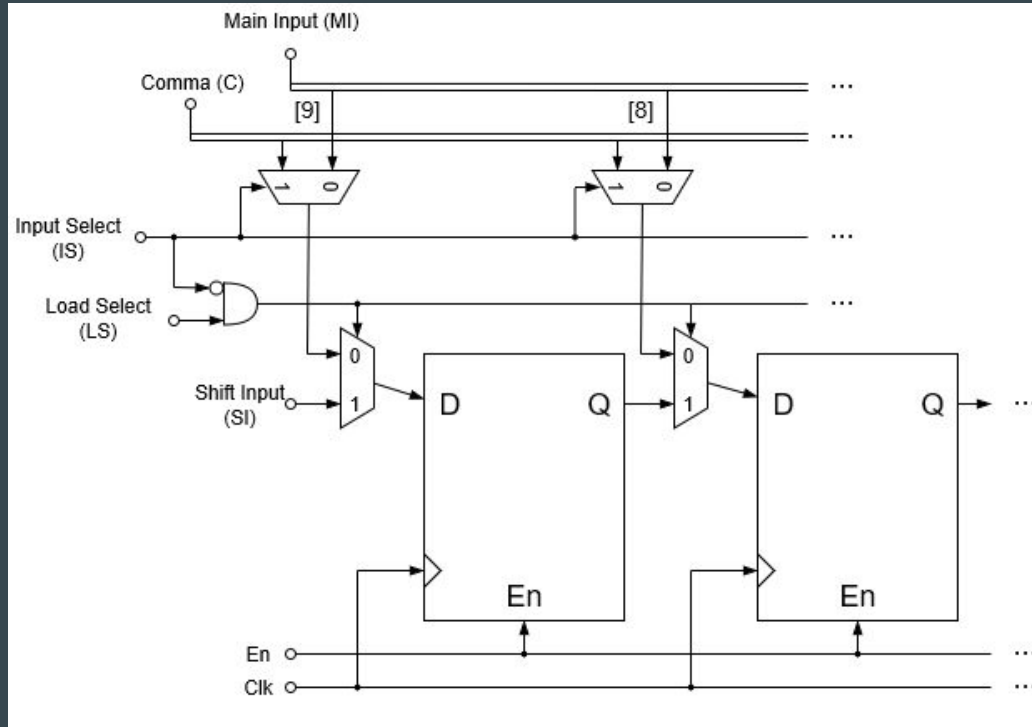

Deserializer Block Diagram

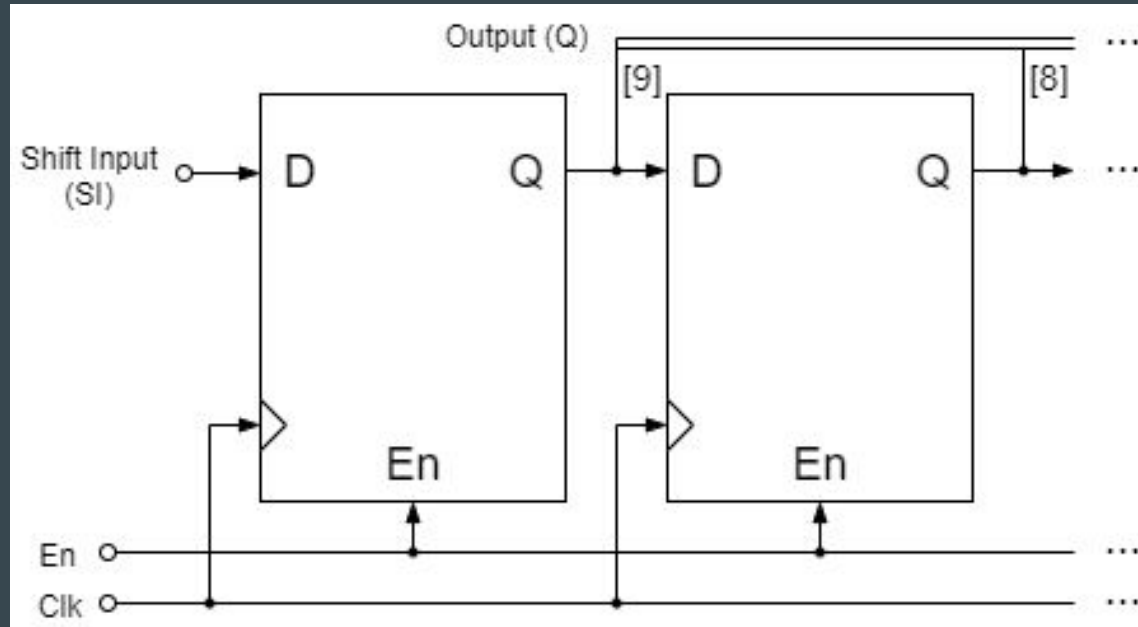

Serializer Testing

#Test Comma

```
force -deposit Mi 2#11111_11111 0
force -deposit Si 1 0
force -deposit Is 1 0
force -deposit Ls 0 0
run 100
```

#Test Main Input

```
force -deposit Mi 2#10101_01010 0
force -deposit Si 1 0
force -deposit Is 0 0
force -deposit Ls 0 0
run 100
```


#Test Shift Input

```
force -deposit Mi 2#11111_11111 0
force -deposit Si 1 0
force -deposit Is 0 0
force -deposit Ls 1 0
run 100
```

#Let shifter propagate out
run 500

```
force -deposit Si 0 0
run 400
```

Serializer Waveform

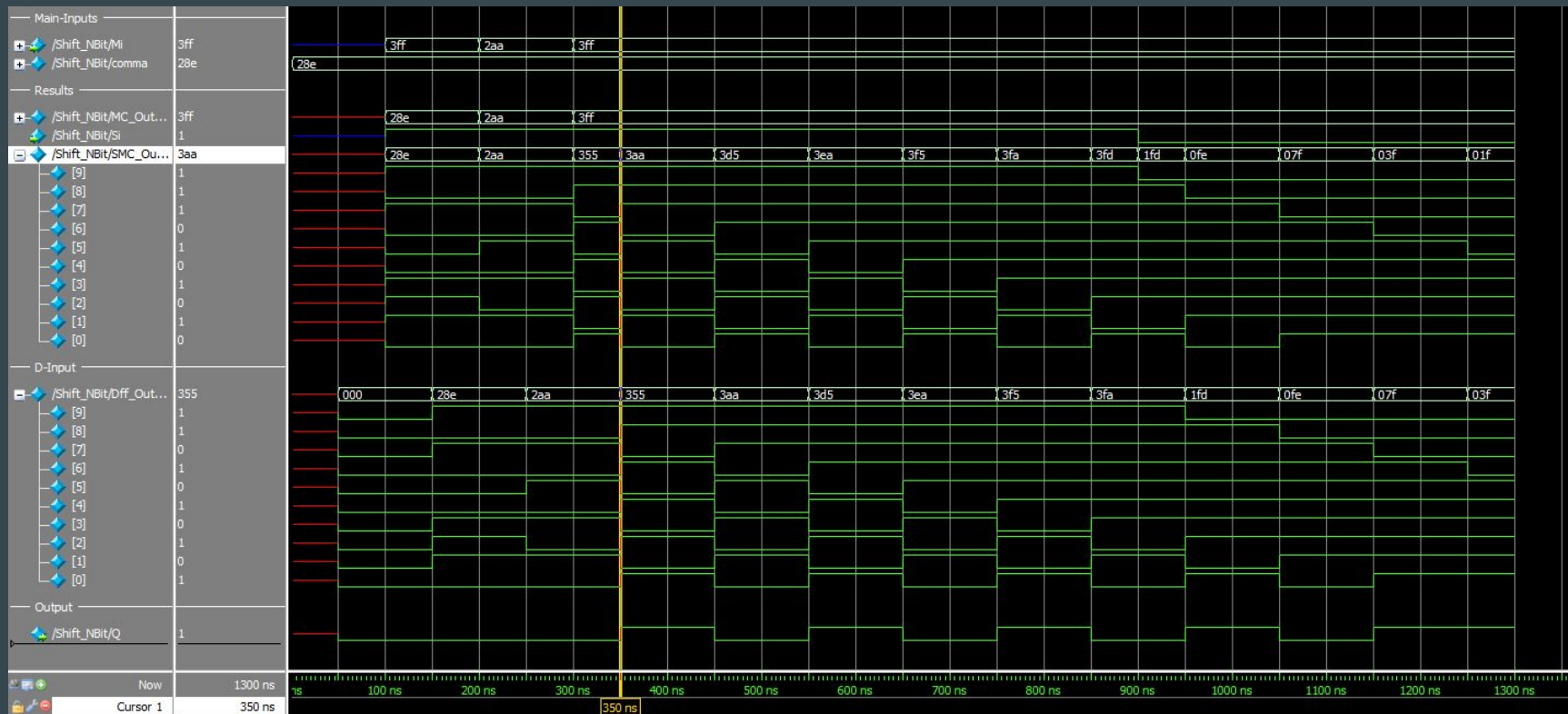

Deserializer Testing

Clearing Things

force -deposit en 1 0

force -deposit rst 1 0

run 100

Commence Test

force -deposit rst 0 0

#Test Shift Input

force -deposit Si 1 0

run 100

force -deposit Si 0 0

run 100

force -deposit Si 1 0

run 100

force -deposit Si 0 0

run 100

force -deposit Si 1 0

run 100

force -deposit Si 1 0

run 100

force -deposit Si 0 0

run 100


force -deposit Si 1 0

run 100

#Allow deserializer to propagate

run 900

Deserializer Waveform

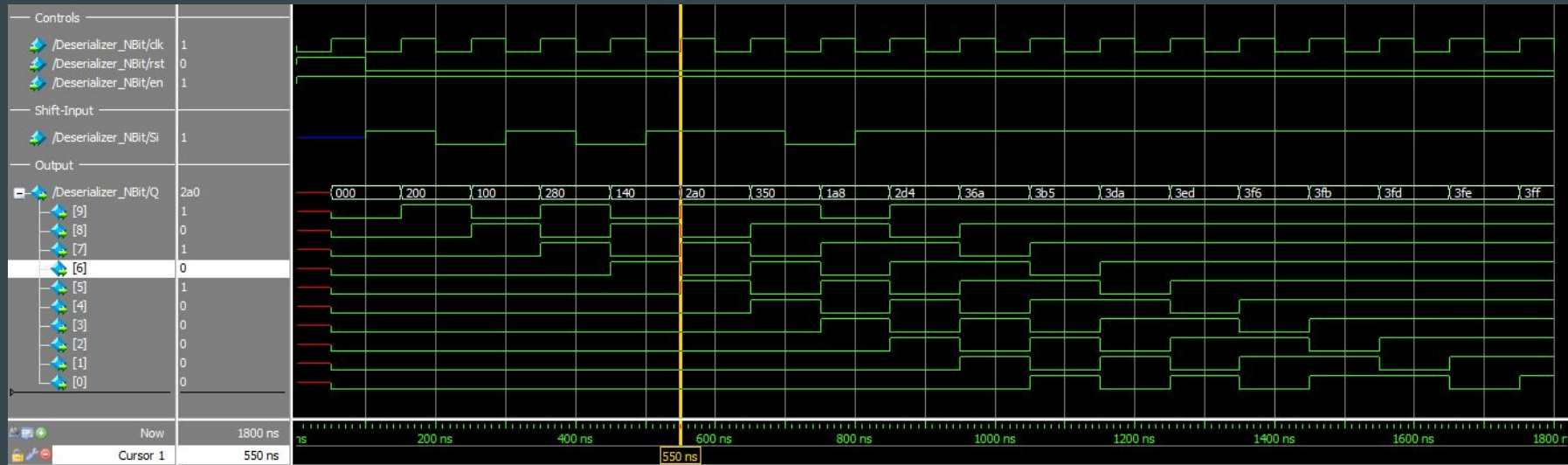

Receiver Synchronization

- In order to detect valid serial input, we need to align the data
- As data is shifted into the Deserializer, we want to be able to detect a start message
- We can devise a “Comma” which heads all serial messages
- When the comma is detected, the decoder is enabled.
- Additionally, a counter is reset to keep track of when a new 10-bit word has appeared

Selecting a Comma

- The comma must maintain that there are no more than 4 consecutive equal bits
- The comma must not appear in any other valid string of input to the Deserializer.
- We wrote a short program to assist in finding an optimal comma
- We selected 10_1000_1110

```
public class FindComma {  
  
    private static String[] five_bit_words = {"00100", "00101", "00110", "01001",  
                                              "01010", "01011", "01100", "01101",  
                                              "10010", "10011", "10100", "10101",  
                                              "10110", "11001", "11010", "11011"};  
  
    private static ArrayList<String> ten_bit_words;  
    private static String[] twenty_bit_words;  
  
    public static void main(String[] args) {  
        ten_bit_words = new ArrayList<String>();  
        twenty_bit_words = new String[65536];  
  
        for(int i = 0; i < 1024; i++){  
            ten_bit_words.add(extendWord(Integer.toBinaryString(i), 10));  
        }  
  
        int n = 0;  
        for(int i = 0; i < 16; i++){  
            for(int j = 0; j < 16; j++){  
                for(int k = 0; k < 16; k++){  
                    for(int l = 0; l < 16; l++){  
                        twenty_bit_words[n] = five_bit_words[i] + five_bit_words[j] + five_bit_words[k] + five_bit_words[l];  
                        //generates all possible, unique 20bit combinations of the 5bit words  
                        n++;  
                    }  
                }  
            }  
        }  
  
        for(int i = 0; i < 65536; i++){  
            String[] frames = new String[10];  
            for(int j = 0; j < 10; j++){  
                frames[j] = twenty_bit_words[i].substring(j, j+10); //gets all possible 10bit frames from each 20bit word  
            }  
  
            //for each 10bit frame  
            for(String s : frames){  
                ten_bit_words.remove(s); //removes the 10bit frame from the list if it exists in the list  
            }  
        }  
  
        for(String s : ten_bit_words){  
            if(countTransitions(s) >= 5) //only display words with 5 or more transitions  
                System.out.println(s + ": " + countTransitions(s)); //the only remaining 10bit words are valid for commas  
        }  
    }  
}
```

Final Test Conditions

Clearing Things

```
force -deposit en 1 0
force -deposit rst 1 0
run 100
```

Commence Test

```
force -deposit rst 0 0
```

#Load Comma

#Setting In to 0xCC to point out that we're loading a 'comma'

```
force -deposit In 2#00110_01100 0
force -deposit Is 1 0
force -deposit Ls 0 0
run 100
```

#And send it over

```
force -deposit Is 0 0
force -deposit Ls 1 0
run 900
```

IMPORTANT

Make sure when we load we do it on
the 1000ns mark
(run 900 -> load, run 100 -> repeat)

#Load Main Input

```
force -deposit In 2#10101_01010 0
force -deposit Is 0 0
force -deposit Ls 0 0
run 100
```

#And send it over

```
force -deposit Is 0 0
force -deposit Ls 1 0
run 900
```


#Load Main Input-1

```
force -deposit In 2#10101_01001 0
force -deposit Is 0 0
force -deposit Ls 0 0
run 100
```


#And send it over


```
force -deposit Is 0 0
force -deposit Ls 1 0
run 900
```


Final Waveform

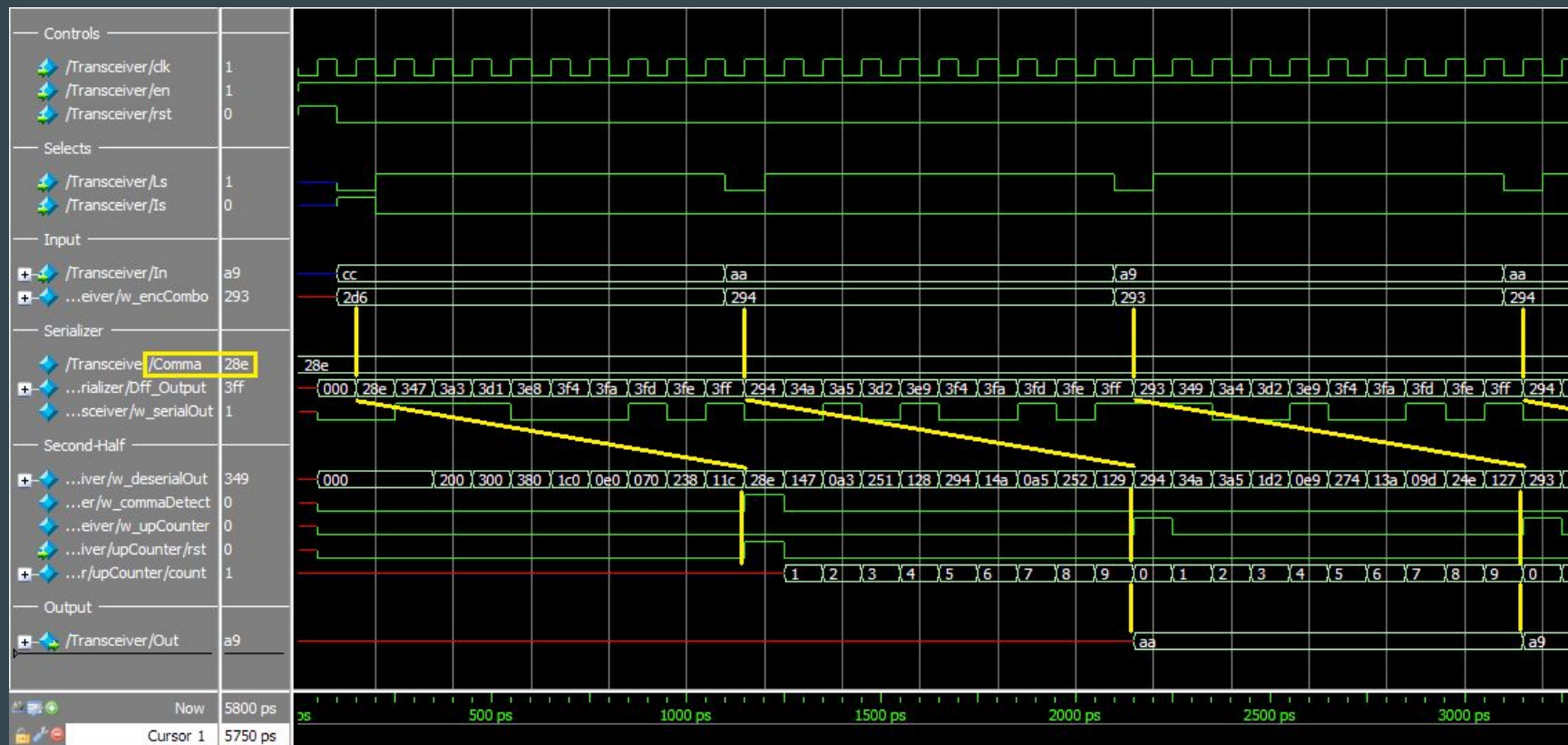

Synthesized Schematic

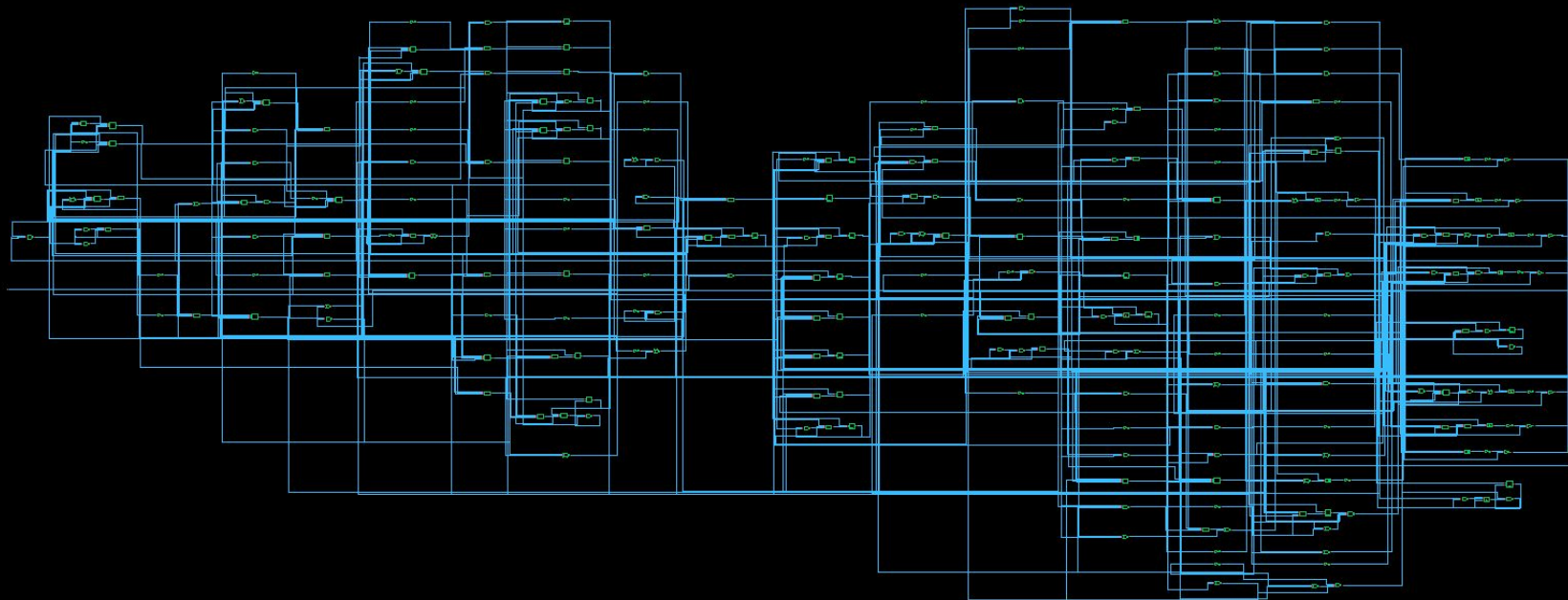


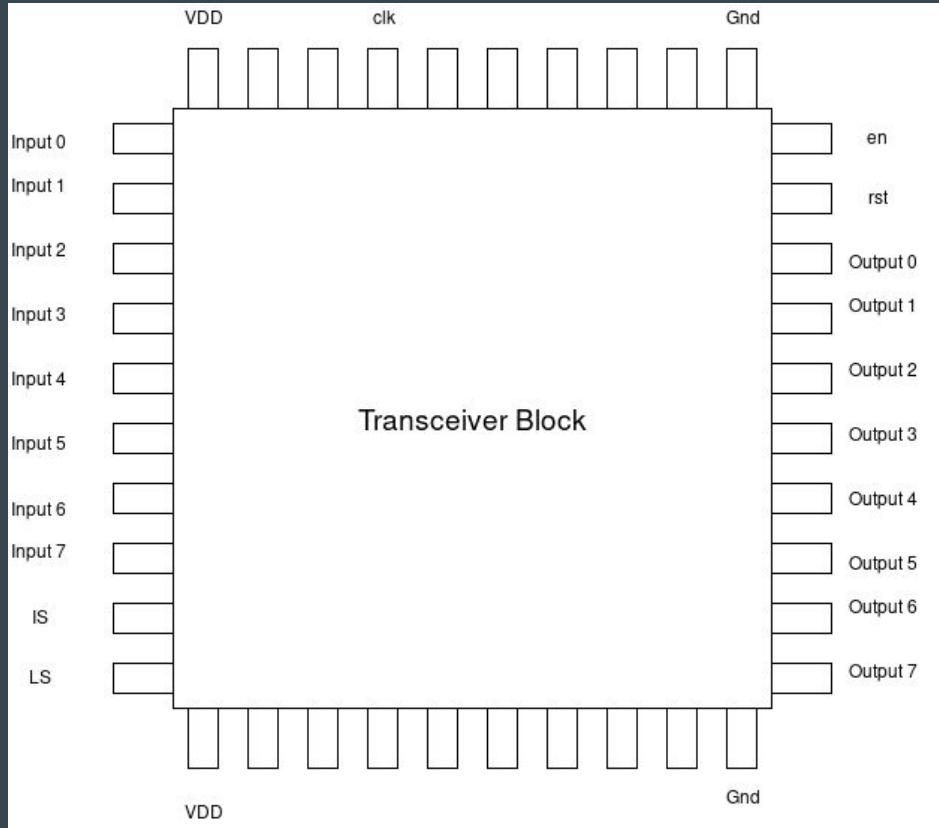

Our planned pinout on a 40-pin frame


Layout and Routing

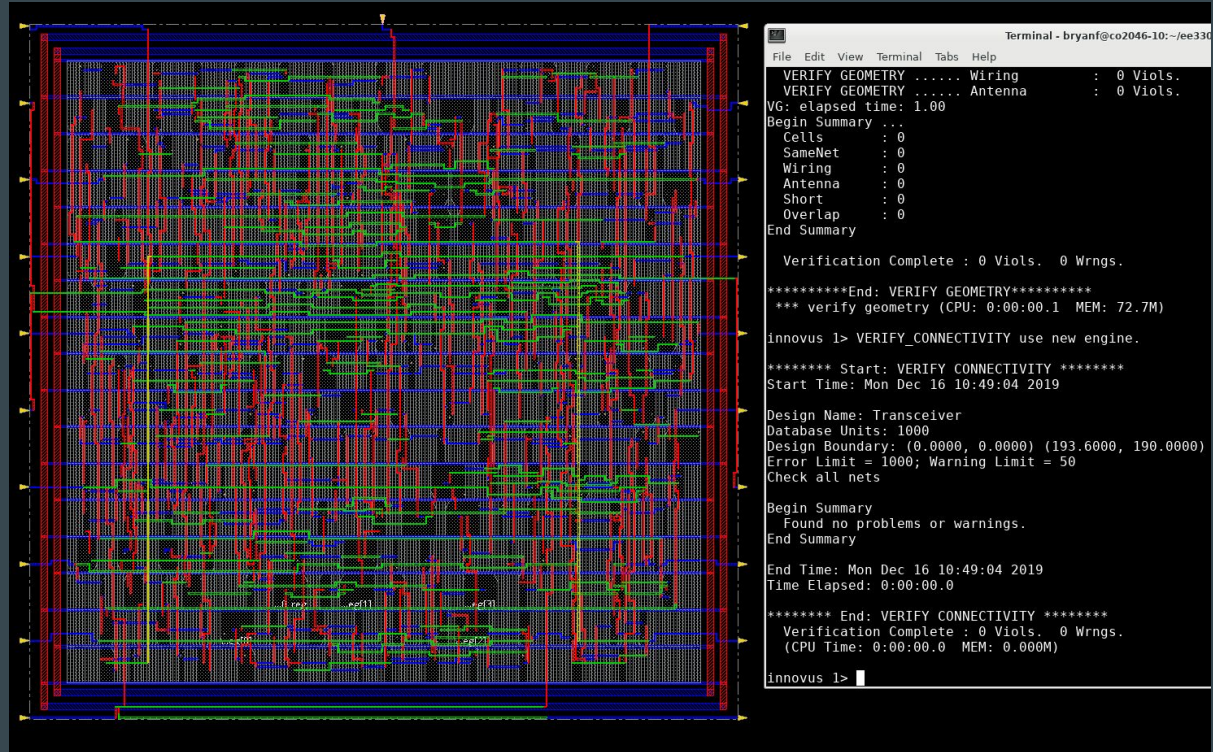- We wanted to maintain a roughly square area for the pad frame
- We had to set up the pins so that they were spread out
- The area was approximately 190 μm by 192 μm , or .0365 mm^2
- Our geometry checks and connectivity checks passed without error




Importing, DRC & LVS

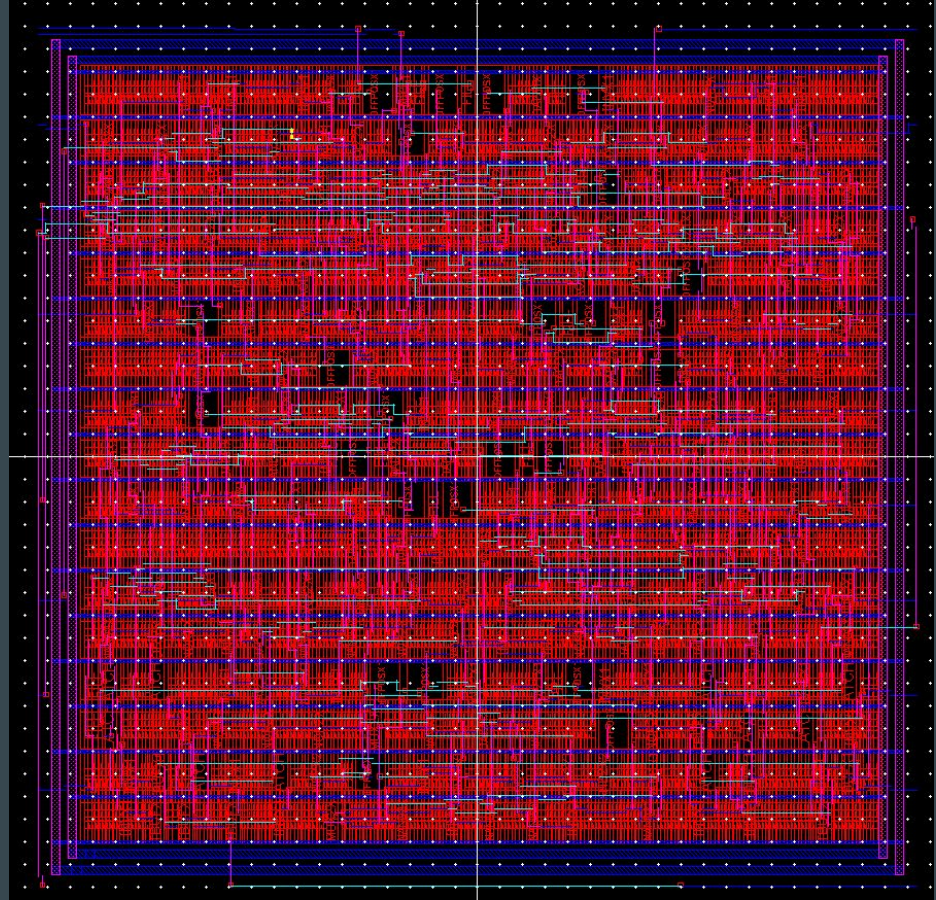- We exported from Innovus and imported into Virtuoso (had to fix a bug)
- DRC and LVS both passed after some troubleshooting / bug fixing




DRC Success

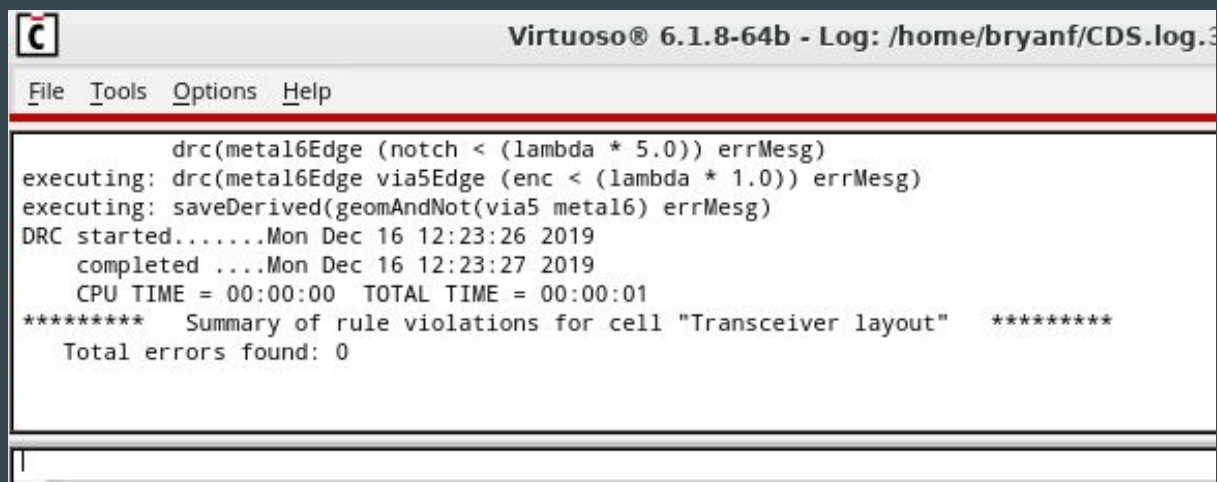

```
Virtuoso® 6.1.8-64b - Log: /home/bryanf/CDS.log.3
File Tools Options Help
drc(metal6Edge (notch < (lambda * 5.0)) errMesg)
executing: drc(metal6Edge via5Edge (enc < (lambda * 1.0)) errMesg)
executing: saveDerived(geomAndNot(via5 metal6) errMesg)
DRC started.....Mon Dec 16 12:23:26 2019
completed ....Mon Dec 16 12:23:27 2019
CPU TIME = 00:00:00 TOTAL TIME = 00:00:01
***** Summary of rule violations for cell "Transceiver layout" *****
Total errors found: 0
```

LVS Success

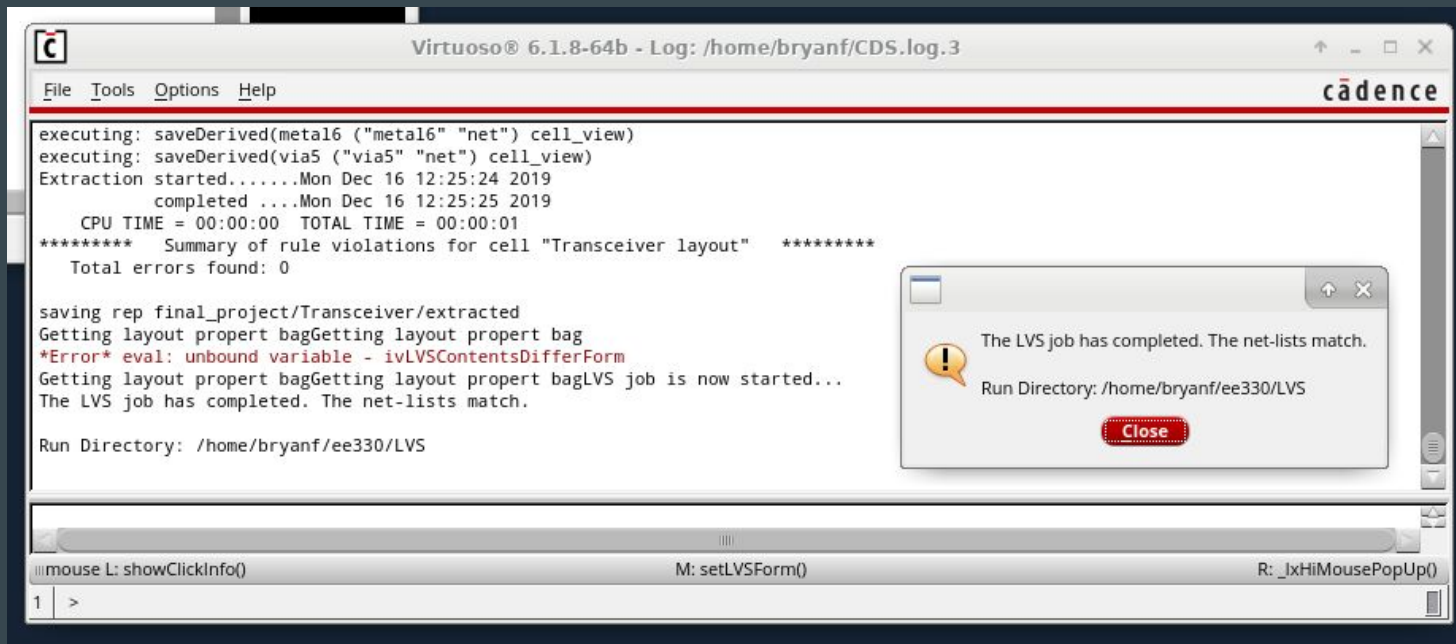

Proof of Concept for Pad Frame

