

Problem 1.

In on 0.5μ CMOS process,

$$V_{gs} = 3.5V, V_{th} = 0.79V, \frac{\mu_{COX}}{2} = \frac{57.8\mu s}{v^2}$$

$$R_{FET} = \frac{2V_{ds}}{2I_D} = \left[\mu_n * C_{OX} * \frac{W}{L} * (V_{gs} - V_T) \right]^{-1} = 3000$$

$$\frac{W}{L} = \frac{1}{3000 * (2 * 57.8 * 10^{-6}) * (3.5 - 0.79)} = 1.064$$

In the IBM 0.13 μ CMOS Process,

$$V_{gs} = 1.5V, V_{th} = 0.41V, \frac{\mu_{COX}}{2} = \frac{308.0\mu s}{v^2}$$

$$R_{FET} = \frac{2V_{ds}}{2I_D} = \left[\mu_n * C_{OX} * \frac{W}{L} * (V_{gs} - V_T) \right]^{-1} = 3000$$

$$\frac{W}{L} = \frac{1}{3000 * (2 * 308.0 * 10^{-6}) * (1.5 - 0.41)} = 0.496$$

Problem 2.

Minimum sized inverter:

$$V_{gs} = 1.5V, \text{ in IBM 0.13 } \mu \frac{W}{L} = \frac{0.16}{0.12}$$

$$C_{GSN} = (0.16)(0.12)(11176 * 10^{-18}) = 214.579aF$$

$$C_{ASP} = (0.16)(0.12)(10496 * 10^{-18}) = 201.523aF$$

$$C_L = C_{ASP} + C_{GSN} = 416.102aF = 0.416fF$$

$$\text{in ON 0.5}\mu: \frac{W}{L} = \frac{3.0}{0.6}$$

$$R_{SWN} = \left(\frac{2 * 57.8 * 10^{-6} * 3.0}{0.6} * (1.5 - 0.79) \right)^{-1} = 2.437k\Omega$$

$$R_{SWP} = \left(\frac{2 * -19.1 * 10^{-6} * 3.0}{0.6} * (-1.5 - 0.79) \right)^{-1} = 9.027k\Omega$$

$$\rightarrow T_{HL} = 2.437k * 416.102a = 1.014pS$$

$$T_{LH} = 9.027k * 416.102a = 3.756pS$$

Problem 3.

$$\left(\frac{1.8 - V_a}{1000} \right) = I_{D_1} + I_{D_2} = 200\mu^2 * \left(5 \frac{fA}{\mu^2} \right) e^{\left(\frac{x}{0.0259} \right)} \rightarrow V_a = 0.543V$$

$$I_{D_1} = 0.318mA ; I_{D_2} = 0.955 mA$$

Problem 4

$$\frac{10 - V_D}{4000} = I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{V_D}{0.0259}\right)} \rightarrow V_D = 0.618 V$$

$$I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.618}{0.0259}\right)} = 2.305 mA$$

Problem 5

$$\frac{0.520 - V_D}{4000} = I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * \left(e^{\left(\frac{V_D}{0.0259}\right)} - 1\right) \rightarrow V_D = 0.478 V$$

$$I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.478}{0.0259}\right)} = 10.356 \mu A$$

Problem 6

$$I_{D1} \sim I_{D2} = 200\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.5}{0.0259}\right)} \sim 200\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.6}{0.0259}\right)} = 48.43\mu A \sim 2.30 mA$$

Problem 7.

- $I_{D1} = \left(100 * 10^{-6} * \frac{8}{3 * 2} (3 - 1)^2\right) = 0.533 mA \rightarrow 5 - 4000 * 0.0006 = 2.87V$
- $I_{D2} = \left(100 * 10^{-6} * \left(\frac{12}{3}\right) * (2 - 1)^2\right) = 0.4 mA \rightarrow 5 - 30k * .4m = -7 \rightarrow$ Must not be in saturation region.
 $V_{DS} < V_{GS} - V_T \rightarrow$ Triode Region
 $\frac{(5 - V_{DS})}{30k} = 100 * 10^{-6} * \frac{12}{1.5} * \left(2 - 1 - \frac{V_{DS}}{2}\right) V_{DS}, (V_{GS} - V_T = 1V)$
 $V_{DS} = 0.224$ or $V_{DS} = 1.86$ as it is in triode region, $V_{out} = 0.224V$
- $I_{D3} = 33 * 10^{-6} * \frac{6}{6} * (2 - 1)^2 = 0.033 mA \rightarrow 5 - 5k * 0.033m = 4.835V$

Problem 8.

$$\frac{9 - V_{out}}{5000} = I_D = 100 * 10^{-6} * \frac{W}{2\mu * 2} (V_{out} - 1)^2 \rightarrow W = 0.96 \mu m$$

Problem 9

- a. Assuming Saturation, $V_{out} = x$

$$I_{D_1} = \mu C_{OX} \left(\frac{W}{2L} \right) (V_{GS} - V_T)^2 = 100 * 10^{-6} * \frac{6}{2 * 2} * (x - 1)^2 = 1.5 * 10^{-4} * (x - 1)^2$$

$$I_{D_2} = 100 * 10^{-6} * \left(\frac{2}{8 * 2} \right) * (6 - x - 1)^2 = 12.5 * 10^{-6} * (6 - x - 1)^2$$

$$I_{D_1} = I_{D_2} \rightarrow 1.5 * 10^{-4} (x - 1)^2 = 12.5 * 10^{-6} (6 - x - 1)^2 \rightarrow V_{out} = x = 1.896 V$$

- b. $V_{DG1} = 0 \rightarrow$ Saturation

$$\text{For } M_1, I_{SD} = \mu C_{OX} \left(\frac{W}{2L} \right) (V_{GS} - V_{TP})^2 = 33 * 10^{-5} * \left(\frac{8}{2 * 2} \right) (V_G - 10 - (-1))^2$$

$$\rightarrow 400 * 10^{-6} = 33 * 10^{-6} * \frac{8}{4} * (V_G - 9)^2 \rightarrow V_G = 6.54V \text{ or } 11.46V$$

$$\rightarrow V_{GS} = -3.46V \text{ or } 1.46V$$

$$\text{For } M_2, I_{SD} = \mu C_{OX} \left(\frac{W}{2L} \right) (V_{GS} - V_{TP})^2 = 33 * 10^{-6} * \left(\frac{12}{2 * 6} \right) (1.46 + 1)^2$$

$$I_{SD} = 200\mu A = I_{OUT}$$

$$\text{Check: } V_D = (1.5k * 200\mu) = 0.3V, V_{DS} = 0.3V - 10V = -9.7V$$

$$V_{GS} - V_{TP} = 1.46 + 1 = 2.46$$

$$V_{DS} < V_{GS} - V_{TP} \rightarrow \text{Saturation}$$

Problem 10.

- a) Saturation for M_1 and M_2

$$I_{D_1} = \frac{100 * 10^{-6}}{2} * \frac{W}{L} (3 - 1)^2 = I_{D_2} = 100 * 10^{-6} * \frac{8}{2 * 2} * (5 - 3.5 - 1)^2$$

$$\rightarrow \frac{\frac{W}{L}}{\frac{8}{2}} = \frac{1}{16} \rightarrow \frac{W}{L} = \frac{1}{4} \rightarrow W = 2\mu m, L = 8\mu m$$

- b) $V_{out} = 0.5V < V_{in} - 1V = 2V \rightarrow M_1$ is in triode region.

$$I_{D_1} = I_{D_2} = 100 * 10^{-6} * \frac{W}{L} * \left(3 - 1 - \frac{V_{out}}{2} \right) V_{out} = 100 * 10^{-6} * \left(\frac{8}{4} \right) * (5 - .5 - 1)^2$$

$$\rightarrow \frac{W}{L} = \frac{28}{1} \rightarrow W = 28\mu m, \quad L = 1\mu m$$

Problem 11.

$$A. \quad V_{OUT} = I(10k\Omega) + 0.575V, V_t = \frac{kT}{g}, I(T) = \left[J_{SX} \left(T^m e^{\frac{-V_{go}}{V_t}} \right) \right] A * e^{\frac{V_D}{V_t}}$$

$$A * J_{SX} \left[T^m e^{\frac{-V_{go}}{V_t}} \right] * e^{\frac{0.575}{V_t}} = \frac{0.5A}{\mu^2} * [1.63 * 10^{-18}] * 200\mu^2 * 287.19 * 10^9$$

$$V_{OUT} = 1.043V$$

- B. $V_{OUT} = 145V \rightarrow 20V$ (clipping)

- C. $V_{OUT} = 12.8kV \rightarrow 20V$ (clipping)

Problem 12.

Assuming saturation:

$$I_{D_1} = 33 * 10^{-6} * \frac{5}{2 * 5} * (5 - 3 - 1)^2 = I_{D_2} = 100 * 10^{-6} \left(\frac{5}{10} \right) (V_{out} - 1)^2$$

$$V_{out} = 1.5745V$$

Problem 13.

$$C = \frac{C_{j0} * A}{\left(1 - \frac{V_d}{\phi_b}\right)^n} \text{ where } \phi \approx 0.6V \text{ and } n \approx 0.5. \text{ At } V_b = 0 \text{ the denominator} \rightarrow 1, \text{ so } C_{j0}A = 500fF$$

$$\text{With } V_b = -4, C = \frac{500 * 10^{-15}}{\left(1 - \left(-\frac{4}{.6}\right)\right)^{0.5}} = 180.6fF$$

$$\text{With } V_b = 0.25V, C = \frac{500 * 10^{-15}}{\left(1 - \left(\frac{.25}{.6}\right)\right)^{0.5}} = 654.7fF$$

Problem 14.

- a) Since there's no protection circuitry the whole voltage will be applied to the IC.

$$\text{HBM1 } V_{INT} = 250V, \quad \text{HBM2 } V_{INT} = 2000V$$

- b) For HBM1 $V_D > V_{DD}$ so diode 2 is on

$$\frac{250 - V_{INT}}{10K} = I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{V_{INT}-5}{0.0259}\right)} \rightarrow V_{INT} = 5.918V$$

For HBM2 $V_D > V_{DD}$ so diode 2 is on

$$\frac{2000 - V_{INT}}{10K} = I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{V_{INT}-5}{0.0259}\right)} \rightarrow V_{INT} = 5.972V$$

- c) For HBM1 $I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{5.918-5}{0.0259}\right)} = 24.73mA$


$$\text{For HBM2 } I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{5.972-5}{0.0259}\right)} = 198.89mA$$

- d) The resistor reduces the current that flows through the diode. The disadvantage is it dissipates a lot of heat.

Problem 15.

$2.5 * 10^{-12} = \left(\frac{2 * 10^{-12}}{\left(1 - \left(\frac{V}{0.6}\right)^{0.5}\right)} \right) \rightarrow V = 0.216V$ so we can design a circuit that provides 0.216V when 4V is applied. This is easiest with a voltage divider. Using $1K\Omega$ as the resistor in series with the capacitor the resistor in parallel will be $0.216 = \frac{x}{1k+x} * 4 \rightarrow x = 57.081\Omega$

Problem 16.

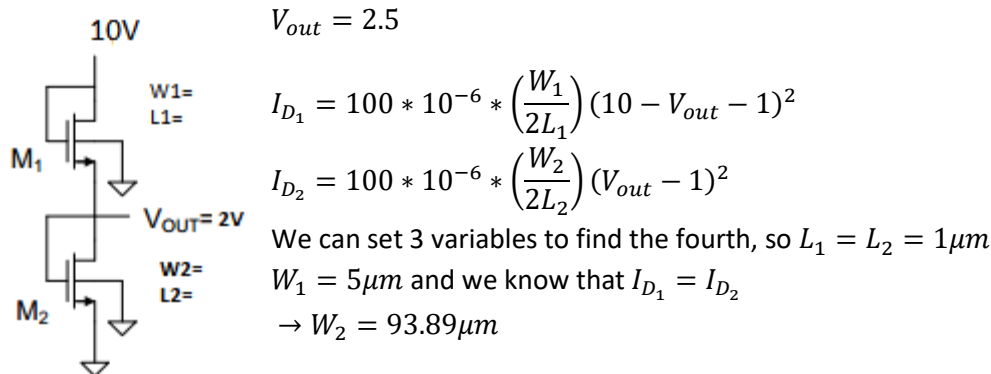

Problem 17.

Verilog Code:

Ln#	
1	
2	<code>`timescale 1ns/1ps</code>
3	
4	<code>module Full_Adder_1b(A, B, Cin, Sum, Cout);</code>
5	<code>input A, B, Cin;</code>
6	<code>output Sum, Cout;</code>
7	<code>reg AxorB, Sum, Cout;</code>
8	
9	<code>always @(A, B, Cin) begin</code>
10	<code>AxorB = A^B;</code>
11	<code>Sum <= AxorB^Cin;</code>
12	<code>Cout <= (Cin*AxorB) (A*B);</code>
13	<code>end</code>
14	
15	<code>endmodule</code>

Testbench:

Ln#	
1	
2	<code>`timescale 1ns/1ps</code>
3	
4	<code>module Full_Adder_1b_tb();</code>
5	<code> reg A, B, Cin;</code>
6	<code> wire S, Co;</code>
7	
8	<code> Full_Adder_1b test(.A(A), .B(B), .Cin(Cin), .Sum(S), .Cout(Co));</code>
9	
10	<code> initial begin</code>
11	<code> A = 0;</code>
12	<code> B = 0;</code>
13	<code> Cin = 0;</code>
14	<code> end</code>
15	
16	<code> always #10 A <= ~A;</code>
17	<code> always #20 B <= ~B;</code>
18	<code> always #40 Cin <= ~Cin;</code>
19	
20	<code>endmodule</code>
21	

Output:

