

Solve any 10 problems.

If references to a semiconductor processes are needed beyond what is given in a specific problem or question, assume a CMOS process is available with the following key process parameters;  $\mu_n C_{OX}=350\mu A/v^2$ ,  $\mu_p C_{OX}=70\mu A/v^2$ ,  $V_{TNO}=0.5V$ ,  $V_{TPO}= - 0.5V$ ,  $C_{OX}=8fF/\mu^2$ ,  $\lambda = 0$ ,  $\gamma = 0$ ,  $L_{MIN}=W_{MIN}=0.18\mu$ , and  $V_{DD}=2V$ .

**Problem 1**


A static CMOS inverter with  $W_n=W_p=2\mu$  and  $L_n=L_p=1\mu$  designed in a  $0.18\mu$  CMOS process is driving a  $4pF$  load. Determine  $t_{HL}$  and  $t_{LH}$  for the output of this inverter.

**Problem 2** If a semiconductor process were available with  $V_{Tn}=0.3V_{DD}$  and  $V_{Tp}= -0.1V$ , determine  $R_{pd}$ ,  $R_{pu}$ ,  $t_{HL}$ ,  $t_{LH}$ , and  $V_{trip}$  of a minimum-sized inverter if it is driving an  $8fF$  load. Assume  $\mu_n C_{OX}=350\mu A/v^2$ ,  $\mu_p C_{OX}=70\mu A/v^2$ , and  $V_{DD}=2V$ .

**Problem 3** In the same semiconductor process described in Problem 2, give a sizing strategy needed to place  $V_{trip}$  at  $V_{DD}/2$ .

**Problem 4** In the same semiconductor process described in Problem 2, give a sizing strategy needed to achieve  $t_{HL}=t_{LH}$ .

 **Problem 5** If the n-channel device is minimum sized ( $W_{min}=L_{min}=0.18\mu$ ), size the device  $M_2$  so that  $V_{TRIP}=V_{DD}/2$ . Assume that  $V_{DD}=2V$ ,




**Problem 6** Determine  $V_H$  and  $V_L$  for the inverter in Problem 5 using the sizing determined in that problem.

**Problem 7** Consider a two-input NOR gate sized for equal worst-case rise and fall times that is driving an identical device.

- Determine the trip points for all combinations of input transitions
- Determine the fastest and slowest  $t_{LH}$  for the output of the first gate in this cascade.

Problem 8 Size the devices in a 4-input NOR gate for equal worst-case rise and fall times.

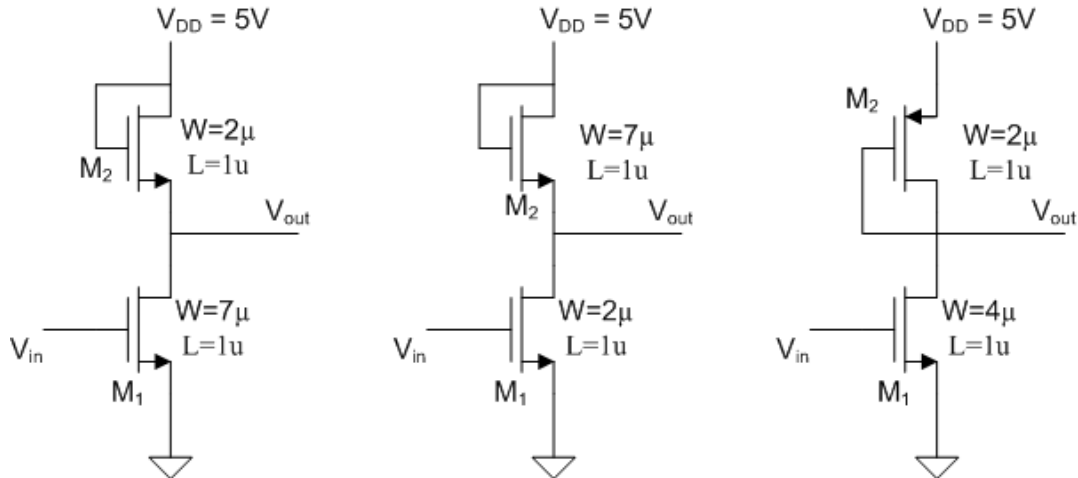
Problem 9 The circuits shown have been proposed as digital inverters. Determine which will behave as digital inverters and which will not. If the circuit performs as a digital inverter, determine  $V_H$  and  $V_L$ . Assume the devices are all in the process with  $\mu C_{ox} = 100 \mu A/V^2$ ,  $V_T = 1V$ ,  $\gamma = 0$  and  $\lambda = 0$ .




Problem 10 What is the maximum value of  $W_1$  in the circuit (a) of the previous problem that can be used if this circuit is to perform as a digital inverter?

 Problem 11 Determine the trip-point,  $V_H$ , and  $V_L$  of the inverter under the following scenarios and comment on how device dimensions affect these key characteristics. Assume  $\mu_n C_{ox} = 350 \mu A/V^2$ ,  $V_{Tn} = 0.5V$ ,  $V_{Tp} = -0.5V$ ,  $V_{DD} = 2V$ ,  $\mu_n/\mu_p = 5$ ,  $\gamma = 0$  and  $\lambda = 0$ .

- $W_1 = 0.18u$ ,  $W_2 = 0.9u$ ,  $L_1 = 0.18u$ ,  $L_2 = 0.18u$
- $W_1 = 3u$ ,  $W_2 = 15u$ ,  $L_1 = 3u$ ,  $L_2 = 3u$
- $W_1 = 0.18u$ ,  $W_2 = 0.18u$ ,  $L_1 = 0.18u$ ,  $L_2 = 0.18u$
- $W_1 = 0.18u$ ,  $W_2 = 0.54u$ ,  $L_1 = 0.18u$ ,  $L_2 = 1.8u$



 Problem 12 Four different implementations of the 8-input NAND function are shown. If the devices are sized for equal worst-case rise and fall times, compare the input capacitance at each input and the total area for these 4 different implementations




Problem 13 Assume a load capacitance of 40fF is to be driven. Determine  $t_{HL}$  and  $t_{LH}$  if it is driven by an equal rise/fall inverter (termed the reference inverter) and if it is driven by a minimum-sized inverter.


Problem 14 Assume a 4-input NAND gate, sized for equal worst-case rise and fall times, is driving 10 equal worst-case rise and fall time inverters (termed reference inverters).

- Determine  $t_{HL}$  and  $t_{LH}$  if the switch-level model is used for the MOS transistors.
- Repeat part a) using the Elmore delay model if there is a parasitic capacitance on each drain and source diffusion of 400Af.

 Problem 15 Determine the propagation delay ( $t_{HL}+t_{LH}$ ) from B to F for the following circuit. Assume all devices sized for equal worst-case rise and fall times.




 Problem 16 Three different circuits are shown driving the same load. The overdrive factors if different than 1 are indicated. Quantitatively compare the propagation delay of these circuits.




 Problem 17 A logic circuit designed in conventional CMOS is shown. Assume all gates are sized for equal worst-case rise and fall times and that the input capacitance of an equal rise/equal fall reference inverter is 1.5fF and that it has a propagation delay ( $T_{HL} + T_{LH}$ ) of 20psec. The overdrive factor, if different than 1, is indicated by the number on the gate symbol.

- Determine the propagation delay ( $T_{HL} + T_{LH}$ ) from the D input to the H output
- Repeat part a) if all devices are minimum sized (the overdrive factor is no longer germane). Assume the input capacitance to the reference inverter is now 0.8fF.



 - Size the devices in the 3-input NAND gate for an overdrive of 6 and the 2-input NOR gate for an overdrive of 3 with the equal rise/fall sizing strategy. The overdrive factors for the inverters are indicated.
- With this sizing, how does the propagation delay from B to G compare to that of a minimum-sized reference inverter driving an identical device?



Problem 20 Assume you are working in a 1u CMOS process (assume  $L_{min} = W_{min} = 1\mu$ ) with  $V_{DD} = 5V$ ,  $V_{TN} = 1.5V$ ,  $V_{TP} = -.5V$ ,  $C_{OX} = 1fF/u^2$  and  $\mu C_{OX} = 100\mu A/V^2$ .

- Problem 21** The overdrive factors on each gate are as indicated. The M indicates minimum sizing. If nothing is indicated, assume sizing for equal worst-case rise and fall times. Determine the propagation delay from A to F in terms of  $t_{REF}$  for the process.

