

EE 330
Homework Assignment 2
Spring 2018 Due Friday Jan 19

On this and subsequent HW assignments there will be problems that require a Verilog or VHDL solution. It will be assumed that students either have a background in Verilog or VHDL or that they will study what is needed to develop this background. There are numerous sources for material on Hardware Description Languages available on line. The text for the course also has a short discussion on HDL in Sec. 1.8 and a more extensive discussion in Appendix A.

Problem 1 1.1 of Weste and Harris (WH) but project to 2020 instead of to 2016.

Problem 2 1.5 of WH but for a 3-input NOR gate instead.

Problem 3 Assume a 300mm wafers cost \$3200. If the defect density on this wafer is $1.4/\text{cm}^2$, determine the cost per good die if the die is square with a side dimension of 3.5 mm. Assume the soft yield is 100%.

Problem 4 Assume the specified offset voltage for each of the 2 amplifiers in a “dual” op amp is 3mV (that is, $|V_{OS}| < 3\text{mV}$). Determine the soft yield for the “dual” op amp integrated circuit if the standard deviation of the offset voltage for each op amp is 1.5 mV and the mean is 0V. Assume the offset voltage for each of the 2 amplifiers are uncorrelated and that the distribution of the offset voltages are Gaussian.

Problem 5 Assume the offset voltage of an operational amplifier is a random variable and that the input offset voltage has a Gaussian distribution with a mean of 0V and a

standard deviation of $\sigma = \frac{A_{VT0}}{\sqrt{A}}$ where A is the gate area of two input transistors of

the op amp and $A_{VT0} = 20\text{mV}\mu\text{m}$ (the units are mV times a micrometer). Determine the area required for the two input transistors if the input offset voltage is to be at most 1mV if a soft yield of 98% is required.

Problem 6 Assume a particular function in a 65nm process being used today requires a die area of 0.5cm^2 and that it is fabricated on 300mm wafers that cost \$3200. Predictions now suggest that in a few years, high-end processes will have 7nm feature sizes on 450mm wafers. If the 450mm wafers cost \$8000 each, what will be the approximate cost per good die of the same function if fabricated in the new high-end process with feature sizes of 7nm? When solving this problem, assume the circuit schematic does not change but the transistor sizes scale with the feature size. Neglect the bonding pad areas. Assume the defect density in both processes is the same and is $1.25/\text{cm}^2$ and that the soft yield is 100%.

- b) Describe what Data Sequence 2 represents
- c) What does the term “open-drain” mean?
- d) The I²C protocol is noted for not having logic contention. What does this mean?
- e) Why can devices with modestly different logic levels coexist on the same I²C bus?

Problem 10 Create in Verilog the following Boolean function. Use only the NOR gate you created in the last homework assignment. Create a test bench to test the Boolean function. Include screenshots of your Verilog code and simulation results.

$$F = \bar{A} \cdot B + A \cdot \bar{B}$$

(The + symbol denotes the Boolean “OR” operation and the • symbol denotes the Boolean “AND” operation. In future designations of Boolean operations, the “•” symbol will be suppressed and the same function F will be designated as $F = \bar{A}B + A\bar{B}$).

Do not solve this problem

Problem 9 and 10 MTV is looking to streamline its production of *Jersey Shore* and has hired you to build a scene sorter. The sorter will have three inputs which MTV feels are crucial to the success of the show:

- Fist pumping (Input FIST)
- GTL (Input GTL)
- Snooki (Input SNOOKI)

The inputs will be Boolean high if the scene contains one of the inputs and low if it does not. It also has three outputs deciding where the scene will be shown:

- Both the episode and the previews (Output PREVIEW)
- Just the episode (Output EPISODE)
- Not used (Output GARBAGE)

If the scene contains two of the three inputs it will be used in the episode. If it contains all three, it will also be used in the preview. If it contains one or less it is not up to MTV's high journalistic standards and will not be used. Boolean high output will represent use in the show. Only one output should be high for a given scene. Design a scene sorter in Verilog with these three inputs and outputs. Demonstrate its correct function with proper simulation.

Problem 7 Design a Verilog system with inputs A, B, and C, and outputs F and G given below. Demonstrate the proper functioning of your circuit with full simulation. Do not simplify the equations.

$$F = ABC + \overline{AC}$$

$$G = AC$$