

EE 330

Lecture 40

Digital Circuits

Ratio Logic





Other MOS Logic Families

Propagation Delay – basic characterization

Device Sizing (Inverter and multiple-input gates)

Review from last lecture

 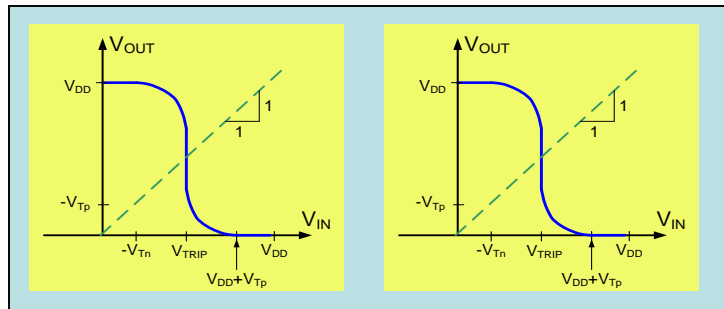 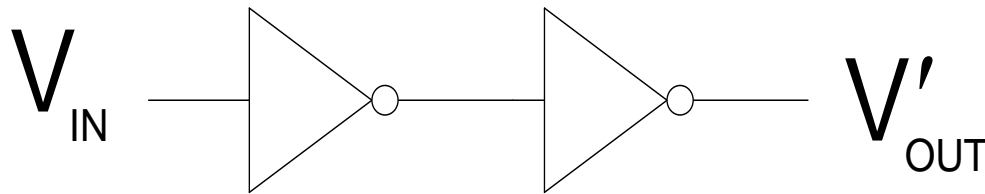Inverter Transfer Characteristics of Inverter Pair for THIS Logic Family




$$V_H = V_{DD} \text{ and } V_L = 0$$

Note this is independent of device sizing for THIS logic family !!

Review from last lecture

Transfer characteristics of the static CMOS inverter

(Neglect λ effects)

 

From Case 3 analysis:

$$V_{IN} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}$$


Correction from Last Lecture

Transfer characteristics of the static CMOS inverter

(Neglect λ effects)

Equations were correct but sketch was not a parabola

Case 2 M_1 triode, M_2 sat

 


Correction from Last Lecture

Transfer characteristics of the static CMOS inverter (Neglect λ effects)

Case 2 M_1 triode, M_2 sat

 Results correctly
shown in region of
relevance



$$V_{OUT} - V_{DD} \leq V_{IN} - V_{DD} - V_{Tp}$$

$$V_{IN} \geq V_{Tn}$$

$$V_{OUT} < V_{IN} - V_{Tn}$$


$$V_{IN} - V_{DD} \leq V_{Tp}$$

Correction from Last Lecture

Transfer characteristics of the static CMOS inverter (Neglect λ effects)

Results for Case 2 were correct!

Case 2 M_1 triode, M_2 sat

 


Correction from Last Lecture

Transfer characteristics of the static CMOS inverter

(Neglect λ effects)

Equations were correct but sketch was not a parabola

Case 4 M_1 sat, M_2 triode

 


Correction from Last Lecture

Transfer characteristics of the static CMOS inverter (Neglect λ effects)

Case 4 M_1 sat, M_2 triode

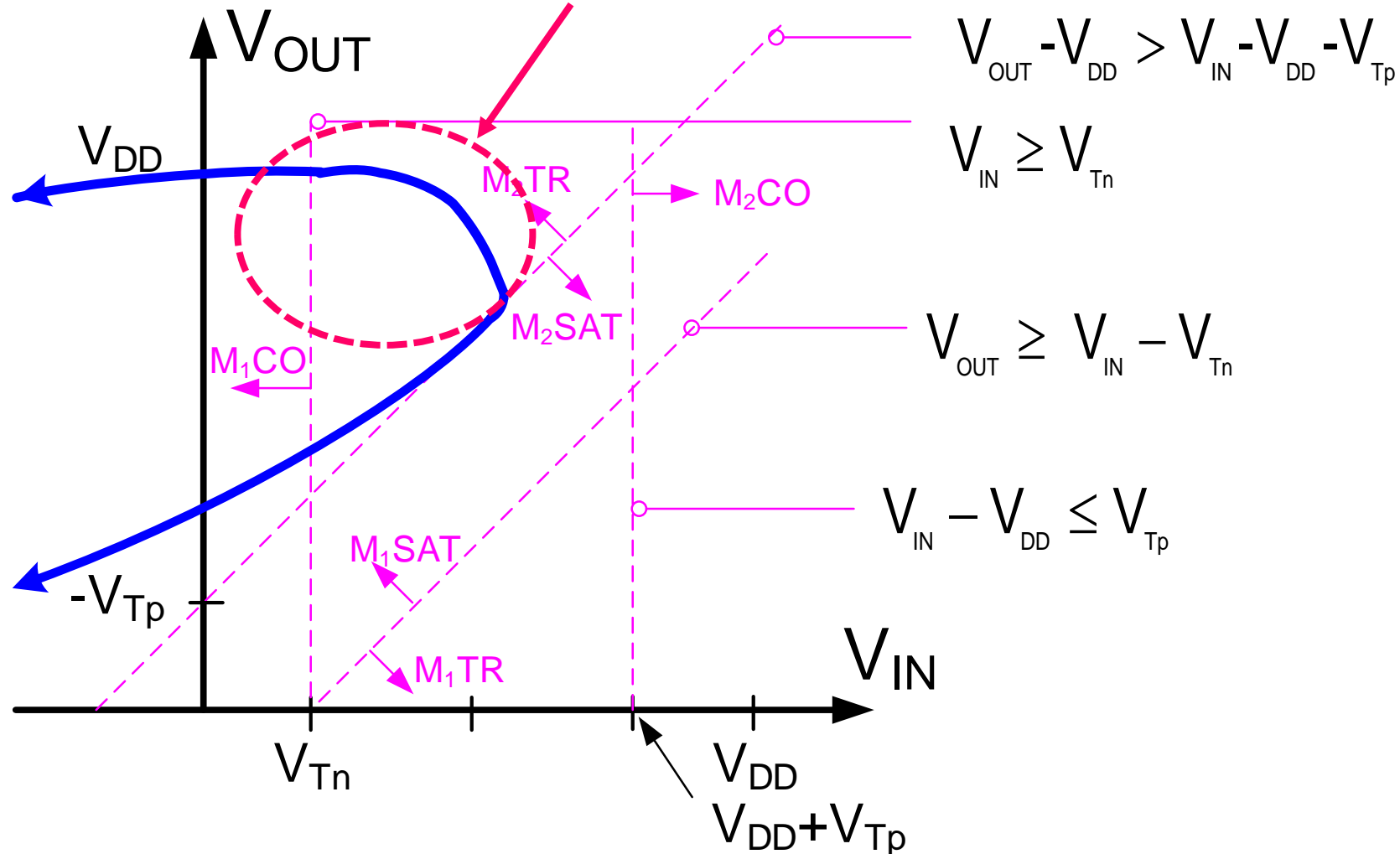Results correctly
shown in region of
relevance




Correction from Last Lecture

Transfer characteristics of the static CMOS inverter

(Neglect λ effects)

Results for Case 4 were correct!

Case 4 M_1 sat, M_2 triode

 

$$V_{OUT} - V_{DD} > V_{IN} - V_{DD} - V_{Tp}$$

$$V_{IN} \geq V_{Tn}$$

$$V_{OUT} \geq V_{IN} - V_{Tn}$$

$$V_{IN} - V_{DD} \leq V_{Tp}$$

Review from last lecture

How should M_1 and M_2 be sized?


pick $L_1=L_2=L_{\min}$

One popular sizing strategy:

1. Pick $W_1=W_{\min}$ to minimize area of M_1

 
2. Pick W_2 to set trip-point at $V_{DD}/2$

Observe Case 3 provides expression for V_{TRIP}



Thus, at the trip point,
 
$$V_{\text{OUT}} = V_{\text{IN}} = V_{\text{TRIP}} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1}}}$$
$$= \frac{V_{DD}}{2}, \quad \text{if } \frac{W_2}{W_1} = \frac{\mu_n}{\mu_p}$$



Other sizing strategies will be discussed later !

Digital Circuit Design


- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
 - Ratio Logic
 - Propagation Delay
 - – Simple analytical models
 - Elmore Delay
- Sizing of Gates
 - The Reference Inverter

- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- Power Dissipation in Logic Circuits
- Other Logic Styles
- Array Logic
- Ring Oscillators

→ **done**

→ **partial**


General Logic Family

 

Compound Gate in CMOS Process


p-channel PUN
n-channel PDN

 $V_H = V_{DD}$, $V_L = 0V$ (same as for inverter!)




**Arbitrary PUN
and PDN**


Other MOS Logic Families

 

Enhancement Load
NMOS


 


Enhancement Load
Pseudo-NMOS

 


Depletion Load
NMOS

Other CMOS/MOS Logic Families

  


NMOS example

 


Enhancement
Load NMOS

V_{TH}	1
$W1/L1$	4
$W2/L2$	1
V_{DD}	5


Inverter

 

Inverter Pair

 


NMOS example

 

V_{TH}		1
W_1/L_1		4
W_2/L_2		1
V_{DD}		5

Inverter Pair


 


$$V_H = 4V$$

$$V_L = 0.55V$$

$$V_{TRIP} = 2V$$


Other CMOS/MOS Logic Families

  


- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when V_{OUT} is low (will sl
- Very economical process
- Termed “ratio logic” (because logic values dependent on device W/L ratios – USE UP DOF!)
- May not work for some device sizes
- Compact layout (no wells !)
- Available to use in standard CMOS proces




Other CMOS/MOS Logic Families

 

Enhancement
Load NMOS

 

k -input NOR

 

k -input NAND



- Multiple-input gates require single transistor for each additional input



- Still useful if many inputs are required
(will be shown that static power does not increase with k)





Other CMOS/MOS Logic Families

  

- High and low swings are reduced
- Response time is slow on LH output transitions
- Static Power Dissipation Large when V_{OUT} is low
- Multiple-input gates require single transistor for each additional input
- Termed “ratio” logic
- Available to use in standard CMOS process







Other CMOS/MOS Logic Families

 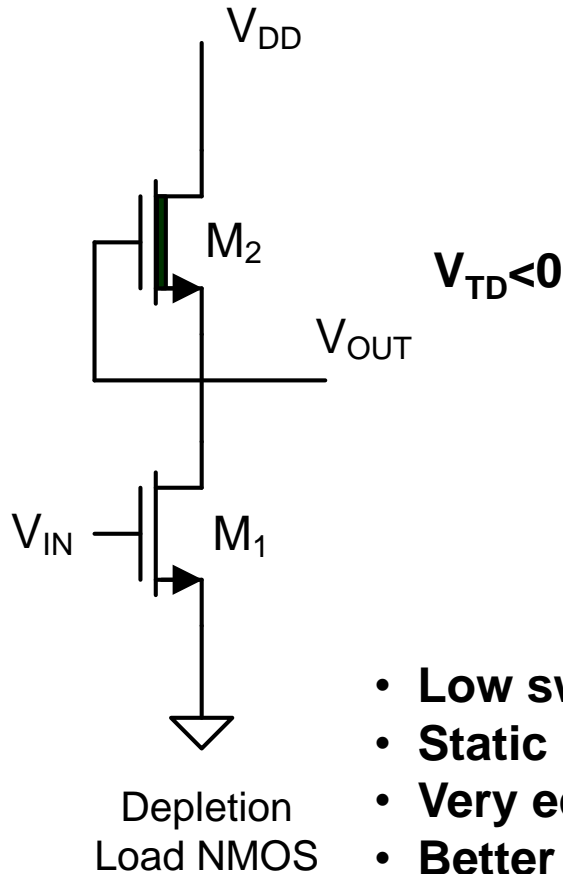





- Low swing is reduced 😞
- Static Power Dissipation Large when V_{OUT} is low 😞
- Very economical process 😊
- Better than Enhancement Load NMOS
- Termed “ratio” logic
- Compact layout (no wells !) 😊
- Response time slow on L-H output transitions 😞
- Dominant MOS logic until about 1985
- Depletion device not available in most processes today 😞

Other CMOS/MOS Logic Families

    





- **Reduced $V_H - V_L$**
- **Device sizing critical for even basic operation**
- **Shallow slope at V_{TRIP}**

Other CMOS/MOS Logic Families

    

- **Reduced $V_H - V_L$**
- **Device sizing critical for even basic operation (DOF)**
- **Shallow slope at V_{TRIP}**

Other CMOS/MOS Logic Families

   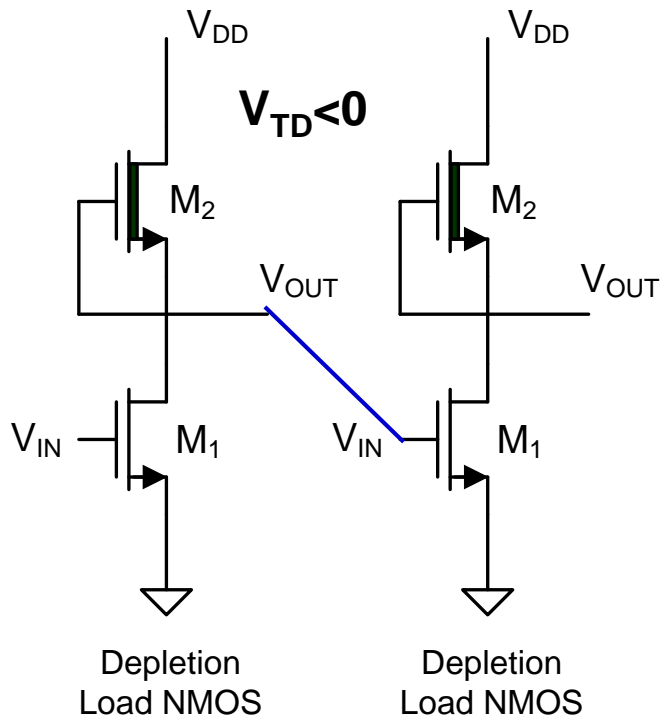

- Reduced $V_H - V_L$
- Device sizing critical for even basic operation
- Shallow slope at V_{TRIP}


Digital Circuit Design

- Hierarchical Design
 - Basic Logic Gates
 - Properties of Logic Families
 - Characterization of CMOS Inverter
 - Static CMOS Logic Gates
 - Ratio Logic
 - Propagation Delay
 - Simple analytical models
 - Elmore Delay
 - Sizing of Gates
 - The Reference Inverter
- Propagation Delay with Multiple Levels of Logic
 - Optimal driving of Large Capacitive Loads
 - • Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

→ **done**

→ **partial**

 Static Power Dissipation in Static CMOS Family




When V_{IN} is Low and V_{OUT} is High, M_1 is off and $I_{D1}=0$

When V_{IN} is High and V_{OUT} is Low, M_2 is off and $I_{D2}=0$

Thus, $P_{STATIC}=0$

 This is a key property of the static CMOS Logic Family → the major reason Static CMOS Logic is so dominant




It can be shown that this zero static power dissipation property can be preserved if the PUN is comprised of p-channel devices, the PDN is comprised of n-channel devices and they are never both driven into the conducting states at the same time

Compound Gate in CMOS Process

Static Power Dissipation in Ratio Logic Families

Example:

 

Assume $V_{DD}=5V$

$V_T=1V$, $\mu C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that V_L is close to V_{Tn}

Observe:

$$V_H = V_{DD} - V_{Tn}$$

If $V_{IN}=V_H$, $V_{OUT}=V_L$ so


$$I_{D1} = \frac{\mu C_{OX} W_1}{L_1} \left(V_{GS1} - V_T - \frac{V_{DS1}}{2} \right) V_{DS1}$$

$$I_{D1} = 10^{-4} \left(5 - 1 - 1 - \frac{1}{2} \right) \cdot 1 = 0.25mA$$

$$P_L = (5V)(0.25mA) = 1.25mW$$

Static Power Dissipation in Ratio Logic Families

Example:

 

Assume $V_{DD}=5V$


$V_T=1V$, $\mu C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that V_L is close to V_{Tn}

$$P_L=(5V)(0.25mA)=1.25mW$$

If a circuit has 100,000 gates and half of them are in the $V_{OUT}=V_L$ state, the static power dissipation will be

Static Power Dissipation in Ratio Logic Families

Example:

 

Enhancement
Load NMOS

Assume $V_{DD}=5V$

$V_T=1V$, $\mu C_{OX}=10^{-4}A/V^2$, $W_1/L_1=1$ and M_2 sized so that V_L is close to V_{Tn}

$$P_L=(5V)(0.25mA)=1.25mW$$

If a circuit has 100,000 gates and half of them are in the $V_{OUT}=V_L$ state, the static power dissipation will be

$$P_{STATIC} = \frac{1}{2} 10^5 \bullet 1.25mW = \mathbf{62.5W}$$

This power dissipation is way too high and would be even larger in circuits with 100 million or more gates – the level of integration common in SoC circuits today

Digital Circuit Design

- Hierarchical Design
- Basic Logic Gates
- Properties of Logic Families
- Characterization of CMOS Inverter
- Static CMOS Logic Gates
 - – Ratio Logic
- Propagation Delay
 - – Simple analytical models
 - – Elmore Delay
- Sizing of Gates
 - – The Reference Inverter


- Propagation Delay with Multiple Levels of Logic
- Optimal driving of Large Capacitive Loads
- • Power Dissipation in Logic Circuits
- Other Logic Styles
- Array Logic
- Ring Oscillators

→ **done**

→ **partial**

Propagation Delay in Static CMOS Family


(Review from earlier discussions)

 

Switch-level model of Static CMOS inverter (neglecting diffusion parasitics)

Propagation Delay in Static CMOS Family


(Review from earlier discussions)

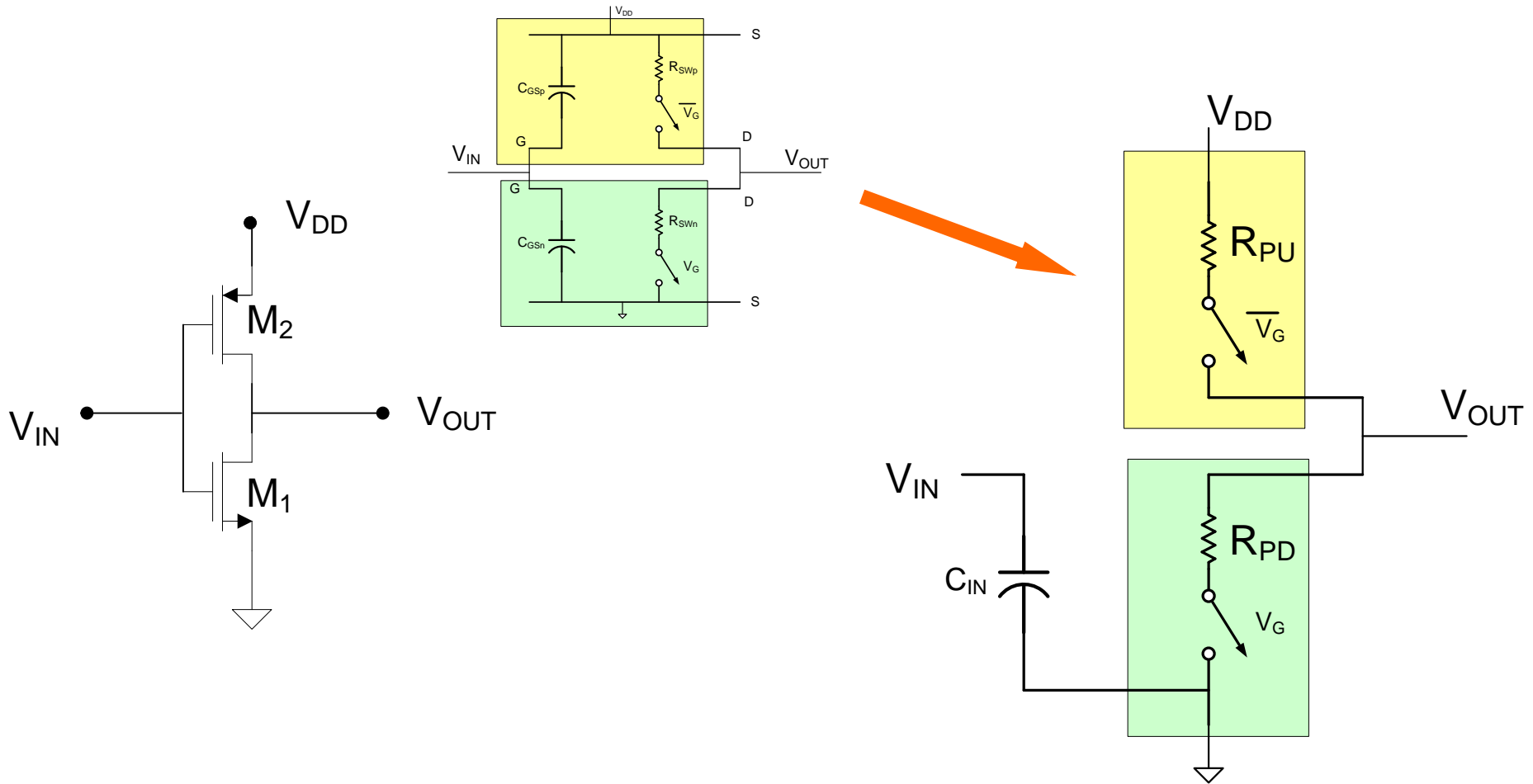

Switch-level model of Static CMOS inverter (neglecting diffusion parasitics)

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

 

Since operating in triode through most of transition:


$$I_D \cong \frac{\mu C_{ox} W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \cong \frac{\mu C_{ox} W}{L} (V_{GS} - V_T) V_{DS}$$

$$R_{PD} = \frac{V_{DS}}{I_D} = \frac{L_1}{\mu_n C_{ox} W_1 (V_{DD} - V_{Tn})}$$

$$I_D = \frac{\mu C_{ox} W}{L} \left(V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \cong \frac{\mu C_{ox} W}{L} (V_{GS} - V_T) V_{DS}$$



$$R_{PU} = \frac{V_{DS}}{I_D} = \frac{L_2}{\mu_p C_{ox} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{ox} (W_1 L_1 + W_2 L_2)$$

 

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

  

$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})}$$

$$R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

Example: Minimum-sized M_1 and M_2

If $\mu_n C_{OX} = 100 \mu A V^{-2}$, $C_{OX} = 4 \text{ fF} \mu^{-2}$, $V_{Tn} = V_{DD}/5$, $V_{Tp} = -V_{DD}/5$, $\mu_n/\mu_p = 3$, $L_1 = W_1 = L_{MIN}$, $L_2 = W_2 = L_{MIN}$, $L_{MIN} = 0.5 \mu$ and $V_{DD} = 5V$

(Note: This C_{OX} is somewhat larger than that in the 0.5u ON process)




$$R_{PD} = \frac{1}{10^{-4} \cdot 0.8 V_{DD}} = 2.5 K\Omega$$

$$C_{IN} = 4 \cdot 10^{-15} \cdot 2 L_{MIN}^2 = 2 \text{ fF}$$

$$R_{PU} = \frac{1}{10^{-4} \cdot \frac{1}{3} \cdot 0.8 V_{DD}} = 7.5 K\Omega$$

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

   

In typical process with **Minimum-sized M_1 and M_2** :


$$R_{PD} \cong 2.5K\Omega$$

$$R_{PU} \cong 3R_{PD} = 7.5K\Omega$$

$$C_{IN} \cong 2fF$$

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

 


In typical process with **Minimum-sized M_1 and M_2** :

$$R_{PD} \cong 2.5K\Omega$$

$$R_{PU} \cong 3R_{PD} = 7.5K\Omega$$

$$C_{IN} \cong 2fF$$

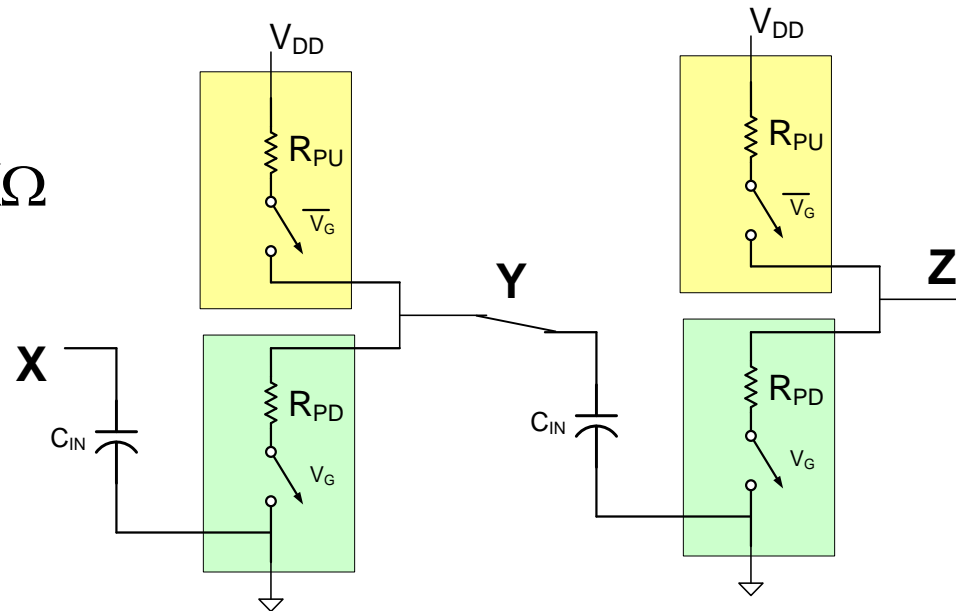


How long does it take for a signal to propagate from x to y?

Propagation Delay in Static CMOS Family


(Review from earlier discussions)

Consider:

 For HL output transition, C_L charged to V_{DD}




Ideally:

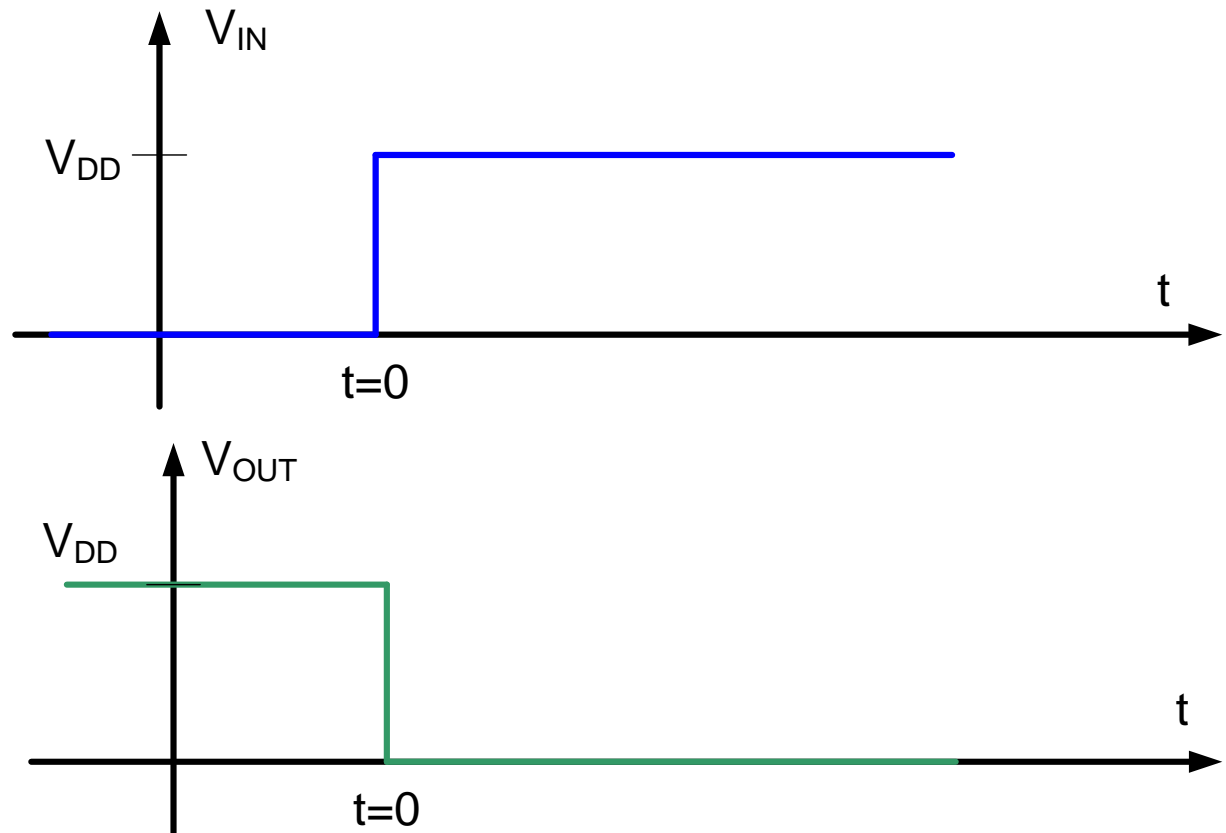


Propagation Delay in Static CMOS Family

(Review from earlier discussions)

 For HL output transition, C_L charged to V_{DD}





Actually:

 

What is the transition time t_{HL} ?

Propagation Delay in Static CMOS Family




(Review from earlier discussions)

  

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

   For HL output transition, C_L charged to V_{DD}



$$V_{OUT}(t) = F + (I - F)e^{\frac{-t}{\tau}} = 0 + (V_{DD} - 0)e^{\frac{-t}{R_{PD}C_L}}$$

$$\frac{V_{DD}}{e} = V_{DD}e^{\frac{-t_1}{R_{PD}C_L}}$$





$$t_1 = R_{PD}C_L$$

If V_{TRIP} is close to $V_{DD}/2$, t_{HL} is close to t_1

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

    For HL output transition, C_L charged to V_{DD}



$$t_{LH} \cong t_2 = R_{PU} C_L$$



Summary: $t_{LH} \cong R_{PU} C_L$

$$t_{HL} \cong R_{PD} C_L$$

For V_{TRIP} close to $V_{DD}/2$

Propagation Delay in Static CMOS Family

(Review from earlier discussions)

  

In typical process with **Minimum-sized M_1 and M_2** :

$$t_{HL} \cong R_{PD}C_L \cong 2.5K \cdot 2fF = 5ps$$

$$t_{LH} \cong R_{PU}C_L \cong 7.5K \cdot 2fF = 15ps$$

(Note: This C_{ox} is somewhat larger than that in the 0.5u ON process)

Note: LH transition is much slower than HL transition


Propagation Delay in Static CMOS Family

Defn: The Propagation Delay of a gate is defined to be the sum of t_{HL} and t_{LH} , that is, $t_{PROP} = t_{HL} + t_{LH}$

$$t_{PROP} = t_{HL} + t_{LH} \cong C_L (R_{PU} + R_{PD})$$

Propagation delay represents a fundamental limit on the speed a gate can be clocked

 For basic two-inverter cascade in static 0.5um CMOS logic



Propagation Delay in Static CMOS Family

$$t_{PROP} = t_{HL} + t_{LH} \cong C_L (R_{PU} + R_{PD})$$

$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})} \quad R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})} \quad C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

$$\text{If } V_{Tn} = -V_{Tp} = V_T$$

$$t_{PROP} = C_{OX} (W_1 L_1 + W_2 L_2) \left(\frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_T)} + \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} - V_T)} \right)$$

$$\text{If } L_2 = L_1 = L_{min}, \mu_n = 3\mu_p,$$

$$t_{PROP} = \frac{L_{min}^2}{\mu_n (V_{DD} - V_T)} (W_1 + W_2) \left(\frac{1}{W_1} + \frac{3}{W_2} \right) = \frac{L_{min}^2}{\mu_n (V_{DD} - V_T)} \left(4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

Note speed is a function of device sizing !

Can t_{PROP} be minimized?

Propagation Delay in Static CMOS Family

For $L_2 = L_1 = L_{\min}$, $\mu_n = 3\mu_p$,

$$t_{PROP} = \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} \left(4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

Can t_{PROP} be minimized?

Assume $W_1 = W_{\min}$

$$\frac{\partial t_{PROP}}{\partial W_2} = \left[\frac{L_{\min}^2}{\mu_n (V_{DD} - V_{TH})} \right] \left[\frac{1}{W_{\min}} - 3 \frac{W_{\min}}{W_2^2} \right] = 0$$

$$\frac{1}{W_{\min}} - 3 \frac{W_{\min}}{W_2^2} = 0$$

$$W_2 = \sqrt{3} W_{\min}$$

$$t_{PROP} = \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} (4 + 2\sqrt{3}) \cong \frac{L_{\min}^2}{\mu_n (V_{DD} - V_T)} (7.5) \quad (7.5)$$

Propagation Delay in Static CMOS Family

$$t_{PROP} = t_{HL} + t_{LH} \cong C_L (R_{PU} + R_{PD})$$

$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})} \quad R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})} \quad C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$

If $V_{Tn} = -V_{Tp} = V_T$

$$t_{PROP} = C_{OX} (W_1 L_1 + W_2 L_2) \left(\frac{L_1}{m_n C_{OX} W_1 (V_{DD} - V_T)} + \frac{L_2}{m_p C_{OX} W_2 (V_{DD} - V_T)} \right)$$

If $L_2 = L_1 = L_{min}$, $m_n = 3m_p$,

$$t_{PROP} = \frac{L_{min}^2}{m_n (V_{DD} - V_T)} (W_1 + W_2) \left(\frac{1}{W_1} + \frac{3}{W_2} \right) = \frac{L_{min}^2}{m_n (V_{DD} - V_T)} \left(4 + \frac{W_2}{W_1} + 3 \frac{W_1}{W_2} \right)$$

For min size:

$$W_2 = W_1 = W_{min}$$

$$t_{PROP} = \frac{8L_{min}^2}{m_n (V_{DD} - V_T)}$$

For equal rise/fall:

$$W_2 = 3W_1$$

$$t_{PROP} = \frac{8L_{min}^2}{m_n (V_{DD} - V_T)}$$

For min delay:

$$W_2 = \sqrt{3}W_1 \quad (4 + 2\sqrt{3}) \cong 7.5$$


$$t_{PROP} = \frac{(4 + 2\sqrt{3})L_{min}^2}{m_n (V_{DD} - V_T)}$$

Approximate BSIM values

process	Lmin	u	VT	VDD	Wmin
500	600	34	0.7	5	900
180	180	35	0.4	1.8	180
130	130	59	0.33	1.3	130
90	100	55	0.26	1.1	100
65	65	49	0.22	1	65
45	45	44	0.22	0.9	45

For min L transistors, mobility will saturate as field strength reaches a certain level.


Propagation Delay in Static CMOS Family

 

The propagation delay through k levels of logic is approximately the sum of the individual delays in the same path

Propagation Delay in Static CMOS Family

Example:

 

$$t_{HL} = t_{HL4} + t_{LH3} + t_{HL2} + t_{LH1}$$


$$t_{LH} = t_{LH4} + t_{HL3} + t_{LH2} + t_{HL1}$$

$$t_{PROP} = t_{LH} + t_{HL} = (t_{LH4} + t_{HL3} + t_{LH2} + t_{HL1}) + (t_{HL4} + t_{LH3} + t_{HL2} + t_{LH1})$$

$$t_{PROP} = t_{LH} + t_{HL} = (t_{LH4} + t_{HL4}) + (t_{LH3} + t_{HL3}) + (t_{LH2} + t_{HL2}) + (t_{LH1} + t_{HL1})$$

$$t_{PROP} = t_{PROP4} + t_{PROP3} + t_{PROP2} + t_{PROP1}$$

Propagation Delay in Static CMOS Family

 

Propagation through k levels of logic

$$t_{HL} \cong t_{HLk} + t_{LH(k-1)} + t_{HL(k-2)} + \dots + t_{XY1}$$

$$t_{LH} \cong t_{LHk} + t_{HL(k-1)} + t_{LH(k-2)} + \dots + t_{YX1}$$

where x=H and Y=L if k odd and X=L and Y=h if k even

$$t_{PROP} = \sum_{i=1}^k t_{PROP_i}$$

Will return to propagation delay after we discuss device sizing

Digital Circuit Design

- Hierarchical Design
 - Basic Logic Gates
 - Properties of Logic Families
 - Characterization of CMOS Inverter
 - Static CMOS Logic Gates
 - Ratio Logic
 - Propagation Delay
 - Simple analytical models
 - Elmore Delay
 - Sizing of Gates
 - The Reference Inverter
- Propagation Delay with Multiple Levels of Logic
 - Optimal driving of Large Capacitive Loads
 - • Power Dissipation in Logic Circuits
 - Other Logic Styles
 - Array Logic
 - Ring Oscillators

→ **done**

→ **partial**

Question:

?

?

?

?

?

Why is $|V_{Tp}| \approx V_{Tn} \approx V_{DD}/5$ in many processes ?



?

?

?

?


Device Sizing

  


Strategies?

Degrees of Freedom?

Will consider the inverter first

 

Device Sizing

 


Degrees of Freedom?

Strategies?

Device Sizing

 - Since not ratio logic, V_H and V_L are independent of device sizes for this inverter
- With $L_1=L_2=L_{\min}$, there are 2 degrees of freedom (W_1 and W_2)



Sizing Strategies


- Minimum Size
- Fixed V_{TRIP}
- Equal rise-fall times
(equal worst-case rise and fall times)
- Minimum power dissipation
- Minimum time required to drive a given load
- Minimum input capacitance

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing Strategy: minimum sized

 $W_n=?$, $W_p=?$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$



$$R_{PD} = \frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})}$$

$$R_{PU} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

$$C_{IN} = C_{OX} (W_1 L_1 + W_2 L_2)$$


Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing Strategy: minimum sized

$W_n=?$, $W_p=?$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$

$$W_1=W_2=W_{MIN}$$

 

also provides minimum input capacitance

$$t_{HL}=R_{PD}C_L$$

$$t_{LH}=3 R_{PD}C_L$$

t_{LH} is longer than t_{HL}

$$t_{PROP}=4R_{PD}C_L$$

$$V_{TRIP} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}$$


$$V_{TRIP} = \frac{(0.2V_{DD}) + (V_{DD} - 0.2V_{DD}) \sqrt{\frac{1}{3}}}{1 + \sqrt{\frac{1}{3}}} = .42V_{DD}$$

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing strategy: Equal (worst case) rise and fall times

 $W_n=?$, $W_p=?$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$




$$R_{PD} = \frac{L_{min}}{\mu_n C_{OX} W_1 (0.8V_{DD})}$$

$$R_{PU} = \frac{L_{min}}{3\mu_n C_{OX} W_2 (0.8V_{DD})}$$

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

 Sizing strategy: Equal (worst case) rise and fall times



$$\frac{t_{LH}}{t_{HL}} = \frac{R_{PU}C_{IN}}{R_{PD}C_{IN}} \Rightarrow R_{PU}=R_{PD}$$

Thus
$$\frac{L_1}{\mu_n C_{OX} W_1 (V_{DD} - V_{Tn})} = \frac{L_2}{\mu_p C_{OX} W_2 (V_{DD} + V_{Tp})}$$

with $L_1=L_2$ and $V_{Tp}=-V_{Tn}$ we must have

$$\frac{W_2}{W_1} = \frac{\mu_n}{\mu_p} \cong 3$$

What about the second degree of freedom?

$$W_1 = W_{MIN}$$


$$V_{TRIP}=?$$

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing strategy: Equal (worst-case) rise and fall times

 $W_n=W_{MIN}$, $W_p=3W_{MIN}$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$



$$V_{TRIP} = \frac{(V_{Tn}) + (V_{DD} + V_{Tp}) \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}}{1 + \sqrt{\frac{\mu_p}{\mu_n} \frac{W_2}{W_1} \frac{L_1}{L_2}}} = \frac{0.2V_{DD} + 0.8V_{DD}}{2} = \frac{V_{DD}}{2}$$

$$t_{HL} = t_{LH} = R_{pd} C_L = \frac{L_{min}}{\mu_n C_{OX} W_{min} (0.8V_{DD})} C_L$$

$$t_{PROP} = 2 R_{pd} C_L$$


For a fixed C_L , how does t_{prop} compare for the minimum-sizing compared to equal rise/fall sizing?

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing strategy: Fixed $V_{TRIP} = V_{DD}/2$

 $W_n=?$, $W_p=?$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$




Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing strategy: Fixed $V_{TRIP}=V_{DD}/2$

 $W_n=?$, $W_p=?$, $V_{trip}=?$, $t_{HL}=?$, $t_{LH}=?$



Set

$$V_{TRIP}=V_{DD}/2$$

$$V_{TRIP} = \frac{(.2V_{DD}) + (V_{DD} - .2V_{DD}) \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}}{1 + \sqrt{\frac{\mu_p W_2 L_1}{\mu_n W_1 L_2}}} = \frac{V_{DD}}{2}$$

Solving, obtain

$$\frac{W_2}{W_1} = \frac{\mu_n}{\mu_p}$$


$$W_n=W_{MIN}, \quad W_p=3W_{MIN}$$

- This is the same sizing as was obtained for equal worst-case rise and fall times so $t_{HL}=t_{LH}=R_{pd}C_L$
- This is no coincidence !!! Why?
- These properties guide the definition of the process parameters provided by the foundry

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing Strategies

 


- Minimum Size
- Fixed V_{TRIP}
- Equal rise-fall times
(equal worst-case rise and fall times)
- Minimum power dissipation
- Minimum time required to drive a given load
- Minimum input capacitance

Device Sizing

Assume $V_{Tn}=0.2V_{DD}$, $V_{Tp}=-0.2V_{DD}$, $\mu_n/\mu_p=3$, $L_1=L_2=L_{min}$

Sizing Strategy Summary

 

	Minimum Size	$V_{TRIP}=V_{DD}/2$	Equal Rise/Fall
Size	$W_n=W_p=W_{min}$ $L_p=L_n=L_{min}$	$W_n=W_{min}$ $W_p=3W_{min}$ $L_p=L_n=L_{min}$	$W_n=W_{min}$ $W_p=3W_{min}$ $L_p=L_n=L_{min}$
t_{HL}	$R_{pd}C_L$	$R_{pd}C_L$	$R_{pd}C_L$
t_{LH}	$3R_{pd}C_L$	$R_{pd}C_L$	$R_{pd}C_L$
t_{PROP}	$4R_{pd}C_L$	$2R_{pd}C_L$	$2R_{pd}C_L$
V_{trip}	$V_{TRIP}=0.42V_{DD}$	$V_{TRIP}=0.5V_{DD}$	$V_{TRIP}=0.5V_{DD}$

- For a fixed load C_L , the minimum-sized structure has a higher t_{PROP} but if the load is another inverter, C_L will also change so the speed improvements become less apparent
- This will be investigated later

End of Lecture 40