

EE 330

Homework 9


Fall 2019

Due Wed Oct 23 at the beginning of class (no late HW accepted)

Unless specified to the contrary, assume all n-channel MOS transistors have model parameters $\mu_n C_{OX} = 100 \mu\text{A}/\text{V}^2$ and $V_{Tn} = 0.8\text{V}$, all p-channel transistors have model parameters $\mu_p C_{OX} = 33 \mu\text{A}/\text{V}^2$ and $V_{Tp} = -0.8\text{V}$. Correspondingly, assume all npn BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. Assume all diodes are characterized by the model parameters $J_{SX} = 0.1 \text{fA}/\mu\text{m}^2$, $V_{G0} = 1.17\text{V}$, and $m = 2.3$.

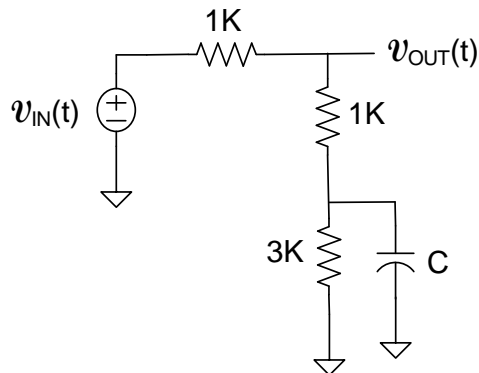
Problem 1 Assume the capacitor C is very large.

- Draw the small-signal equivalent circuit
- Determine the quiescent output voltage
- Determine the small-signal voltage gain.
- Determine the output voltage if $v_{IN}(t) = 2\sin 500t$




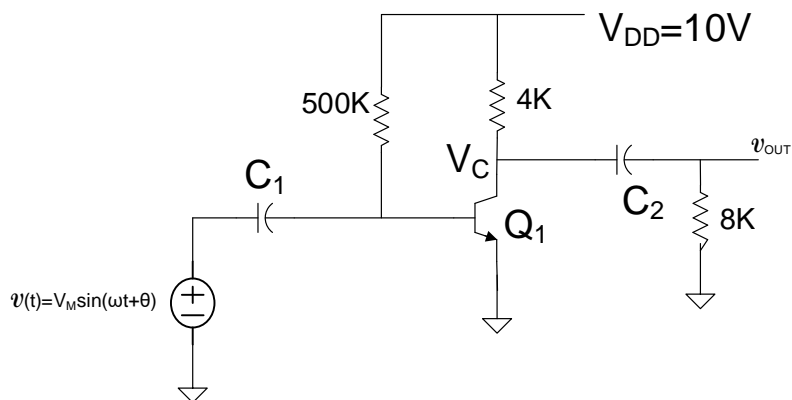Problem 2 Assume the capacitors are very large and V_M is small.

- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of V_C and V_{OUT}




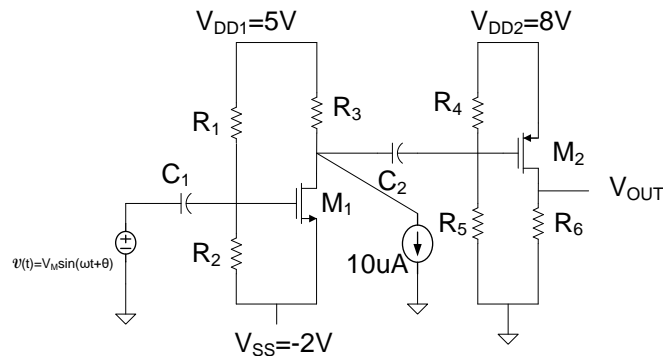Problem 3 Obtain the small signal equivalent circuit for the following network. Assume the transistors are operating in the saturation region, all capacitors are large, and V_M is small. You need not solve the circuit.



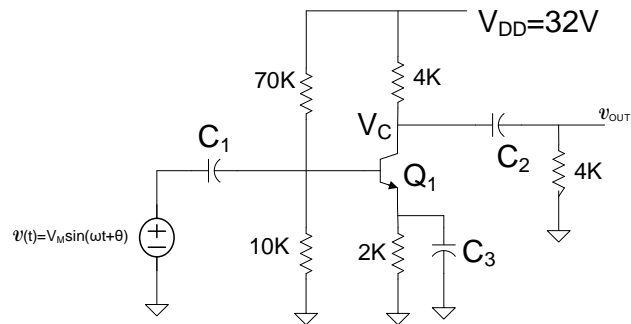
Problem 4 Assume the capacitors are all very large and V_m is small.

- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of V_C and V_{OUT}



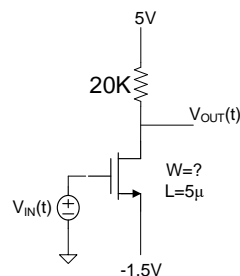Problem 5 Consider the following circuit

- Determine the width W so that the quiescent drain current is 0.1mA
- Draw the small-signal equivalent circuit
- With the drain current specified in part a), determine the small-signal voltage gain (do not use small-signal device models to solve this part of the problem)
- Determine the THD if the input is a 1KHz sinusoidal signal of amplitude 200mV 0-p



Problem 6 Assume V_{IN} is a low frequency nearly sinusoidal waveform that is below 10mV 0-P and that $W=12\mu\text{m}$, $L=1\mu\text{m}$ for the MOSFET.

- a) Determine the voltage gain of this circuit if $V_{XX}=2.5\text{V}$.
- b) How does the voltage gain change if V_{XX} is swept between 1.5V and 4V?

