

Problem 1:

$$A_V = -\frac{2I_{DQ}R}{V_{EB}} = -\frac{40000I_{DQ}}{0.25}$$

with preset variables $R = 20k$, $V_{EB} = (1 - 0.5) = 0.5$

$$A_V = -\frac{40000I_{DQ}}{0.5} = -4 \rightarrow I_{DQ} = 0.1mA$$

$$V_{outq} = 1 - 20000I_{DQ} = 0V$$

So this I_{DQ} works for both constraints, setting $L = 1\mu$

$$I_{DQ} = 350e - 6 * \left(\frac{W}{2}\right) 0.25 = 0.0001$$

$$W = 2.28\mu, l = 1\mu$$

Problem 2:

Choose $V_{GTMax} = 0.9V$ (at $0^\circ C$) and $I_{GT} = 200 \mu A$

$$\rightarrow R_{GG} = \frac{15 - 0.9}{200 \mu} = 70.5k\Omega$$

$$b) I_{Fmax} = \frac{80 - 1.6}{40} = 1.96 A, V_F = 1.6 \rightarrow P = IV = 1.96 * 1.6 = 3.136W$$

$$c) V_{GT} = .8, I_G = \frac{15 - 0.8}{70.5k} = 201.4 \mu A \rightarrow P = 161.13 \mu W$$

Problem 3:

a)

Upper portion of potentiometer = $500 * (1 - 0.1) = 450$

Lower portion of potentiometer = $500 * 0.1 = 50$

$$V_{TM} = 1.6 \text{ V}, \quad V_{GT} = V_{AC} \left(\frac{50}{500 * 2} \right) = 3 \sin(2\pi * 60 * t)$$

$$\rightarrow V_F = \begin{cases} 1.6 \text{ V} & t_0 < t < t_1, \quad t_2 < t < t_3 \\ V_{AC} & \text{otherwise} \end{cases}$$

where $t_3 = 602\pi n, t_1 = 60\pi n$ and

$$V_g = 2.5 = 4 \sin(60 * 2\pi t_0)$$

$$\frac{2.5}{4} = \sin(60 * 2\pi t_0)$$

$$60 * 2\pi t_0 = \sin^{-1} \left(\frac{2.5}{4} \right)$$

$$t_0 = \frac{\sin^{-1} \left(\frac{2.5}{4} \right)}{120\pi}$$

Then it is simple to see that

$$t_3 = \frac{\sin^{-1} \left(-\frac{2.5}{4} \right)}{120\pi}$$

b)

$$V_{RMS} = \frac{80 - 1.6}{\sqrt{2}} = 55.43, \rightarrow I_L = \frac{V_{RMS}}{R_L} = 2772 \text{ A}_{RMS}$$

$$P = V * I_L = 1.6 * 2.065 = 3.304 \text{ W}_{RMS}$$

c)

Quadrants 1 and 3

Problem 4:

$$\text{Turn on voltage is } 0.8 \text{ V so at } 2\pi/8 \text{ we need, } 0.8 = \frac{R_1}{R_1 + 10000} * 170 \sin \left(\frac{\pi}{4} \right) \rightarrow R_1 = 67 \Omega$$

Problem 5

$$V_{GS} = 0 \text{ and } V_{DS} > V_{GS} - V_P \rightarrow V_{out} = I_{DSS} * 6k = 0.6 \text{ V}$$

Problem 6:

a)

$$V_{GSH} = 20 \text{ mV, assume } V_{DS} > V_{GS} - V_P$$


$$V_{out1} = 5 - I_D * 5k = 5 - I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 * 5k = 4.482$$

$$\text{Verify} \rightarrow V_{DS} > V_{GS} - V_P \rightarrow 4.48 > 1.025$$

$$V_{GSL} = -20 \text{ mV, assume } V_{DS} > V_{GS} - V_P$$

$$V_{out1} = 5 - I_D * 5k = 5 - I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 * 5k = 4.519$$
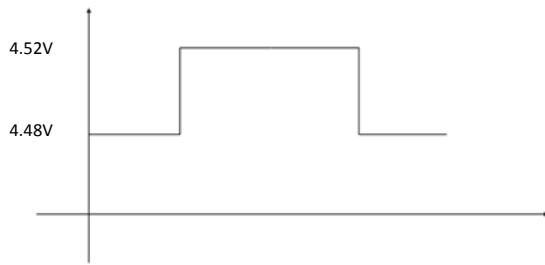
$$\text{Verify} \rightarrow V_{DS} > V_{GS} - V_P \rightarrow 4.52 > 1.025$$



b) $V_{in} < V_{GSM_{ax}} = 0.3 \text{ V}$ (From lecture slides)

Problem 7:

$$I = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_G - V_{out} - V_{TN})^2 = I_{DSS} * \left(1 - \frac{V_{in}}{V_P}\right)^2$$

$$\rightarrow \frac{350 * 10^{-6}}{2} * \left(\frac{W}{12}\right) (5 - 3 - 0.75)^2 = 350 * 10^{-6} * \left(1 - \frac{-0.5}{-1}\right)^2 \rightarrow W = 3.84 \mu m$$

Problem 7:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = -2 * \frac{I_{DSSP}}{-V_P} \left(1 - \frac{V_{GS}}{V_P}\right) (1 - \lambda V_{DS}) \approx 2 * \frac{I_{DSSP0}}{V_P} \left(\frac{W}{L}\right) \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \lambda * I_{DSSP} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

Problem 8:

$$I_{DQ} = \frac{30\mu * 10}{15} * \left(1 - \frac{0}{1}\right)^2 = \frac{V_{outQ} - (-5)}{50k} \rightarrow V_{outQ} = -4V, I_{DQ} = 20\mu A$$

$$g_m = \frac{2}{V_P} \frac{I_{DQ}}{\left(1 - \frac{V_{GS}}{V_P}\right)} \rightarrow A_V = \frac{V_{out}}{V_{in}} = -g_m * 50k = 2V/V$$

Problem 9

Guess Saturation

$$I_{DQ} = I_{DSSp0} \frac{W}{L} \left(1 - \frac{V_{GS}}{V_P}\right)^2 = 30e - 6 \left(\frac{10}{15}\right) \left(1 - \frac{0}{1}\right) = 20\mu A$$

$$V_{DS} = -5 + 20 * 10^{-6} * 50000 = -4V$$

$$A_V = -g_m * 50000 = \frac{2}{1} \left(\frac{20e-6}{1 - \frac{0}{1}}\right) 50000 = 2 \frac{V}{V}$$

Problem 10

$$a) A_V = \left(\frac{R_{in1}}{R_{impede} + R_{in1}}\right) A_{V1} \left(\frac{R_{in2}}{R_{o1} + R_{in2}}\right) A_{V2} \left(\frac{R_{load}}{R_{o2} + R_{load}}\right) = \left(\frac{4}{4+2}\right) (-10) \left(\frac{20}{20+0.5}\right) (-20) \left(\frac{0.5}{5+0.5}\right) = 11.83$$

$$b) A_V = \left(\frac{R_{in2}}{R_{impede} + R_{in2}}\right) A_{V2} \left(\frac{R_{in1}}{R_{o2} + R_{in1}}\right) A_{V1} \left(\frac{R_{load}}{R_{o1} + R_{load}}\right) = \left(\frac{20}{20+2}\right) (-20) \left(\frac{4}{4+5}\right) (-10) \left(\frac{0.5}{0.5+0.5}\right) = 40.4$$

Problem 11

$$a) R_{in} = R_{in1} = 4k\Omega, A_{VR} = 0, R_{out} = R_{o2} = 5k\Omega$$


$$A_V = A_{V1} \left(\frac{R_{in2}}{R_{o1} + R_{in2}}\right) A_{V2} = -10 \left(\frac{20}{20+0.5}\right) (-20) = 195.12$$

$$b) \text{ Adding in the source input impedance and load,}$$

$$A_V = \left(\frac{R_{in}}{R_{in} + R_{impede}}\right) A_V \left(\frac{R_{load}}{R_{out} + R_{load}}\right) = \left(\frac{4}{4+2}\right) (195.12) \left(\frac{0.5}{5+0.5}\right) = 11.83$$

Yes, they match.

Problem 12:

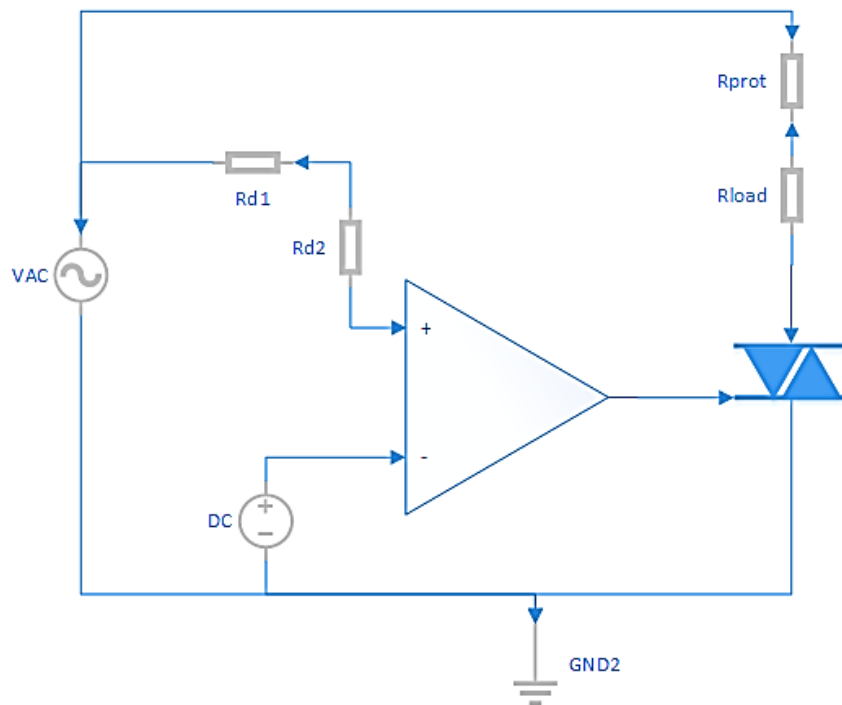

The above is one design. R_{prot} would protect R_{load} by keeping $I_{MAX} < I_{safe}$, whatever I_{safe} is by taking

$$\frac{V_{MAX}}{(R_{prot} + R_{load})} < I_{safe}.$$

R_{d1} and R_{d2} create a voltage divider so $V_{gateMax} = V_{GT} = 0.8V$, since we have $120V_{AC}$, we need

$$\frac{R_{d2}}{R_{d2} + R_{d1}} (120) = 0.8$$

$$\frac{R_{d2}}{R_{d2} + R_{d1}} = \frac{1}{150}$$

so I will use $R_{d2} = 10\Omega$, $R_{d1} = 1.49k\Omega$

Then the adder causes this to cross V_{GT} when turned on, until the wave is always greater than V_{GT} at $DC = 5V$