

CprE 381: Computer Organization and Assembly Level Programming

Processor Design

Henry Duwe
Electrical and Computer Engineering
Iowa State University

Administrative



- Exam 1
 - Graded, returned on Canvas
 - Mean/Median/Mode = 60
 - Min:max: 8:99
 - Will curve, currently raw score on Canvas
 - If you scored <40%, you should be very concerned; come see me
 - Any grading/counting/scoring issues:
 - In writing as e-mail to me

Administrative

- HW4
 - Redo problem you lost the most points on (total points).
 - Make it perfect
 - Ask questions
 - Talk with each other, but make sure your solution write-up is yours
 - Turn it in as pdf on Canvas

Review: Fetching Instructions

  
- Fetching instructions involves
 - reading the instruction from the Instruction Memory
 - updating the PC value to be the address of the next (sequential) instruction



- PC is updated every clock cycle, so it does not need an explicit write control signal – just a clock signal
- Reading from the Instruction Memory is a combinational activity

Review: Decoding Instructions

 
- Decoding instructions involves
 - Sending the fetched instruction's **opcode** and **function** field bits to the control unit




- Reading two values from the Register File
 - Register File addresses are contained in the instruction

Review: Executing R Format Operations

 - R format operations (**add**, **sub**, **slt**, **and**, **or**)



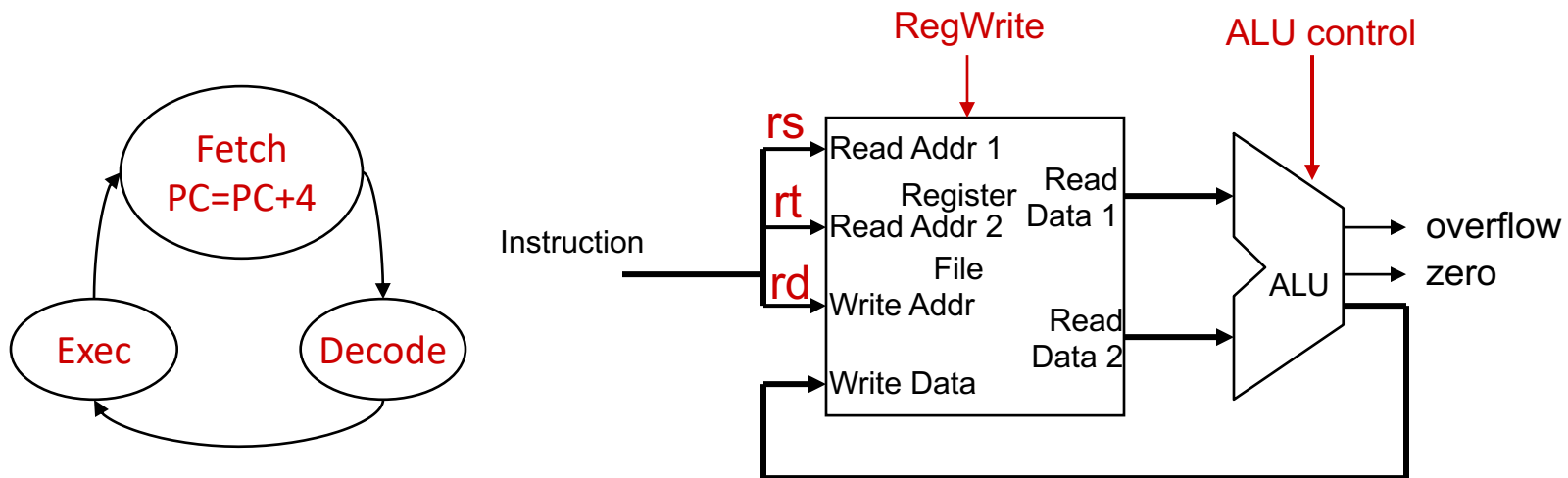- Perform operation (**op** and **funct**) on values in **rs** and **rt**
- Store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g. **sw** or **jr**), so we need an explicit write control signal for the Register File

Consider the `s1t` Instruction

- Remember the R format instruction `s1t`


```
s1t $t0, $s0, $s1    # if $s0 < $s1  
                     # then $t0 = 1  
                     # else $t0 = 0
```

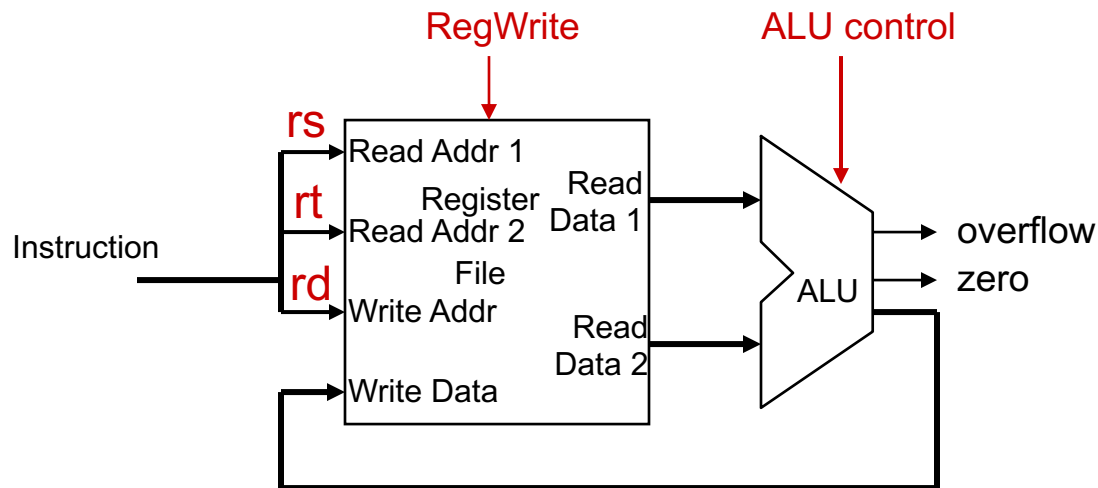- Where does the 1 (or 0) come from to store into `$t0` in the Register File at the end of the execute cycle?




Review: Executing Load and Store Operations

- Load and store operations have to:

 

- Compute a memory address by adding the base register (in **rs**) to the 16-bit signed offset field in the instruction
 - Base register was read from the Register File during decode
 - Offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value
- **Store** value, read from the Register File during decode, must be written to the Data Memory
- **Load** value, read from the Data Memory, must be stored in the Register File

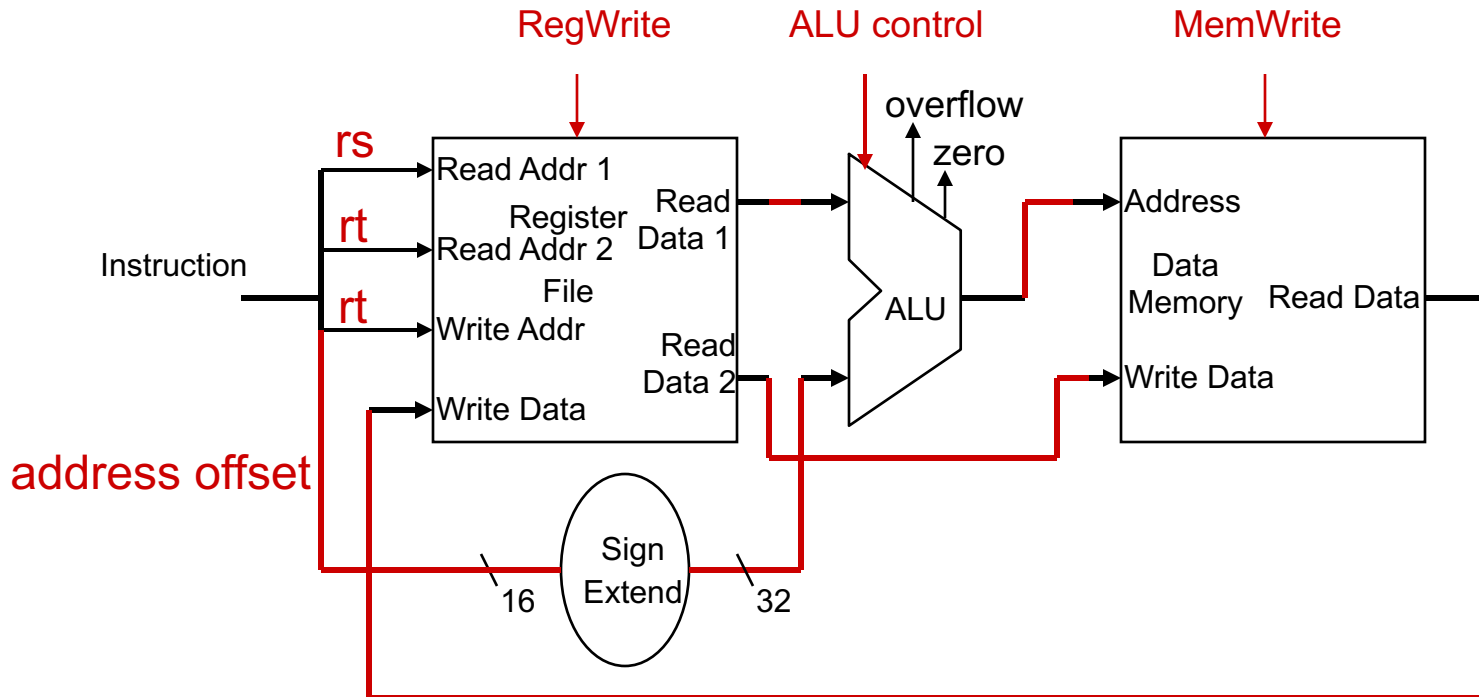Executing Load / Store Operations (cont.)




Executing Load / Store Operations (cont.)

In-class Assessment!


Access Code: RTGIF381

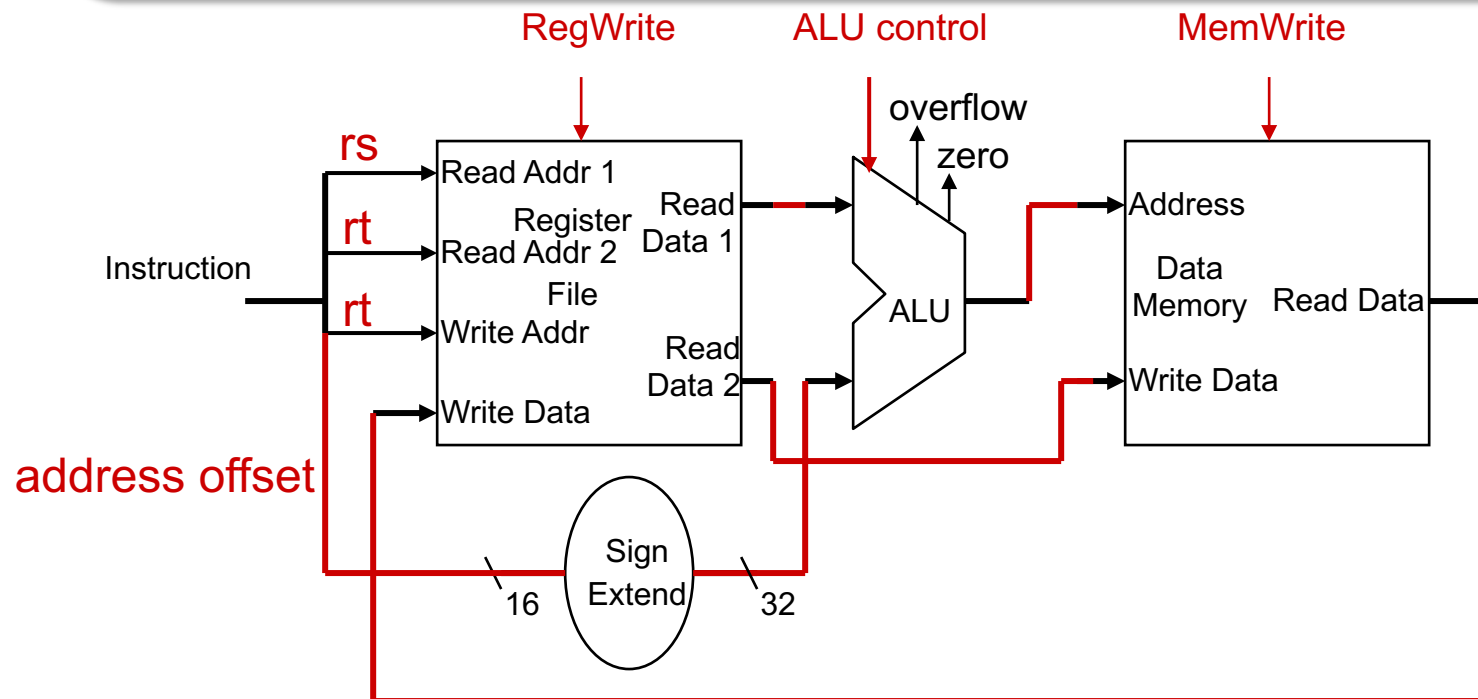Note: sharing access code to those outside of classroom or using access while outside of classroom is considered cheating




Executing Branch Operations

- Branch operations have to

 

- Compare the operands read from the Register File during decode (**rs** and **rt** values) for equality (**zero** ALU output)
- Compute the branch target address by adding the updated PC to the sign extended 16-bit signed offset field in the instruction
 - The “base register” is the **updated** PC
 - Offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value and then shifted left 2 bits to turn it into a word address

Executing Branch Operations (cont.)

 


Executing Jump Operations

- Jump operations have to



 
- Replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits




Creating a Single Datapath from the Parts

- Assemble the datapath elements, add control lines as needed, and design the control path
- Fetch, decode and execute each instructions in one clock cycle – **single cycle** design
 - One instruction can't use same resource/structure twice (ergo Harvard split memory architecture)
 - Two different instructions need **multiplexors** at the input of the shared elements with control lines to do the selection
- Cycle time is determined by length of the longest path


Fetch, R, and Memory Access Portions

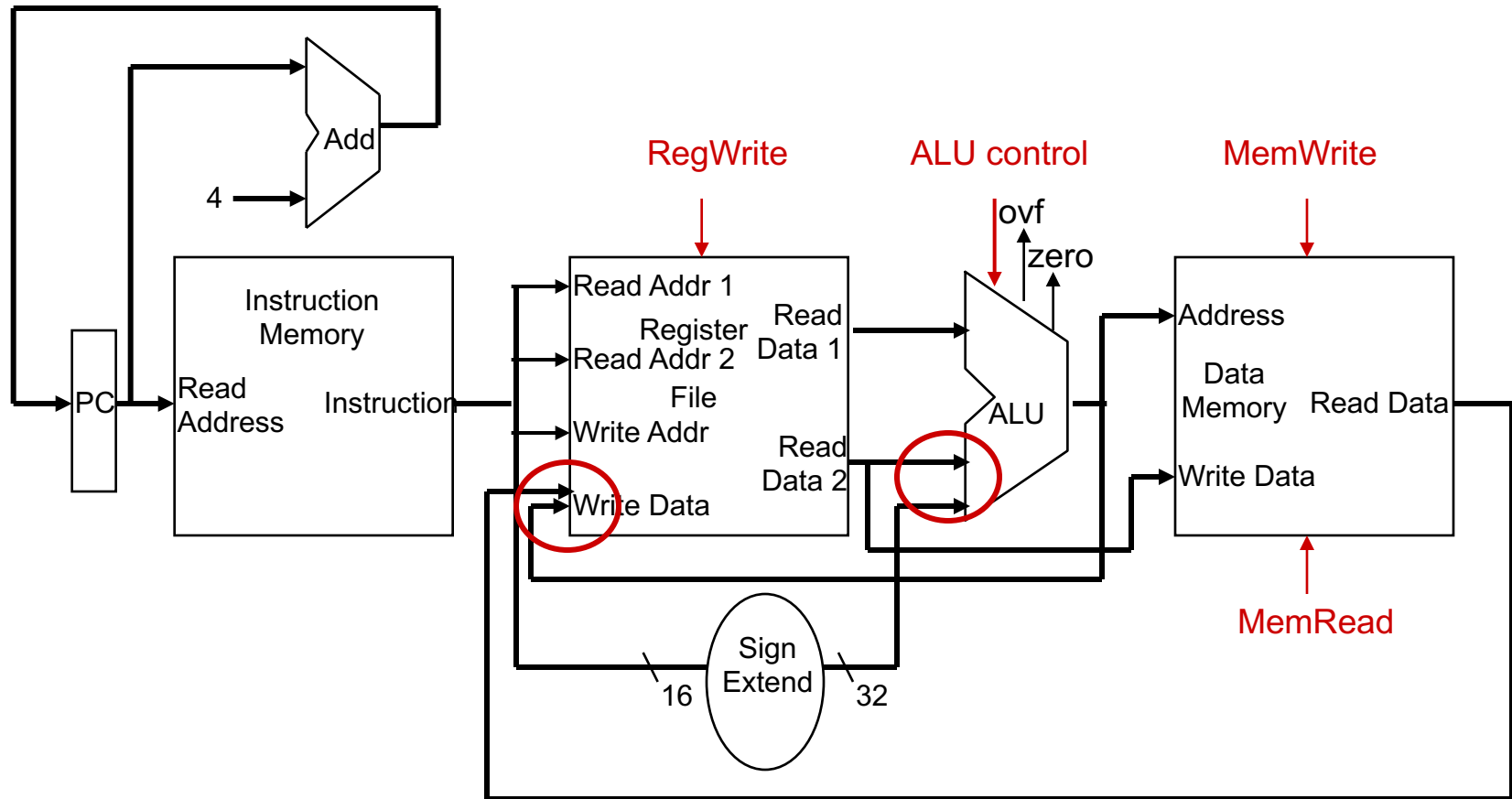


Multiplexor Insertion

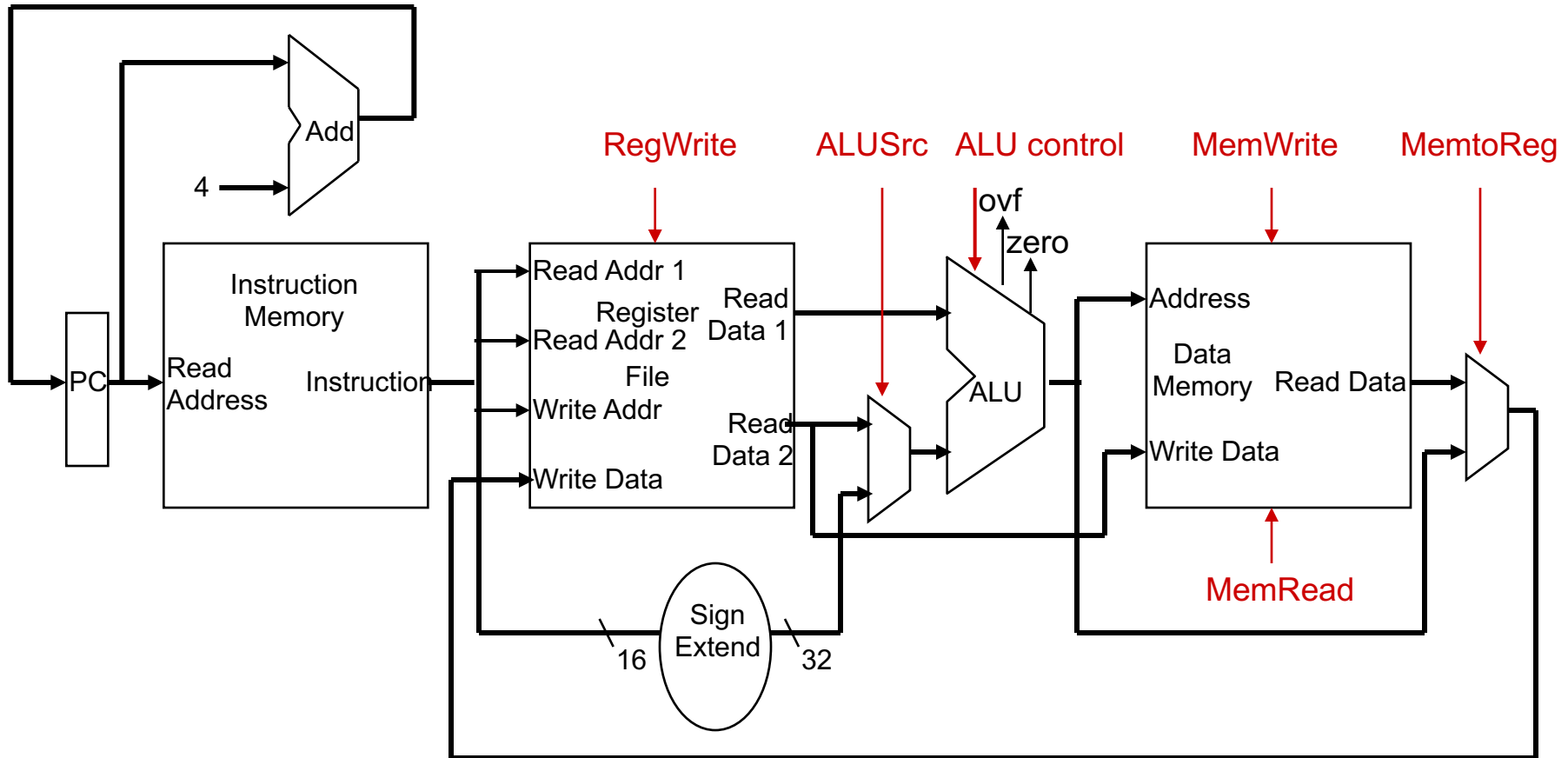

Clock Distribution

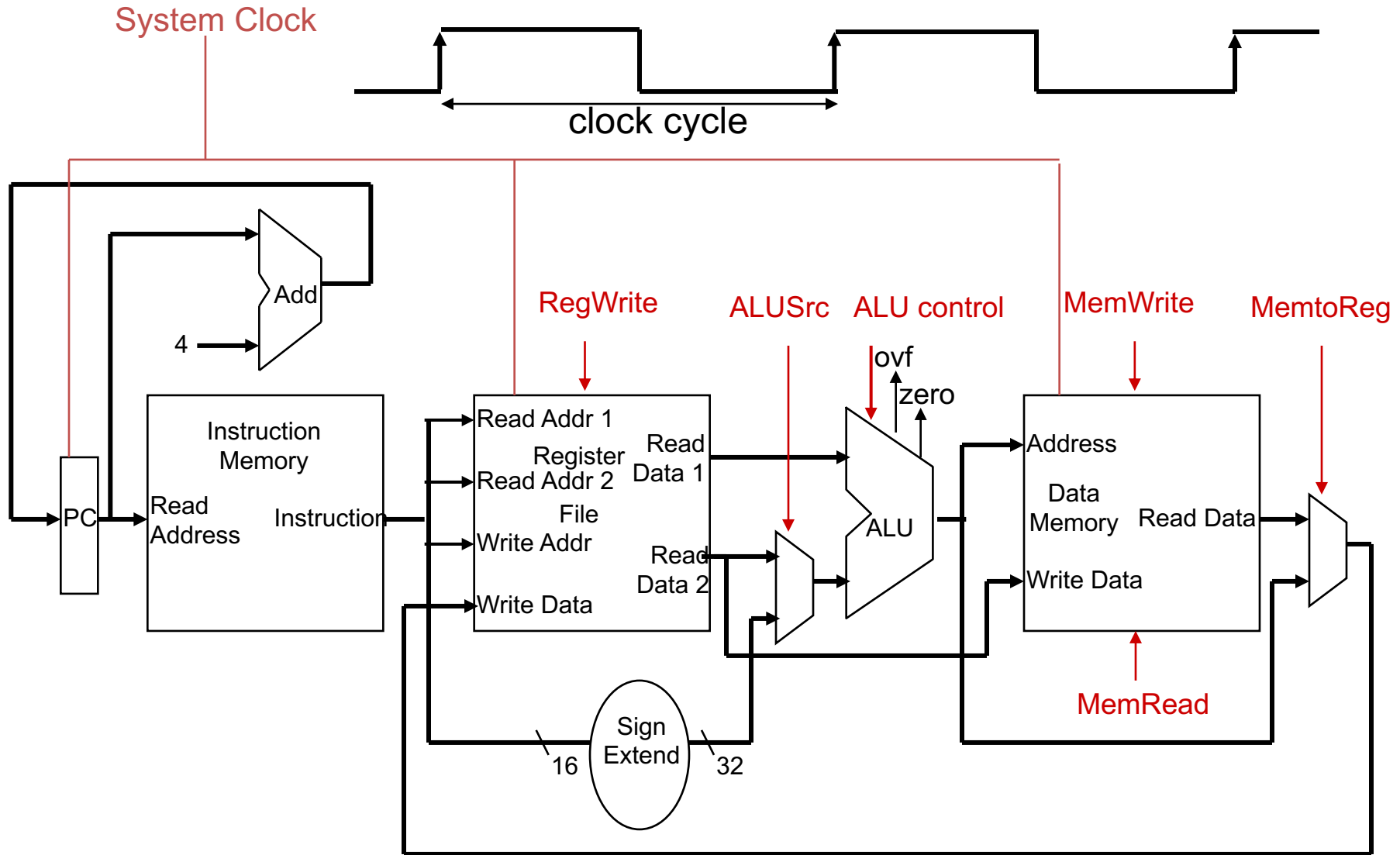


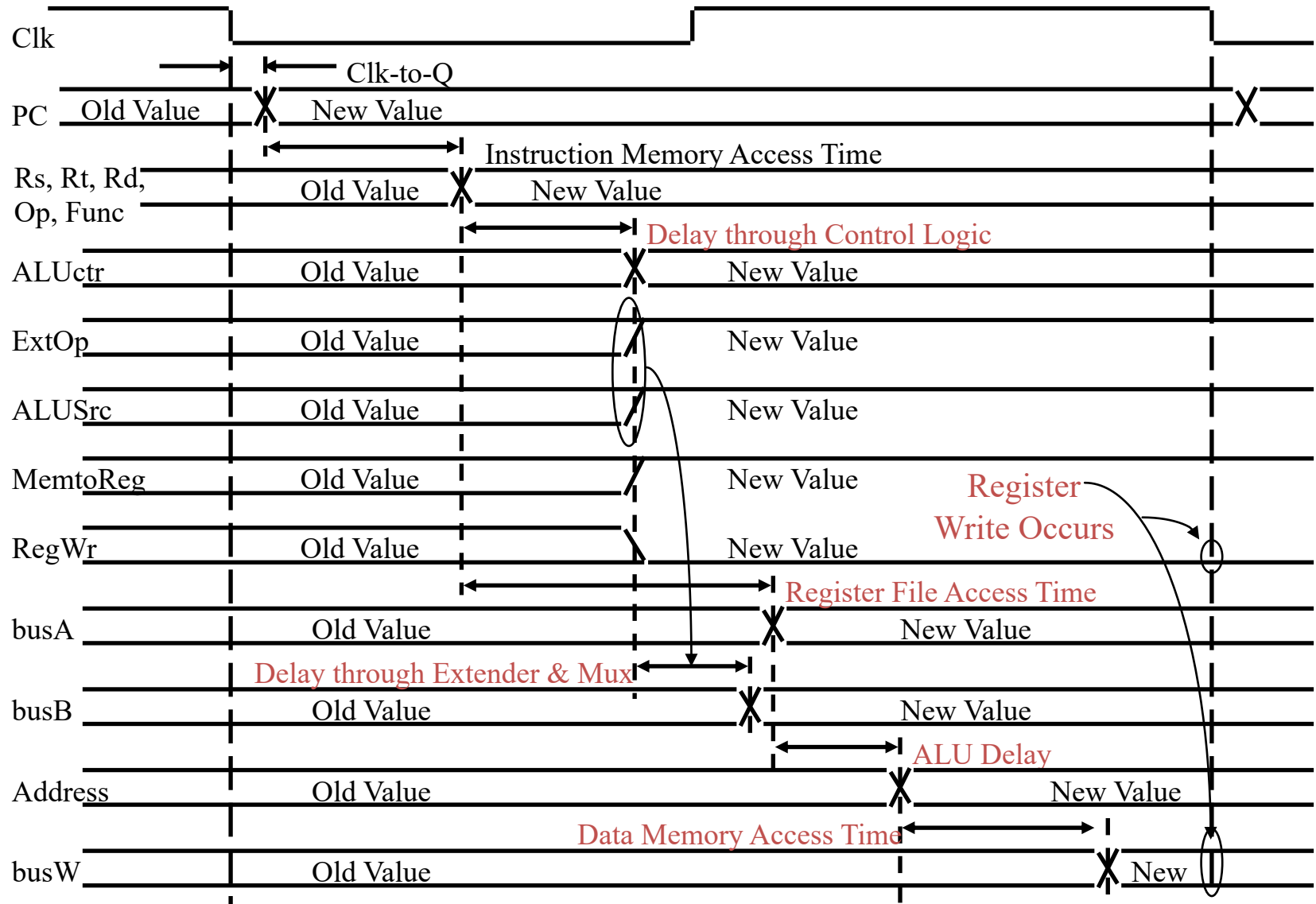Preview: Worst Case Timing (Load Instruction)



Preview: Adding the Control

 - Selecting the operations to perform (ALU, Register File and Memory read/write)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction



- Observations
 - op field always in bits 31-26
 - addr of two registers to be read are **always** specified by the rs and rt fields (bits 25-21 and 20-16)
 - base register for **lw** and **sw** always in rs (bits 25-21)
 - addr. of register to be written is in one of **two** places – in rt (bits 20-16) for **lw**; in rd (bits 15-11) for R-type instructions
 - offset for **beq**, **lw**, and **sw** always in bits 15-0

Acknowledgments

- These slides contain material developed and copyright by:
 - Joe Zambreno (Iowa State)
 - David Patterson (UC Berkeley)
 - Mary Jane Irwin (Penn State)
 - Christos Kozyrakis (Stanford)
 - Onur Mutlu (Carnegie Mellon)
 - Krste Asanović (UC Berkeley)