

Homework 2 Fall 2017 TA: Joseph Aymond


Problem 1:

In figure 1.4 we can find the count of transistors in the processor increases by about ~10 times per seven years. In 2002 the count was about 0.1 Billion, so we can predict the count in 2020 to be about

$$0.1 \text{ billion} * 10^{(18/7)} = \mathbf{37.28 \text{ billion.}}$$

 Problem 2:

The transistor level schematic for a CMOS 3-input NAND gate can be made like this (other ways are possible)



A, B, and C are inputs

Out is the output

$$\text{Out} = \overline{A * B * C}$$

Problem 3:

$$\text{Area of die} = A_{\text{die}} = (3\text{mm})^2 = 9\text{mm}^2 = 0.09\text{cm}^2$$

$$\text{Area of wafer} = A_{\text{wafer}} = \left(\frac{300}{2}\right)^2 * \pi = 70685\text{mm}^2 = 706.85\text{cm}^2$$

$$\text{Hard yield of die } Y_H = e^{-A_{\text{die}} * d} = e^{-0.09 * 1.3} = e^{-0.117} = 0.890$$

$$\text{The total yield } Y = Y_H * Y_S = 0.890 * 1 = 0.890$$

$$\text{The cost per good die } C_{\text{good}} = \frac{C_{\text{wafer}}}{A_{\text{wafer}}/A_{\text{die}}} * \frac{1}{Y} = \frac{\$3200}{\frac{70685}{9}} * \frac{1}{0.890} = \mathbf{\$0.458}$$

Problem 4:

$$Y = \frac{x - u}{g} = \frac{4\text{mv} - 0\text{mv}}{2\text{mv}} = \frac{4}{2} = 2$$

$$P_{\text{Soft_Amp}} = \int_{-2}^2 f(x)dx = 2F_N(2) - 1 = \mathbf{0.9545}$$

$$\text{Four Op Amps per chip } P_{\text{Soft_chip}} = 0.9545^4 = \mathbf{0.830}$$

Problem 5:

Since the input offset voltage follow Gaussian distribution we have the soft yield θ :

$$Y_s = P_{soft} = 2F_N(y) - 1 = 0.95 \Rightarrow F_N(y) = 0.975$$

$$\therefore y = 1.96 = \frac{x - u}{g} = \frac{2mv - 0}{\left(\frac{A_{VTO}}{\sqrt{A}}\right)} \Rightarrow A = 600 \mu m^2$$

Problem 6:

$$\text{The area of a die in new process} = A_{die} = \left(\frac{7}{65}\right)^2 * 0.5 cm^2 = 5.7988 * 10^{-3} cm^2$$


$$\text{The hard yield} = Y_H = e^{-A_{die} * d} = e^{-0.00725} = 0.9928$$

$$\text{The yield } Y = Y_H * Y_s = 0.9928$$

$$C_{good} = \frac{C_{wafer}}{(A_{wafer}/A_{die})} * \frac{1}{Y} = \frac{\$8000}{\frac{1590.4}{0.005799}} * \frac{1}{0.9928} = \$0.0294$$

Problem 7:

This switch level model assumes $A = 0$ and $\bar{C} = 0$.

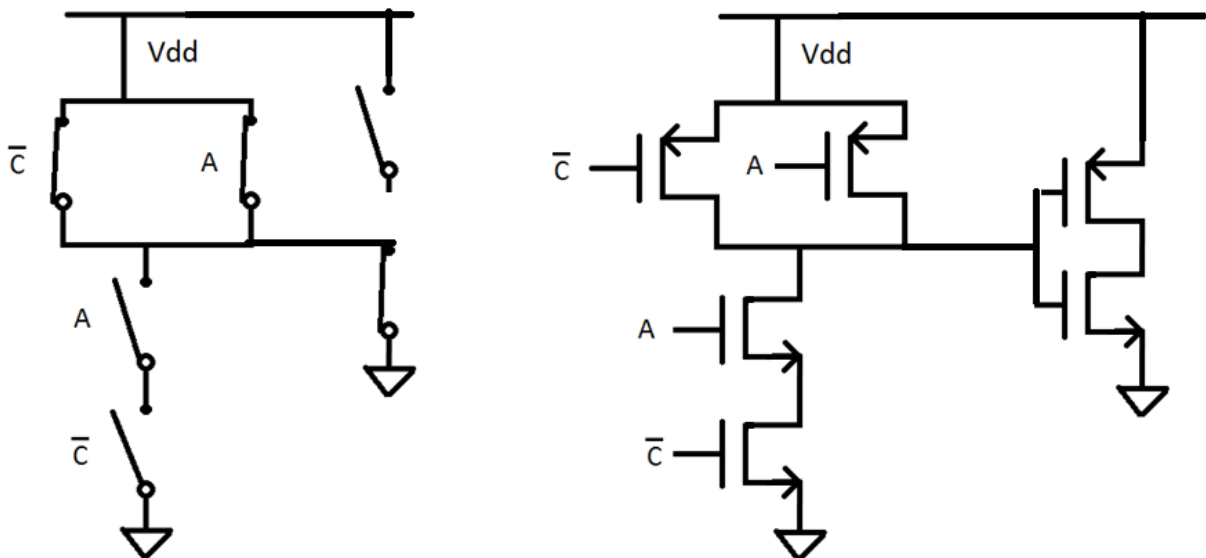

Problem 8:

When both inputs are 0V the output is VDD = 3V

When one input is 0V and the other is 3V the output is VDD = 3V

When both inputs are 3V the output is VSS = 0V

Problem 9:

- a- The master is addressing a slave and requesting data. Data is transferred to the master.
- b- The master is sending data to slave and receiving acknowledgement again just like part a.
- c- Open drain refers to the exposed drain of a transistor typically used as the output.
- d- Logic contention refers to data being driven at any time from several devices. I2C follows a protocol so that the contention doesn't appear.
- e- Due to the I2C open drain protocols the bus remains on a low threshold voltage. Devices can drive past the threshold so that the different logic levels are apparent

Problem 10:

Here is one solution to this problem

Ln#	
1	timescale 1ns/1ps
2	module NOR2 (i_A, i_B, o_F);
3	input i_A, i_B;
4	output o_F;
5	
6	assign o_F = ~(i_A i_B);
7	
8	endmodule
9	

Ln#	
1	
2	timescale 1ns/1ps
3	module OR2 (i_A, i_B, o_F);
4	input i_A, i_B;
5	output o_F;
6	wire A_nor_B;
7	
8	NOR2 nor0(.i_A(i_A), .i_B(i_B), .o_F(A_nor_B));
9	NOR2 nor1(.i_A(A_nor_B), .i_B(A_nor_B), .o_F(o_F));
10	
11	endmodule
12	
13	

Ln#	
1	
2	`timescale 1ns/1ps
3	module OR3 (i_A, i_B, i_C, o_F);
4	input i_A, i_B, i_C;
5	output o_F;
6	wire A_or_B;
7	
8	OR2 nor0(.i_A(i_A), .i_B(i_B), .o_F(A_or_B));
9	OR2 nor1(.i_A(i_C), .i_B(A_or_B), .o_F(o_F));
10	
11	endmodule
12	
13	
14	

Ln#	
1	
2	`timescale 1ns/1ps
3	module AND2 (i_A, i_B, o_F);
4	input i_A, i_B;
5	output o_F;
6	wire A_not, B_not;
7	
8	NOR2 nor0(.i_A(i_A), .i_B(i_A), .o_F(A_not));
9	NOR2 nor1(.i_A(i_B), .i_B(i_B), .o_F(B_not));
10	NOR2 nor2(.i_A(A_not), .i_B(B_not), .o_F(o_F));
11	
12	endmodule

Ln#	
1	
2	`timescale 1ns/1ps
3	module AND3 (i_A, i_B, i_C, o_F);
4	input i_A, i_B, i_C;
5	output o_F;
6	wire A_and_B;
7	
8	AND2 and0(.i_A(i_A), .i_B(i_B), .o_F(A_and_B));
9	AND2 and1(.i_A(A_and_B), .i_B(i_C), .o_F(o_F));
10	
11	endmodule

Ln#	
1	
2	
3	`timescale 1ns/1ps
4	module Function (i_A, i_B, i_C, o_F);
5	input i_A, i_B, i_C;
6	output o_F;
7	wire w_nA, w_nB, w_nC;
8	wire w_A1, w_A2, w_A3;
9	
10	NOR2 nor0(.i_A(i_A), .i_B(i_A), .o_F(w_nA));
11	NOR2 nor1(.i_A(i_B), .i_B(i_B), .o_F(w_nB));
12	NOR2 nor2(.i_A(i_C), .i_B(i_C), .o_F(w_nC));
13	AND3 and1(.i_A(w_nA), .i_B(i_B), .i_C(i_C), .o_F(w_A1));
14	AND3 and2(.i_A(i_A), .i_B(w_nB), .i_C(i_C), .o_F(w_A2));
15	AND3 and3(.i_A(i_A), .i_B(i_B), .i_C(w_nC), .o_F(w_A3));
16	OR3 or0(.i_A(w_A1), .i_B(w_A2), .i_C(w_A3), .o_F(o_F));
17	
18	endmodule
19	
20	
21	

Ln#	
1	`timescale 1ns/1ps
2	module Function_TB();
3	reg r_A, r_B, r_C;
4	wire w_F;
5	
6	initial
7	begin
8	r_A = 1'b0;
9	r_B = 1'b0;
10	r_C = 1'b0;
11	end
12	
13	always
14	#10 r_C=~r_C;
15	always
16	#20 r_B=~r_B;
17	always
18	#40 r_A=~r_A;
19	
20	Function U(.i_A(r_A), .i_B(r_B), .i_C(r_C), .o_F(w_F));
21	
22	endmodule
23	
24	
25	

