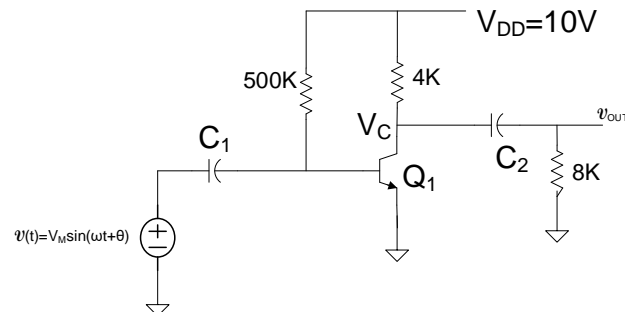


Unless specified to the contrary, assume all n-channel MOS transistors have model parameters $\mu_n C_{OX} = 350 \mu\text{A}/\text{V}^2$ and $V_{Tn} = 0.5\text{V}$, all p-channel transistors have model parameters $\mu_p C_{OX} = 70 \mu\text{A}/\text{V}^2$ and $V_{Tp} = -0.5\text{V}$. Correspondingly, assume all npn BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. If parameters are needed for CMOS process characterization beyond what is given, use the measured parameters from the TSMC 0.18μ process given below as model parameters. Assume all diodes are characterized by the model parameters $J_{SX} = 0.5 \text{A}/\mu\text{m}^2$, $V_{G0} = 1.17\text{V}$, and $m = 2.3$.


Problem 1 Assume the capacitors are very large and V_M is small.

- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of V_C and V_{OUT}
- Determine the voltage gain in terms of the small-signal y-parameters (or equivalently the g-parameters) for the transistor. Assume the parameter y_{21} in the model of the transistor is 0.
- Determine the numerical value for the small-signal voltage gain



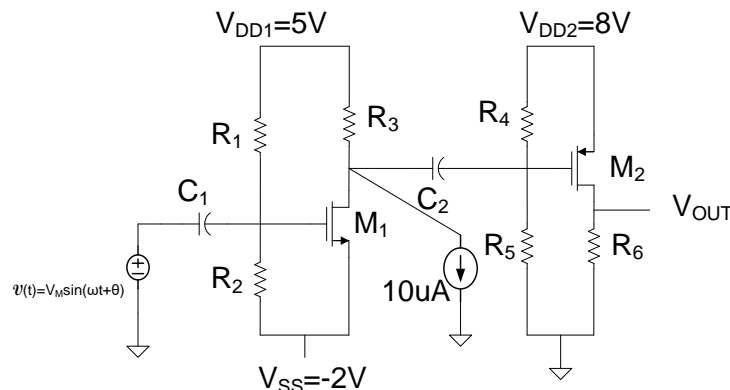
Problem 2 Obtain the small signal equivalent circuit for the following network.

Assume the transistors are operating in the saturation region, all capacitors are large, and V_M is small. You need not solve the circuit.



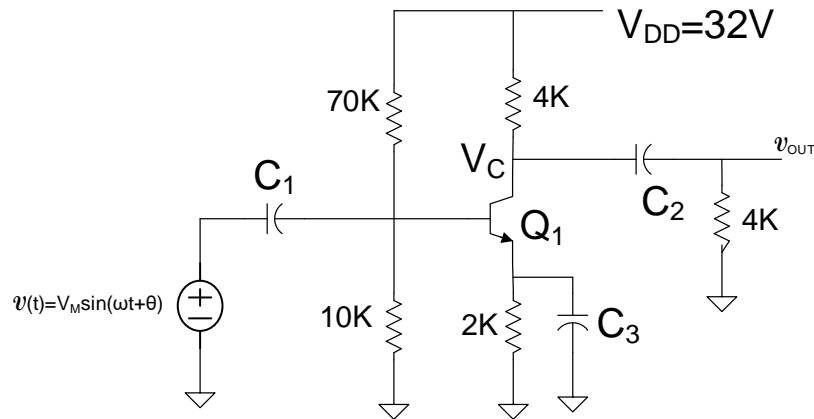Problem 3 Assume the capacitors are all very large and V_m is small.


- Draw the small signal equivalent circuit for the amplifier shown
- Determine the quiescent value of V_C and V_{OUT}
- Determine the small-signal voltage gain in terms of the small-signal g parameters
- Numerically determine the small-signal voltage gain.



Problem 4 Consider a device characterized by the equations

$$I_1 = V_1 V_2^2$$


$$I_2 = 0.1e^{0.2V_1^2 V_2}$$

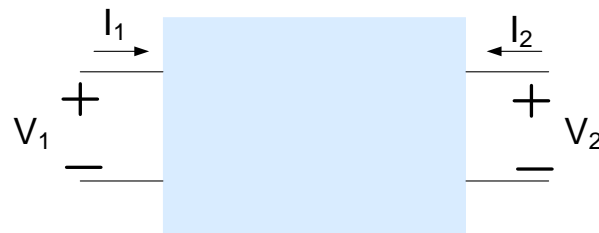


- Determine the small signal model for a two-terminal device characterized by the equations given above
- Determine the numerical values for the small signal model parameters if the quiescent value of the port voltages are $V_2=1V$, $V_1=5V$.
- Determine the quiescent currents at the Q-point established in part b.
- Determine the small signal currents i_1 and i_2 if the small signal voltages v_1 and v_2 were measured to be $1mV_{RMS}$ and $2mV_{RMS}$ respectively. Assume the same Q-point as established in part b.

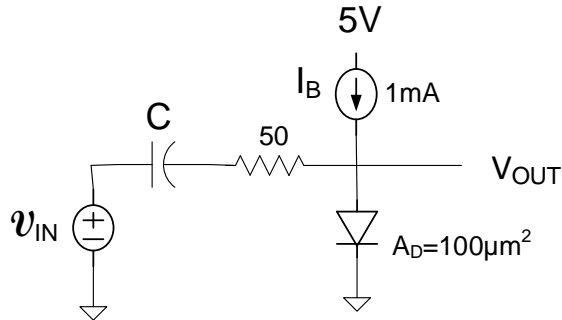Problem 5 Consider the following circuit operating at $T=300K$. Assume the capacitor C is very large and the v_{IN} is a small-signal input.

- Determine the quiescent output voltage.
- Draw the small-signal equivalent circuit
- Determine the small-signal voltage gain from the input to the output.
- Repeat part c) if the current I_B is increased to 5mA




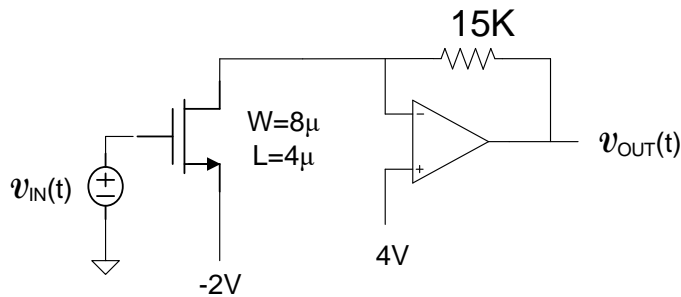Problem 6 Determine the small signal output voltage if the small signal input voltage is a sinusoidal 1KHz signal with 0-P amplitude of 25mV.



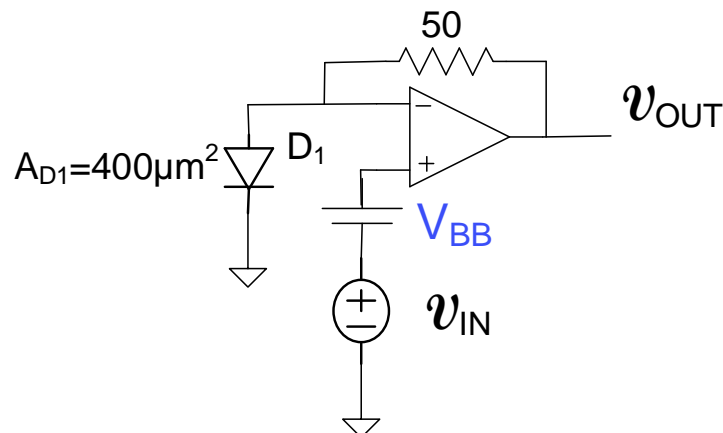
Problem 7 Consider the following circuit operating at $T=300K$. Assume v_{IN} is a small-signal voltage source.

- If the voltage V_{BB} is adjusted so that the quiescent diode current is 1mA, determine the small signal voltage gain $A_v = \frac{v_{OUT}}{v_{IN}}$
- Repeat part a) if V_{BB} is adjusted so that the quiescent diode current is 10mA




Problem 8 Consider the following circuits.

- Obtain the small signal impedance between the two terminals exiting the box in terms of the small-signal model parameters. Assume the MOSFET is operating in the Saturation region and the BJT in the Forward Active region
- Numerically determine the small-signal impedances if the quiescent currents are both 1mA, the width and length of the MOSFET are both $5\mu\text{m}$, and the emitter of the BJT is square and is $5\mu\text{m}$ on a side. Assume $V_{AF}=\infty$ and $\lambda=0$.

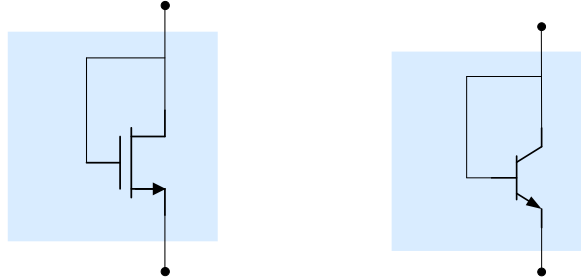


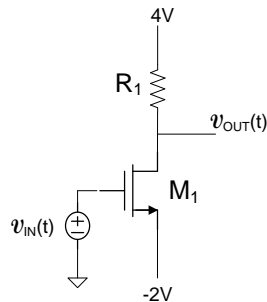Problem 9

- Determine the maximum value of R_1 that will keep M_1 in saturation. M_1 has dimensions $W=18\mu$ and $L=2\mu$ and is in a process with $\mu_n C_{OX}=100\mu\text{A}/\text{V}^2$, $\mu_p C_{OX}=30\mu\text{A}/\text{V}^2$, $V_{TNO}=0.5\text{V}$, $V_{TPO}=-0.5\text{V}$, $C_{OX}=2\text{fF}/\mu^2$, $\lambda=0$, $\gamma=0$.
- If R_1 is $1/3$ of the value determined in Part a), determine the small signal voltage gain of this circuit
- With the value of R_1 used in part b), determine the total output voltage if $v_{IN}(t)=.001\sin(5000t+75^\circ)$.



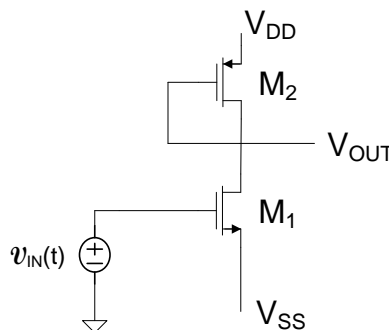Problem 10 Obtain an expression for the small signal output voltage in terms of the small signal parameters if the input is given by the expression $v_{IN}(t)=V_M\cos(\omega t+\theta)$. Assume M_1 is operating in the saturation region.



Problem 11 Determine the total output voltage for the circuit in Problem 10 if $V_{DD}=5V$, $V_{SS}=-2V$, $W_1=10\mu$, $L_1=2\mu$, $W_2=6\mu$ and $L_2=1\mu$. Assume the devices are from a process with parameters $\mu_n C_{OX}=100\mu A/v^2$, $\mu_p C_{OX}=30\mu A/v^2$, $V_{TNO}=0.5V$, $V_{TPO}= -0.5V$, $C_{OX}=2fF/\mu^2$, $\lambda = 0$, $\gamma = 0$.

Problem 12 Design an amplifier using only BJT transistors, resistors, capacitors and voltage sources that has a voltage gain of -5 when driving a 2K resistor.

Problem 13 Design an amplifier using only MOS transistors, capacitors, and voltage sources that has a voltage gain of -10 when driving an external 10K resistor.

[illegible]

COMMENTS: DSCN6M018_TSMC

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM V _{th}	0.27/0.18	0.50	-0.51	volts
SHORT I _{dss}	20.0/0.18	547	-250	uA/um
V _{th}		0.51	-0.51	volts
V _{pt}		4.8	-5.6	volts
WIDE I _{ds0}	20.0/0.18	14.4	-4.7	pA/um
LARGE V _{th}	50/50	0.43	-0.42	volts
V _{jbk}		3.1	-4.3	volts
I _{jl}		<50.0	<50.0	pA
K' (U _o *C _{ox} /2)		175.4	-35.6	uA/V^2
Low-field Mobility		416.52	84.54	cm^2/V*s

Design Technology	XL (um)	XW um)
SCN6M_DEEP (lambda=0.09)	0.00	-0.01
thick oxide	0.00	-0.01
SCN6M_SUBM (lambda=0.10)	-0.02	0.00
thick oxide	-0.02	0.00

FOX TRANSISTORS	GATE	N+ACTIVE	P+ACTIVE	UNITS
Vth	Poly	>6.6	<-6.6	volts

Page 6

Sheet Resistance	6.7	7.8	8.0	59.7	313.6	0.08	0.08	ohms/sq
Contact Resistance	10.6	11.0	10.0				4.79	ohms
Gate Oxide Thickness	41							angstrom

PROCESS PARAMETERS	M3	POLY_HRI	M4	M5	M6	N_W	UNITS
Sheet Resistance	0.08		0.08	0.08	0.03	930	ohms/sq
Contact Resistance	9.24		14.05	18.39	20.69		ohms

COMMENTS: BLK is silicide block.

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS
Area (substrate)	942	1163	106	34	14	9	6	5	3		123		125	aF/um^2
Area (N+active)			8484	55	20	13	11	9	8					aF/um^2
Area (P+active)			8232											aF/um^2
Area (poly)				66	17	10	7	5	4					aF/um^2
Area (metal1)					37	14	9	6	5					aF/um^2
Area (metal2)						35	14	9	6					aF/um^2
Area (metal3)							37	14	9					aF/um^2
Area (metal4)								36	14					aF/um^2
Area (metal5)									34			984		aF/um^2
Area (r well)	920													aF/um^2
Area (d well)										582				aF/um^2
Area (no well)	137													aF/um^2
Fringe (substrate)	212	235		41	35	29	21	14						aF/um
Fringe (poly)				70	39	29	23	20	17					aF/um
Fringe (metal1)					52	34		22	19					aF/um
Fringe (metal2)						48	35	27	22					aF/um
Fringe (metal3)							53	34	27					aF/um
Fringe (metal4)								58	35					aF/um
Fringe (metal5)									55					aF/um
Overlap (N+active)			895											aF/um
Overlap (P+active)			737											aF/um

CIRCUIT PARAMETERS		UNITS
Inverters	K	
Vinv	1.0	0.74 volts
Vinv	1.5	0.78 volts
Vol (100 uA)	2.0	0.08 volts
Voh (100 uA)	2.0	1.63 volts
Vinv	2.0	0.82 volts
Gain	2.0	-23.72
Ring Oscillator Freq.		
D1024_THK (31-stg, 3.3V)	300.36	MHz
DIV1024 (31-stg, 1.8V)	363.77	MHz
Ring Oscillator Power		
D1024_THK (31-stg, 3.3V)	0.07	uW/MHz/gate
DIV1024 (31-stg, 1.8V)	0.02	uW/MHz/gate

Note: Go back to HW 9 of Fall 17 to include the small signal gain calculations for the first few problems on this assignment