

Problem 1.

In on 0.5μ CMOS process,

$$V_{gs} = 3.5V, V_{th} = 0.79V, \frac{\mu_{COX}}{2} = \frac{57.8\mu s}{v^2}$$

$$R_{FET} = \frac{2V_{ds}}{2I_D} = \left[ \mu_n * C_{OX} * \frac{W}{L} * (V_{gs} - V_T) \right]^{-1} = 3500$$

$$\frac{W}{L} = \frac{1}{3500 * (2 * 57.8 * 10^{-6}) * (3.5 - 0.79)} = 0.912$$

In the IBM 0.13 μ CMOS Process,

$$V_{gs} = 1.5V, V_{th} = 0.41V, \frac{\mu_{COX}}{2} = \frac{308.0\mu s}{v^2}$$

$$R_{FET} = \frac{2V_{ds}}{2I_D} = \left[ \mu_n * C_{OX} * \frac{W}{L} * (V_{gs} - V_T) \right]^{-1} = 3500$$

$$\frac{W}{L} = \frac{1}{3500 * (2 * 308.0 * 10^{-6}) * (1.5 - 0.41)} = 0.426$$

Problem 2.

Minimum sized inverter:

$$V_{gs} = 1.5V, \text{ in IBM 0.13 } \mu \frac{W}{L} = \frac{0.16}{0.12}$$

$$C_{GSN} = (0.16)(0.12)(11176 * 10^{-18}) = 214.579aF$$

$$C_{ASP} = (0.16)(0.12)(10496 * 10^{-18}) = 201.523aF$$

$$C_L = C_{ASP} + C_{GSN} = 416.102aF = 0.416fF$$

$$\text{in ON 0.5}\mu: \frac{W}{L} = \frac{3.0}{0.6}$$

$$R_{SWN} = \left( \frac{2 * 57.8 * 10^{-6} * 3.0}{0.6} * (1.5 - 0.79) \right)^{-1} = 2.437k\Omega$$

$$R_{SWP} = \left( \frac{2 * -19.1 * 10^{-6} * 3.0}{0.6} * (-1.5 - 0.79) \right)^{-1} = 9.027k\Omega$$

$$\rightarrow T_{HL} = 2.437k * 416.102a = 1.014pS$$

$$T_{LH} = 9.027k * 416.102a = 3.756pS$$

Problem 3.

$$\left( \frac{1.6 - V_a}{1000} \right) = I_{D_1} + I_{D_2} = (50 + 250)\mu^2 * \left( 5 \frac{fA}{\mu^2} \right) e^{\left( \frac{x}{0.0259} \right)} \rightarrow V_a = 0.528V$$

$$I_{D_1} = 0.178mA ; I_{D_2} = 0.892 mA$$

Problem 4

$$\frac{15 - V_D}{2000} = I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{V_D}{0.0259}\right)} \rightarrow V_D = 0.647 V$$

$$I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.647}{0.0259}\right)} = 7.063 mA$$

Problem 5

$$\frac{0.520 - V_D}{4000} = I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * \left(e^{\left(\frac{V_D}{0.0259}\right)} - 1\right) \rightarrow V_D = 0.510 V$$

$$I_D = 100\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.478}{0.0259}\right)} = 35.62 \mu A$$

Problem 6

$$I_{D1} \sim I_{D2} = 200\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.55}{0.0259}\right)} \sim 200\mu^2 * \left(1 \frac{fA}{\mu^2}\right) * e^{\left(\frac{0.65}{0.0259}\right)} = 333.81 \mu A \sim 15.86 mA$$

Problem 7.

- $I_{D1} = \left(100 * 10^{-6} * \frac{8}{3 * 2} (3 - 1)^2\right) = 0.533 mA \rightarrow 5 - 4000 * 0.0006 = 2.87V$
- $I_{D2} = \left(100 * 10^{-6} * \left(\frac{12}{3}\right) * (2 - 1)^2\right) = 0.4 mA \rightarrow 5 - 30k * .4m = -7 \rightarrow$  Must not be in saturation region.  
 $V_{DS} < V_{GS} - V_T \rightarrow$  Triode Region  
 $\frac{(5 - V_{DS})}{30k} = 100 * 10^{-6} * \frac{12}{1.5} * \left(2 - 1 - \frac{V_{DS}}{2}\right) V_{DS}, (V_{GS} - V_T = 1V)$   
 $V_{DS} = 0.224$  or  $V_{DS} = 1.86$  as it is in triode region,  $V_{out} = 0.224V$
- $I_{D3} = 33 * 10^{-6} * \frac{6}{6} * (2 - 1)^2 = 0.033 mA \rightarrow 5 - 5k * 0.033m = 4.835V$

Problem 8.

$$\frac{9 - V_{out}}{5000} = I_D = 100 * 10^{-6} * \frac{W}{2\mu * 2} (V_{out} - 1)^2 \rightarrow W = 12.0 \mu m$$

Problem 9

- a. Assuming Saturation,  $V_{out} = x$

$$I_{D_1} = \mu C_{OX} \left( \frac{W}{2L} \right) (V_{GS} - V_T)^2 = 100 * 10^{-6} * \frac{6}{2 * 2} * (x - 1)^2 = 1.5 * 10^{-4} * (x - 1)^2$$

$$I_{D_2} = 100 * 10^{-6} * \left( \frac{2}{12 * 2} \right) * (6 - x - 1)^2 = 8.33 * 10^{-6} * (6 - x - 1)^2$$

$$I_{D_1} = I_{D_2} \rightarrow 1.5 * 10^{-4} (x - 1)^2 = 8.33 * 10^{-6} (6 - x - 1)^2 \rightarrow V_{out} = x = 1.763 V$$

- b.  $V_{DG1} = 0 \rightarrow$  Saturation

$$\text{For } M_1, I_{SD} = \mu C_{OX} \left( \frac{W}{2L} \right) (V_{GS} - V_{TP})^2 = 33 * 10^{-5} * \left( \frac{8}{2 * 2} \right) (V_G - 10 - (-1))^2$$

$$\rightarrow 400 * 10^{-6} = 33 * 10^{-6} * \frac{8}{4} * (V_G - 9)^2 \rightarrow V_G = 6.54V \text{ or } 11.46V$$

$$\rightarrow V_{GS} = -3.46V \text{ or } 1.46V$$

$$\text{For } M_2, I_{SD} = \mu C_{OX} \left( \frac{W}{2L} \right) (V_{GS} - V_{TP})^2 = 33 * 10^{-6} * \left( \frac{10}{2 * 6} \right) (1.46 + 1)^2$$

$$I_{SD} = 166 \mu A = I_{OUT}$$

$$\text{Check: } V_D = (1.5k * 166 \mu) = 0.249, V_{DS} = 0.249V - 10V = -9.751V$$

$$V_{GS} - V_{TP} = 1.46 + 1 = 2.46$$

$$V_{DS} < V_{GS} - V_{TP} \rightarrow \text{Saturation}$$

Problem 10.

- a) Saturation for  $M_1$  and  $M_2$

$$I_{D_1} = \frac{100 * 10^{-6}}{2} * \frac{W}{L} (2 - 1)^2 = I_{D_2} = 100 * 10^{-6} * \frac{8}{2 * 2} * (5 - 3.5 - 1)^2$$

$$\rightarrow \frac{\frac{W}{L}}{\frac{8}{2}} = \frac{1}{4} \rightarrow \frac{W}{L} = 1 \rightarrow W = 2 \mu m, L = 2 \mu m$$

- b)  $V_{out} = 0.8 V < V_{in} - 1V = 1V \rightarrow M_1$  is in triode region.

$$I_{D_1} = I_{D_2} = 100 * 10^{-6} * \frac{W}{L} * \left( 3 - 1 - \frac{V_{out}}{2} \right) V_{out} = 100 * 10^{-6} * \left( \frac{8}{4} \right) * (5 - .5 - 1)^2$$

$$\rightarrow \frac{W}{L} = \frac{16}{1} \rightarrow W = 16 \mu m, \quad L = 1 \mu m$$

Problem 11.

$$A. V_{OUT} = I(10k\Omega) + 0.575V, V_t = \frac{kT}{q}, I(T) = \left[ J_{SX} \left( T^m e^{\frac{-V_{go}}{V_t}} \right) \right] A * e^{\frac{V_D}{V_t}}$$

$$A * J_{SX} \left[ T^m e^{\frac{-V_{go}}{V_t}} \right] * e^{\frac{0.575}{V_t}} = \frac{0.5A}{\mu^2} * [1.66 * 10^{-18}] * 100 \mu^2 * 284.47 * 10^9 = 23.64 \mu A$$

$$V_{OUT} = 0.811V$$

- B.  $V_{OUT} = 72.7V \rightarrow 20V$  (clipping)

- C.  $V_{OUT} = 10.86kV \rightarrow 20V$  (clipping)

Problem 12.

Assuming saturation:

$$I_{D_1} = 33 * 10^{-6} * \frac{5}{2 * 5} * (5 - 3 - 1)^2 = I_{D_2} = 100 * 10^{-6} \left( \frac{5}{10} \right) (V_{out} - 1)^2$$

$$V_{out} = 1.5745V$$

Problem 13.

$$C = \frac{C_{j0} * A}{\left(1 - \frac{V_d}{\phi_b}\right)^n} \text{ where } \phi \approx 0.6V \text{ and } n \approx 0.5. \text{ At } V_b = 0 \text{ the denominator} \rightarrow 1, \text{ so } C_{j0}A = 200fF$$

$$\text{With } V_b = -3, C = \frac{200 * 10^{-15}}{\left(1 - \left(-\frac{3}{.6}\right)\right)^{0.5}} = 81.65fF$$

$$\text{With } V_b = 0.25V, C = \frac{200 * 10^{-15}}{\left(1 - \left(\frac{.25}{.6}\right)\right)^{0.5}} = 261.86fF$$

Problem 14.

- a) Since there's no protection circuitry the whole voltage will be applied to the IC.

$$\text{HBM1 } V_{INT} = 250V, \quad \text{HBM2 } V_{INT} = 2000V$$

- b) For HBM1  $V_D > V_{DD}$  so diode 2 is on

$$\frac{250 - V_{INT}}{10K} = I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{V_{INT}-5}{0.0259}\right)} \rightarrow V_{INT} = 5.918V$$

For HBM2  $V_D > V_{DD}$  so diode 2 is on

$$\frac{2000 - V_{INT}}{10K} = I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{V_{INT}-5}{0.0259}\right)} \rightarrow V_{INT} = 5.972V$$

- c) For HBM1  $I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{5.918-5}{0.0259}\right)} = 24.73mA$

$$\text{For HBM2 } I_D = 1000\mu^2 * \left(10^{-20} \frac{A}{\mu^2}\right) * e^{\left(\frac{5.972-5}{0.0259}\right)} = 198.89mA$$


- d) The resistor reduces the current that flows through the diode. The disadvantage is it dissipates a lot of heat.

Problem 15.

$$2.5 * 10^{-12} = \left( \frac{2 * 10^{-12}}{\left(1 - \left(\frac{V}{0.6}\right)\right)^{0.5}} \right) \rightarrow V = 0.216V \text{ so we can design a circuit that provides } 0.216V \text{ when } 3.8V$$

is applied. This is easiest with a voltage divider. Using  $1K\Omega$  as the resistor in series with the capacitor the resistor in parallel will be  $0.216 = \frac{x}{1k+x} * 3.8 \rightarrow x = 60.268\Omega$

Problem 16.

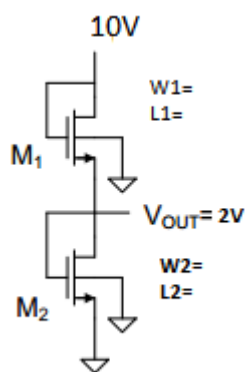

$$V_{out} = 2.0V, V_{DD} = 6.0V$$

$$I_{D1} = 100 * 10^{-6} * \left( \frac{W_1}{2L_1} \right) (6 - V_{out} - 1)^2$$

$$I_{D2} = 100 * 10^{-6} * \left( \frac{W_2}{2L_2} \right) (V_{out} - 1)^2$$

We can set 3 variables to find the fourth, so  $L_1 = L_2 = 1\mu m$

$$W_1 = 5\mu m \text{ and we know that } I_{D1} = I_{D2}$$

$$\rightarrow W_2 = 45\mu m$$

Problem 17.

Testbench:

Ln#	
1	<code>`timescale 1ns/1ps</code>
2	
3	<code>module JKFF_tb();</code>
4	<code>reg J, K, CLK;</code>
5	<code>wire Q, Q_not;</code>
6	
7	<code>JKFF ff1(.iJ(J), .iK(K), .oQ(Q), .oQ_not(Q_not), .iCLK(CLK));</code>
8	
9	<code>initial begin</code>
10	<code>J = 1'b0;</code>
11	<code>K = 1'b0;</code>
12	<code>CLK = 1'b0;</code>
13	<code>end</code>
14	
15	<code>always #10 CLK = ~CLK;</code>
16	<code>always #20 J = ~J;</code>
17	<code>always #40 K = ~K;</code>
18	<code>endmodule</code>
19	

## Verilog Code:

```

Ln#
1
2 module JKFF(iJ, iK, oQ, oQ_not, iCLK);
3     input iJ, iK, iCLK;
4     output oQ, oQ_not;
5
6     reg Q;
7
8     assign oQ = Q;
9     assign oQ_not = ~Q;
10
11     initial begin
12         Q = 1'b0;
13     end
14
15     always @(posedge iCLK) begin
16         if(iJ==1 & iK==1) begin
17             Q = ~Q;
18         end else if(iJ==0 & iK==1) begin
19             Q = 0;
20         end else if(iJ==1 & iK==0) begin
21             Q = 1;
22         end else begin
23             Q = Q;
24         end
25     end
26
27     end
28
29
30 endmodule
31

```

## Output:

