


EE 330

Lecture 7

- Propagation Delay
- Stick Diagrams
- Technology Files
 - Design Rules

Pass Transistor Logic

Review from Last Time

 

$$Y = A \bullet B$$


Requires only 1 transistor (and a resistor)

- Pass transistor logic can offer significant reductions in complexity for some functions (particularly noninverting)
- Resistor may require more area than several hundred or even several thousand transistors
- Signal levels may not go to V_{DD} or to 0V
- Static power dissipation may not be zero
- Signals may degrade unacceptably if multiple gates are cascaded
- “resistor” often implemented with a transistor to reduce area but signal swing and power dissipation problems still persist
- Pass transistor logic is widely used

Review from Last Time


MOS Transistor

 Qualitative Discussion of n-channel Operation



n-channel MOSFET


For V_{GS} small

 

n-channel MOSFET

For V_{GS} large

 
- Electrically created inversion layer forms a “thin “film” resistor
- Capacitance from gate to channel region is distributed
- Lumped capacitance much easier to work with



Review from Last Time


MOS Transistor

 Qualitative Discussion of p-channel Operation




p-channel MOSFET

For $|V_{GS}|$ small

 


p-channel MOSFET

 

For $|V_{GS}|$ large

- Electrically created inversion layer forms a “thin “film” resistor
- Capacitance from gate to channel region is distributed
- Lumped capacitance much easier to work with

Improved Switch-Level Model

 


C_{GS} and R_{SW} dependent upon device sizes and process

For minimum-sized devices in a 0.5u process with $V_{DD}=5V$

$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$


Considerable emphasis will be placed upon device sizing to manage C_{GS} and R_{SW}

 Is a capacitor of 1.5fF small enough to be neglected?



Area allocations shown to relative scale:

 
Is a capacitor of 1.5fF small enough to be neglected?




Area allocations shown to relative scale:

- Not enough information at this point to determine whether this very small capacitance can be neglected
- Will answer this important question later


Model Summary (for n-channel)

 

1. Switch-Level model

 


2. Improved switch-level model

 


Switch closed for $V_{GS} = \text{large}$
Switch open for $V_{GS} = \text{small}$

Other models will be developed later


Model Summary (for p-channel)

 

1. Switch-Level model

 


2. Improved switch-level model

 

Switch closed for $|V_{GS}| = \text{large}$
Switch open for $|V_{GS}| = \text{small}$


Other models will be developed later

- Pass Transistor Logic
- Improved Switch-Level Model
-  • Propagation Delay
- Stick Diagrams
- Technology Files

Example

What are t_{HL} and t_{LH} ?


Assume $V_{DD}=5V$

 

With basic switch level model ?


With improved switch level model ?

Example


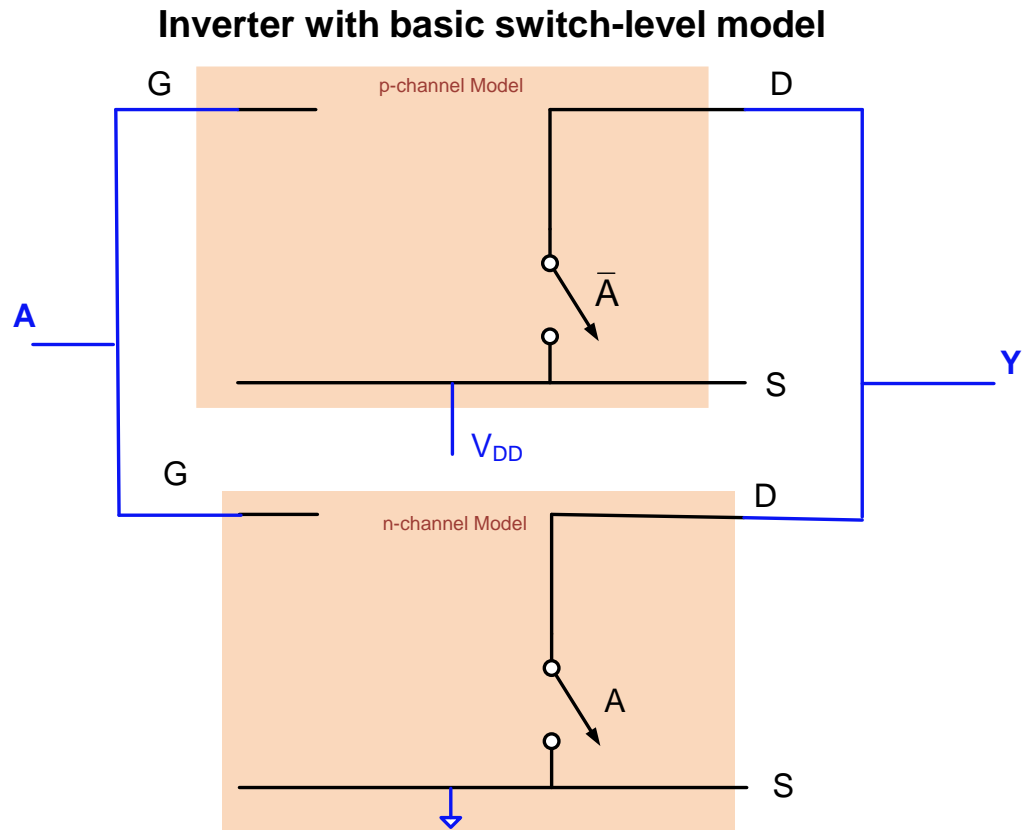


Example

What are t_{HL} and t_{LH} ?

 


With basic switch level model

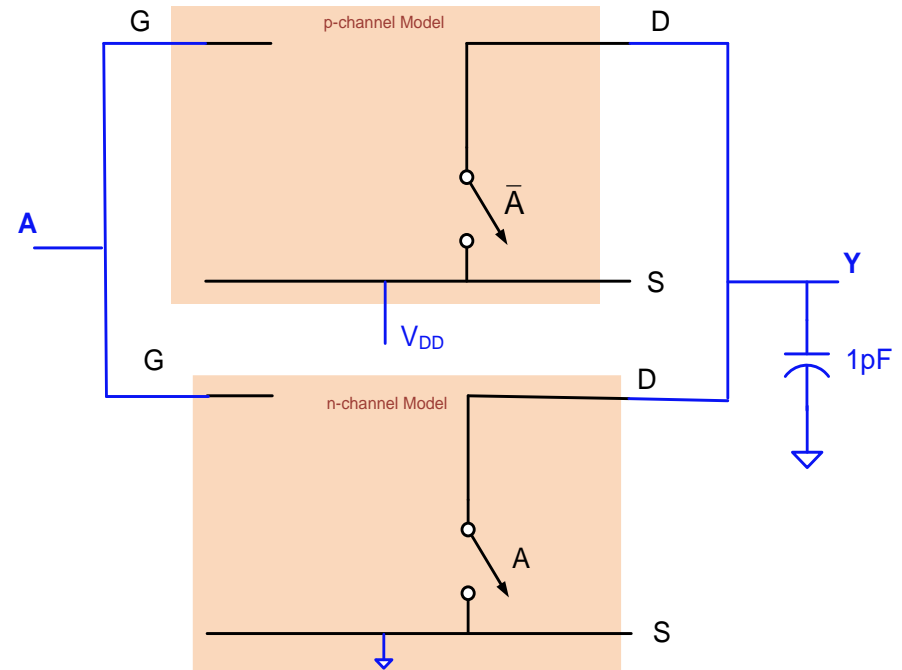 


$$t_{HL}=t_{LH}=0$$

 Example (cont)


With simple switch-level model $t_{HL}=t_{LH}=0$



With improved model ?

 


Inverter Model?

 


Example (cont)

Inverter with improved model

Inverter Model


 


Inverter with Improved Model

 


Example (cont)

With improved model $t_{HL}=?$

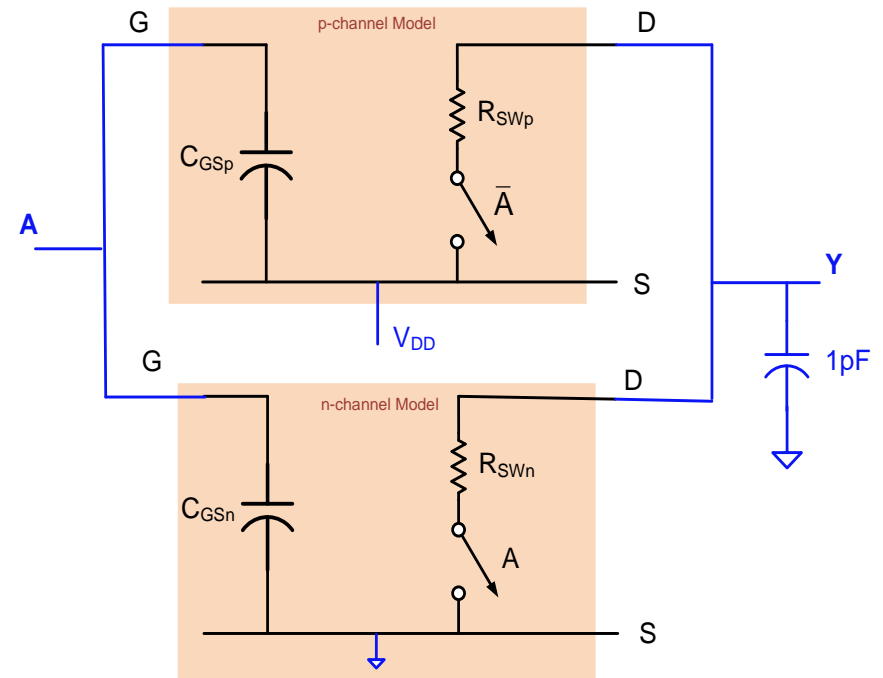 

 
To initiate a HL output transition, assume Y has been in the high state for a long time and lower switch closes at time $t=0$



Example (cont)

With improved model

$$t_{HL}=?$$

 

Recognize circuit as a first-order RC network

Recall: Step response of any first-order network with LHP pole can be written as

$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$


where F is the final value, I is the initial value and τ is the time constant of the circuit

(from Chapter 7 of Nilsson and Riedel)

For the circuit above, $F=0$, $I=5$ and $\tau = R_{SWn} C_L$

Example (cont)

With improved model

 


$$t_{HL}=?$$

$$V_{OUT}(t) = F + (1 - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 5e^{-\frac{t}{\tau}}$$



$$\tau = R_{SWn} C_L$$

 

how is t_{HL} defined?

Example (cont)

$$t_{HL}=?$$

  


Define t_{HL} to be the time taken for output to drop to I/e

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad \frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$

t_{HL} as defined here has proved useful at analytically predicting response time of circuits

Example (cont)

With improved model

 

$$\frac{I}{e} = F + (I - F)e^{-\frac{t_{HL}}{\tau}}$$

$$\frac{I}{e} = Ie^{-\frac{t_{HL}}{\tau}}$$

$$\frac{1}{e} = e^{-\frac{t_{HL}}{\tau}}$$


$$t_{HL} = \tau$$




$$t_{HL} = R_{SWn} C_L$$

Example (cont)

With improved model $t_{LH}=?$

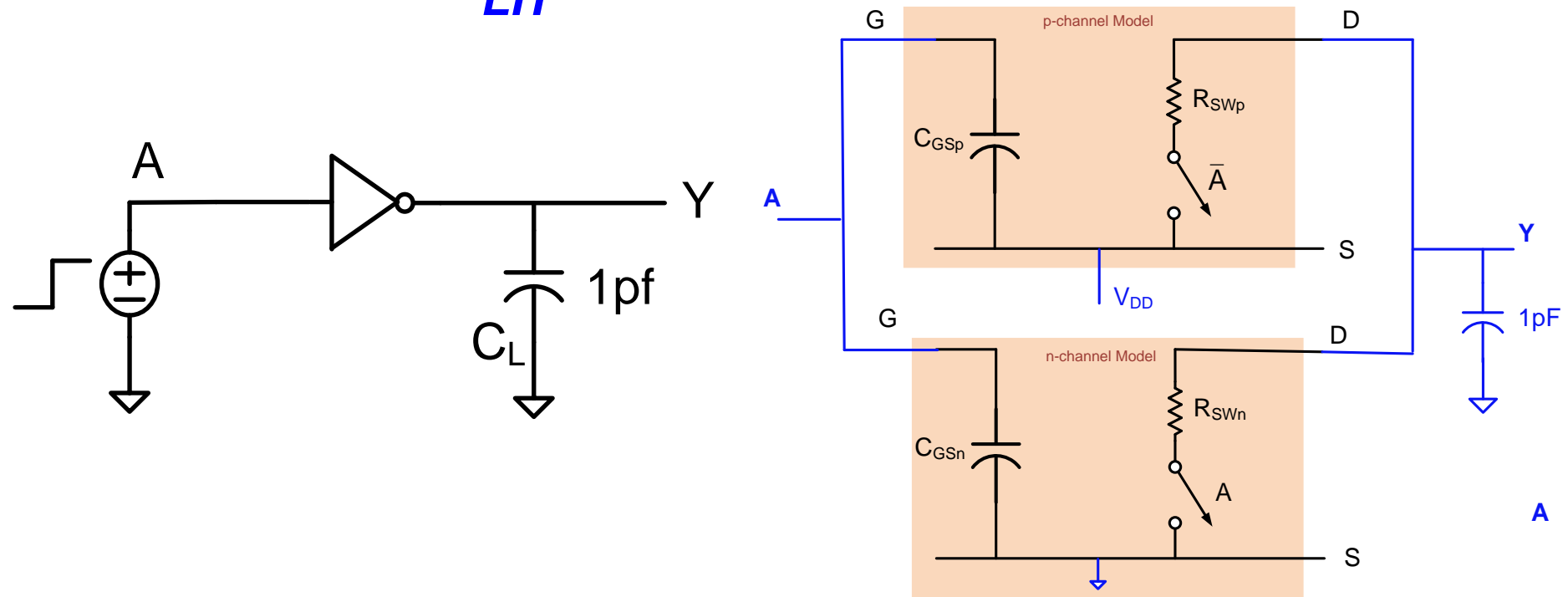

 
Assume output in low state for a long time and upper switch closes at time $t=0$



0V is the initial condition on C_L

Example (cont)

With improved model $t_{LH}=?$

 


$$y(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

For this circuit, $F=5$, $I=0$ and $\tau = R_{SWp} C_L$

Example (cont)

With improved model

 


$t_{LH}=?$

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}}$$

$$V_{OUT}(t) = 5\left(1 - e^{-\frac{t}{\tau}}\right)$$

$$\tau = R_{SWp} C_L$$

 



how is t_{LH} defined?

Example (cont)

With improved model

$t_{LH}=?$

Define t_{LH} as shown on figure

  

t_{LH} as defined has proven useful for analytically predicting response time of circuits

$$V_{OUT}(t) = F + (I - F)e^{-\frac{t}{\tau}} \quad \longrightarrow \quad F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$

Example (cont)

With improved model

$$t_{LH}=?$$

$$F\left(1 - \frac{1}{e}\right) = F + (I - F)e^{-\frac{t_{LH}}{\tau}}$$


$$F\left(1 - \frac{1}{e}\right) = F + (F)e^{-\frac{t_{LH}}{\tau}}$$

$$1 - \frac{1}{e} = 1 + e^{-\frac{t_{LH}}{\tau}}$$

$$t_{LH} = \tau$$





$$t_{LH} = R_{SWp} C_L$$

 

Example (cont)

With improved model

  

$$t_{HL} \cong R_{SWn} C_L$$

In the ON 0.5u process
 $= 2K \bullet 1pF = 2nsec$

$$t_{LH} \cong R_{SWp} C_L$$


$$= 6K \bullet 1pF = 6nsec$$

Note this circuit is quite fast !

Note that t_{HL} is much shorter than t_{LH}

Often C_L will be even smaller and the circuit will be much faster !!

 Summary: What is the delay of a minimum-sized inverter driving a 1pF load?





In the ON 0.5μ process

$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 1pF = 2n \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 1pF = 6n \text{ sec}$$

Improved switch-level model

  

Switch closed for $V_{GS} = \text{large}$


Switch open for $V_{GS} = \text{small}$

- Previous example showed why R_{SW} in the model was important
- But of what use is the C_{GS} which did not enter the previous calculations?

For minimum-sized devices in a 0.5μ process


$$C_{GS} \cong 1.5\text{fF} \quad R_{sw} \cong \left. \begin{array}{l} 2\text{K}\Omega \text{ n-channel} \\ 6\text{K}\Omega \text{ p-channel} \end{array} \right\}$$

 One gate often drives one or more other gates !



What are t_{HL} and t_{LH} ?

 Example: What is the delay of a minimum-sized inverter driving another identical device?




?




Load on first inverter

C_{GSn} and C_{GSp} both 1.5fF

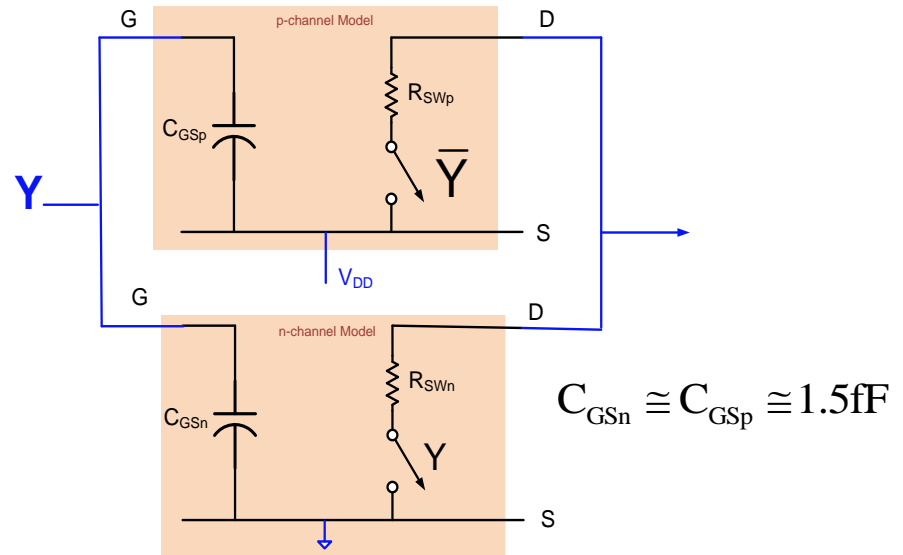


 Loading effects same whether C_{GSp} and/or C_{GSn} connected to V_{DD} or GND



For convenience, will reference both to ground


 
Is a capacitor of 1.5fF small enough to be neglected?




Area allocations shown to relative scale:

- This example will provide insight into the answer of the question

  Example: What is the delay of a minimum-sized inverter driving another identical device? Assume $V_{DD}=5V$



 
Generalizing the Previous Analysis to Arbitrary Load



$$t_{HL} \cong R_{SWn} C_L$$

$$t_{LH} \cong R_{SWp} C_L$$

 Example: What is the delay of a minimum-sized inverter driving another identical device?




$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 3fF = 6p \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 3fF = 18p \text{ sec}$$

Do gates really operate this fast?

What would be the maximum clock rate for acceptable operation?

 Example: What is the delay of a minimum-sized inverter driving another identical device?



$$t_{HL} \cong R_{SWn} C_L = 6p \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 18p \text{ sec}$$

What would be the maximum clock rate for acceptable operation?


$$T_{CLK-min} = t_{HL} + t_{LH}$$
$$f_{CLK-max} = \frac{1}{T_{CLK-min}} = \frac{1}{24psec} = 40GHz$$

And much faster in a finer feature process !!

??????

What would be the implications of allowing for 10 levels of logic and 10 loads (FanOut=10)?

 Example: What is the delay of a minimum-sized inverter driving another identical device? SUMMARY




$$t_{HL} \cong R_{SWn} C_L = 2K \bullet 3fF = 6p \text{ sec}$$

$$t_{LH} \cong R_{SWp} C_L = 6K \bullet 3fF = 18p \text{ sec}$$

Note this is very fast but even the small 1.5fF capacitors are not negligible !

Response time of logic gates

 

$$t_{HL} \cong R_{SWn} C_L$$


$$t_{LH} \cong R_{SWp} C_L$$

- Logic Circuits can operate very fast
- Extremely small parasitic capacitances play key role in speed of a circuit

Stick Diagrams



- It is often necessary to obtain information about placement, interconnect and physical-layer structure
- Stick diagrams are often used for small component-count blocks
- Approximate placement, routing, and area information can be obtained rather quickly with the use of stick diagrams

Stick Diagrams

 

Additional layers can be added and color conventions are personal

Stick Diagram

 
 


A stick diagram is not a layout but gives the basic structure (including location,, orientation and interconnects) that will be instantiated in the actual layout itself



Modifications can be made much more quickly on a stick diagram than on a layout


Iteration may be needed to come up with a good layout structure

Stick Diagram

  


Alternate Representations

  

 

Technology Files

 

- Provide Information About Process
 - Process Flow (Fabrication Technology)
 - Model Parameters
 - Design Rules
- Serve as Interface Between Design Engineer and Process Engineer
- Insist on getting information that is deemed important for a design
 - Limited information available in academia
 - Foundries often sensitive to who gets access to information
 - Customer success and satisfaction is critical to foundries

Technology Files

- Design Rules
- Process Flow (Fabrication Technology) (will discuss next)
- Model Parameters (will discuss in substantially more detail after device operation and more advanced models are introduced)

First – A preview of what the technology files look like !

Typical Design Rules

TABLE 2B.2
Design rules for a typical p-well CMOS process
 (See Table 2B.3 in color plates for graphical interpretation)

		Dimensions	
		Microns	Scalable
1.	p-well (CIF Brown, Mask #1 ^a)		
1.1	Width	5	4 λ
1.2	Spacing (different potential)	15	10 λ
1.3	Spacing (same potential)	9	6 λ
2.	Active (CIF Green, Mask #2)		
2.1	Width	4	2 λ
2.2	Spacing	4	2 λ
2.3	p ⁺ active in n-subs to p-well edge	8	6 λ
2.4	n ⁺ active in n-subs to p-well edge	7	5 λ
2.5	n ⁺ active in p-well to p-well edge	4	2 λ
2.6	p ⁺ active in p-well to p-well edge	1	λ
3.	Poly (POLY I) (CIF Red, Mask #3)		
3.1	Width	3	2 λ
3.2	Spacing	3	2 λ
3.3	Field poly to active	2	λ
3.4	Poly overlap of active	3	2 λ
3.5	Active overlap of poly	4	2 λ
4.	p ⁺ select (CIF Orange, Mask #4)		
4.1	Overlap of active	2	λ
4.2	Space to n ⁺ active	2	λ
4.3	Overlap of channel ^b	3.5	2 λ
4.4	Space to channel ^b	3.5	2 λ
4.5	Space to p ⁺ select	3	2 λ
4.6	Width	3	2 λ

Typical Design Rules (cont)

5.	Contact ^c (CIF Purple, Mask #6)		
5.1	Square contact, exactly	3×3	$2\lambda \times 2\lambda$
5.2	Rectangular contact, exactly	3×8	$2\lambda \times 6\lambda$
5.3	Space to different contact	3	2λ
5.4	Poly overlap of contact	2	λ
5.5	Poly overlap in direction of metal 1	2.5	2λ
5.6	Space to channel	3	2λ
5.7	Metal 1 overlap of contact	2	λ
5.8	Active overlap of contact	2	λ
5.9	p ⁺ select overlap of contact	3	2λ
5.10	Subs./well shorting contact, exactly	3×8	$2\lambda \times 6\lambda$
6.	Metal 1 ^d (CIF Blue, Mask #7)		
6.1	Width	3	2λ
6.2	Spacing	4	3λ
6.3	Maximum current density	0.8 mA/ μ	0.8 mA/ μ


Typical Design Rules (cont)

7. Via ^e (CIF Purple Hatched, Mask #C1)		
7.1	Size, exactly	3×3 $2\lambda \times 2\lambda$
7.2	Separation	3 2λ
7.3	Space to poly edge	4 2λ
7.4	Space to contact	3 2λ
7.5	Overlap by metal 1	2 λ
7.6	Overlap by metal 2	2 λ
7.7	Space to active edge	3 2λ
8. Metal 2 (CIF Orange Hatched, Mask #C2)		
8.1	Width	5 3λ
8.2	Spacing	5 3λ
8.3	Bonding pad size	100×100 $100 \mu \times 100 \mu$
8.4	Probe pad size	75×75 $75 \mu \times 75 \mu$
8.5	Bonding pad separation	50 50μ
8.6	Bonding to probe pad	30 30μ
8.7	Probe pad separation	30 30μ
8.8	Pad to circuitry	40 40μ
8.9	Maximum current density	$0.8 \text{ mA}/\mu$ $0.8 \text{ mA}/\mu$
9. Passivation ^f (CIF Purple Dashed, Mask #8)		
9.1	Bonding pad opening	90×90 $90 \mu \times 90 \mu$
9.2	Probe pad opening	65×65 $65 \mu \times 65 \mu$
10. Metal 2 crossing coincident metal 1 and poly ^g		
10.1	Metal 1 to poly edge spacing when crossing metal 2	2 λ
10.2	Rule domain	2 λ
11. Electrode (POLY II) ^h (CIF Purple Hatched, Mask #A1)		
11.1	Width	3 2λ
11.2	Spacing	3 2λ
11.3	POLY I overlap of POLY II	2 λ
11.4	Space to contact	3 2λ

Typical Design Rules (cont)

SCMOS Layout Rules - Poly

Rule	Description	Lambda		
		SCMOS	SUBM	DEEP
3.1	Minimum width	2	2	2
3.2	Minimum spacing over field	2	3	3
3.2.a	Minimum spacing over active	2	3	4
3.3	Minimum gate extension of active	2	2	2.5
3.4	Minimum active extension of poly	3	3	4
3.5	Minimum field poly to active	1	1	1

 

Typical Process Description

Process scenario of major process steps in typical p-well CMOS process^a

1. Clean wafer
2. GROW THIN OXIDE
3. Apply photoresist
4. PATTERN P-WELL (MASK #1)
5. Develop photoresist
6. Deposit and diffuse p-type impurities
7. Strip photoresist
8. Strip thin oxide
9. Grow thin oxide
10. Apply layer of Si_3N_4
11. Apply photoresist
12. PATTERN Si_3N_4 (active area definition) (MASK #2)
13. Develop photoresist
14. Etch Si_3N_4
15. Strip photoresist
Optional field threshold voltage adjust
 - A.1 Apply photoresist
 - A.2 PATTERN ANTIMOAT IN SUBSTRATE (MASK #A1)
 - A.3 Develop photoresist
 - A.4 FIELD IMPLANT (n-type)
 - A.5 Strip photoresist
16. GROW FIELD OXIDE
17. Strip Si_3N_4
18. Strip thin oxide
19. GROW GATE OXIDE
20. POLYSILICON DEPOSITION (POLY I)
21. Apply photoresist
22. PATTERN POLYSILICON (MASK #3)
23. Develop photoresist
24. ETCH POLYSILICON

Typical Process Description (cont)

- | | | |
|-------|--|------------|
| 25. | Strip photoresist | |
| | <i>Optional steps for double polysilicon process</i> | |
| | B.1 Strip thin oxide | |
| | B.2 GROW THIN OXIDE | |
| | B.3 POLYSILICON DEPOSITION (POLY II) | |
| | B.4 Apply photoresist | |
| | B.5 PATTERN POLYSILICON | (MASK #B1) |
| | B.6 Develop photoresist | |
| | B.7 ETCH POLYSILICON | |
| | B.8 Strip photoresist | |
| | B.9 Strip thin oxide | |
| <hr/> | | |
| 26. | Apply photoresist | |
| 27. | PATTERN P-CHANNEL DRAINS AND SOURCES AND P ⁺ GUARD RINGS (p-well ohmic contacts) | (MASK #4) |
| 28. | Develop photoresist | |
| 29. | p ⁺ IMPLANT | |
| 30. | Strip photoresist | |
| 31. | Apply photoresist | |
| 32. | PATTERN N-CHANNEL DRAINS AND SOURCES AND N ⁺ GUARD RINGS (top ohmic contact to substrate) | (MASK #5) |
| 33. | Develop photoresist | |
| 34. | n ⁺ IMPLANT | |
| 35. | Strip photoresist | |
| 36. | Strip thin oxide | |
| 37. | Grow oxide | |
| 38. | Apply photoresist | |
| 39. | PATTERN CONTACT OPENINGS | (MASK #6) |
| 40. | Develop photoresist | |
| 41. | Etch oxide | |
| 42. | Strip photoresist | |
| 43. | APPLY METAL | |
| 44. | Apply photoresist | |
| 45. | PATTERN METAL | (MASK #7) |
| 46. | Develop photoresist | |
| 47. | Etch metal | |

Typical Process Description (cont)

- 48. Strip photoresist
 - Optional steps for double metal process*
 - C.1 Strip thin oxide
 - C.2 DEPOSIT INTERMETAL OXIDE
 - C.3 Apply photoresist
 - C.4 PATTERN VIAS (MASK #C1)
 - C.5 Develop photoresist
 - C.6 Etch oxide
 - C.7 Strip photoresist
 - C.8 APPLY METAL (Metal 2)
 - C.9 Apply photoresist
 - C.10 PATTERN METAL (MASK #C2)
 - C.11 Develop photoresist
 - C.12 Etch metal
 - C.13 Strip photoresist
- 49. APPLY PASSIVATION
- 50. Apply photoresist
- 51. PATTERN PAD OPENINGS (MASK #8)
- 52. Develop photoresist
- 53. Etch passivation
- 54. Strip photoresist
- 55. ASSEMBLE, PACKAGE AND TEST

Typical Model Parameters

Process parameters for a typical^a p-well CMOS process

	Typical	Tolerance ^b	Units
Square law model parameters			
V_{T0} (threshold voltage)			
n-channel (V_{TN0})	0.75	± 0.25	V
p-channel (V_{TP0})	-0.75	± 0.25	V
K' (conduction factor)			
n-channel	24	± 6	$\mu\text{A}/\text{V}^2$
p-channel	8	± 1.5	$\mu\text{A}/\text{V}^2$
γ (body effect)			
n-channel	0.8	± 0.4	$\text{V}^{1/2}$
p-channel	0.4	± 0.2	$\text{V}^{1/2}$
λ (channel length modulation)			
n-channel	0.01	$\pm 50\%$	V^{-1}
p-channel	0.02	$\pm 50\%$	V^{-1}
ϕ (surface potential)			
n- and p-channel	0.6	± 0.1	V
Process parameters			
μ (channel mobility)			
n-channel	710		$\text{cm}^2/(\text{V} \cdot \text{s})$
p-channel	230		$\text{cm}^2/(\text{V} \cdot \text{s})$
Doping^c			
n^+ active	5	± 4	$10^{18}/\text{cm}^3$
p^+ active	5	± 4	$10^{17}/\text{cm}^3$
p-well	5	± 2	$10^{16}/\text{cm}^3$
n-substrate	1	± 0.1	$10^{16}/\text{cm}^3$

Typical Model Parameters (cont)

Physical feature sizes			
T_{ox} (gate oxide thickness)	500	± 100	\AA
Total lateral diffusion			
n-channel	0.45	± 0.15	μ
p-channel	0.6	± 0.3	μ
Diffusion depth			
n ⁺ diffusion	0.45	± 0.15	μ
p ⁺ diffusion	0.6	± 0.3	μ
p-well	3.0	$\pm 30\%$	μ
Insulating layer separation			
POLY I to POLY II	800	± 100	\AA
Metal 1 to Substrate	1.55	± 0.15	μ
Metal 1 to Diffusion	0.925	± 0.25	μ
POLY I to Substrate (POLY I on field oxide)	0.75	± 0.1	μ
Metal 1 to POLY I	0.87	± 0.7	μ
Metal 2 to Substrate	2.7	± 0.25	μ
Metal 2 to Metal I	1.2	± 0.1	μ
Metal 2 to POLY I	2.0	± 0.07	μ

Typical Model Parameters (cont)

Capacitances ^d			
C_{OX} (gate oxide capacitance, n- and p-channel)	0.7	± 0.1	fF/ μ^2
POLY I to substrate, poly in field	0.045	± 0.01	fF/ μ^2
POLY II to substrate, poly in field	0.045	± 0.01	fF/ μ^2
Metal 1 to substrate, metal in field	0.025	± 0.005	fF/ μ^2
Metal 2 to substrate, metal in field	0.014	± 0.002	fF/ μ^2
POLY I to POLY II	0.44	± 0.05	fF/ μ^2
POLY I to Metal 1	0.04	± 0.01	fF/ μ^2
POLY I to Metal 2	0.039	± 0.003	fF/ μ^2
Metal 1 to Metal 2	0.035	± 0.01	fF/ μ^2
Metal 1 to diffusion	0.04	± 0.01	fF/ μ^2
Metal 2 to diffusion	0.02	± 0.005	fF/ μ^2
n ⁺ diffusion to p-well (junction, bottom)	0.33	± 0.17	fF/ μ^2
n ⁺ diffusion sidewall (junction, sidewall)	2.6	± 0.6	fF/ μ
p ⁺ diffusion to substrate (junction, bottom)	0.38	± 0.12	fF/ μ^2
p ⁺ diffusion sidewall (junction, sidewall)	3.5	± 2.0	fF/ μ
p-well to substrate (junction, bottom)	0.2	± 0.1	fF/ μ^2
p-well sidewall (junction, sidewall)	1.6	± 1.0	fF/ μ
Resistances			
Substrate	25	$\pm 20\%$	Ω -cm
p-well	5000	± 2500	Ω/\square
n ⁺ diffusion	35	± 25	Ω/\square
p ⁺ diffusion	80	± 55	Ω/\square
Metal	0.003	$\pm 25\%$	Ω/\square
Poly	25	$\pm 25\%$	Ω/\square
Metal 1–Metal 2 via ($3\mu \times 3\mu$ contact)	<0.1		Ω
Metal 1 contact to POLY I ($3\mu \times 3\mu$ contact)	<10		Ω
Metal 1 contact to n ⁺ or p ⁺ diffusion ($3\mu \times 3\mu$ contact)	<5		Ω

Typical Model Parameters (cont)

Breakdown voltages, leakage currents, migration currents and operating conditions

Punchthrough voltages (Gate oxide, POLY I to POLY II)	>10	V
Diffusion reverse breakdown voltage	>10	V
p-well to substrate reverse breakdown voltage	>20	V
Metal 1 in field threshold voltage	>10	V
Metal 2 in field threshold voltage	>10	V
Poly-field threshold voltage	>10	V
Maximum operating voltage	7.0	V
n ⁺ diffusion to p-well leakage current	0.25	fA/ μ^2
p ⁺ diffusion to substrate leakage current	0.25	fA/ μ^2
p-well leakage current	0.25	fA/ μ^2
Maximum metal current density	0.8	mA/ μ width
Maximum device operating temperature	200	°C

Typical Model Parameters (cont)

SPICE MOSFET model parameters of a typical p-well CMOS process (MOSIS^a)

Parameter (Level 2 model)	n-channel	p-channel	Units
VTO	0.827	-0.895	V
KP	32.87	15.26	$\mu\text{A}/\text{V}^2$
GAMMA	1.36	0.879	$\text{V}^{1/2}$
PHI	0.6	0.6	V
LAMBDA	1.605E-2	4.709E-2	V^{-1}
CGSO	5.2E-4	4.0E-4	fF/ μ width
CGDO	5.2E-4	4.0E-4	fF/ μ width
RSH	25	95	Ω/\square
CJ	3.2E-4	2.0E-4	pF/μ^2
MJ	0.5	0.5	
CJSW	9.0E-4	4.5E-4	pF/μ perimeter
MJSW	0.33	0.33	
TOX	500	500	\AA
NSUB	1.0E16	1.12E14	$1/\text{cm}^3$
NSS	0	0	$1/\text{cm}^2$
NFS	1.235E12	8.79E11	$1/\text{cm}^2$
TPG	1	-1	
XJ	0.4	0.4	μ
LD	0.28	0.28	μ
UO	200	100	$\text{cm}^2/(\text{V} \cdot \text{s})$
UCRIT	9.99E5	1.64E4	V/cm
UEXP	1.001E-3	0.1534	
VMAX	1.0E5	1.0E5	m/s
NEFF	1.001E-2	1.001E-2	
DELTA	1.2405	1.938	

Typical Model Parameters (cont)

.MODEL CMOSN NMOS {			LEVEL	= 49	
+VERSION	= 3.1	TNOM	= 27	TOX	= 1.4E-8
+XJ	= 1.5E-7	NCH	= 1.7E17	VTH0	= 0.6656437
+K1	= 0.875093	K2	= -0.0943223	K3	= 25.0562441
+K3B	= -8.5140476	WO	= 1.01582E-8	NLX	= 1E-9
+DVTOW	= 0	DVT1W	= 0	DVT2W	= 0
+DVTO	= 2.670658	DVT1	= 0.4282172	DVT2	= -0.1373089
+UO	= 452.3081836	UA	= 3.061716E-13	UB	= 1.515137E-18
+UC	= 1.166279E-11	VSAT	= 1.682414E5	AO	= 0.6297744
+AGS	= 0.1384489	BO	= 2.579158E-6	B1	= 5E-6
+KETA	= -3.615287E-3	A1	= 1.054571E-6	A2	= 0.3379035
+RDSW	= 1.380341E3	PRWG	= 0.0301426	PRWB	= 0.0106493
+WR	= 1	WINT	= 2.594349E-7	LINT	= 7.489566E-8
+XL	= 1E-7	XW	= 0	DWG	= -9.471353E-9
+DWB	= 3.537786E-8	VOFF	= 0	NFACTOR	= 1.0754804
+CIT	= 0	CDSC	= 2.4E-4	CDSCD	= 0
+CDSCB	= 0	ETAO	= 2.332015E-3	ETAB	= -1.531255E-4
+DSUB	= 0.076309	PCLM	= 2.6209353	PDIBLC1	= 1
+PDIBLC2	= 2.23243E-3	PDIBLCB	= -0.0436947	DROUT	= 1.0300278
+PSCBE1	= 6.619472E8	PSCBE2	= 2.968801E-4	PVAG	= 9.970995E-3
+DELTA	= 0.01	RSH	= 80.9	MOBMOD	= 1
+PRT	= 0	UTE	= -1.5	KT1	= -0.11
+KT1L	= 0	KT2	= 0.022	UA1	= 4.31E-9
+UB1	= -7.61E-18	UC1	= -5.6E-11	AT	= 3.3E4
+WL	= 0	WLN	= 1	WW	= 0
+WWN	= 1	WWL	= 0	LL	= 0
+LLN	= 1	LW	= 0	LWN	= 1
+LWL	= 0	CAPMOD	= 2	XPART	= 0.5
+CGDO	= 2.34E-10	CGSO	= 2.34E-10	CGBO	= 1E-9
+CJ	= 4.240724E-4	PB	= 0.9148626	MJ	= 0.4416777
+CJSW	= 3.007134E-10	PBSW	= 0.8	MJSW	= 0.2025106
+CJSWG	= 1.64E-10	PBSWG	= 0.8	MJSWG	= 0.2025106
+CF	= 0	PVTHO	= 0.0526696	PRDSW	= 110.1539295
+PK2	= -0.0283027	WKETA	= -0.0191754	LKETA	= 8.469064E-4

98 parameters in this BSIM Model !

Typical Model Parameters (cont)

```
.MODEL CMOSF PMOS (
+VERSION = 3.1          TNOM    = 27          LEVEL    = 49
+XJ      = 1.5E-7       NCH     = 1.7E17       TOX      = 1.4E-8
+K1      = 0.5600277    K2      = 9.302429E-3   VTH0     = -0.9633249
+K3B     = -1.0103515   WO      = 1.010628E-8   K3       = 7.2192028
+DVTOW   = 0           DVT1W   = 0           NLX      = 5.826683E-8
+DVTO    = 2.2199372   DVT1    = 0.5378964     DVT2W    = 0
+UO      = 220.5729225  UA      = 3.141811E-9     DVT2     = -0.1158128
+UC      = -5.76898E-11 VSAT   = 1.342779E5      UB       = 1.085892E-21
+AGS     = 0.157364    BO      = 9.735259E-7     AO       = 0.9333822
+KETA    = -2.42686E-3  A1     = 3.447019E-4     B1       = 5E-6
+RDSW    = 3E3         PRWG    = -0.0418484     A2       = 0.3701317
+WR      = 1           WINT    = 3.097872E-7     PRWB     = -0.0212357
+XL      = 1E-7       XW      = 0           LINT     = 1.040878E-7
+DWB     = 1.629532E-8 VOFF   = -0.0823738     DWG      = -1.983686E-8
+CIT      = 0         CDSC    = 2.4E-4         NFACTOR  = 0.969384
+CDSCB   = 0         ETAO    = 0.4985496     CDSCD    = 0
+DSUB    = 1         PCLM    = 2.1142057     ETAB     = -0.0653358
+PDIBLC2 = 3.172604E-3 PDIBLCB = -0.0511673     PDIBLC1  = 0.0256688
+PSCBE1  = 1.851867E10 PSCBE2  = 1.697939E-9     DROUT    = 0.1695622
+DELTA   = 0.01       RSH     = 103.6         PVAG     = 0
+PRT      = 0         UTE     = -1.5         MOBMOD   = 1
+KT1L    = 0         KT2     = 0.022        KT1      = -0.11
+UB1     = -7.61E-18  UC1     = -5.6E-11      UA1      = 4.31E-9
+WL      = 0         WLN     = 1           AT       = 3.3E4
+WWN     = 1         WWL     = 0           WW       = 0
+LLN     = 1         LW      = 0           LL       = 0
+LWL     = 0         CAPMOD  = 2           LWN      = 1
+CGDO    = 3.09E-10   CGSO    = 3.09E-10     XPART    = 0.5
+CJ      = 7.410008E-4 PB      = 0.9665307     CGBO     = 1E-9
+CJSW    = 2.487127E-10 PBSW    = 0.99          MJ       = 0.4978642
+CJSWG   = 6.4E-11   PBSWG   = 0.99          MJSW     = 0.3877813
+CF      = 0         PVTHO   = 5.98016E-3     MJSWG    = 0.3877813
+PK2     = 3.73981E-3 WKETA   = 2.870507E-3   PRDSW    = 14.8598424
-          -          -          -          LKETA    = -4.823171E-3
```

End of Lecture 7