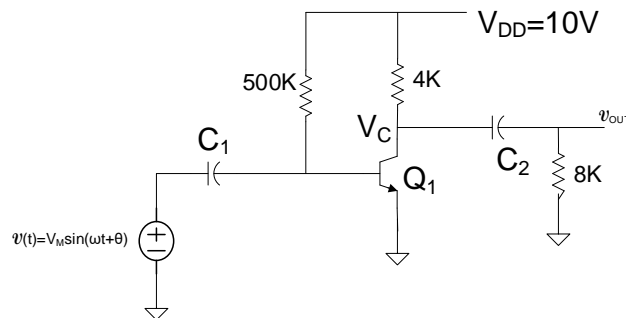


EE 330
Homework 10
Fall 2019
Due Friday Nov 1

Unless specified to the contrary, assume all n-channel MOS transistors have model parameters $\mu_n C_{OX} = 100 \mu\text{A}/\text{V}^2$ and $V_{Tn} = 0.8\text{V}$, all p-channel transistors have model parameters $\mu_p C_{OX} = 33 \mu\text{A}/\text{V}^2$ and $V_{Tp} = -0.8\text{V}$. Correspondingly, assume all npn BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} \text{A}/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. Assume all diodes are characterized by the model parameters $J_{SX} = 0.1 \text{fA}/\mu\text{m}^2$, $V_{G0} = 1.17\text{V}$, and $m = 2.3$.


Problem 1 Assume the capacitors are very large and V_M is small.

- Draw the small signal equivalent circuit for the amplifier shown (from HW 9)
- Determine the quiescent value of V_C and V_{OUT} (from HW 9)
- Determine the voltage gain in terms of the small-signal y-parameters (or equivalently the g-parameters) for the transistor. Assume the parameter y_{21} in the model of the transistor is 0.
- Determine the numerical value for the small-signal voltage gain



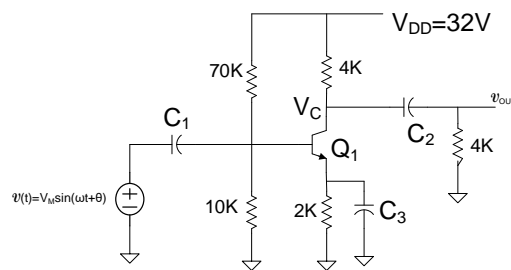
Problem 2 Assume the capacitors are all very large and V_m is small.

- Draw the small signal equivalent circuit for the amplifier shown (from HW 9)
- Determine the quiescent value of V_C and V_{OUT} (from HW 9)
- Determine the voltage gain in terms of the small-signal y-parameters (or equivalently the g-parameters) for the transistor. Assume the parameter y_{21} in the model of the transistor is 0.
- Determine the numerical value for the small-signal voltage gain



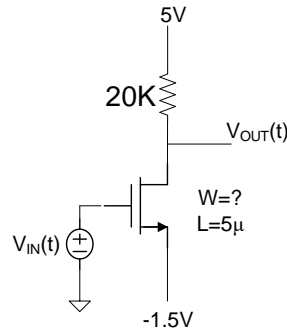Problem 3 Consider the following circuit


- Determine W so that the quiescent drain current is 0.1mA (from HW 9)
- Draw the small-signal equivalent circuit (from HW 9)
- With the drain current specified in part a), determine the small-signal voltage gain using a small-signal analysis and compare the results with those obtained on last weeks assignment using nonlinear analysis techniques,



Problem 4 Consider a device characterized by the equations

$$I_1 = V_1 V_2^2$$


$$I_2 = 0.1e^{0.2V_1^2 V_2}$$

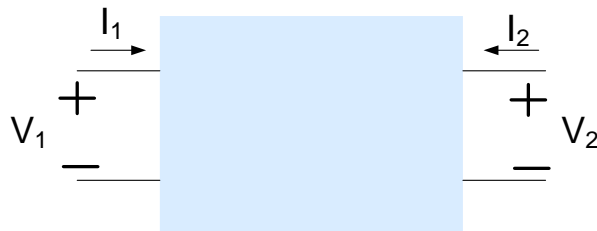

- Determine the small signal model for a two-terminal device characterized by the equations given above
- Determine the numerical values for the small signal model parameters if the quiescent value of the port voltages are $V_2=1\text{V}$, $V_1=5\text{V}$.
- Determine the quiescent currents at the Q-point established in part b.
- Determine the small signal currents i_1 and i_2 if the small signal voltages v_1 and v_2 were measured to be 1mV_{RMS} and 2mV_{RMS} respectively. Assume the same Q-point as established in part b.

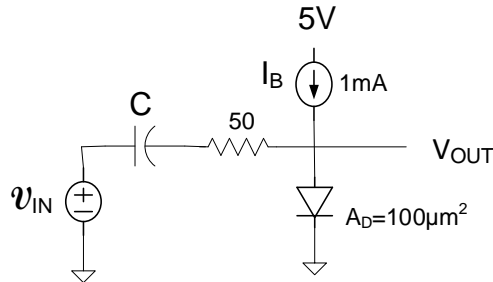
Problem 5 Consider the following circuit operating at $T=300K$. Assume the capacitor C is very large and the v_{IN} is a small-signal input.

- Determine the quiescent output voltage.
- Draw the small-signal equivalent circuit
- Determine the small-signal voltage gain from the input to the output.
- Repeat part c) if the current I_B is increased to 5mA



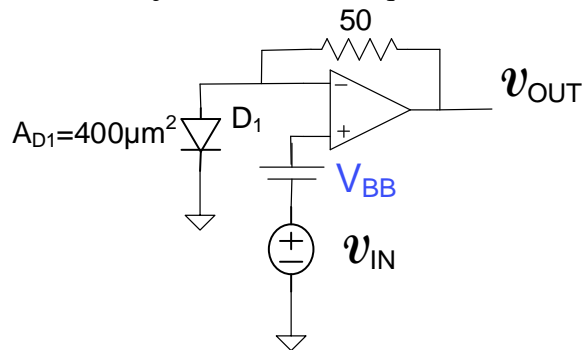
Problem 6 Consider the following circuit operating at $T=300K$. Assume v_{IN} is a small-signal voltage source.

- If the voltage V_{BB} is adjusted so that the quiescent diode current is 1mA, determine the small signal voltage gain $A_v = \frac{v_{OUT}}{v_{IN}}$
- Repeat part a) if V_{BB} is adjusted so that the quiescent diode current is 10mA




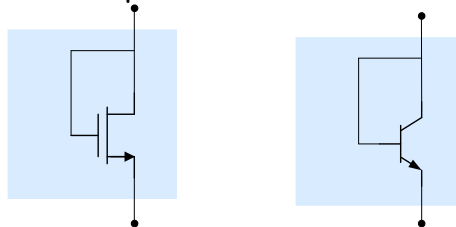Problem 7 Consider the following circuits.


- Obtain the small signal impedance between the two terminals exiting the box in terms of the small-signal model parameters. Assume the MOSFET is operating in the Saturation region and the BJT in the Forward Active region
- Numerically determine the small-signal impedances if the quiescent currents are both 1mA, the width and length of the MOSFET are both $5\mu m$, and the emitter of the BJT is square and is $5\mu m$ on a side. Assume $V_{AF}=\infty$ and $\lambda=0$.



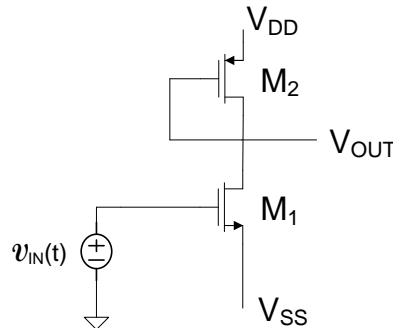Problem 8 Obtain an expression for the small signal output voltage in terms of the small signal parameters if the input is given by the expression $v_{IN}(t)=V_M \cos(\omega t + \theta)$. Assume M_1 is operating in the saturation region.



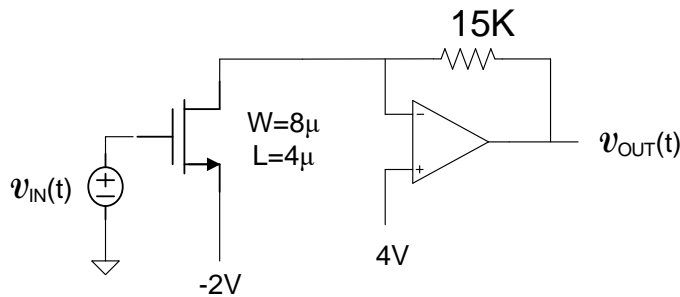Problem 9 Determine the small signal output voltage if the small signal input voltage is a sinusoidal 1KHz signal with 0-P amplitude of 25mV.



Problem 10 Determine the total output voltage for the circuit in Problem 10 if $V_{DD}=5V$, $V_{SS}=-2V$, $W_1=10\mu$, $L_1=2\mu$, $W_2=6\mu$ and $L_2=1\mu$. Assume the devices are from a process with parameters $\mu_n C_{OX}=100\mu A/v^2$, $\mu_p C_{OX}=30\mu A/v^2$, $V_{TNO}=0.5V$, $V_{TPO}= -0.5V$, $C_{OX}=2fF/\mu^2$, $\lambda = 0$, $\gamma = 0$.

Problem 11 Design an amplifier using only BJT transistors, resistors, capacitors and voltage sources that has a voltage gain of -5 when driving a 2K resistor.

Problem 12 Design an amplifier using only MOS transistors, capacitors, and voltage sources that has a voltage gain of -10 when driving an external 10K resistor.