

Olouwole Eteka

EE 330 Lab 10

Design and Simulation of Digital Circuits using Hardware Description Languages

Introduction

In this lab we will learn how to implement Hardware Description Language. We will be using Verilog code to design a digital circuit. We will be using also ModelSim for testing out our test bench. We will also be converting codes to schematic and to layout using RTL compiler and Encounter and then make the layout out of it.

Part 1: Inverter

This part of the lab will touch some key point of the features from ModelSim we can use to manipulate a digital Boolean equation and creating test bench to test if it's working correctly. The code for my design is provided below.

Code

The code for the Boolean function to implement.

```
1  module boolean_function(F, A, B, C);  
2      output F;  
3      input A, B, C;  
4      assign F = (~A&B&C) | (A&~B&C) | (A&B&~C);  
5  endmodule
```

Followed by the test bench for it


```


1  `timescale 1ns/1ps
2
3  module boolean_function_tb();
4      wire F;
5      reg A,B,C;
6      boolean_function BF(.F(F), .A(A), .B(B), .C(C));
7
8      initial
9      begin
10         A=1'b0; B=1'b0; C=1'b0; #20;
11         A=1'b0; B=1'b0; C=1'b1; #20;
12         A=1'b0; B=1'b1; C=1'b0; #20;
13         A=1'b0; B=1'b1; C=1'b1; #20;
14         A=1'b1; B=1'b0; C=1'b0; #20;
15         A=1'b1; B=1'b0; C=1'b1; #20;
16         A=1'b1; B=1'b1; C=1'b0; #20;
17         A=1'b1; B=1'b1; C=1'b1; #20;
18
19     end
20 endmodule
21

```

Stimulation

From this graph bellow we can conclude the code does it job and the graph is the correct as expected and matches the wave form from the same process in lab 4.

 


 

Part 2: Verilog Synthesis with RTL Compiler


In this part we will be using RTL compiler to synthesize our Verilog code. We can do so by following steps I listed below as specified by the lab.

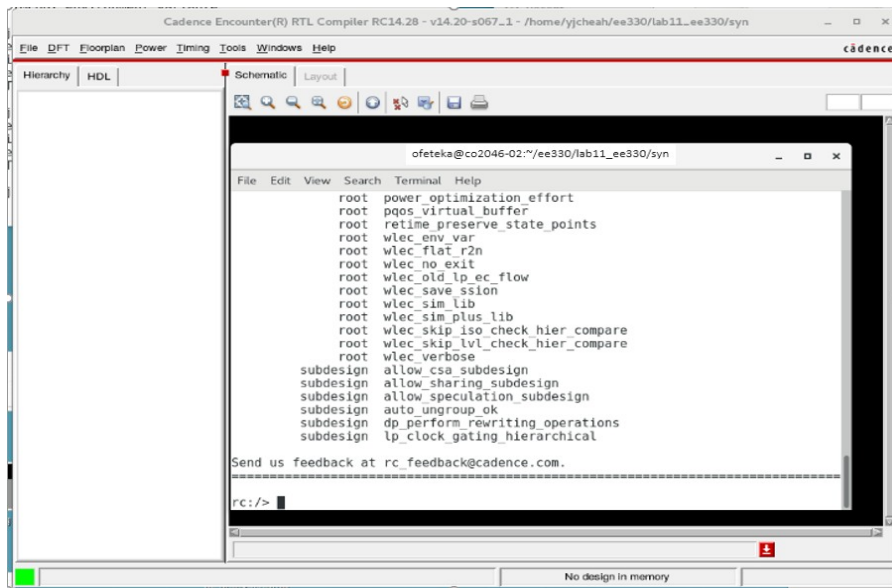1. Setup standard cell library
2. Setup RTL compiler
3. Copy over the "boolean_function.v" Verilog file created from ModelSim and move into the directory "lab11_ee330/rtl/":
`cp ~/ee330/boolean_function.v ~/ee330/lab_ee330/rtl`
4. Source the "ic" and "rc" software program, direct terminal to "lab11_ee330/syn/" and open
5. A GUI window should appear and terminal will change to the RC command line:



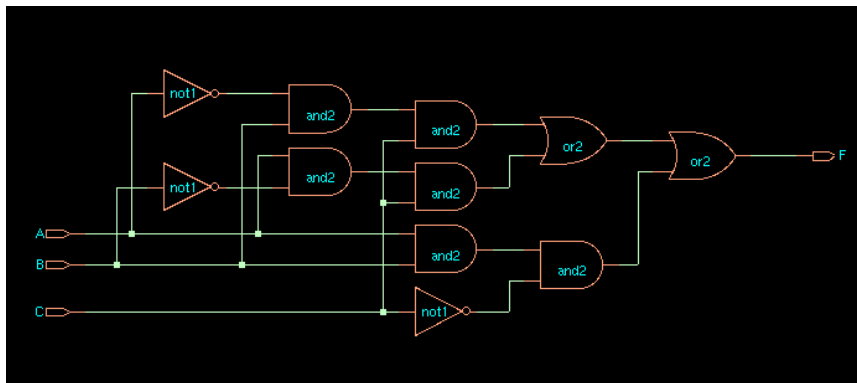6. In the RC command window, load the correct standard cell libraries and run the synthesis script (Ignore the warnings):
7. In the RC command window, load and elaborate "boolean_function.v"
8. RTL Compiler should have generated an unoptimized version of "boolean_function.v" and should show up in the GUI:


By doing the number 8 of this process I got the graph bellow :



9. Synthesize the design and export it:
 We can do so by using the code provided in the lab: "synthesize -to_mapped -eff high -no_incr write -mapped > \${DESIGN}_synth.v write_sdc > \${DESIGN}.sdc"

"

10. Finally, part 10 can Import the synthesized design schematic to Cadence Virtuoso:
 After this step we should have an imported Schematic design to Cadence Virtuoso

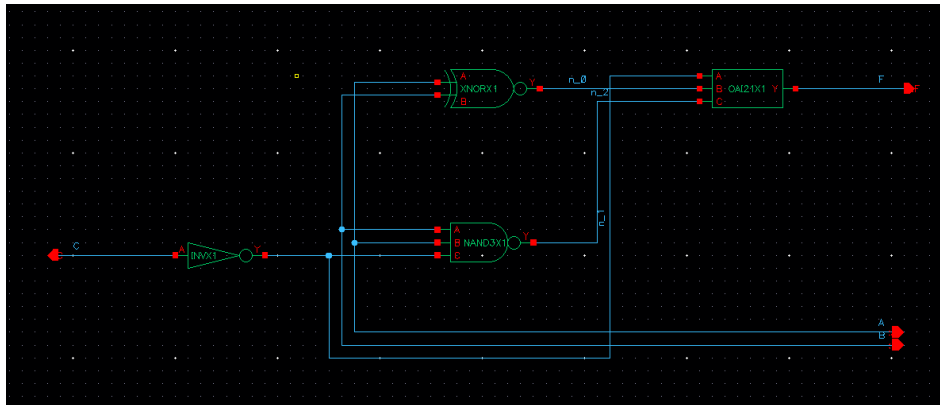


Part 3: Layout of Digital Circuits with Encounter

In this part of the lab, we will be creating a layout from the synthesized schematic from HDL.

To do so we need the follow the steps listed bellow

1. In "lab11_ee330" directory, create a folder named "encounter".
2. In terminal, we can launch the encounter by the command:
encounter
3. In the encounter, we go to File -> Import RTL and fill as specify by the lab
4. Go to File -> Import Design and fill in as below:
5. Now we should have an empty "die" appear in the Encounter GUI, then now we are going to add a Floorplan. Go to Floorplan -> Specify Floorplan:
 - i. Aspect ratio (height/width) = 1.0
 - ii. Core Utilization = 0.5
 - iii. Core Margins = 10 for all left, right, top and bottom
6. Then adding power planning. Go to Power -> Power Planning -> Add Rings
 - i. Set the power plan to be around the I/O boundary.
 - ii. Enter "GND VDD" in the Net(s) field.
 - iii. Verify that the width and spacing comply with the process design rules and are a multiple of lambda.
7. Now, placement is needed. Go to Place -> Standard Cells -> Click OK
8. Adding routing.
 - i. Go to Route -> Special Route:
Unselect Block pins, Pad pins, and Pad rings then click OK
 - ii. Go to Route -> NanoRoute -> Route -> Click OK
9. Adding filler cells. Go to Place -> Physical Cell -> Add Filler.
 - i. In Cell Name(s) field, click "Select" and select the only on filler cell in OSU018 library that named "FILL".
 - ii. Click OK.

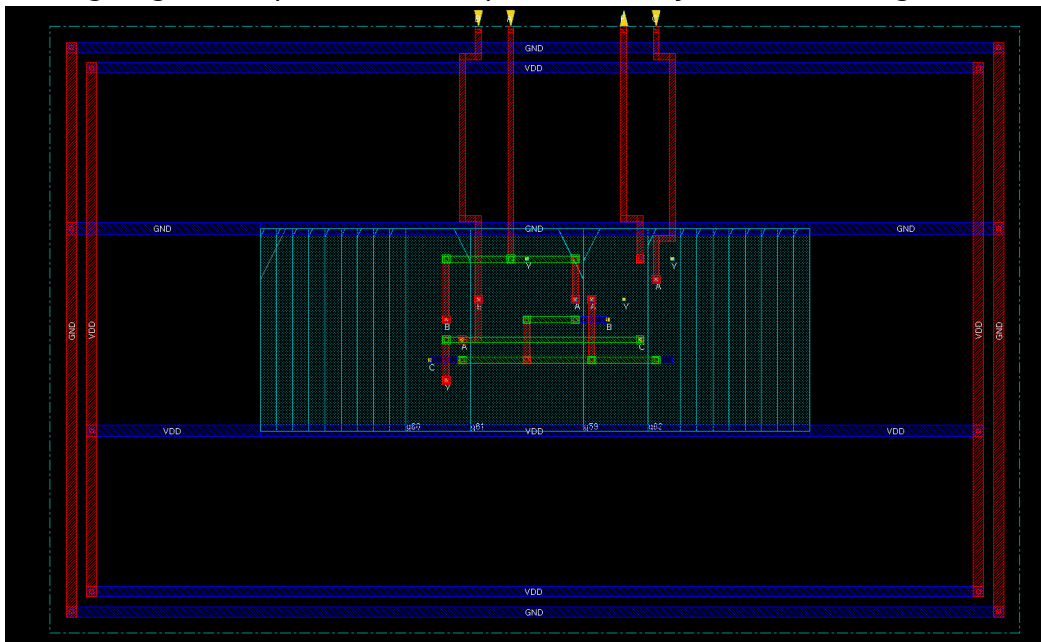10. Now we can verify for errors:
 - i. Verify -> Verify Geometry, Verify -> Verify Connectivity
 - ii. The error reports can be seen from terminal
11. Save the design file by going to File -> Save Design (Save in encounter format).
12. GDS Export of Layout from Encounter. Go to File -> Save -> GDS/OASIS...
Then fill it as specify by the lab
After going to the process we imported the layout as showing bellow.



Part 4 Import the layout into Cadence


This part of the lab consists of importing the layout from Encounter into Cadence Virtuoso, then test them up by running DRC, LVS tests to compare between the schematic imported from RTL Compiler and layout imported from encounter, they should match.

We can do this by following the steps below.

1. GDS import of layout into Virtuoso. On the CIW (Virtuoso window where errors and messages appear)
 - i. Go to File -> Import -> Stream, enter the following:




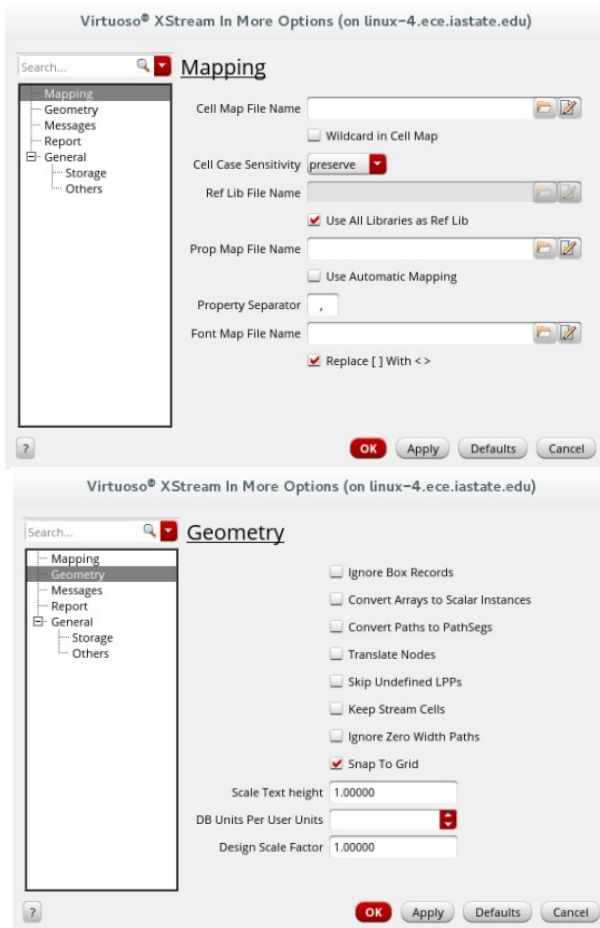ii. In the same window, click More Options and check as follow:




iii. Click OK and then in the pop-up, Click Translate (We should receive 0 errors with little or no warnings).

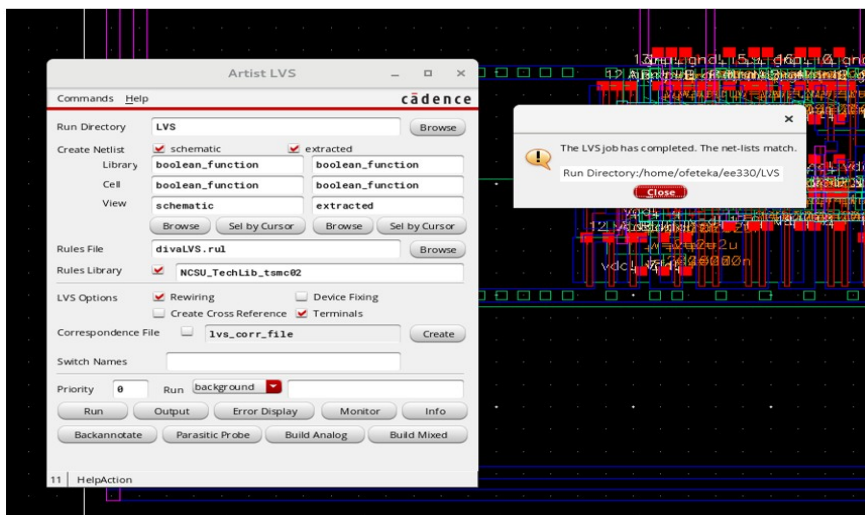2. Now we have the layout successfully imported to Cadence Virtuoso, but since the DRC will not pass due to “dubious Data” errors that happen because Encounter create the pin names as metal layer text instead of just text layer. Therefore, we should follow the following steps:
 - i. Add Metal 2 pins at their respective places
 - (a) Input: “A”, “B”, “c”
 - (b) Output: “F”
 - (c) Input/output: “vdd!”, “gnd!” (Note that we didn’t use VDD and GND because in the schematic that we imported from RTL Compiler, it uses the names “vdd!” and “gnd!” for VDD and GND and in order for LVS to works, they have to use the same pin names)
 - ii. Delete the metal layer texts “A”, “B”, “C”, “F”, “VDD”, and “GND”
3. Run LVS test and make sure it matches:



 The final stage is looking like the graph below



Conclusion

This lab was useful to learn the process of changing Hardware Description Languages into Layout Design by first creating a HDL Verilog code. I learned how to do a proper testing using a test bench also some tricks to perform a better layout. Importing both schematic and layout designs into Cadence Virtuoso was a good way of comparing make sure the layout is working properly by running DRC and LVS tests.