

Due 9/28/2012


10pts 1. AMI .5μ CMOS Process

$$\frac{W}{L} = \frac{1}{R \times (\mu_{ox}) \times (V_{gs} - V_t)} = \frac{1}{1K \times (57.8E-6) \times (3.5 - .79)} = \boxed{3.19}$$

IBM 0.13μ CMOS Process

$$\frac{W}{L} = \frac{1}{1K \cdot (308E-6.2) \cdot (1.5 - .41)} = \boxed{1.49}$$

5pts 2.

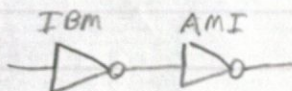

$$\text{AMI: } \min \frac{W}{L} = \frac{3}{.6}$$

$$W_{\text{active to Poly}} = 2434 \text{ aF}/\mu\text{m}^2$$

$$P_{\text{active to Poly}} = 2351 \text{ aF}/\mu\text{m}^2$$

$$C_{\text{Load}} = 3 \cdot 6 (2434 \text{ aF} + 2351 \text{ aF}) = 8.613E-15 \text{ F}$$

$$\text{IBM: } \min W/L = .16/.12$$

$$R_{\text{sw}} = \frac{1}{W/L \times (\mu_{ox}) \times (V_{gs} - V_t)} = \frac{1}{.16/.12 \cdot 308E-6.2 \cdot (1.5 - .41)} = 1,117 \Omega$$

$$R_{\text{swp}} = \frac{1}{.16/.12 \cdot 48.8E-6.2 \cdot (1.5 - .42)} = 7,115.21$$

$$t_{HL} = R_{\text{sw}} \times C_{\text{load}} = \boxed{9.621 \text{ ps}}$$

$$t_{LH} = R_{\text{swp}} \cdot C_{\text{load}} = \boxed{61.3 \text{ ps}}$$



$$5\text{pts } 3. R_{\text{onSC}} = \frac{1}{\frac{q_2}{q_1} \mu_{ox} (V_{gs} - V_t)^{\alpha/2}} = \frac{1}{.1 \cdot 308E-6.2 \cdot (1.5 - .41)^{.25}} = \boxed{1538 \Omega}$$

$$R_{\text{onIC}} = \frac{1}{\frac{1}{1} \cdot 308E-6.2 \cdot (1.5 - .41)} = \boxed{1,489 \Omega}$$



4.

(a)

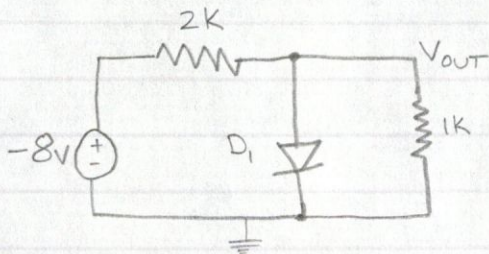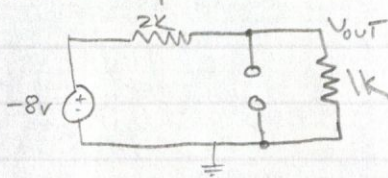
Guess  $D_1 = \text{OFF}$ 

$$V_{out} = (-8V) \left( \frac{1k}{1k + 2k} \right)$$

$$V_{out} = -2.667V$$

Check:  $V_{D1} = V_{out} = -2.667 < 0.6 \checkmark D_1 \Rightarrow \text{OFF}$  ← correct guess

(b)

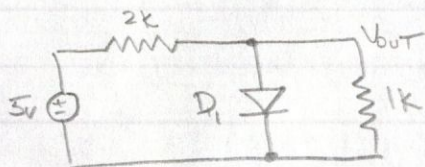

$$\frac{5 - V_{out}}{2k} = I_D + \frac{V_{out}}{1k} \quad \text{let } I_s = (50 \mu m^2) (10^{-15} \frac{A}{\mu m^2})$$

$$I_D = I_s \left( e^{\frac{V_D}{V_T}} - 1 \right) = (50)(10^{-15}) \left( e^{\frac{V_D}{26mV}} - 1 \right) \quad V_D = V_{out}$$


$$-V_{out} \left( \frac{1}{2k} + \frac{1}{1k} \right) + \frac{5}{2k} = (50)(10^{-15}) \left( e^{\frac{V_{out}}{26mV}} - 1 \right)$$

$$V_{out} = 0.628V$$

$$I_{R2} = \frac{V_{out}}{1k}$$

$$I_{R2} = 0.628mA$$


(c)

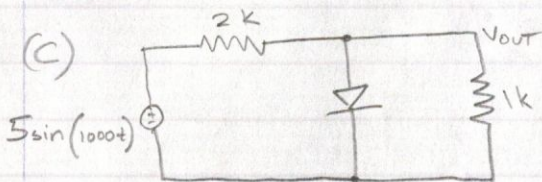

\*use 0.6V model for diode

for  $V_{out} < 0.6V \Rightarrow \text{Reverse bias} \rightarrow \text{Part a}$ for  $V_{out} > 0.6V \Rightarrow \text{forward bias} \rightarrow \text{Part b}$ 
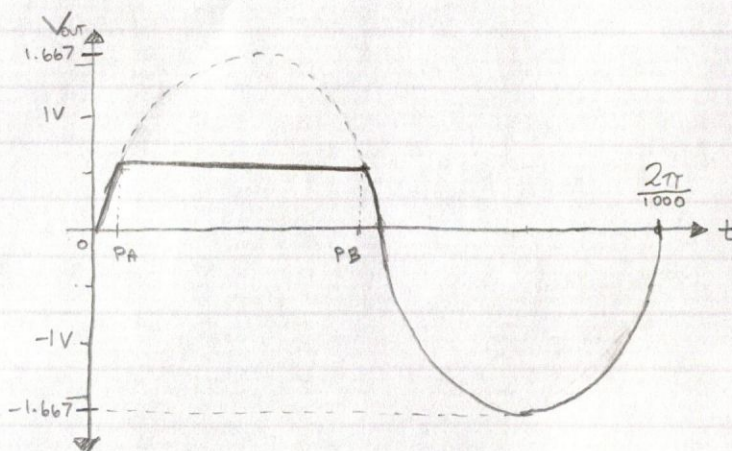
$$\text{for } V_{out} = \begin{cases} 0.6V & V_{in} \geq 1.8V \\ \frac{1}{3} V_{in} & V_{in} < 1.8V \end{cases}$$



$$t(PA) = \frac{1}{1000} \sin^{-1} \left( 0.6 \cdot \frac{3}{5} \right) = 0.368ms$$


$$t(PB) = \frac{\left( \frac{2\pi}{1000} \right)}{2} - t(PA)$$

$$t(PB) = 2.77ms$$



5

10 points

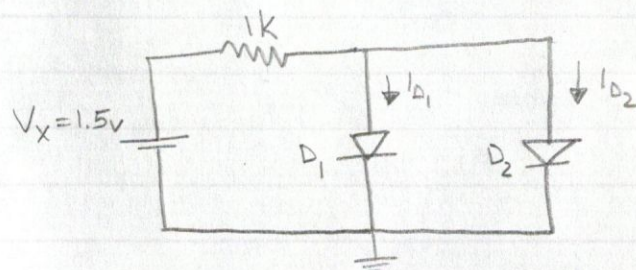

$$A_{D1} = 100 \mu\text{m}^2$$

$$A_{D2} = 4 \cdot A_{D1} = 400 \mu\text{m}^2$$

$$J_S = 5 \frac{\text{fA}}{\mu\text{m}^2}$$

$$V_{D1} = V_{D2}$$

$$I_S = I_{D1} + I_{D2}$$

$$\frac{1.5 - V_{D1}}{1\text{K}} = (A_{D1})(J_S) \left( e^{\frac{V_{D1}}{V_T}} - 1 \right) + 4 \cdot (A_{D1})(J_S) \left( e^{\frac{V_{D1}}{V_T}} - 1 \right)$$

$$\frac{1.5 - V_{D1}}{1\text{K}} = 5 \left( 100 \mu\text{m}^2 \right) \left( 5 \frac{\text{fA}}{\mu\text{m}^2} \right) \left( e^{\frac{V_{D1}}{26\text{mV}}} - 1 \right)$$


$$V_{D1} = 0.5146 \text{ V}$$

$$\text{then } I_{D1} = (100 \mu\text{m}^2) \left( 5 \frac{\text{fA}}{\mu\text{m}^2} \right) \left( e^{\frac{0.5146}{0.026}} - 1 \right)$$

$$I_{D1} = 0.1971 \text{ mA}$$

6 (a)

10 points

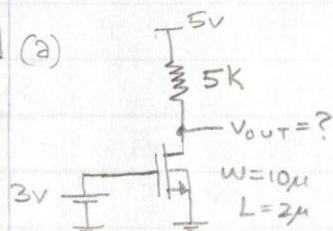

$$V_{TN} = 1\text{V}$$

$$\mu_n C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2}$$

Guess triode

$$V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T$$

$$(V_{GS} = 3\text{V}) \geq 1 \quad V_{DS} < (3 - 1)$$

$$I_D = \mu_n C_{ox} \cdot \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) \cdot V_{DS}$$


$$V_{DS} = V_{OUT}$$

$$\frac{5 - V_{DS}}{5\text{K}} = \left( 100 \frac{\mu\text{A}}{\text{V}^2} \right) \left( \frac{10}{2} \right) \left( 3 - 1 - \frac{V_{DS}}{2} \right) \cdot V_{DS}$$

$$V_{OUT} = 1.07335 \text{ V}$$

triode ✓

(b)

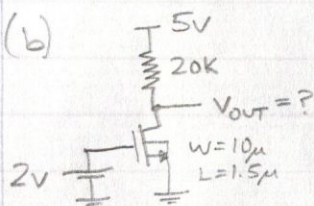

Guess triode

$$V_{GS} \geq V_T$$

$$2\text{V} \geq 1\text{V} \quad \checkmark$$

$$V_{DS} < V_{GS} - V_T$$

$$(V_{DS} = V_{OUT}) < (2 - 1)$$

$$I_D = \frac{5 - V_{DS}}{20\text{K}} = \left( 100 \frac{\mu\text{A}}{\text{V}^2} \right) \left( \frac{10}{1.5} \right) \left( 2 - 1 - \frac{V_{DS}}{2} \right) \cdot V_{DS}$$

$$V_{DS} = V_{OUT}$$

$$V_{DS} = V_{OUT} = 0.43811 \text{ V}$$


triode ✓



7

(a)

10 points

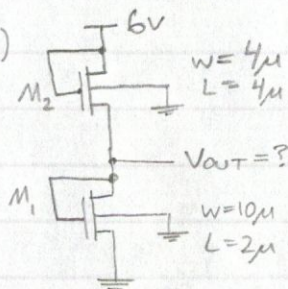

$$V_{TN} = 1 \quad \mu_n C_{ox} = 100 \frac{\mu A}{V^2}$$

SATURATION since  $V_{DS} = V_{GS} + V_{TN} = 1$   
 $\hookrightarrow$  for Both  $M1 + M2$


$$I_{D1} = I_{D2}$$

$$\mu_n C_{ox} \frac{W_2}{2 \cdot L_2} \cdot (V_{GS2} - V_T)^2 = \mu_n C_{ox} \frac{W_1}{2 \cdot L_1} \cdot (V_{GS1} - V_T)^2$$

$$\frac{4}{2 \cdot 4} ((6 - V_{OUT}) - 1)^2 = \frac{10}{2 \cdot 2} \cdot (V_{OUT} - 1)^2$$

$$V_{OUT} = 2.236 [V]$$

(b)

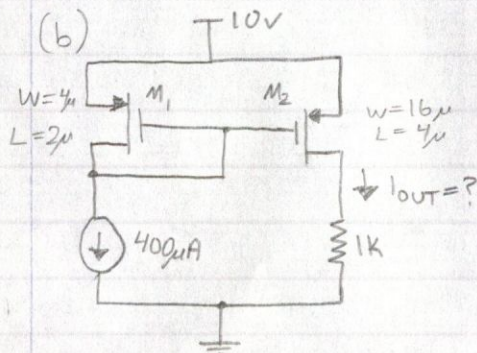

Guess saturation

$$\mu_p C_{ox} = 33 \frac{\mu A}{V^2}$$

$$V_{TP} = -1V$$

$$I_{D1} = 400 \mu A = \mu_p C_{ox} \frac{W_1}{2 \cdot L_1} \cdot (V_{GS1} - V_{TP})^2$$

$$400 \mu A = (33 \frac{\mu A}{V^2}) (\frac{4}{2 \cdot 2}) (V_{GS1} + 1)^2$$

$$V_{GS1} = -4.48155$$

$$V_{GS1} = V_{GS2}$$

$$I_{D2} = 33 \frac{\mu A}{V^2} (\frac{16}{2 \cdot 4}) (-4.48155 + 1)^2$$

$$I_{D2} = 800 \mu A$$

check  
saturation

$$V_{DS} = (800 \mu A \cdot 1k) - 10 = -9.2$$


$$V_{GS} = -4.48155 V$$

$$(-9.2) < (-4.48 + 1) \quad \checkmark \text{ saturation}$$



8 (a)

15 points

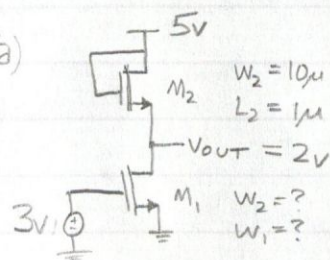

$$V_{TN} = 1V \quad \mu_n C_{ox} = 100 \frac{\mu A}{V^2}$$

saturation for  $M_1 + M_2$ 

$$I_{D1} = I_{D2}$$

$$\mu_n C_{ox} \frac{W_2}{2 \cdot L_2} (V_{GS2} - V_T)^2 = \mu_n C_{ox} \frac{W_1}{2 \cdot L_1} (V_{GS1} - V_T)^2$$

$$\frac{10}{2 \cdot 1} ((5-2)-1)^2 = \frac{W_1}{L_1} \cdot \left(\frac{1}{2}\right) \cdot (3-1)^2$$

$$\boxed{\frac{W_1}{L_1} = 10}$$

pick

$$\boxed{\frac{W_1}{L_1} = 10 \mu}$$

(b) for  $V_{OUT} = 0.5V$  $M_2 \Rightarrow$  saturation $M_1 \Rightarrow$  triode

$$0.5 < 3-1$$

$$I_{D1} = I_{D2}$$

$$\mu_n C_{ox} \cdot \frac{W_2}{2 \cdot L_2} \cdot (V_{GS2} - V_T)^2 = \mu_n C_{ox} \cdot \frac{W_1}{L_1} \cdot (V_{GS1} - V_T - \frac{V_{DS1}}{2}) \cdot V_{DS1}$$

$$\frac{10}{2 \cdot 1} \cdot ((5-0.5)-1)^2 = \frac{W_1}{L_1} \cdot (3-1 - \frac{0.5}{2}) \cdot 0.5$$


$$\boxed{\frac{W_1}{L_1} = 70}$$

pick


$$\boxed{\frac{W_1}{L_1} = 70 \mu}$$



9 10 points

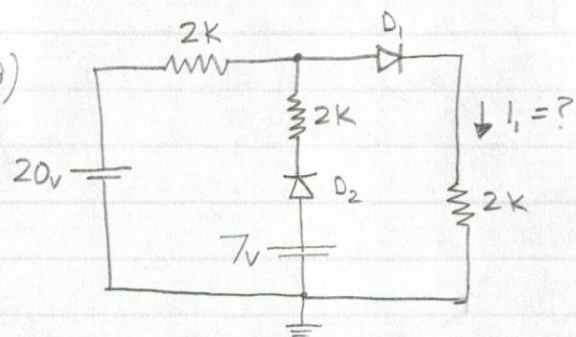


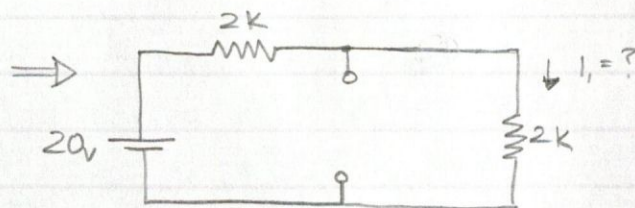Guess  $D_1 \Rightarrow \text{ON} \checkmark$  (+current) (ideal = short)  
 $D_2 \Rightarrow \text{OFF} \checkmark$  (-voltage) (ideal = open)




$$I_1 = \frac{20V}{4K\Omega}$$

$$I_1 = 5mA$$

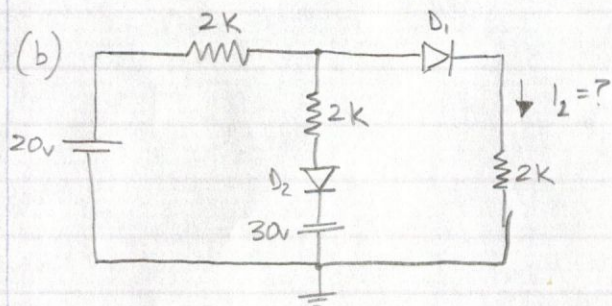

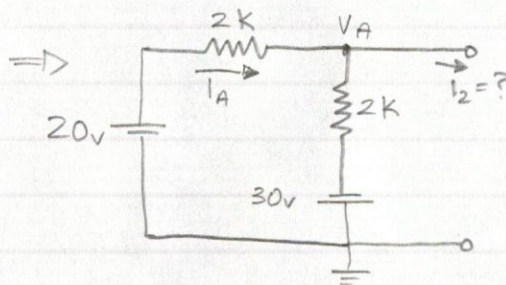Guess  $D_1 \Rightarrow \text{OFF}$  (-voltage) ideal = open  
 $D_2 \Rightarrow \text{ON}$  (+current) ideal = short



$$-20 + 2K \cdot I_A + 2K \cdot I_A - 30 = 0$$

$$I_A = \frac{50V}{4K\Omega} = 12.5mA$$

$$V_A = 20 - 2K \cdot I_A = -5V$$

$$V_A = -5V$$

since the current through  $D_2$  is positive (forward bias)  
 and the voltage across  $D_1$  is negative (reverse bias)  
 the current  $I_2 = 0A$



10pts 10.  $I = \frac{1}{2} \mu_n C_{ox} \cdot \frac{W}{L} (V_{GS} - V_{th})^2 = \frac{1}{2} \mu_p C_{ox} \cdot \frac{W}{L} (V_{GS} - V_{tp})^2$   
assuming saturation

$$I = \frac{1}{2} \cdot 100E-6 \cdot \frac{1}{1} (V_{out} - 1)^2 = \frac{1}{2} \cdot 33E-6 \cdot \frac{1}{1} (-2 + 1)^2$$


$$V_{out} = 1.57 V$$

Saturation confirmed


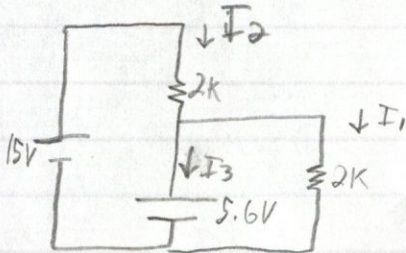
# Extra Credit

+10pts 11.  $I_1 = ?$  Assume Forward Bias




$$I_1 = 5.6 / 2k = \boxed{2.8 \text{ mA}}$$

$$I_2 = (15 - 5) / 2k = 5 \text{ mA}$$

$$I_3 = I_2 - I_1 = 2.2 \text{ mA}$$

Since  $I_3$  is positive, it confirms the diode is in forward bias

$I_2 = ?$  Assume Reverse Bias

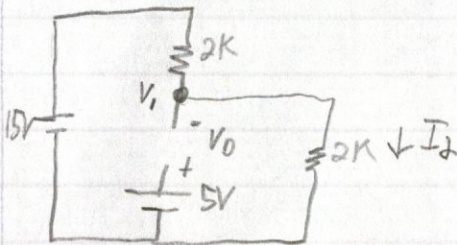

$$I_2 = 15 / 4k = 3.75 \text{ mA}$$

$$V_1 = 15 / 2 = 7.5 \text{ V}$$

$$V_0 = 5 - 7.5 = -2.5 < 0 \therefore \text{confirms reverse bias}$$

+10pts 12.  $I = [J_{sx} \cdot A (T^m e^{-V_{g0}/V_t})] \cdot e^{V_0/V_t}$   
 $J_{sx} = .5$   $V_{g0} = 1.17$   $m = 2.33$   $A = 100$   $V_0 = .575 \text{ V}$   
 $V_t = K \cdot T / q = 1.38 \text{ E-}23 \cdot T / 1.602 \text{ E-}19$

a)  $T = -20^\circ \text{C} = 253.15 \text{ K}$   $V_t = .0218 \text{ V}$

$$I = 2.36 \text{ E-}5 \text{ A}$$

$$V_{out} = I \cdot 10k + .575 = \boxed{.811 \text{ V}}$$

b)  $T = 40^\circ \text{C} = 313.15 \text{ K}$   $V_t = .0270 \text{ V}$

$$I = 7.390 \text{ E-}3 \text{ A}$$

This current would create a voltage greater than the bias voltage  $\therefore \boxed{V_{out} = 20 \text{ V}}$

c)  $T = 120^\circ \text{C} = 393.15 \text{ K}$   $V_t = .0339 \text{ V}$

$$I = 1.106 \text{ A}$$

This current again would create a voltage greater than the bias voltage  $\therefore \boxed{V_{out} = 20 \text{ V}}$



# Extra Credit – Problem 13 (20 Points)

```

1  module Counter_0_9(INPUT, count, seg);
2      input INPUT;
3      output reg [6:0] seg; // 7 segment display register [A B C D E F G]
4      output reg [3:0] count;
5
6      always @(posedge(INPUT)) // always on rising edge of the clock (INPUT)
7      begin
8          case (count) // increase the counter
9              4'b0000: count<=4'b0001; // 0 -> 1
10             4'b0001: count<=4'b0010; // 1 -> 2
11             4'b0010: count<=4'b0011; // 2 -> 3
12             4'b0011: count<=4'b0100; // 3 -> 4
13             4'b0100: count<=4'b0101; // 4 -> 5
14             4'b0101: count<=4'b0110; // 5 -> 6
15             4'b0110: count<=4'b0111; // 6 -> 7
16             4'b0111: count<=4'b1000; // 7 -> 8
17             4'b1000: count<=4'b1001; // 8 -> 9
18             4'b1001: count<=4'b0000; // 9 -> 0
19             default: count<=4'b0000; // default value of 0
20          endcase
21          case(count) // create the 7_seg output
22              4'b0000: seg <= 7'b1111110; // display 0
23              4'b0001: seg <= 7'b0110000; // display 1
24              4'b0010: seg <= 7'b1101101; // display 2
25              4'b0011: seg <= 7'b1111001; // display 3
26              4'b0100: seg <= 7'b0110011; // display 4
27              4'b0101: seg <= 7'b1011011; // display 5
28              4'b0110: seg <= 7'b1011111; // display 6
29              4'b0111: seg <= 7'b1110000; // display 7
30              4'b1000: seg <= 7'b1111111; // display 8
31              4'b1001: seg <= 7'b1110011; // display 9
32              default: seg <= 7'b1111110; // defaults to a display of 0
33          endcase
34      end
35  endmodule

```

Figure 1: Problem 13: 7 segment counter from 0 -> 9: code


```

1  `timescale 1ns / 1ps
2
3  module Counter_0_9_tb();
4      reg clk_t; // INPUT
5      wire [6:0] out_t; // 7 segment display register
6      wire [3:0] count_t; // counter register
7
8      Counter_0_9 Counter_0_9_t(clk_t, count_t, out_t);
9
10     initial
11     begin
12         repeat(21) begin
13             clk_t<=0;
14             #1 $display("Counter = %b", count_t);
15             #2 $display("7 seg = %b", out_t);
16
17             clk_t<=1;
18             #1 $display("Counter = %b", count_t);
19             #2 $display("7 seg = %b", out_t);
20         end
21     end
22 endmodule

```

Figure 2: 7 segment counter from 0 to 9 testbench code



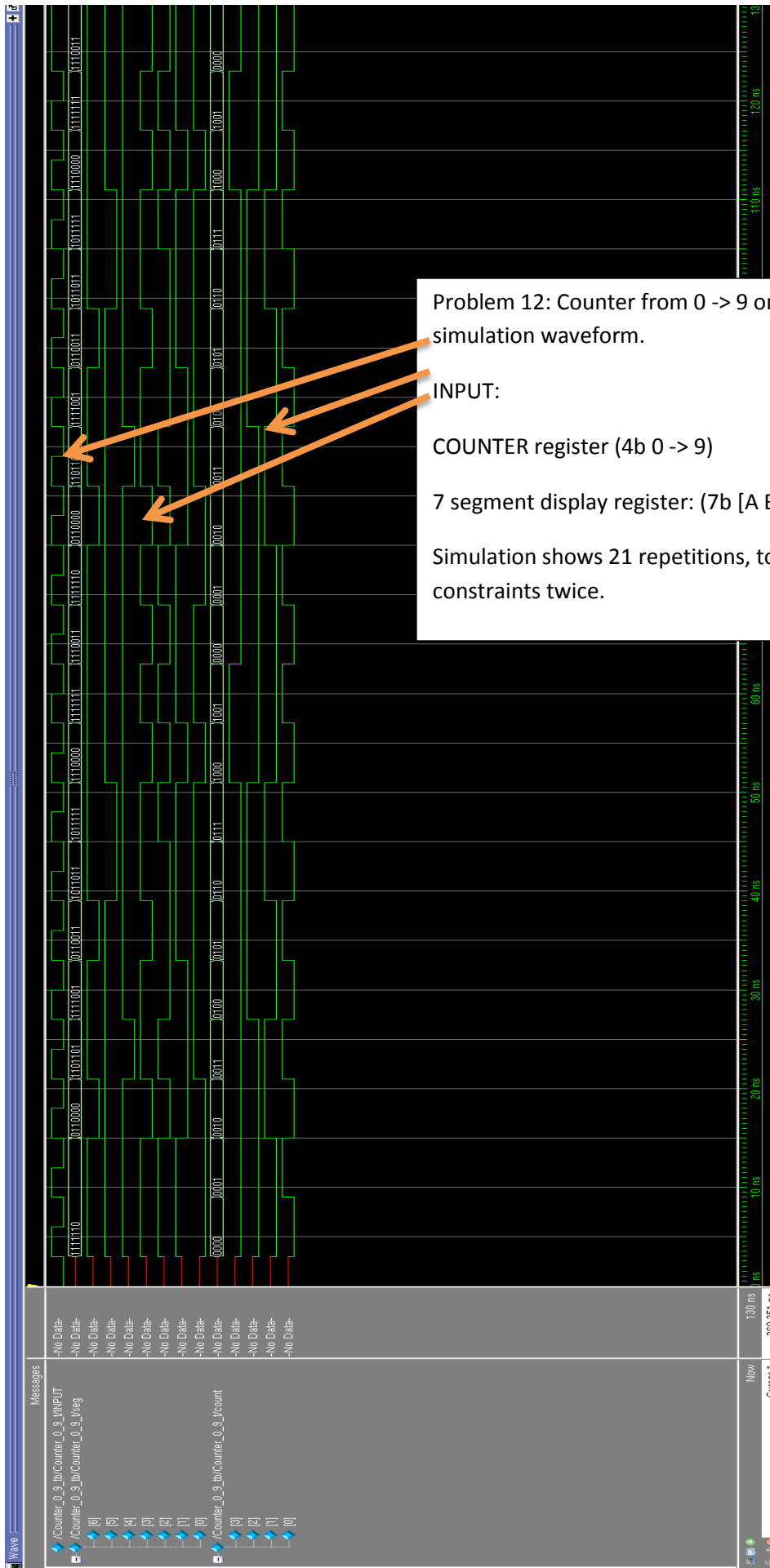

Problem 12: Counter from 0 -> 9 on a 7 segment display simulation waveform.

INPUT:

COUNTER register (4b 0 -> 9)

7 segment display register: (7b [A B C D E F G] of segment)

Simulation shows 21 repetitions, to show the 0->9->0 constraints twice.