 


Problem 1:


$$Y = \overline{(AB + C)}D$$

One possible design with static CMOS gates,



This design uses 16 transistors.

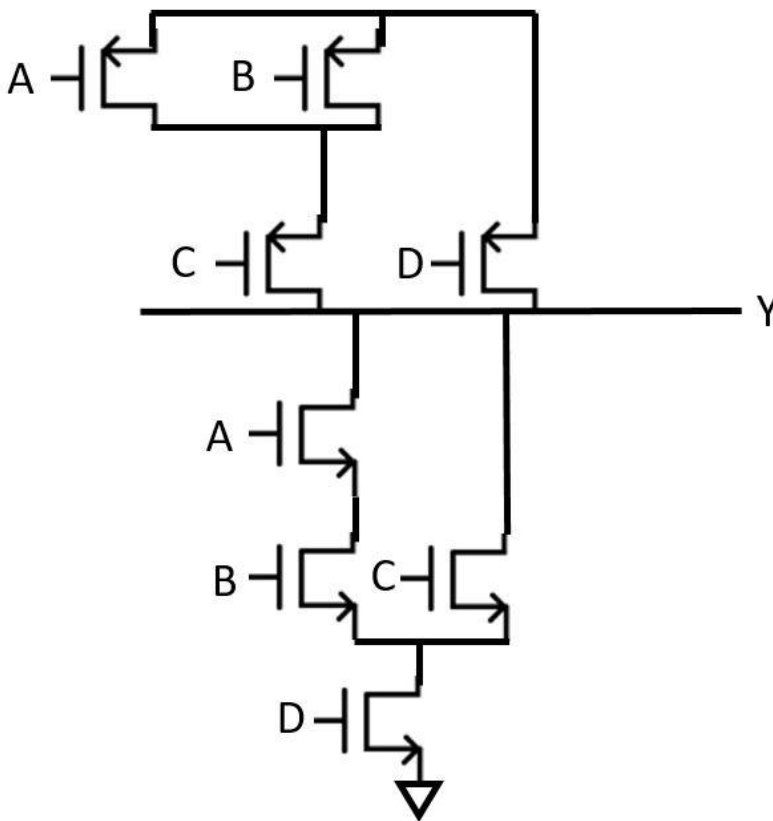
The below is one design for a compound CMOS gate



This design uses 8 transistors

Problem 2:

$$Y = \bar{A}\bar{B} + AB$$

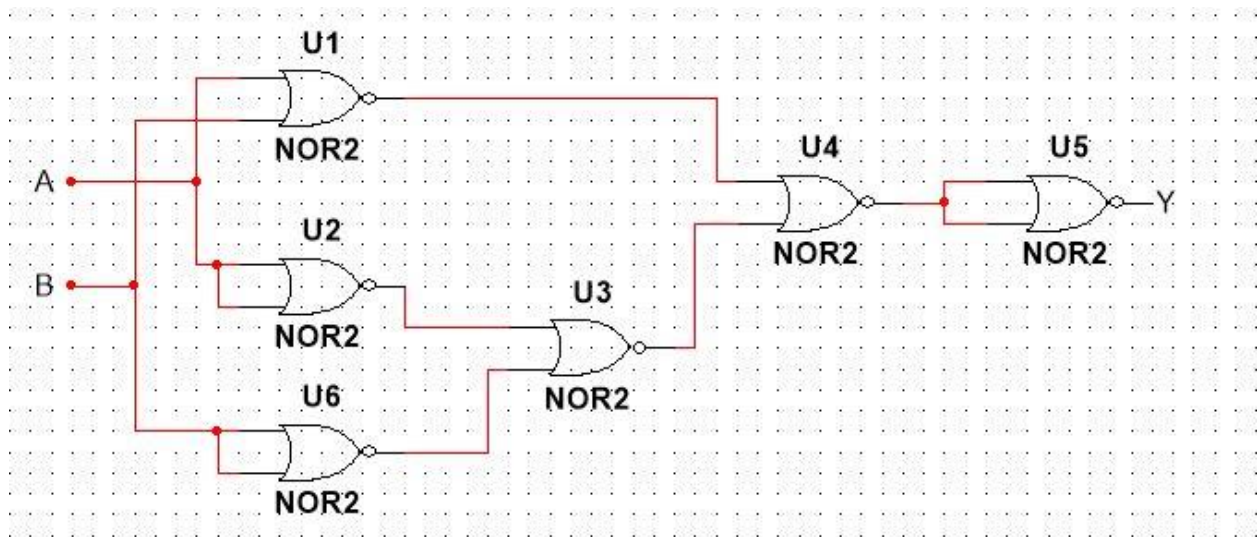


Problem 3:

For minimum sized 2 input NAND,


$$R_{SWN} = 2k\Omega, R_{SWP} = 6k\Omega, C = 40fF$$

$$T_{HL} = 2 * R_{SWn} * C = 4k * 40f = 160 * 10^{-12} \text{seconds} = 160 \text{pS}$$

Problem 4

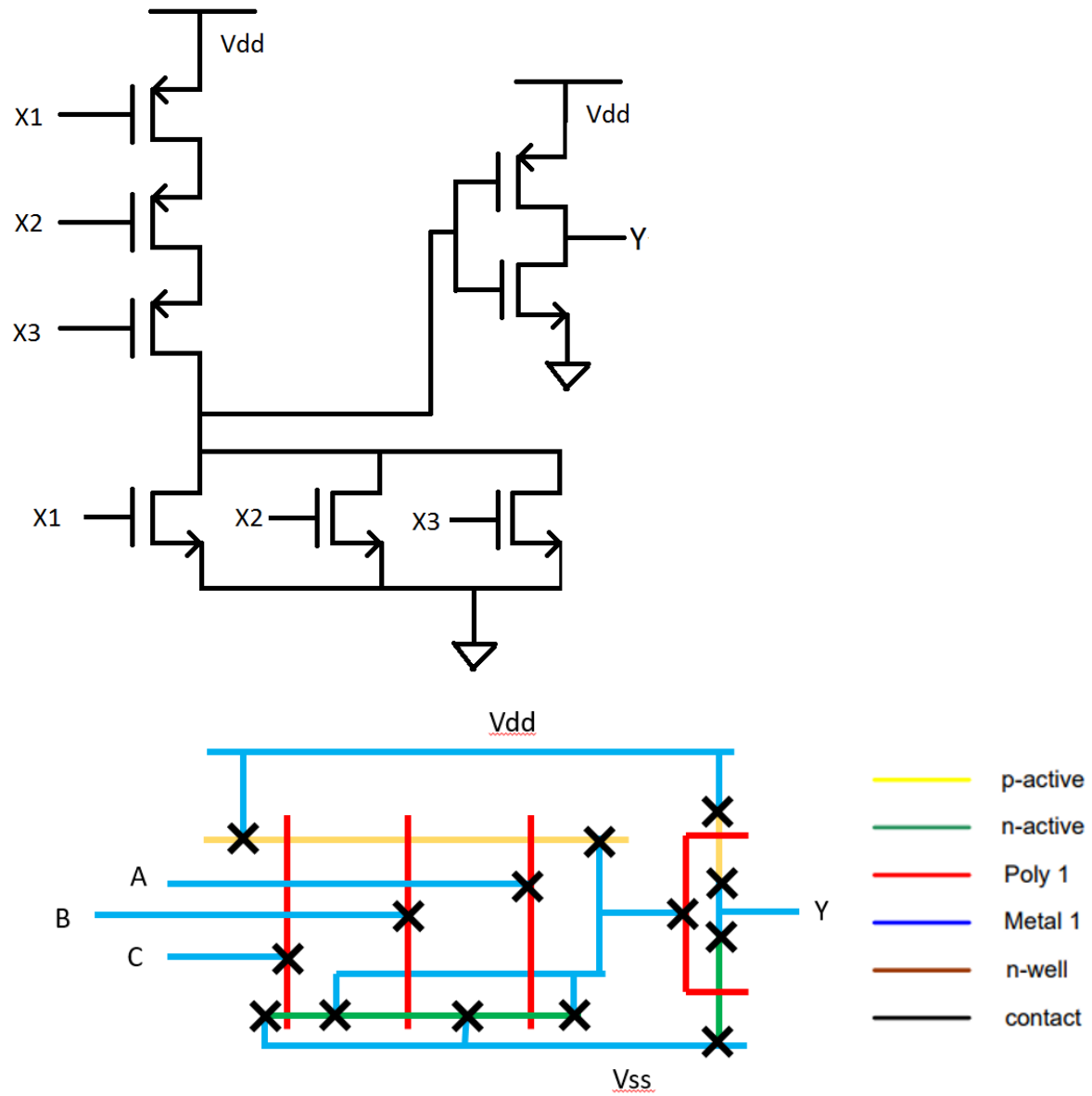


Problem 5

 

The second inverter is combined with the transmission gate, rather than two separate components.

Problem 6

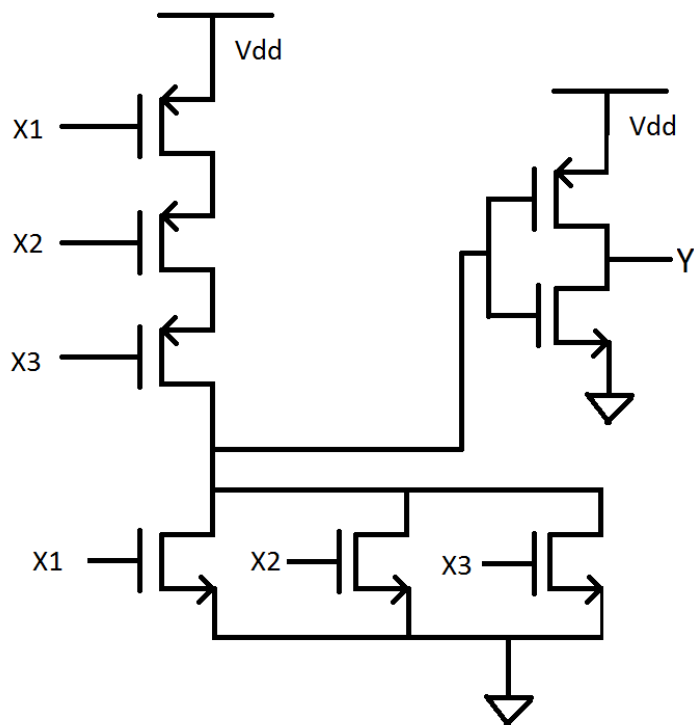


Problem 7

There should not be a contact between B and N_{active}

N_{active} region is missing one contact with V_{SS}

There should be a contact between Y and P_{active}

The metal contact between A and B that connects N_{active} and V_{SS} needs to be removed.

 

Problem 8

$$a) R_{W_Aluminum} = \frac{2.8 \cdot 10^{-8}}{0.2 \cdot 10^{-6}} \cdot \frac{180}{5} + \frac{2.8 \cdot 10^{-8}}{0.2 \cdot 10^{-6}} \cdot \frac{40-5}{5} = 6.02 \Omega$$

$$V_{wire} = 5 \cdot \frac{6.02}{100 + 6.02} = 283.9 \text{ mV}$$

$$V_{Resistor} = 5V - V_{wire} = 5 - 0.2839 = 4.716 \text{ V}$$

$$b) R_{W_Copper} = 3.655 \Omega$$

$$V_{wire} = 5 \cdot \frac{3.655}{100 + 3.655} = 0.176 \text{ V}$$

$$V_{Resistor} = 5 \cdot \left(\frac{100}{100 + 3.655} \right) = 4.824 \text{ V}$$

$$c) V_{RW} < 5V \cdot 5\% = 0.25V$$

$$5V \cdot \left(\frac{R_W}{100 + R_W} \right) < 0.25V \rightarrow R_W < 5.263 \Omega$$

$$R_W = 6.02 \cdot \frac{5 \mu m}{Width_{wire}} \rightarrow Width_{wire} \geq 5.72 \mu m$$

Problem 9:

Each inverter has $C_L = 1.5 \text{ fF} + 1.5 \text{ fF} = 3 \text{ fF}$

total load capacitance $C = 3 \text{ pF} \cdot 16 = 48 \text{ fF}$

$R_{SWp} = 6k\Omega \rightarrow T_{LH} = 6 \text{ k} \cdot 48 \text{ f} = 288 \cdot 10^{-12} \text{ s} = 288 \text{ pS}$

Problem 10

Mux4to1 code

```
h /home/jaaymond/ee330/verilog/EE330Homework/4to1MUX.v (/M
Ln#
1  `timescale 1ns/1ps
2  module MUX4to1(A, B, C, D, s1, s2, out);
3      input [3:0] A, B, C, D;
4      input s1, s2;
5      output [3:0] out;
6      reg [3:0] o;
7
8      assign out = o;
9
10     always @(*) begin
11         if(s1 == 0) begin
12             if(s2 == 0) begin
13                 o <= A;
14             end
15             else begin
16                 o <= C;
17             end
18         end
19         else begin
20             if(s2 == 0) begin
21                 o <= B;
22             end
23             else begin
24                 o <= D;
25             end
26         end
27     end
28 endmodule
```

Test bench Code

```
h /home/jaaymond/ee330/verilog/EE330Homework/MUX_tb.v (/M
Ln#
1  `timescale 1ns/1ps
2
3  module MUX_tb();
4
5      reg [3:0] A, B, C, D;
6      reg s1, s2;
7      wire [3:0] out;
8
9      MUX4to1 mux(.A(A), .B(B), .C(C), .D(D),
10         .s1(s1), .s2(s2), .out(out));
11
12     initial begin
13         A = 4'b0001;
14         B = 4'b0010;
15         C = 4'b0100;
16         D = 4'b1000;
17         s1 = 0;
18         s2 = 0;
19     end
20
21     always #20 s1 <= ~s1;
22     always #40 s2 <= ~s2;
23
24 endmodule
```

Simulation results

