

```

library IEEE;
use IEEE.std_logic_1164.all;

entity DFF_sync is
    port(i_D      : in std_logic;
          i_Clk   : in std_logic;
          i_Rst    : in std_logic;

          o_Q      : out std_logic);
end DFF_sync;

architecture behavior of DFF_sync is
begin
    process(i_Clk, i_Rst)
    begin

        -- We are now asynchronously resettable
        if(i_Rst = '1') then
            o_Q <= '0';
        elsif(rising_edge(i_Clk)) then
            o_Q <= i_D;
        end if;

    end process;
end behavior;

```

```

library IEEE;
use IEEE.std_logic_1164.all;
use ieee.numeric_std.all;

entity Mux2to1Modded is
    port(i_A  : in std_logic;
          i_B  : in std_logic;
          i_S  : in std_logic;
          o_F  : out std_logic);

end Mux2to1Modded;

architecture dataflow of Mux2to1Modded is
begin
    o_F <= i_A when (i_S = '0') else i_B;
    --o_F <= (i_A and (not i_S)) or (i_B and i_S);

end dataflow;

```

```

library IEEE;
use IEEE.std_logic_1164.all;
use ieee.numeric_std.all;

entity ClockDivider is
    port(i_Clk : in std_logic;
         i_Rst  : in std_logic;
         i_Sel  : in std_logic;

         o_F    : out std_logic);

end ClockDivider;

architecture structure of ClockDivider is

    component DFF_sync
        port(i_D      : in std_logic;
             i_Clk    : in std_logic;
             i_Rst    : in std_logic;
             o_Q      : out std_logic);
    end component;

    component Mux2to1Modded
        port(i_A      : in std_logic;
             i_B      : in std_logic;
             i_S      : in std_logic;
             o_F      : out std_logic);
    end component;

    signal s_D1, s_D2      : std_logic;
    signal s_notD1, s_notD2 : std_logic;

begin

    DFF1: DFF_sync
    port map( i_D      => s_notD1,
              i_Clk    => i_Clk,
              i_Rst    => i_Rst,
              o_Q      => s_D1);

    s_notD1 <= not s_D1;

    DFF2: DFF_sync
    port map( i_D      => s_notD2,

```

```


        i_Clk => s_notD1,
        i_Rst => i_Rst,
        o_Q      => s_D2);

s_notD2 <= not s_D2;

mux: Mux2to1Modded
port map(    i_A      => s_D1,
            i_B      => s_D2,
            i_S      => i_Sel,
            o_F      => o_F);

end structure;

```

 

```

library IEEE;
use IEEE.std_logic_1164.all;

-- 1Mhz => 1 us

entity Div_tb is
end Div_tb;

architecture behavior of Div_tb is
    signal s_clk      : std_logic := '1';

    signal s_Sel      : std_logic;
    signal s_Rst      : std_logic;
    signal s_F        : std_logic;
begin

DUT : entity work.ClockDivider
    port map (i_Clk => s_clk,

```

```

        i_Rst => s_Rst,
        i_Sel => s_Sel,

        o_F    => s_F);

    s_clk <= not s_clk after 500 ns;

process is
begin

    s_Rst    <= '1';
    s_Sel <= '0';
    wait for 4 us;
    -- Reset everything
    -- Wait for four clock pulses

    s_Rst    <= '0';
    s_Sel <= '0';
    wait for 4 us;
    -- Wait for four clock pulses

    s_Rst    <= '0';
    s_Sel <= '1';
    wait for 4 us;
    -- Wait for four clock pulses

    s_Rst    <= '1';
    s_Sel <= '0';
    wait for 4 us;
    -- Wait for four clock pulses

    s_Rst    <= '1';
    s_Sel <= '1';
    wait for 4 us;
    -- Wait for four clock pulses

end process;
end behavior;

```