

## EE 330 Fall 2012

### Homework 5

**Due Friday September 21 at the beginning of the lecture. You MUST clearly indicate your name and SECTION on the first page of your HW. Submissions that do not include the section WILL NOT be graded.**

If parameters are needed for process characterization, use the measured parameters from the ON (formerly AMI) T6AU process run that is attached at the end of this HW. On those problems that involve the design of passive components, a sketch of the design is sufficient provided you indicate dimensions (i.e. it need not be done in Cadence).

#### Problem 1 (10 points):


Design an 8k resistor in the ON 0.5u CMOS process. Use Poly 1 for the resistor. The width-to-length ratio of an imaginary box contacting on 4 sides but enclosing the resistor should be between 1:2 and 2:1.

#### Problem 2 (10 points):

Design a 2pF capacitor in the ON 0.5u CMOS process.
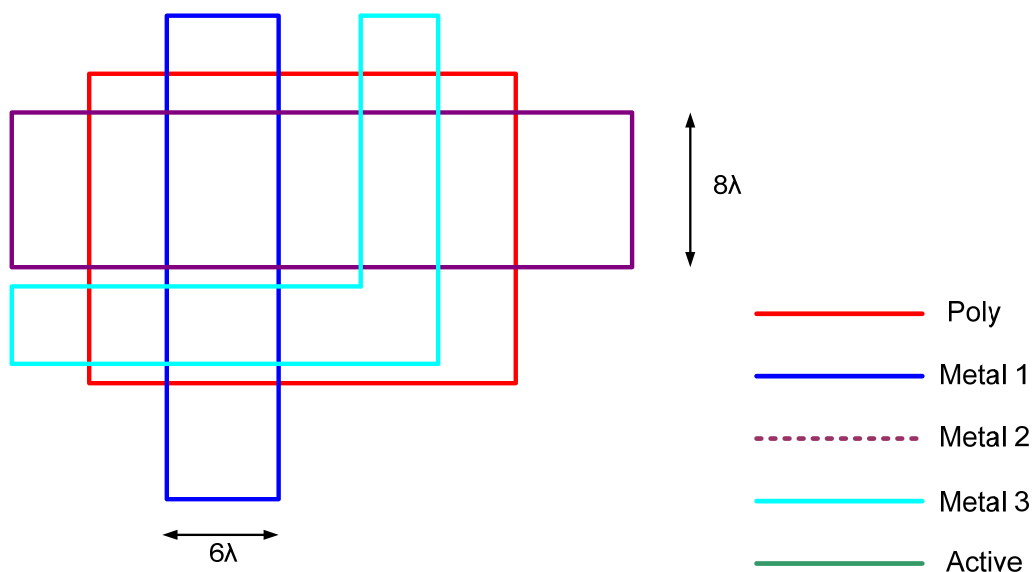
#### Problem 3 (15 points):

Four non-contacting regions are shown. Identify the parasitic capacitances and their size if this is fabricated in the 0.5u CMOS process. Don't forget that there is substrate below all layers. (Assume this drawing is to scale).




#### Problem 4 (10 points):

If the voltage of a forward-biased pn junction is varied from 0.55V to 0.65V, what is the corresponding range in the diode current? The area of the diode is  $50\mu\text{m}^2$  and  $J_s = 10^{-15} \text{A}/\text{u}^2$ .

**Problem 5 (10 points):**

Accurately determine the current  $I_D$  if  $V_X=5V$  for the below circuit. Repeat if  $V_X=450mV$ .

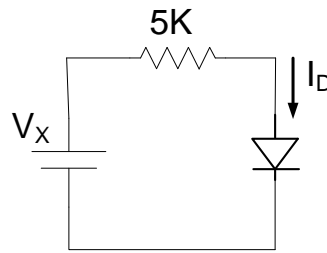**Problem 6 (5 points):**

Assume a  $1k\Omega$  resistor has a resistance of  $1.0345k\Omega$  at  $T=250^\circ K$ . If the TCR of this resistor is constant and equals  $100ppm/^\circ C$ , what will be the resistance at  $T=400^\circ K$ ?

**Problem 7 (20 points):**

Diodes are often used to build temperature sensors. Assuming that the standard diode equation accurately characterizes the I-V relationship for the diode under modest forward bias, and then taking the natural logarithm of both sides, an alternate equivalent expression for the diode equation can be written as:

$$I_D = I_S e^{\frac{V_D}{V_t}} \quad \rightarrow \quad V_D = T \left( \frac{k}{q} \right) \ln \left( \frac{I_D}{I_S} \right)$$

where  $T$  is in K. In the second equation, we have replaced  $V_t$  with  $kT/q$  to explicitly show the temperature dependence of this term. Looking at the second form, it could be argued that if a constant current were used to excite the diode, then the diode voltage would be proportional to temperature, and thus the diode could serve as a very linear temperature sensor. Unfortunately, this argument falls apart because the parameter  $I_S$  in the diode equation itself has some temperature dependence. However, the following equation explicitly shows the full temperature dependence of the diode equation:


$$I(T) = \left( J_{SX} A \left[ T^m e^{\frac{-V_{G0}}{V_t}} \right] \right) e^{\frac{V_D}{V_t}}$$

where the parameters  $J_{SX}$ ,  $V_{G0}$ , and  $m$  are constants that are independent of temperature and where  $A$  is the cross-sectional area of the diode.

- If  $J_{SX}=0.45A/\mu^2$ ,  $V_{G0}=1.17V$ ,  $m=2.3$ , and  $A=100 \mu^2$ , obtain an expression for  $I_S$  and plot it versus temperature from  $T=0^\circ C$  to  $T=100^\circ C$ .
- If  $I_S$  was measured in the laboratory at  $t=27^\circ C$ , what percent change in  $I_S$  would occur if the temperature in the room is increased to  $30^\circ C$ .
- Comment on the accuracy you can expect to obtain in measuring  $I_S$  in the laboratory if the heating/cooling in the room has a ripple temperature of  $2^\circ C$  peak to peak.

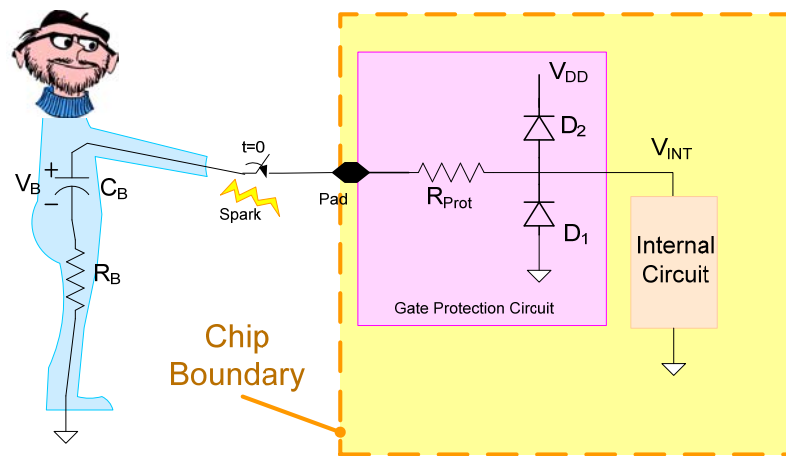**Problem 8 (20 points):**

Gate protection circuits are used to protect the sensitive gate oxide of devices connected to the input of an integrated circuit from modest short-duration over voltages. Although no input protection circuit can protect from all unknown over-voltages, the Human Body Model (HBM) is often used to model the type of over-voltages that are common when humans might become statically charged during normal activities. Such a model is shown below. In this model,  $R_B$  is the body resistance,  $C_B$  is the body capacitance and  $V_B$  is the charge on the body capacitance. At  $t=0$  it is assumed that the switch is closed and this inserts a voltage into the input pad of the IC. In the absence of the gate protection circuit, the pad voltage will appear directly on the voltage  $V_{INT}$ .



Assume the Internal Circuit has an input that is the two gates of a minimum sized inverter designed in the ON 0.5u CMOS process. Assume that the diodes  $D_1$  and  $D_2$  can be modeled as an ideal diode with  $J_S=10^{-20} \text{ A/u}^2$ , and that the area of the two diode junctions is  $1000 \text{ u}^2$ . Consider two HBMs. One is termed a low-voltage model and the other a high-voltage model. These are characterized respectively by:


HBM<sub>1</sub>:  $V_B=250\text{V}$ ,  $C_B=150\text{pF}$ ,  $R_B=1.5\text{K}$

HBM<sub>2</sub>:  $V_B=2\text{KV}$ ,  $C_B=150\text{pF}$ ,  $R_B=1.5\text{K}$

- What will be the peak value of the voltage  $V_{INT}$  when the switch is closed if the gate protection circuit is absent (i.e. the Pad is directly connected to the Internal Circuit) with each of the models.
- What will be the peak value of the voltage  $V_{INT}$  with each of the models when the switch is closed if the gate protection circuit is present? Assume  $R_{PROT}=15\text{K}$ .
- What will be the peak current in  $D_2$  with each of the models? Assume  $R_{PROT}=15\text{K}$ .
- What is the purpose of including the resistor  $R_{PROT}$  and what are the disadvantages of including this resistor in the gate protection circuit?

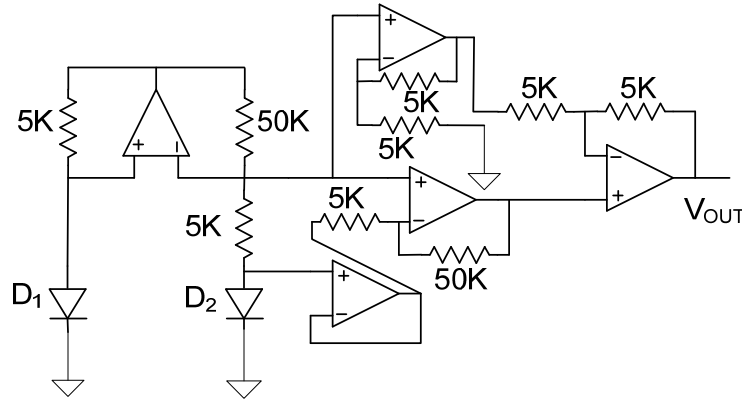**Problem 9 (10 points, not required but will count for extra credit):**


Obtain an expression for the output voltage versus temperature for the circuit shown below. Assume  $D_1$  and  $D_2$  are matched.



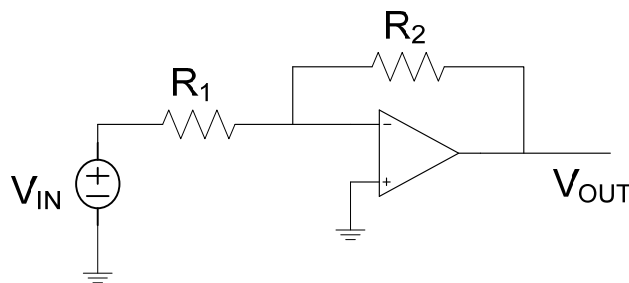**Problem 10 (10 points, not required but will count for extra credit):**

The audio amplifier shown below has a gain determined by the resistors  $R_1$  and  $R_2$ .  $R_1$  is a 1k ideal resistance, while  $R_2$  is 10k when the voltage across it is 0V and has a voltage coefficient of resistance of 400ppm/V.

- If  $V_{IN} = 0.1 \sin 2000t$ , what is the maximum error this amplifier will make in amplifying this signal due to the voltage coefficient of  $R_2$ ?
- Repeat part a) if  $V_{IN} = \sin 2000t$



# MOSIS WAFER ACCEPTANCE TESTS

RUN: T6AU  
TECHNOLOGY: SCN05  
microns

VENDOR: AMIS  
FEATURE SIZE: 0.5

Run type: SKD

INTRODUCTION: This report contains the lot average results obtained by MOSIS

from measurements of MOSIS test structures on each wafer of this fabrication lot. SPICE parameters obtained from similar measurements on a selected wafer are also attached.

COMMENTS: American Microsystems, Inc. C5

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM	3.0/0.6			
Vth		0.79	-0.92	volts
SHORT	20.0/0.6			
Idss		446	-239	uA/um
Vth		0.68	-0.90	volts
Vpt		10.0	-10.0	volts
WIDE	20.0/0.6			
Ids0		< 2.5	< 2.5	pA/um
LARGE	50/50			
Vth		0.68	-0.95	volts
Vjbkd		10.9	-11.6	volts
Ijlk		<50.0	<50.0	pA
Gamma		0.48	0.58	V^0.5
K' (Uo*Cox/2)		56.4	-18.2	uA/V^2
Low-field Mobility		463.87	149.69	cm^2/V*s

COMMENTS: Poly bias varies with design technology. To account for mask bias use the appropriate value for the parameter XL in your SPICE model card.

Design Technology	XL (um)	XW (um)
-----	-----	-----
SCMOS_SUBM (lambda=0.30)	0.10	0.00
SCMOS (lambda=0.35)	0.00	0.20

FOX TRANSISTORS	GATE	N+ACTIVE	P+ACTIVE	UNITS
Vth	Poly	>15.0	<-15.0	volts

PROCESS PARAMETERS	N+	P+	POLY	PLY2_HR	POLY2	M1	M2	UNITS
Sheet Resistance	83.5	105.3	23.5	999	44.2	0.09	0.10	ohms/sq
Contact Resistance	64.9	149.7	17.3		29.2		0.97	ohms
	M3	N\PLY	N_W					UNITS
Sheet Resistance	0.05	824	816					ohms/sq
Contact Resistance	0.79							ohms
Gate Oxide Thickness	142							angstrom

COMMENTS: N\POLY is N-well under polysilicon.

CAPACITANCE PARAMETERS	N+	P+	POLY	POLY2	M1	M2	M3	N_W	UNITS
Area (substrate)	425	731	84		27	12	7	37	aF/um^2
Area (N+active)			2434		35	16	11		aF/um^2
Area (P+active)			2335						aF/um^2
Area (poly)				938	56	15	9		aF/um^2
Area (poly2)					49				aF/um^2
Area (metall1)						31	13		aF/um^2
Area (metal2)							35		aF/um^2
Fringe (substrate)	344	238			49	33	23		aF/um
Fringe (poly)					59	38	28		aF/um
Fringe (metall1)						51	34		aF/um
Fringe (metal2)							52		aF/um
Overlap (N+active)			232						aF/um
Overlap (P+active)			312						aF/um

CIRCUIT PARAMETERS			UNITS
Inverters	K		
Vinv	1.0	2.02	volts
Vinv	1.5	2.28	volts
Vol (100 uA)	2.0	0.13	volts
Voh (100 uA)	2.0	4.85	volts
Vinv	2.0	2.46	volts
Gain	2.0	-19.72	
Ring Oscillator Freq.			
DIV256 (31-stg,5.0V)		95.31	MHz
D256_WIDE (31-stg,5.0V)		147.94	MHz
Ring Oscillator Power			
DIV256 (31-stg,5.0V)		0.49	uW/MHz/gate
D256_WIDE (31-stg,5.0V)		1.01	uW/MHz/gate

COMMENTS: SUBMICRON  
T6AU SPICE BSIM3 VERSION 3.1 PARAMETERS

SPICE 3f5 Level 8, Star-HSPICE Level 49, UTMOST Level 8

\* DATE: Jan 11/07  
\* LOT: T6AU WAF: 7101  
\* Temperature\_parameters=Default

```
.MODEL CMOSN NMOS (
+VERSION = 3.1          TNOM = 27          LEVEL = 49
+XJ = 1.5E-7           NCH = 1.7E17        TOX = 1.42E-8
+K1 = 0.8976376        K2 = -0.09255       VTH0 = 0.629035
+K3B = -8.2369696      W0 = 1.041146E-8    K3 = 24.0984767
+DVT0W = 0             DVT1W = 0           NLX = 1E-9
+DVT0 = 2.7123969      DVT1 = 0.4232931    DVT2W = 0
+U0 = 451.2322004      UA = 3.091785E-13   DVT2 = -0.1403765
+UC = 1.22401E-11      VSAT = 1.715884E5   UB = 1.702517E-18
+AGS = 0.130484        B0 = 2.446405E-6     A0 = 0.6580918
+KETA = -3.043349E-3   A1 = 8.18159E-7       B1 = 5E-6
+RDSW = 1.367055E3     PRWG = 0.0328586      A2 = 0.3363058
+WR = 1                WINT = 2.443677E-7   PRWB = 0.0104806
+XL = 1E-7             XW = 0              LINT = 6.999776E-8
+DWB = 3.676235E-8     VOFF = -1.493503E-4      DWG = -1.256454E-8
+CIT = 0               CDSC = 2.4E-4        NFACTOR = 1.0354201
+CDSCB = 0             ETA0 = 2.342963E-3   CDSCD = 0
+DSUB = 0.0764123      PCLM = 2.5941582      ETAB = -1.5324E-4
+PDIBLC2 = 2.366707E-3 PDIBLCB = -0.0431505   PDIBLC1 = 0.8187825
+PSCBE1 = 6.611774E8   PSCBE2 = 3.238266E-4   DROUT = 0.9919348
+DELTA = 0.01          RSH = 83.5          PVAG = 0
+PRT = 0               UTE = -1.5          MOBMOD = 1
+KT1L = 0              KT2 = 0.022          KT1 = -0.11
+UB1 = -7.61E-18       UC1 = -5.6E-11        UA1 = 4.31E-9
+WL = 0                WLN = 1            AT = 3.3E4
+WWN = 1               WWL = 0            WW = 0
+LLN = 1               LW = 0             LL = 0
+LWL = 0               CAPMOD = 2          LWN = 1
+CGDO = 2.32E-10       CGSO = 2.32E-10        XPART = 0.5
+CJ = 4.282017E-4      PB = 0.9317787       CGBO = 1E-9
+CJSW = 3.034055E-10   PBSW = 0.8             MJ = 0.4495867
+CJSWG = 1.64E-10      PBSWG = 0.8            MJSW = 0.1713852
+CF = 0                PVTH0 = 0.0520855    MJSWG = 0.1713852
+PK2 = -0.0289036      WKETA = -0.0237483    PRDSW = 112.8875816
                        LKETA = 1.728324E-3
*)
```

```

.MODEL CMOSF PMOS (
+VERSION = 3.1
+XJ      = 1.5E-7
+K1      = 0.5464347
+K3B     = -0.8373484
+DVT0W   = 0
+DVT0    = 2.0973823
+U0      = 220.5922586
+UC      = -6.19354E-11
+AGS     = 0.1447245
+KETA    = -1.093365E-3
+RDSW    = 3E3
+WR      = 1
+XL      = 1E-7
+DWB     = 1.706031E-8
+CIT     = 0
+CDSCB   = 0
+DSUB    = 1
+PDIBLC2 = 3.201161E-3
+PSCBE1  = 4.876974E9
+DELTA   = 0.01
+PRT     = 0
+KT1L    = 0
+UB1     = -7.61E-18
+WL      = 0
+WWN     = 1
+LLN     = 1
+LWL     = 0
+CGDO    = 3.12E-10
+CJ      = 7.254264E-4
+CJSW    = 2.496599E-10
+CJSWG   = 6.4E-11
+CF      = 0
+PK2     = 3.73981E-3
)
*
TNOM     = 27
NCH      = 1.7E17
K2       = 8.119291E-3
W0       = 1.30945E-8
DVT1W    = 0
DVT1     = 0.5356454
UA       = 3.144939E-9
VSAT     = 1.176415E5
B0       = 1.149181E-6
A1       = 3.467482E-4
PRWG     = -0.0418549
WINT     = 3.007497E-7
XW       = 0
VOFF     = -0.0801591
CDSC     = 2.4E-4
ETA0     = 0.4060383
PCLM     = 2.2703293
PDIBLCB  = -0.057478
PSCBE2   = 5E-10
RSH      = 105.3
UTE      = -1.5
KT2      = 0.022
UC1      = -5.6E-11
WLN      = 1
WWL      = 0
LW       = 0
CAPMOD   = 2
CGSO     = 3.12E-10
PB       = 0.9682229
PBSW     = 0.99
PBSWG    = 0.99
PVTH0    = 5.98016E-3
WKETA    = 7.286716E-4
LEVEL    = 49
TOX      = 1.42E-8
VTH0     = -0.9232867
K3       = 5.1623206
NLX      = 5.772187E-8
DVT2W    = 0
DVT2     = -0.1185455
UB       = 1E-21
A0       = 0.8441929
B1       = 5E-6
A2       = 0.4667486
PRWB     = -0.0212201
LINT     = 1.040439E-7
DWG      = -2.133809E-8
NFACTOR  = 0.9468597
CDSCD    = 0
ETAB     = -0.0633609
PDIBLC1  = 0.0279014
DROUT    = 0.1718548
PVAG     = 0
MOBMOD   = 1
KT1      = -0.11
UA1      = 4.31E-9
AT       = 3.3E4
WW       = 0
LL       = 0
LWN      = 1
XPART    = 0.5
CGBO     = 1E-9
MJ       = 0.4969013
MJSW     = 0.386204
MJSWG    = 0.386204
PRDSW    = 14.8598424
LKETA    = -4.768569E-3

```