

EE 230 Lab

Lab 2 report

Report: **First-order filters**

Lab work done by _____ Sean Gordon _____

and _____ Tejas Agarwal _____

Lab work date: 2/13/2019

Report submission date:

Lab Section: E


Graded by _____

Score _____

Introduction

This lab works through the relationships of filter circuits and frequencies, giving a more hands on approach to the results we had seen in class. It focuses on a series of different filter types, gradually getting more complex until the design portion at the end.

A. RC low -pass


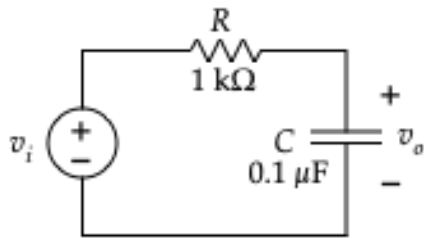


Include the calculation for the transfer function and corner frequency.

$$V_o = (1/sC)/(R + 1/sC) \Rightarrow 1/(RSC + 1) = T = 10,000/s$$


Figures: Insert the magnitude and phase frequency response plots that you calculated and measured.

	A	B	C	D	E	F	G
1	frequency (Hz)	Xc	predicted magnitude	Vo	measured magnitude	predicted phase	measured phase
2	10	159154.9431	0.999980261	2.46	0.98	-0.35999526	-1.9
3	15	106103.2954	0.999998875	2.51	1.00	-0.53998401	-2
4	25	63661.97724	0.999996875	2.52	1.01	-0.89992599	-2.1
5	40	39788.73577	0.999992	2.53	1.01	-1.43969692	-2.8
6	65	24485.37586	0.999978876	2.522	1.01	-2.33870029	-4.3
7	100	15915.49431	0.999950004	2.515	1.01	-3.59527378	-6.6
8	150	10610.32954	0.999887519	2.5	1.00	-5.38409592	-11
9	250	6366.197724	0.999687646	2.456	0.98	-8.92705487	-16
10	400	3978.873577	0.999200959	2.36	0.94	-14.1078024	-22
11	650	2448.537586	0.997894171	2.166	0.87	-22.2154504	-30
12	1000	1591.549431	0.99503719	1.86	0.74	-32.1419076	-40
13	1500	1061.032954	0.988936353	1.5	0.60	-43.3038073	-52
14	2500	636.6197724	0.9701425	1.05	0.42	-57.5183634	-63
15	4000	397.8873577	0.928476691	0.76	0.30	-68.303016	-71
16	6500	244.8537586	0.838443616	0.47	0.19	-76.2416041	-78
17	10000	159.1549431	0.707106781	0.32	0.13	-80.9569389	-82
18	15000	106.1032954	0.554700196	0.22	0.09	-83.9433894	-85
19	25000	63.66197724	0.371390676	0.13	0.05	-86.3573531	-86
20	40000	39.78873577	0.242535625	0.082	0.03	-87.7214753	-88
21	65000	24.48537586	0.152057184	0.083	0.03	-88.5973716	-89
22	100000	15.91549431	0.099503719	0.084	0.03	-89.0881863	-90

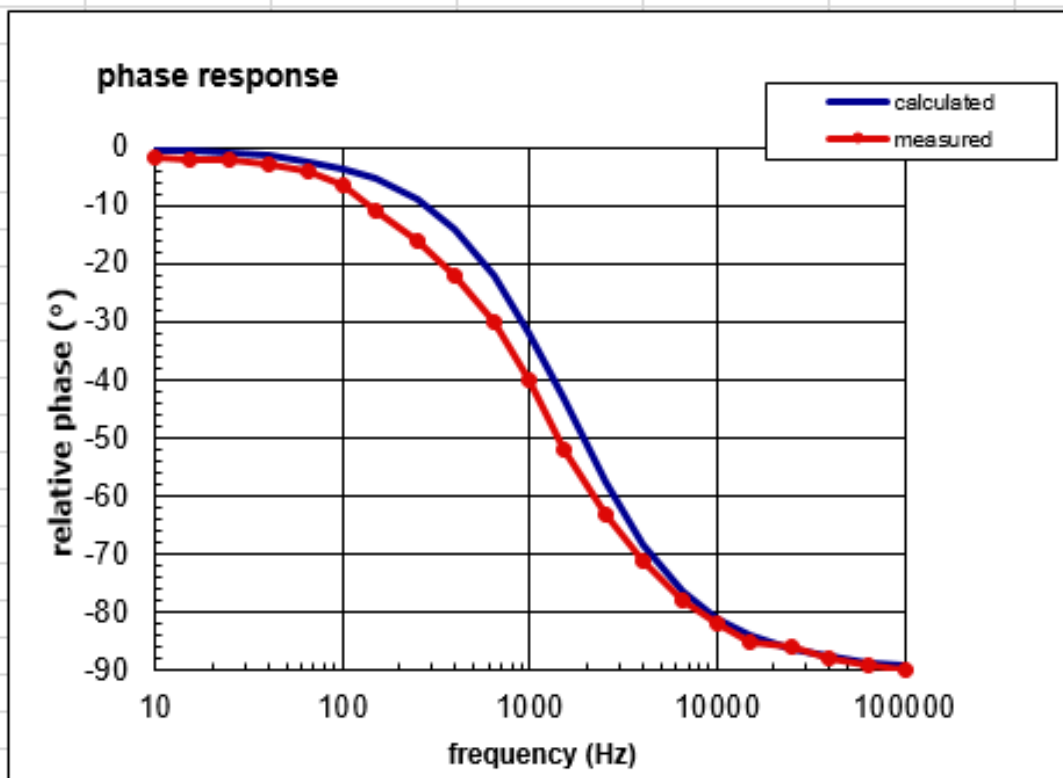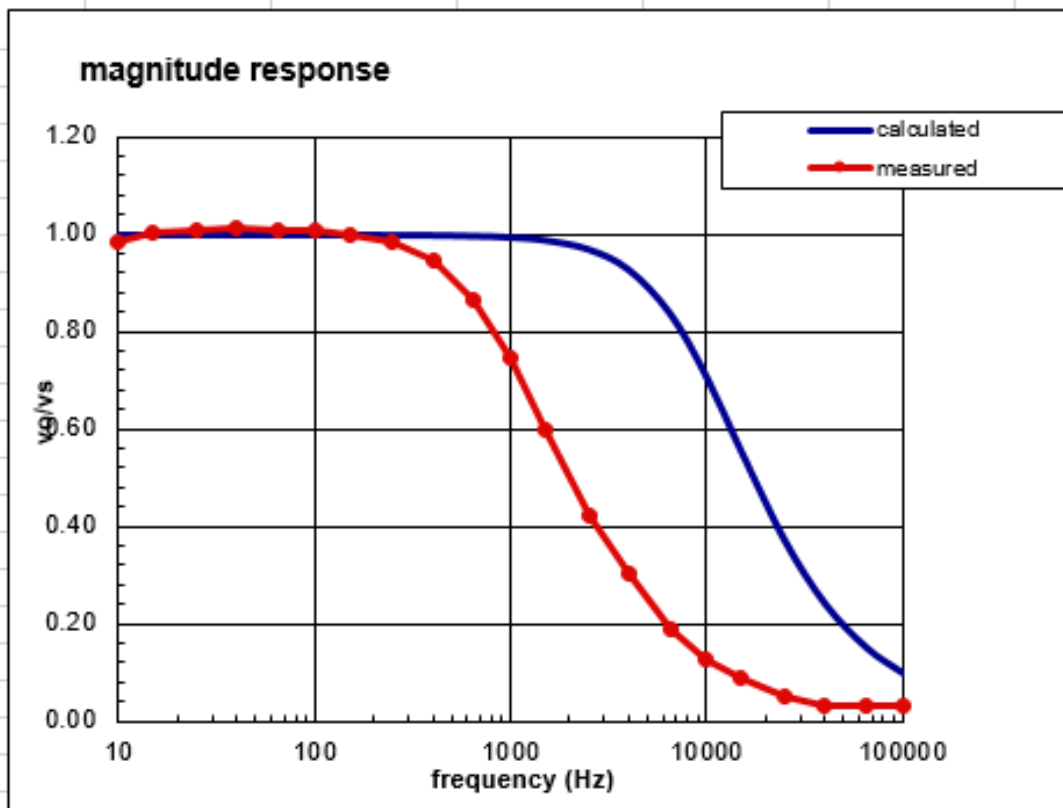

B. RL

low-pass

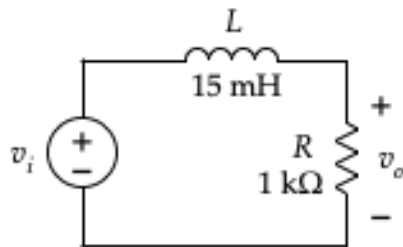

Include the calculation for the transfer function and corner frequency and your measurement of the low-frequency transfer-function magnitude and corner frequency.

$$T = R/(R+SL) = 1000/(1000+s*.015)$$


$$\text{low-freq: } 1/(1+(w(L/R))^2)^{1/2}$$

$$\text{Calc. magnitude} = 1/(1+(1000(.015/1000))^2)^{1/2} = .999$$

$$\text{Meas. Voltage} = 2.365 \Rightarrow V_o/2.5 = .946$$

$$2.365/(2)^{1/2} = 1.672 \quad \text{freq} = 11.47 \text{ kHz}$$

C. Active low-pass filter.

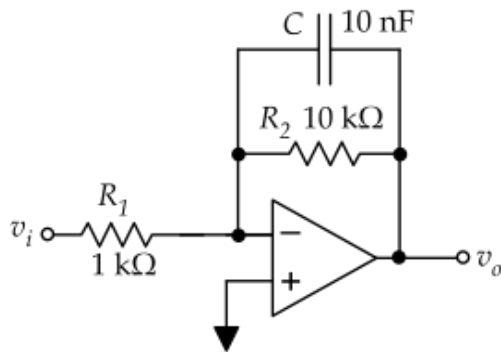


Include the calculation for the transfer function, the corner frequency, and the pass-band gain.

$$T = \frac{-10}{(10^{-4}s + 1)}$$


$$\omega_c = 10000$$

$$\text{PassBand} = T = \frac{-10}{(10^{-4}s + 1)}$$

Figure: Insert the magnitude frequency response that you measured.

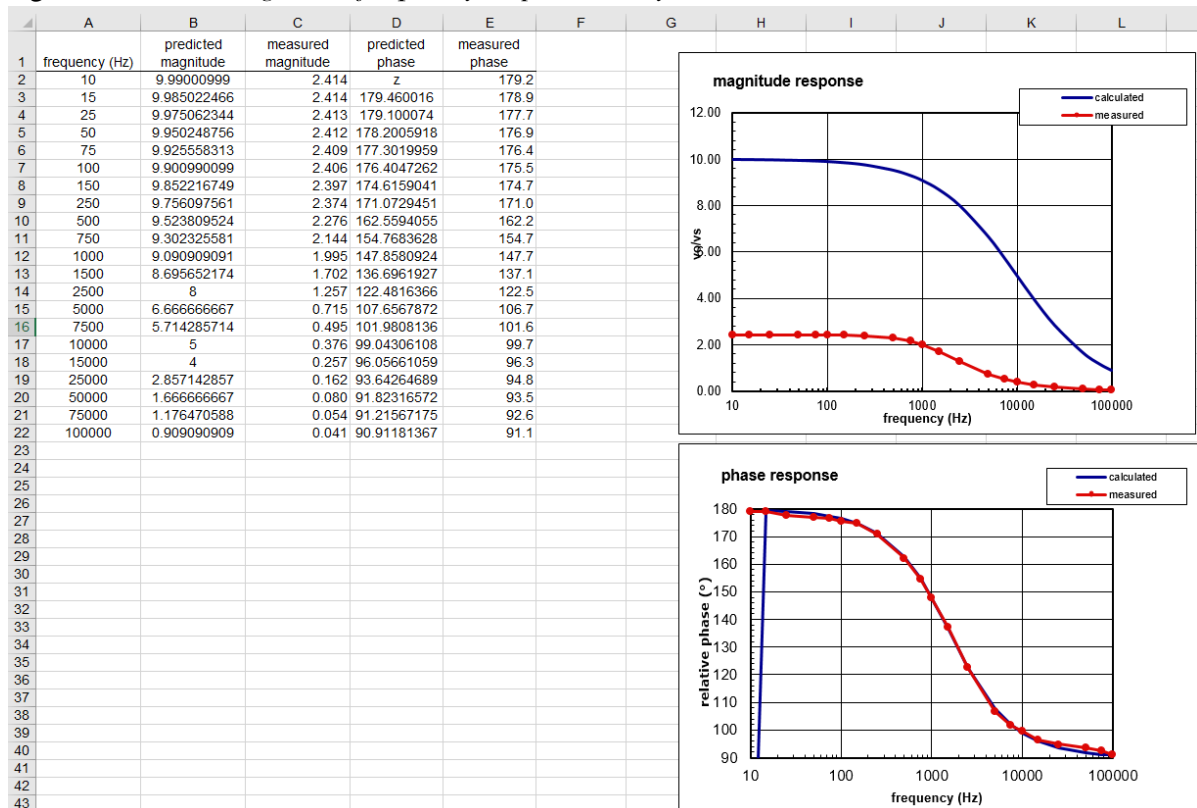


D. RC high-pass

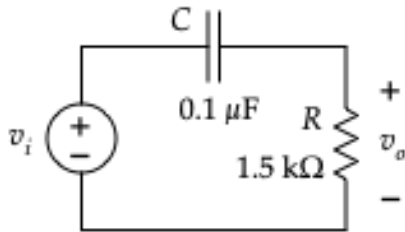


Include the calculation for the transfer function and corner frequency.

$$T = \frac{1.5 \cdot 10^{-4} \text{ s}}{(1.5 \cdot 10^{-4})s + 1} = \frac{s}{s + 1/10^{-4}} \quad \omega_c = 6666.6$$

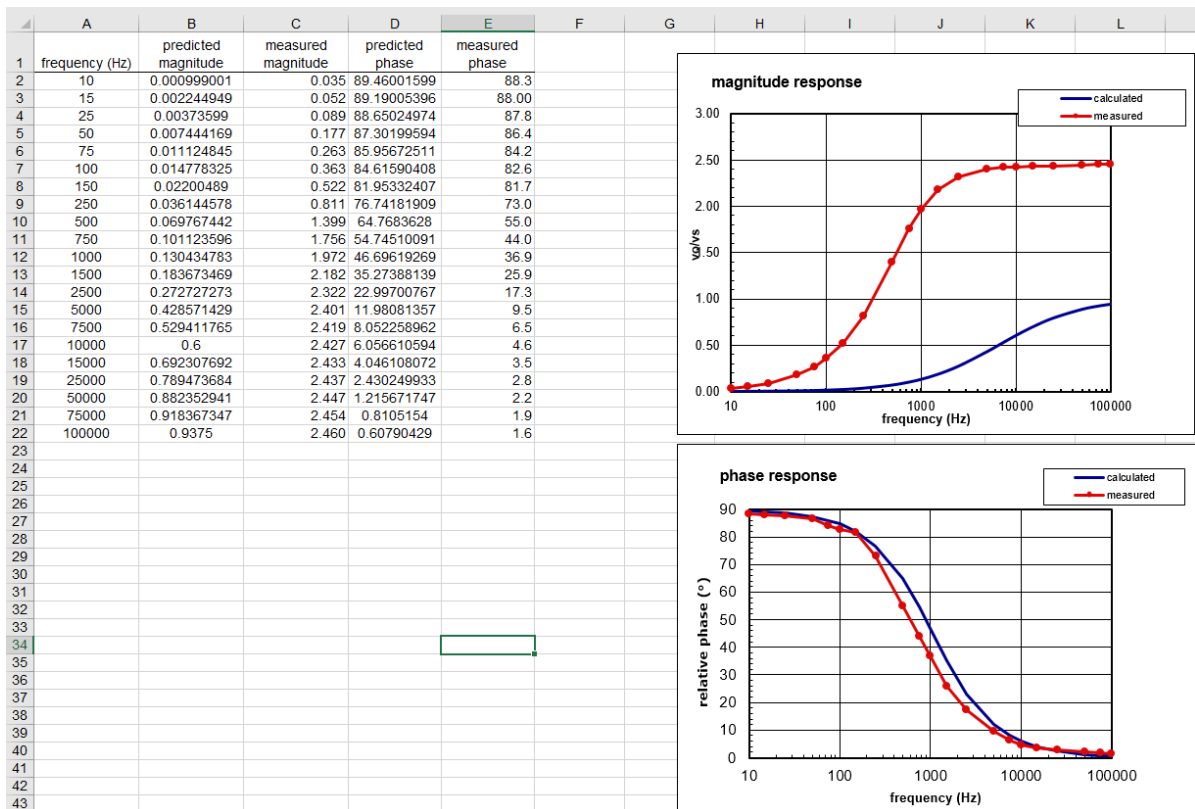Figures: Insert the magnitude and phase frequency response plots that you calculated and measured.




E. Passive low-pass design

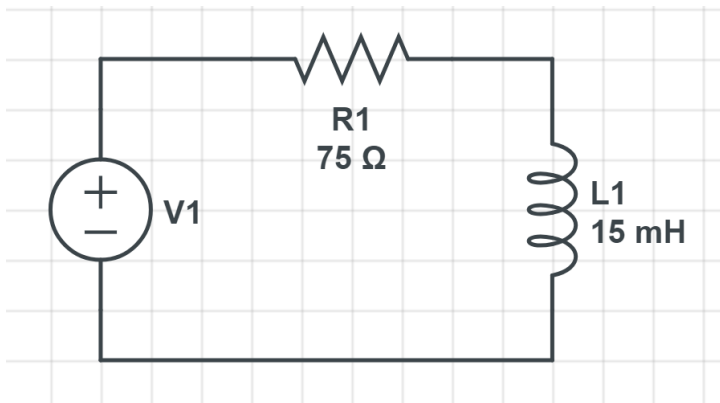


$$T(s) = (R/L)/(R/L + s) = G_0 \cdot \omega_c / (\omega_c + s)$$

$$\omega_c = R/L = 10\ \text{kHz} \quad G_0 = 1/2$$

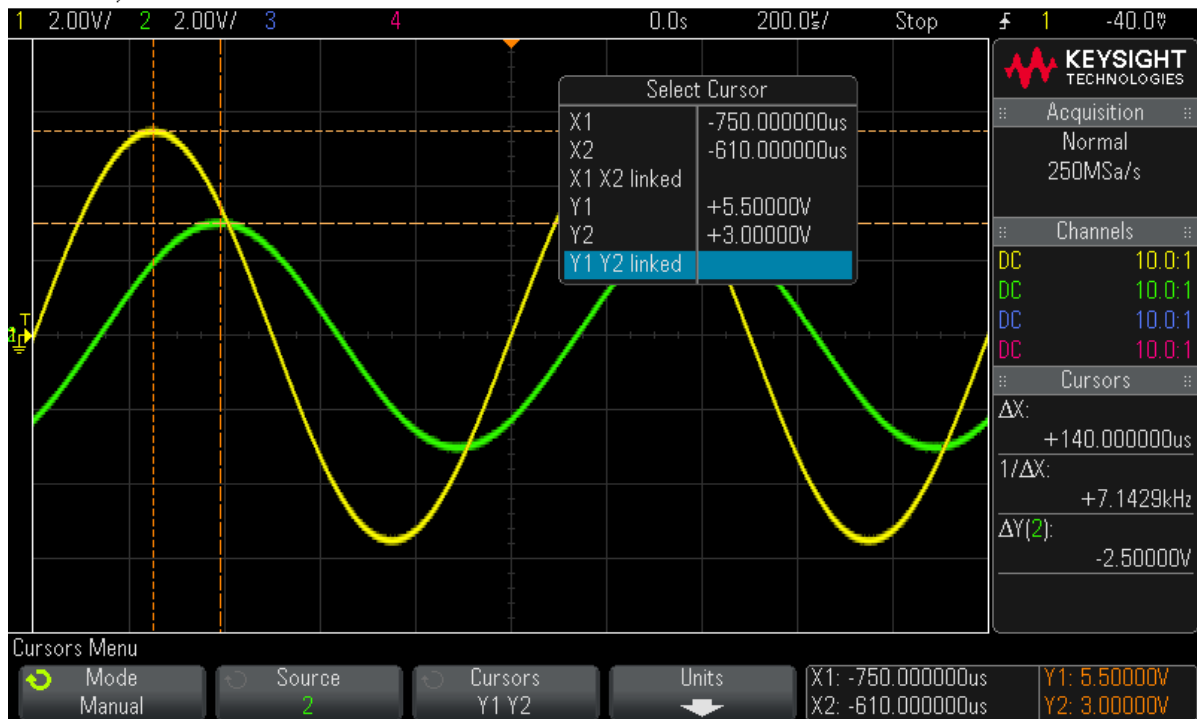DSO-X 2024A, MY55140904: Thu Feb 21 07:53:57 2019




F. Active high-pass design

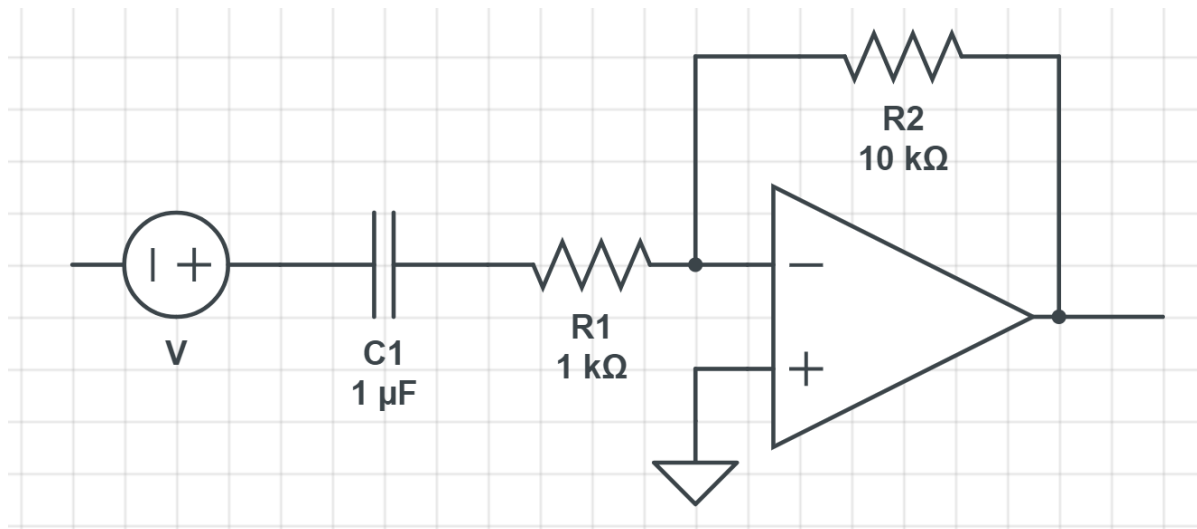

$$T(s) = \frac{R_2}{R_1 + 1/sC} = \frac{R_2/R_1}{s/(s + 1/CR_1)} = G_0 \frac{s}{\omega_c + s}$$

$$\omega_c = 1/CR_1 = 1000\text{Hz} \quad G_0 = -R_2/R_1 = -10$$

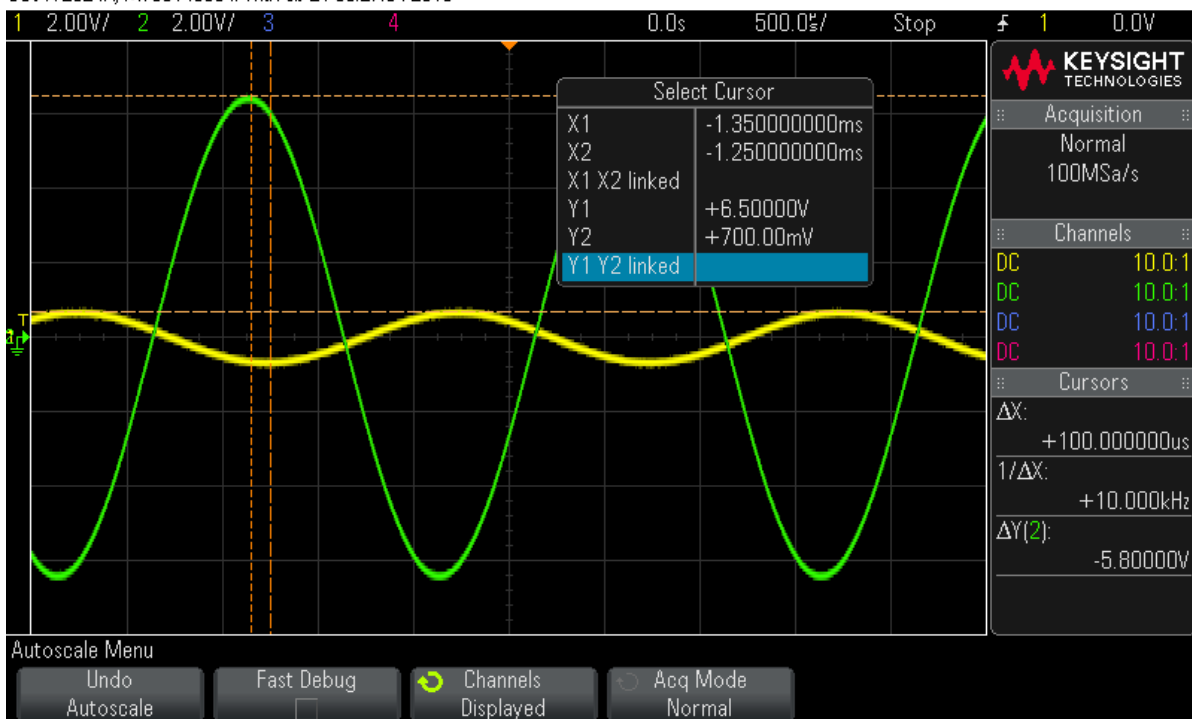DSO-X 2024A, MY55140904: Thu Feb 21 08:27:04 2019



Conclusion

EE 230 Lab

Lab 2 report

The lab focused on several different high and low pass circuits, with a design portion at the end. We had some issues with measurements in the beginning of the lab, but things smoothed out as we moved forward and exchanged some parts.