

## EE 230 Lab

## lab 1 report

Report: **Basic op-amp circuits**

Lab work done by \_\_\_\_\_ Sean Gordon \_\_\_\_\_

and \_\_\_\_\_ Tejas Agarwal \_\_\_\_\_

Lab work date: 1/23/2019

Report submission date:

Lab Section: E


Graded by \_\_\_\_\_

Score \_\_\_\_\_

### Introduction

This lab acts as an initial review of op-amps, eventually sprinkling in newer concepts that use op amps in their implementations. The lab ensures experimentation with each device, and adds several questions for contemplation throughout the lab.

## A. Non-inverting amp

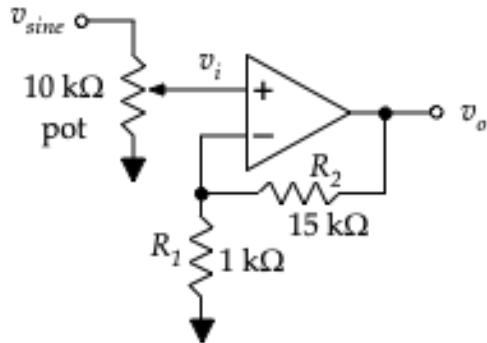

(Don't forget units in all the right places!)

Using 324 Amp

$$G = 1 + R_2/R_1 = 1 + 15/1 = 16$$

Expected gain :  $G = \underline{\hspace{1cm}}16\underline{\hspace{1cm}}$

Measured  $v_i = \underline{\hspace{1cm}}1.44V_{\text{rms}}\underline{\hspace{1cm}}$

Measured  $v_o = \underline{\hspace{1cm}}12.78V\underline{\hspace{1cm}}$

Measure gain :  $G = \underline{\hspace{1cm}}14\underline{\hspace{1cm}}$

Figure 1: Insert an image of the oscilloscope trace of undistorted  $v_o$  and  $v_i$  together.


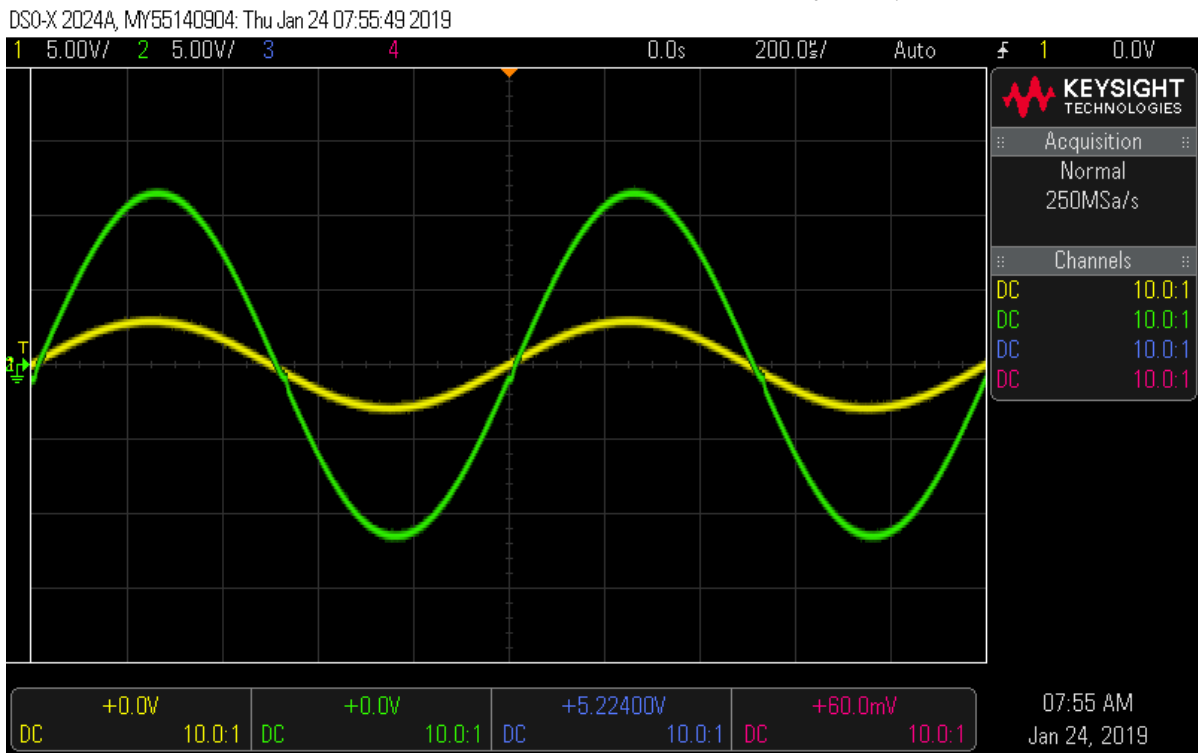


Figure 2: Insert an image of the oscilloscope trace of *clipped*  $v_o$  and  $v_i$  together.

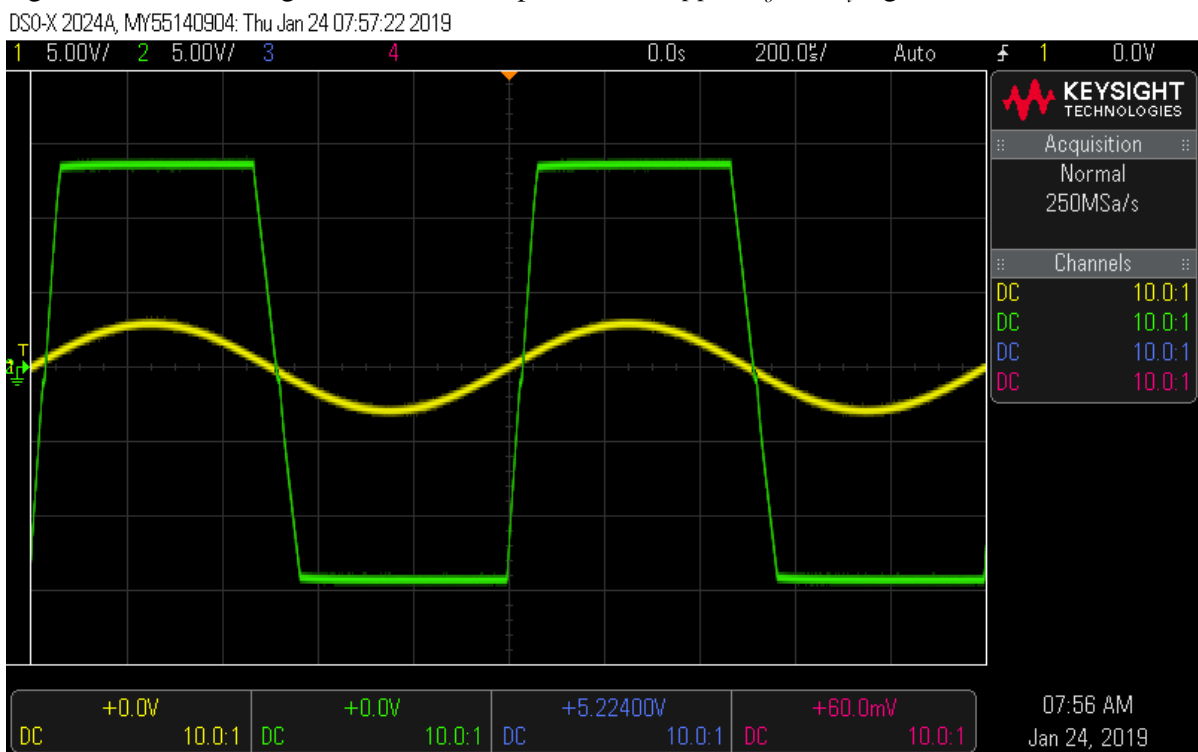

Maximum output without clipping:  $v_o(\max) = \underline{\hspace{2cm}} 13\text{V} \underline{\hspace{2cm}}$

## B. Transfer characteristic

Figure 3: Insert an oscilloscope image of the transfer characteristic when the output *is not* clipped.

/++


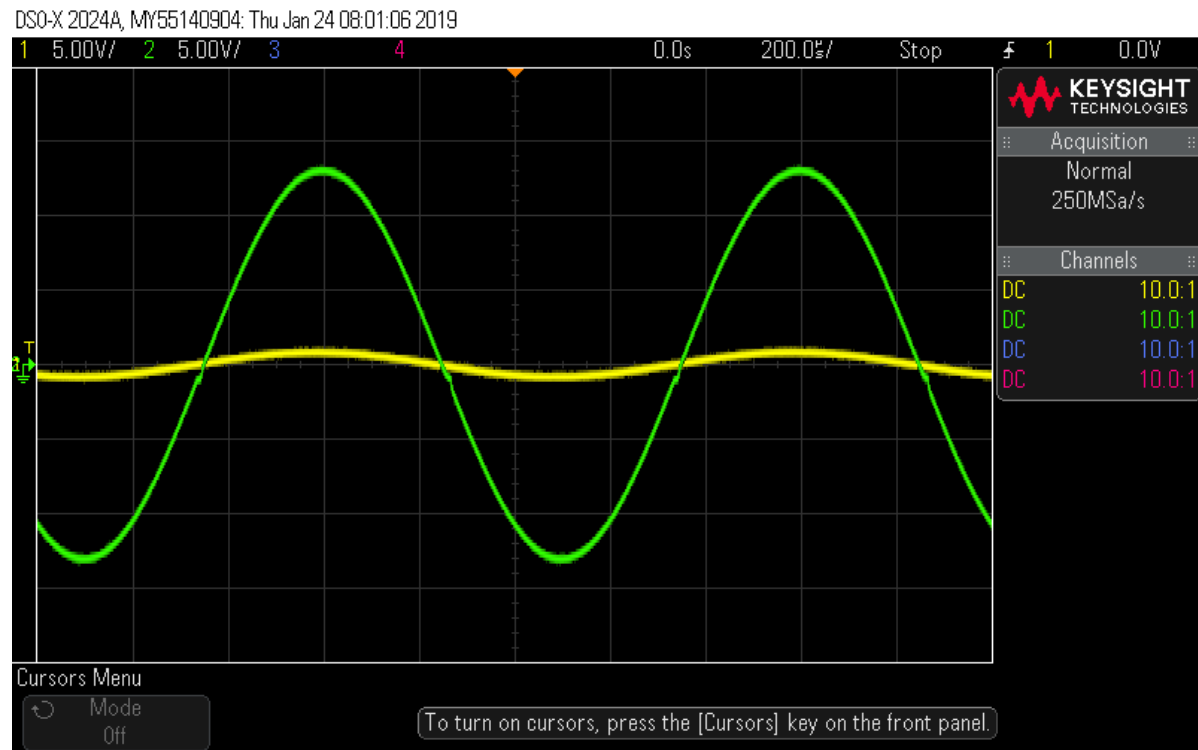


Figure 4: Insert an image of transfer characteristic when the output *is* clipped.

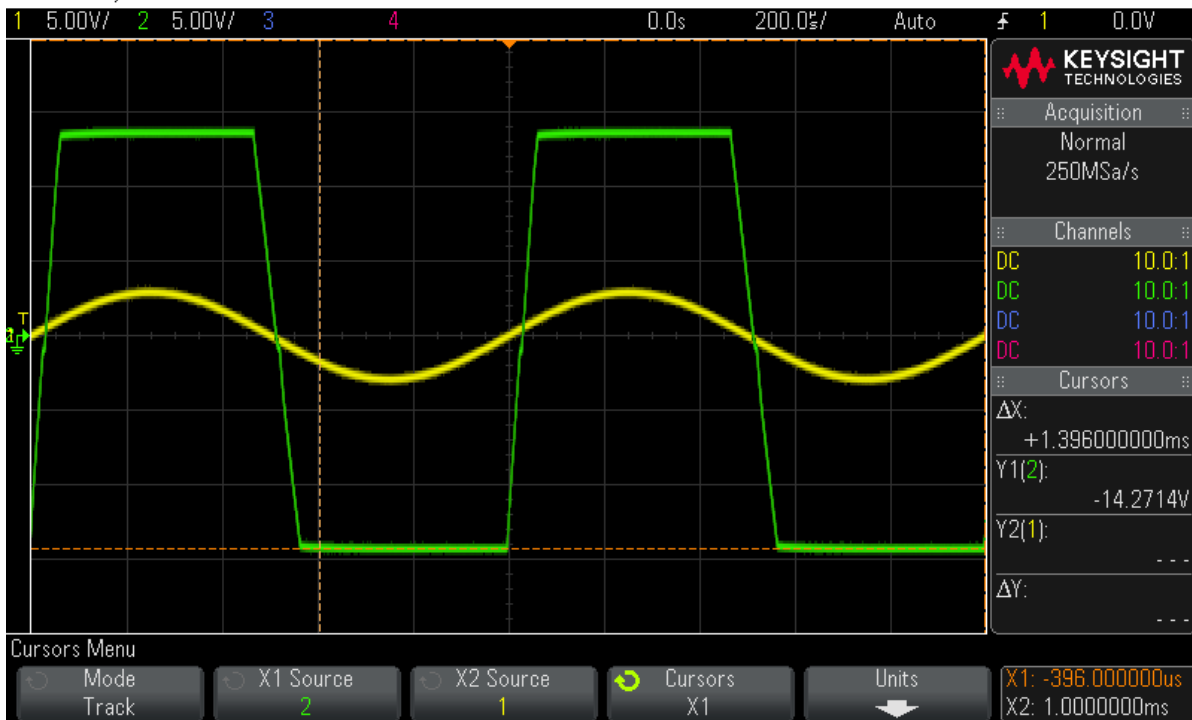DSO-X 2024A, MY55140904: Thu Jan 24 08:03:59 2019




### C. Unity-gain buffer

<i>pot. position</i>	<i>a-calculated</i>	<i>a-measured</i>	<i>b - calculated</i>	<i>b - measured</i>	<i>c - measured</i>
25%	11.25v	9.5	4.32	7.7	12.3
50%	7.5	5.27	2.57	4.06	7.55
75%	3.75	3.6	1.67	3.25	2.55

Write a paragraph explaining how the buffer amplifier works and how that leads to the results seen here.

The buffer amplifier uses negative feedback to provide an electrical impedance transformation. This buffers the output from anything the load may produce, driving the load as an ideal voltage source.

## D. Inverting amplifier

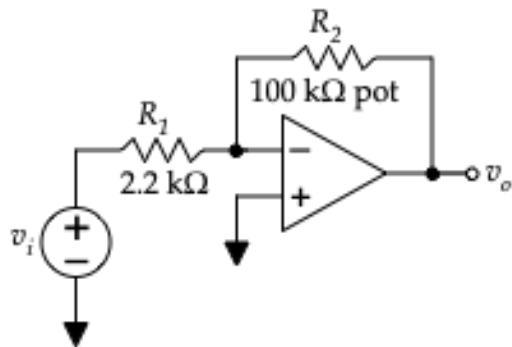

$$G = -R_2/R_1 = -50k/2.2k = -45.45$$


Using 324 Amp

Expected gain :  $G =$  \_\_\_\_\_ -22.72 \_\_\_\_\_

Measured  $v_i =$  \_\_\_\_\_ -13.67v \_\_\_\_\_

Measured  $v_o =$  \_\_\_\_\_ 4.5v \_\_\_\_\_

Measure gain :  $|G| =$  \_\_\_\_\_ -3 \_\_\_\_\_

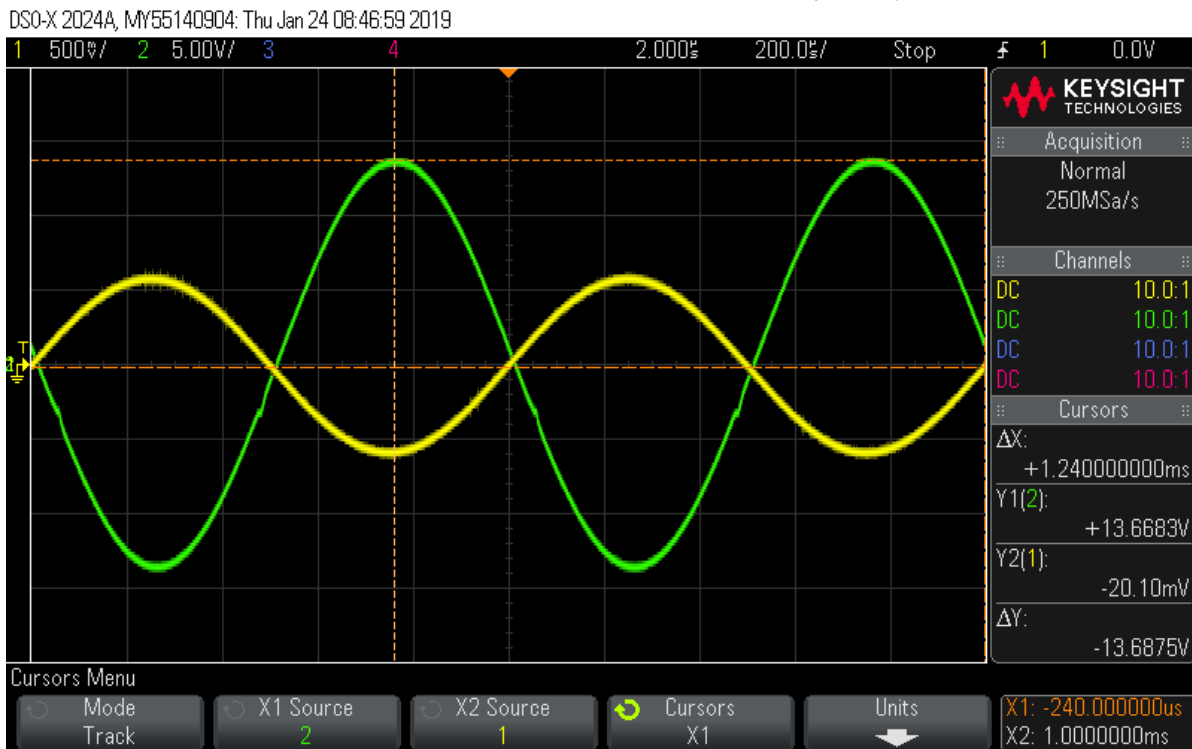Figure 5: Insert an image of the oscilloscope trace of undistorted  $v_o$  and  $v_i$  together.Figure 6: Insert an image of the oscilloscope trace of *clipped*  $v_o$  and  $v_i$  together.

Maximum output without clipping:  $v_o(\max) =$  \_\_\_\_\_ 13.6v \_\_\_\_\_

Figure 7: Insert an oscilloscope image of the inverting transfer characteristic when the output *is not* clipped.



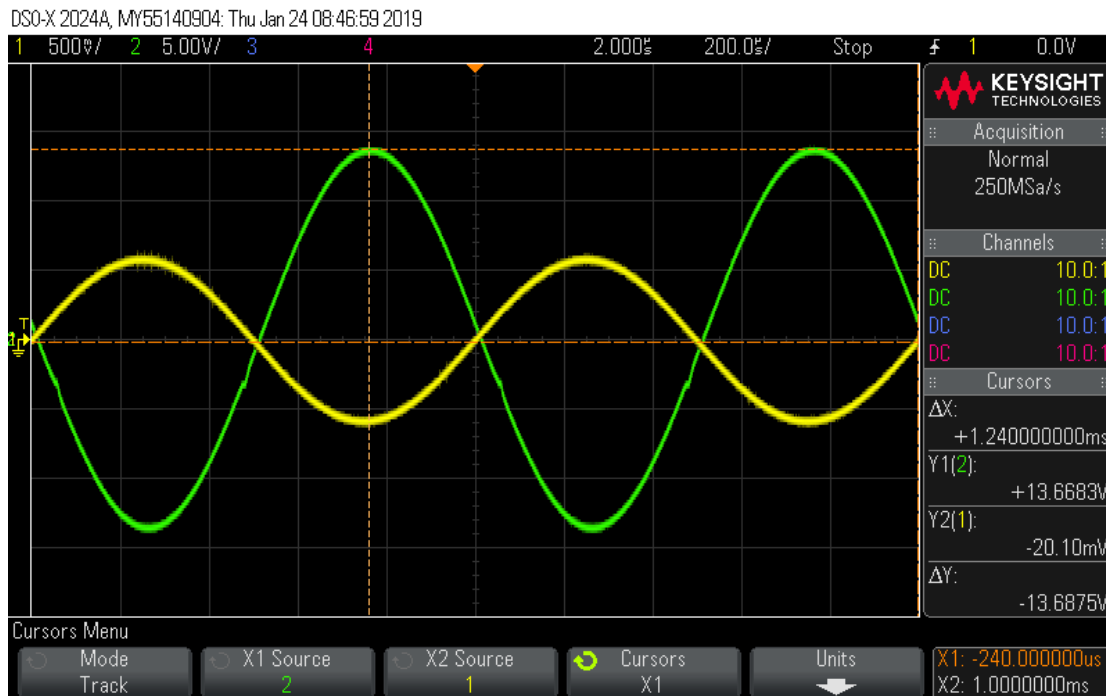


Figure 8: Insert an image of inverting transfer characteristic when the output *is* clipped.

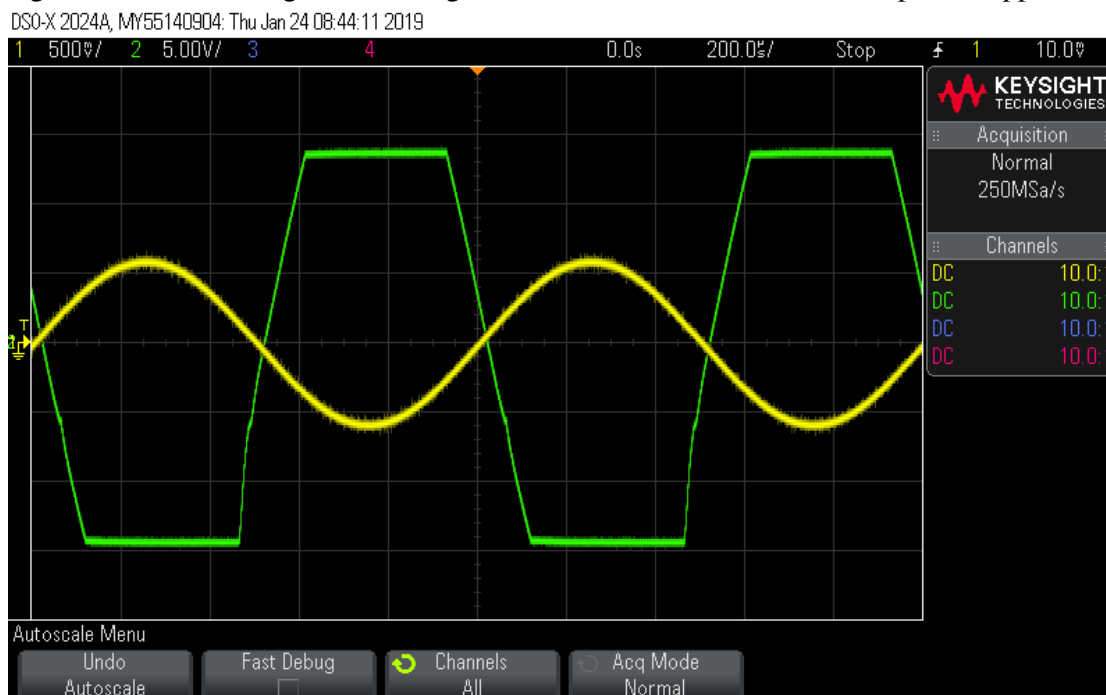

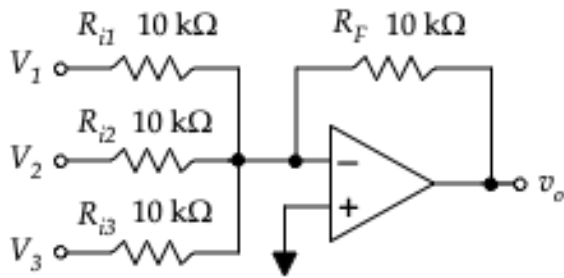

## E. Summing amplifier




Expected out function :  $v_o = \text{f}(V_1, V_2, V_3) = V_1 + V_2 + V_3$

$$V_o = -R_f/R_1 * V_1 - R_f/R_2 * V_2 - \dots \Rightarrow -V_1 - V_2 - V_3$$


$V_1$	$V_2$	$V_3$	$v_o(\text{calculated})$	$v_o(\text{measured})$
1 V	1 V	1 V	-3v	-3v
2 V	1 V	1 V	-4V	-4
2 V	-2 V	4 V	-4V	-4
4 V	-3 V	5 V	-6V	-6

Figure 9: Insert an oscilloscope image of the  $v_o$  when the one of the inputs is a sinusoid and the other two inputs are some combination of DC values. (Be sure to list the voltages used.)

All voltages 1v

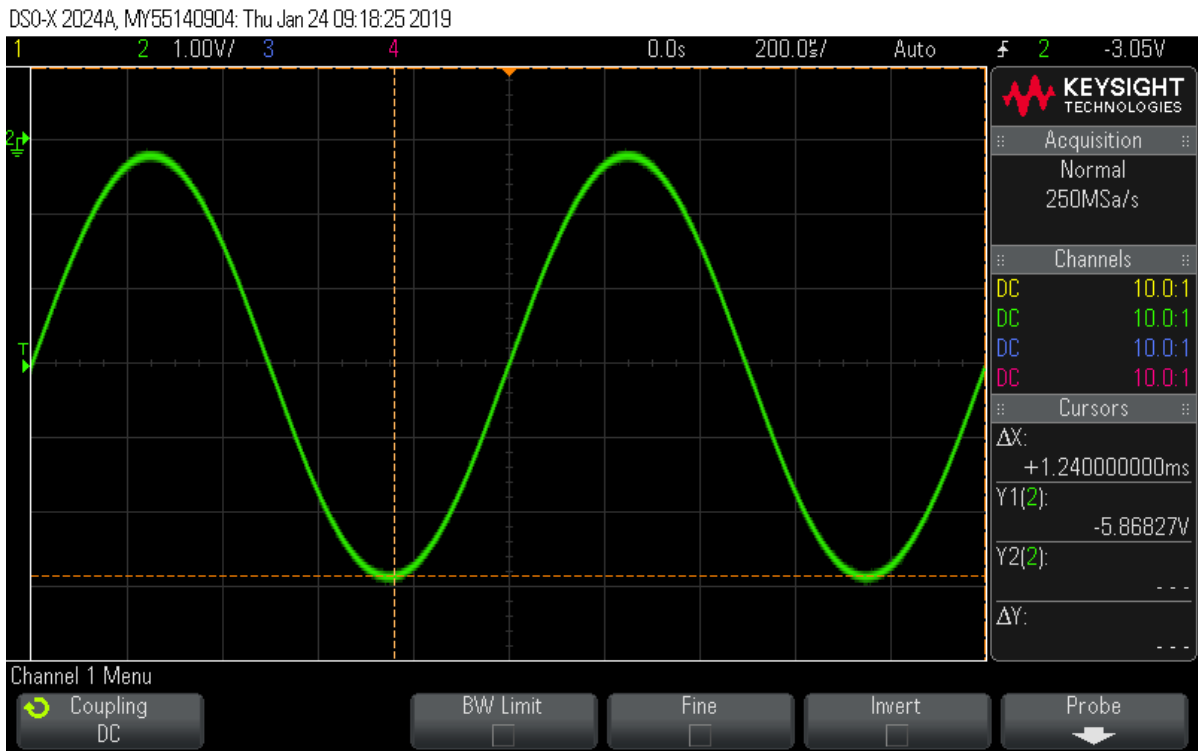

## F. Integrating amplifier

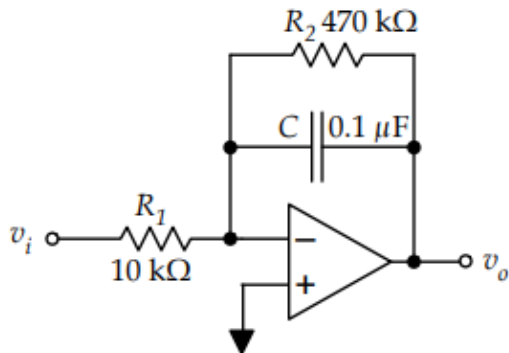

Sketch the expected output voltage when the input is a 5-V square-wave on the graph below.

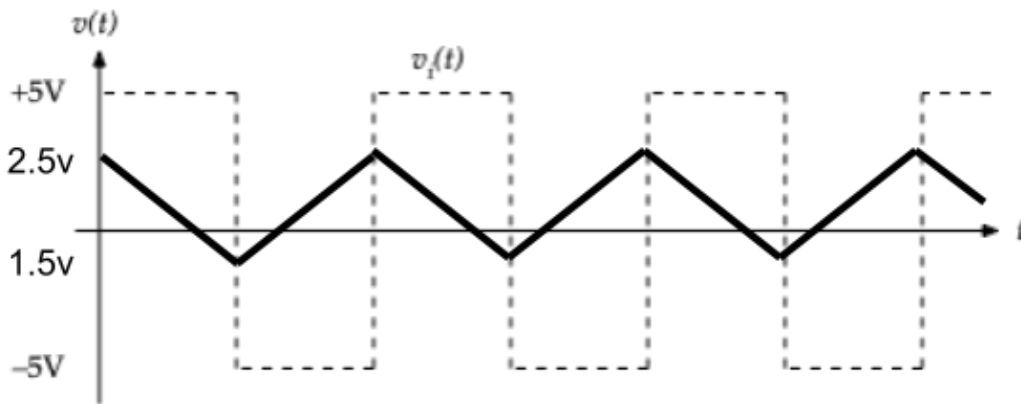


Figure 10. Oscilloscope trace of measured square-wave input and integrator output together.

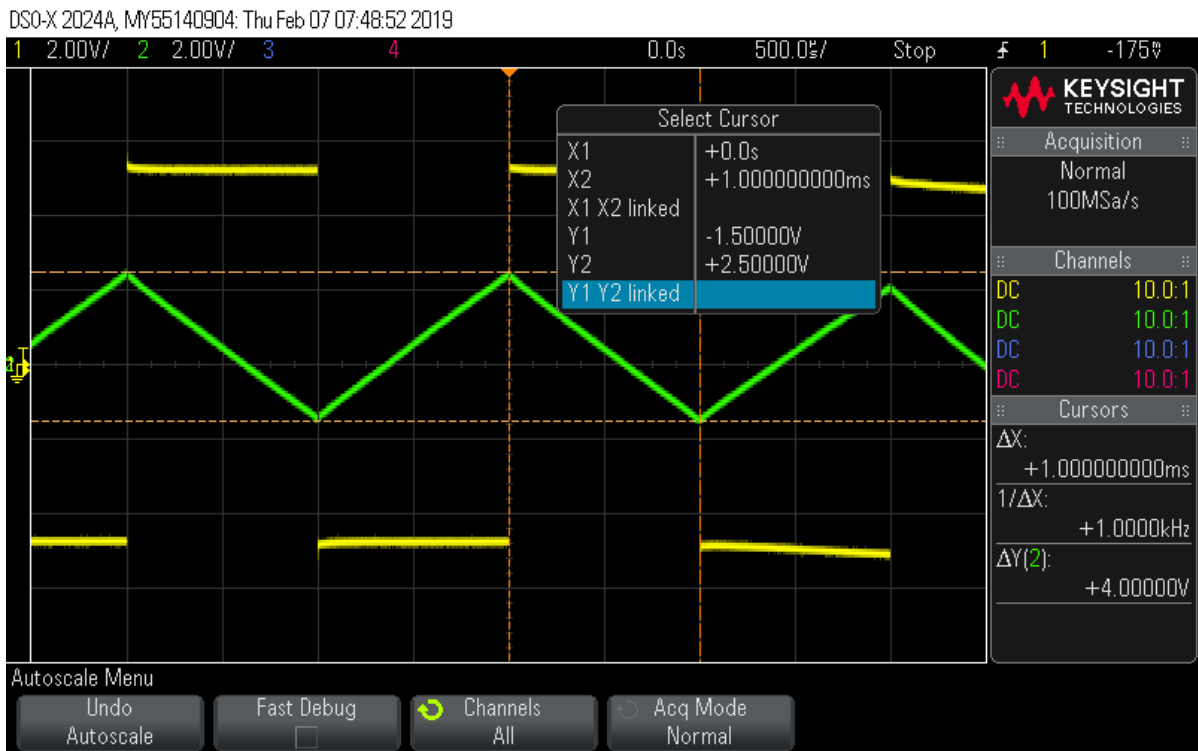


Figure 11. Oscilloscope trace of measured ramp-wave input and integrator output together.



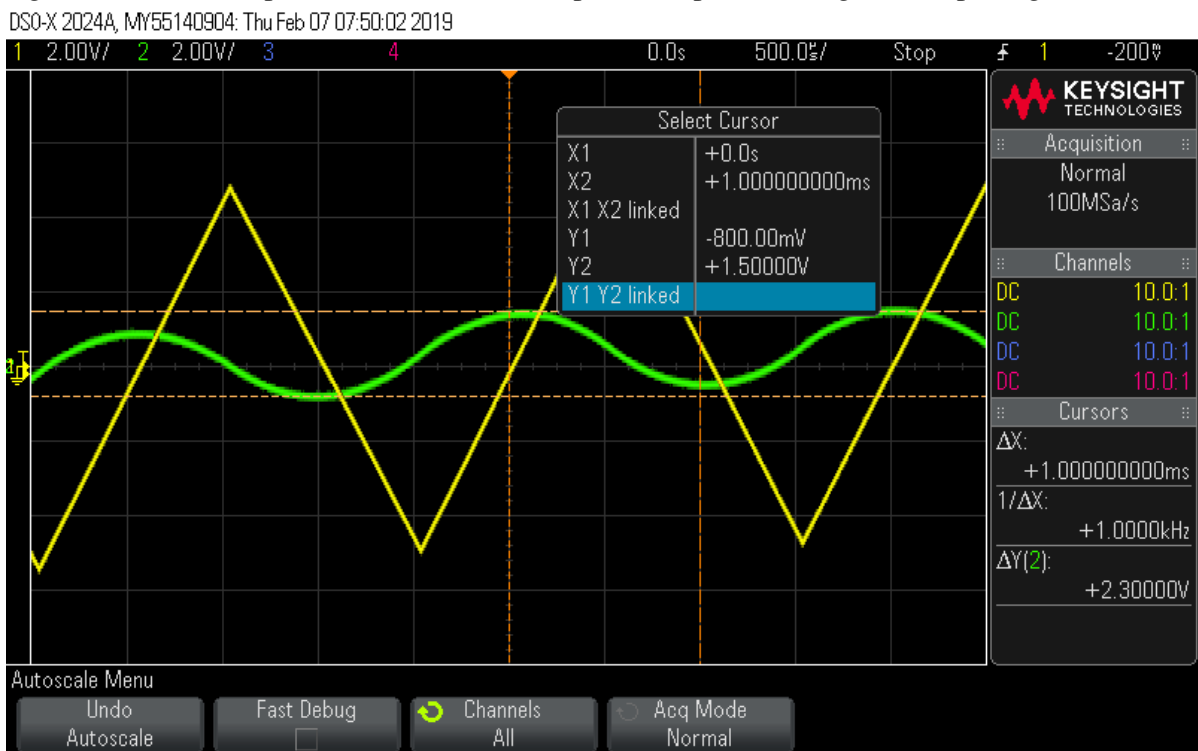


Figure 12. Oscilloscope trace of measured sinusoidal input and integrator output together.

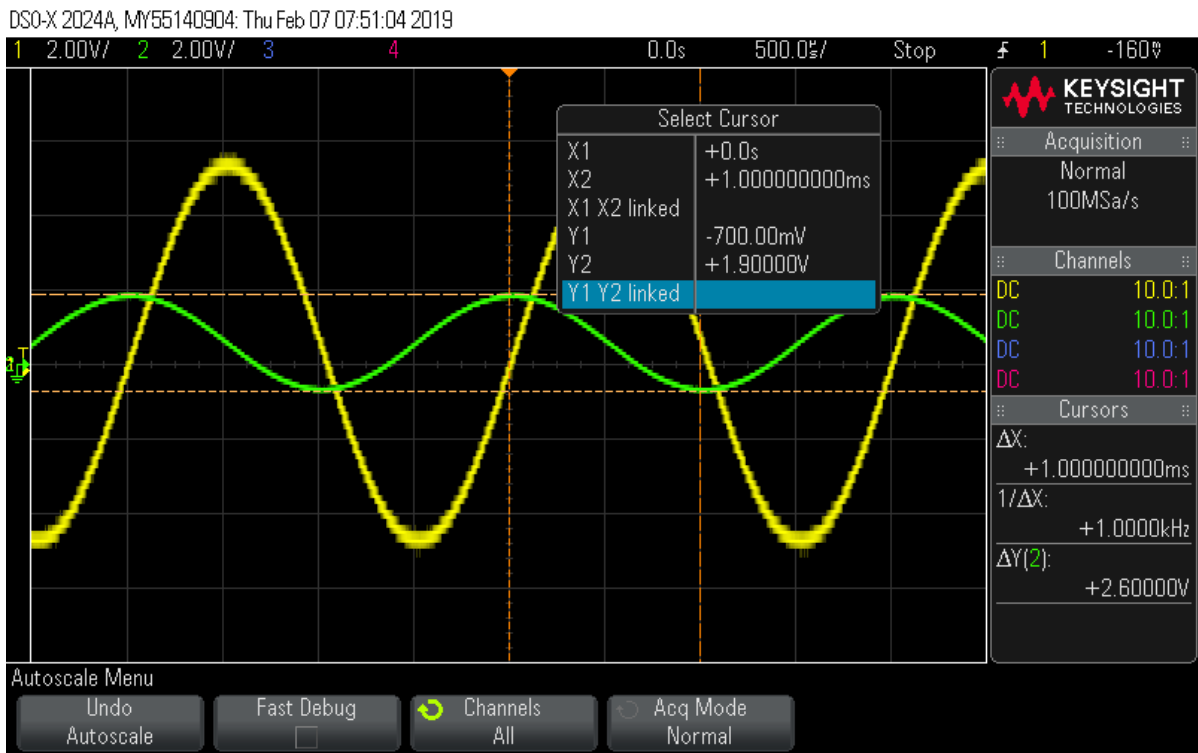

## G. Difference amplifier

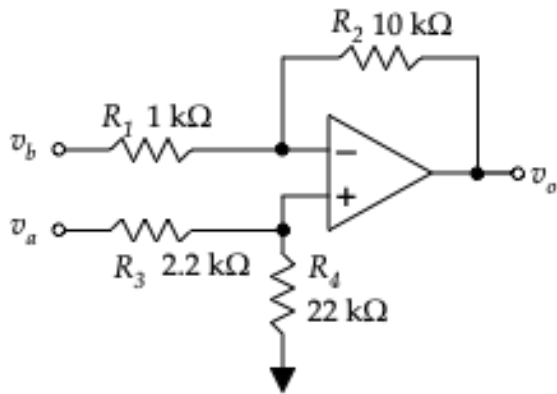

Expected out function :  $v_o =$  \_\_\_\_\_

With  $v_b$  grounded:

$v_a =$  \_\_\_\_\_ .35v \_\_\_\_\_,  $v_o =$  \_\_\_\_\_ 3.58v \_\_\_\_\_,  $G_a =$  \_\_\_\_\_ 10.2 \_\_\_\_\_



With  $v_a$  grounded:

$v_b =$  \_\_\_\_\_ .35v \_\_\_\_\_,  $v_o =$  \_\_\_\_\_ 3.45v \_\_\_\_\_,  $G_b =$  \_\_\_\_\_ 9.86 \_\_\_\_\_

With  $v_a = v_b = v_c$  (common-mode operation)

$v_c =$  \_\_\_\_\_ 7.07v \_\_\_\_\_,  $v_o =$  \_\_\_\_\_ 6.5v \_\_\_\_\_,  $G_c =$  \_\_\_\_\_ .919 \_\_\_\_\_

CMRR = \_\_\_\_\_ -20.9 \_\_\_\_\_

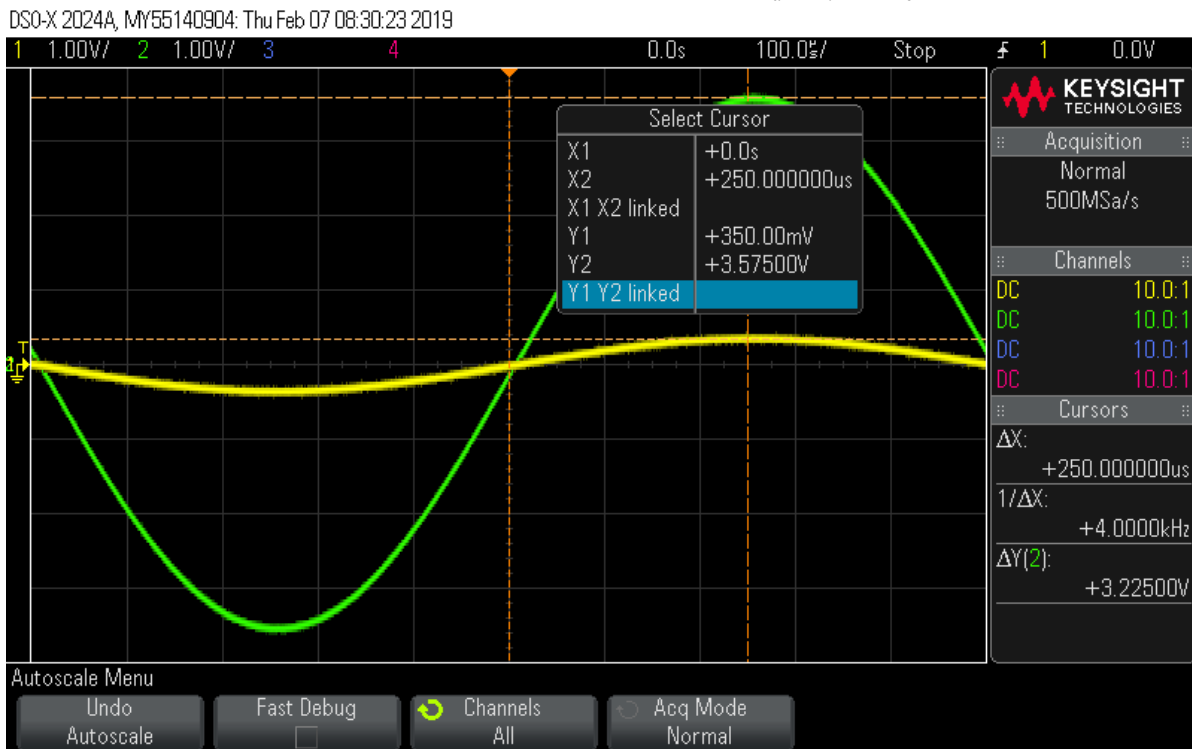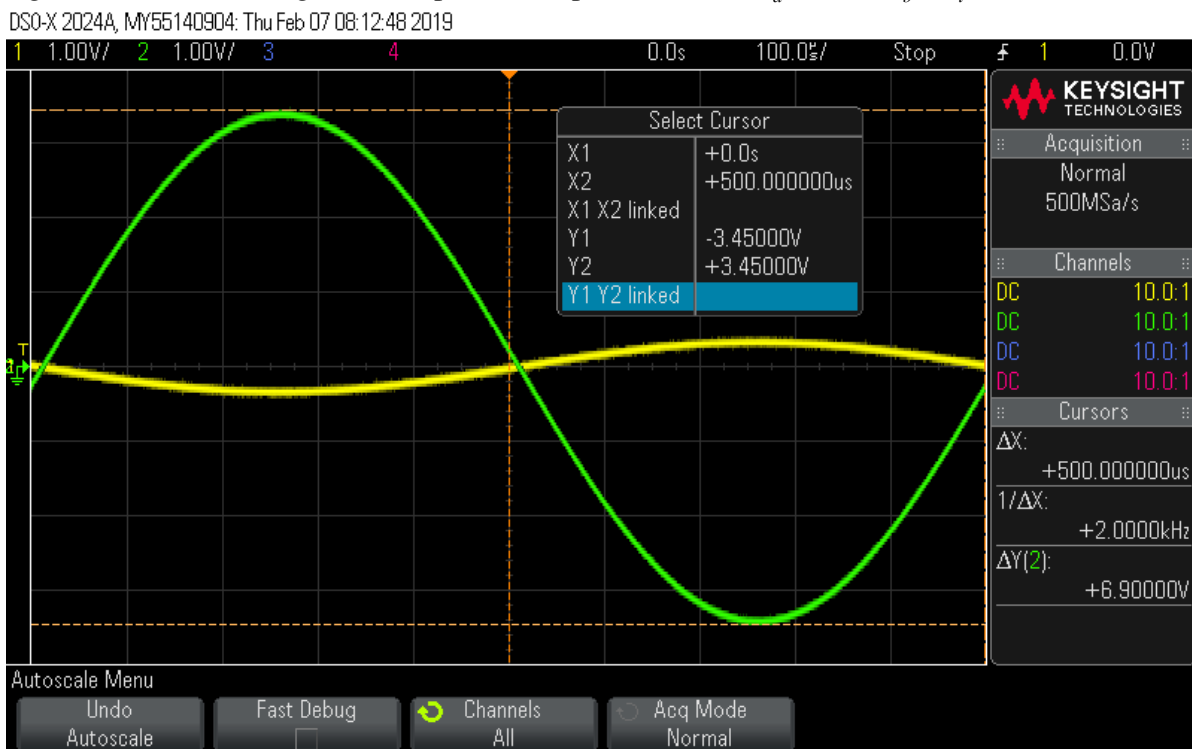Figure 13: Insert an image of the input and output traces with  $v_a = v_i$  and  $v_b = 0$ . (Green is input here)Figure 14: Insert an image of the input and output traces with  $v_a = 0$  and  $v_b = v_i$ .

## EE 230 Lab

## lab 1 report

*Add a short paragraph regarding CMRR.*

CMRR is the ratio of differential voltage gain to common mode voltage gain. CMRR is calculated in decibels, using the equation  $db = 20\log(CMRR)$ . Common means both inputs are equal.



## H. Instrumentation amplifier

Expected difference-mode gain :  $G =$  \_\_\_\_\_

Measured difference-mode gain :


$v_i =$  \_\_\_\_\_ .35v \_\_\_\_\_,  $v_o =$  \_\_\_\_\_ 3.6v \_\_\_\_\_,  $G =$  \_\_\_\_\_ 10.29 \_\_\_\_\_

With  $v_1 = v_2 = v_c$  (common-mode operation)

$v_c =$  \_\_\_\_\_ .35v \_\_\_\_\_,  $v_o =$  \_\_\_\_\_ 7.125v \_\_\_\_\_,  $G_c =$  \_\_\_\_\_ 20.36 \_\_\_\_\_

CMRR = \_\_\_\_\_ 26.17 \_\_\_\_\_

Figure 15: Insert an image of the input and output traces with  $v_i = v_i$  and  $v_b = 0$ .

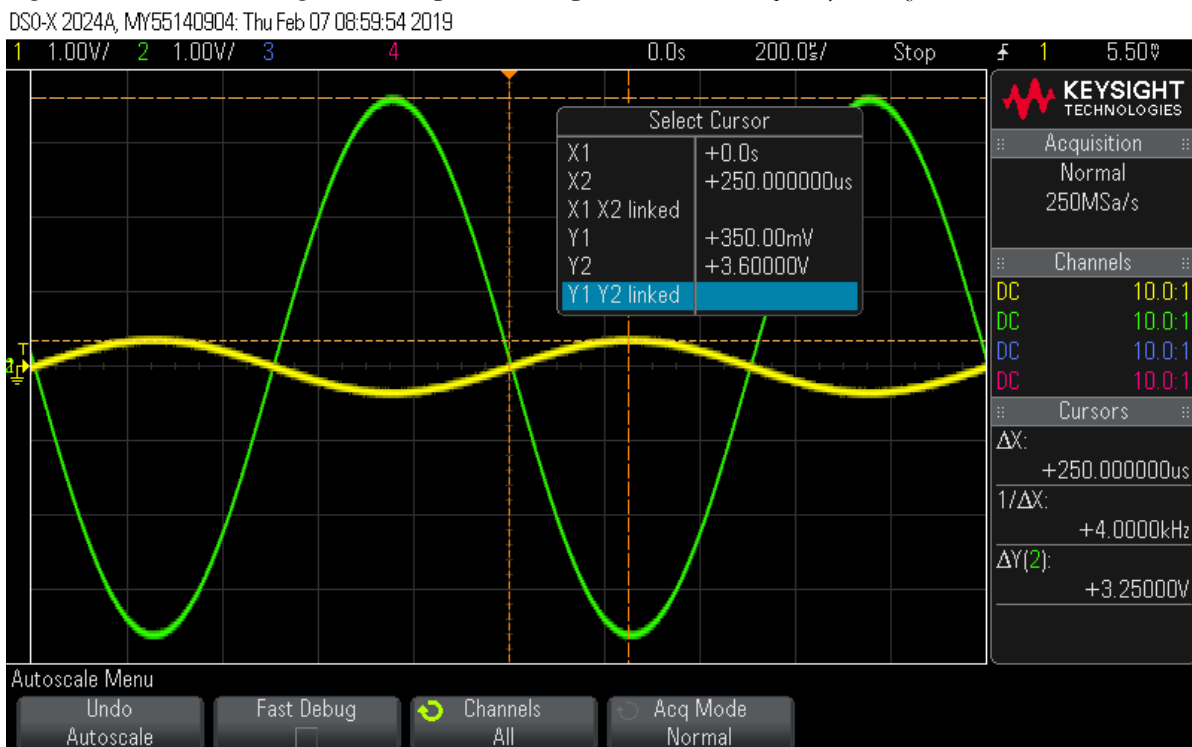

## **EE 230 Lab**

### **lab 1 report**

#### **Conclusion**

The lab went smoothly, with each section taking around the same time to complete. There were some measurement issues in part C that I was unsure of, but the rest of the lab seems relatively consistent to calculations.