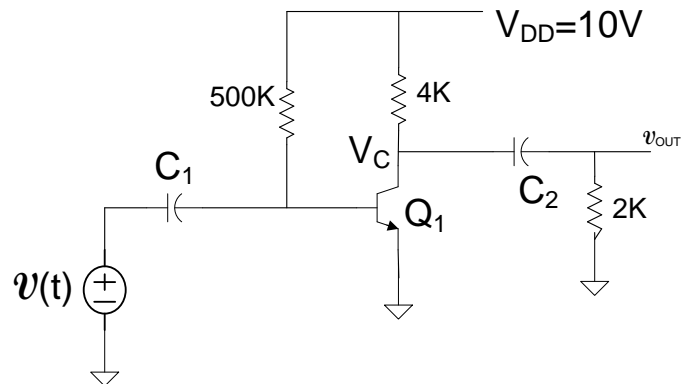



EE 330  
Homework 8  
Fall 2018  
Due Friday October 12

Solve Problem 12 and any 8 of the remaining problems. Each problem is worth 10 points except Problem 12 which is worth 20 points. Unless stated to the contrary, assume all MOS transistors have model parameters  $\mu_n C_{OX}=300\mu A/V^2$ ,  $V_{Tn}=0.5V$ ,  $\mu_n/\mu_p=4$ ,  $V_{Tp}=-0.5V$ ,  $C_{OX}=4fF/\mu^2$ ,  $\lambda = 0$ ,  $\gamma = 0$ , and all BJT transistors have model parameters  $J_S A= 10^{-12}A$ ,  $\beta_n=100$ , and  $\beta_p=30$ .

**Problem 1** Assume the capacitors are very large. Determine the quiescent value of  $V_C$  and  $V_{OUT}$




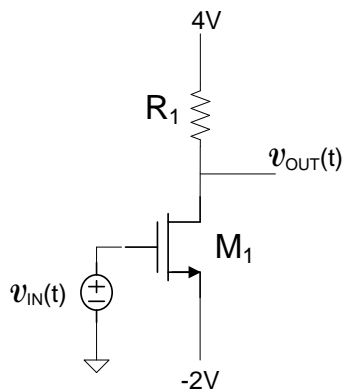**Problem 2** Determine the maximum value of  $R_1$  that will keep  $M_1$  in saturation.  $M_1$  has dimensions  $W=12\mu$  and  $L=2\mu$ .




**Problem 3** Determine the small-signal voltage gain of the circuit in the previous problem if the value of  $R_1$  is  $\frac{1}{2}$  the value needed to keep  $M_1$  in saturation

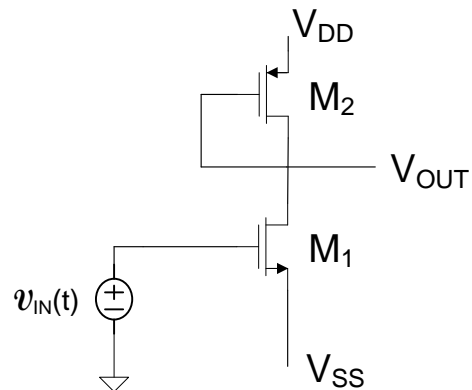
**Problem 4** Consider the following circuit. Determine the quiescent output voltage if  $V_{DD}=1V$ ,  $V_{SS}=-1V$ ,  $W_1=10u$ ,  $L_1=2u$ ,  $W_2=50u$  and  $L_2=1u$ . Assume the magnitude of the input is arbitrarily small.



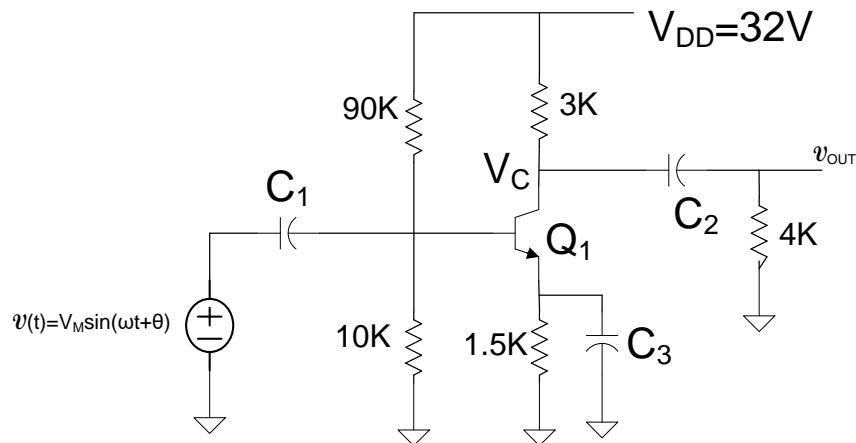**Problem 5** Assume the capacitors are all very large. Determine the quiescent value of  $V_C$  and  $V_{OUT}$




**Problem 6** Obtain the quiescent output voltage

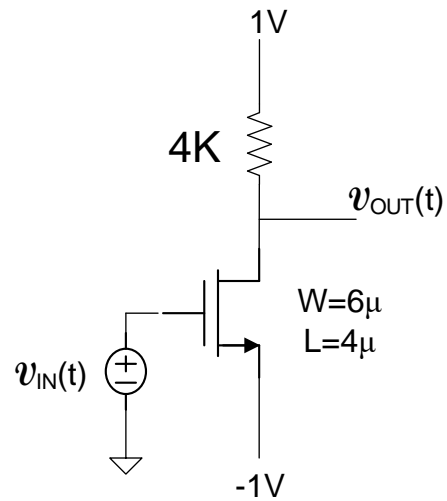


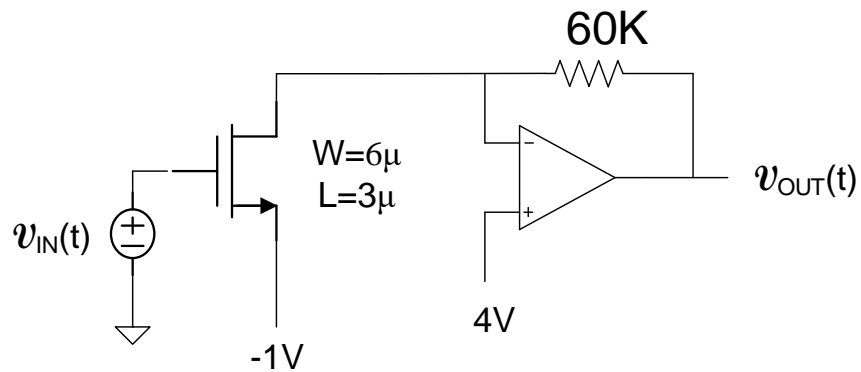**Problem 7**

- Determine the quiescent output voltage
- If the input is a  $1KHz$  square wave with high and low values of  $0V$  and  $25mV$ , determine the output voltage





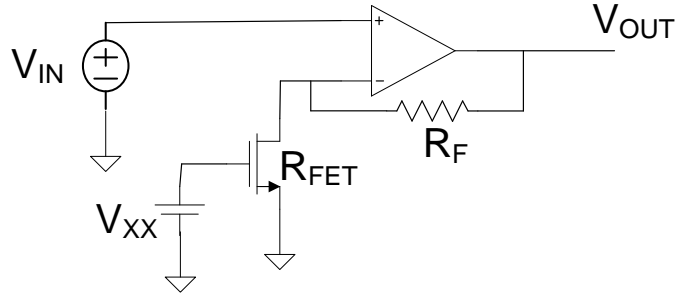**Problem 8** Assume  $V_{IN}$  is a low frequency sinusoidal waveform given by the expression  $V_{IN}=0.025\sin 1000t$  and assume that  $W=4\mu\text{m}$ ,  $L=1\mu\text{m}$  for the MOSFET. The output voltage of this circuit should be a sinusoidal waveform of the same frequency as the input. Define the voltage gain to be the ratio of the p-p value of the output sinusoidal signal to the p-p value of the sinusoidal input signal. With this definition of gain, determine the voltage gain of this circuit if  $V_{XX}=1\text{V}$ .



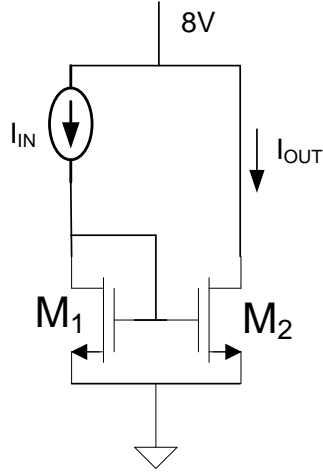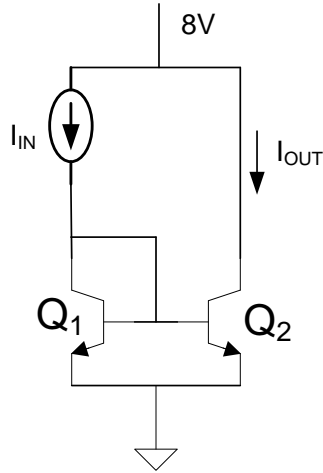
**Problem 9** Consider the two circuits shown.

- Determine the output current for the bipolar circuit if  $A_{E1}=300\mu^2$  and  $A_{E2}=1200\mu^2$  and  $I_{IN}=1\text{mA}$ . Assume  $\beta$  is very large.
- Determine the output current for the MOS circuit if  $W_1/L_1=10$  and  $W_2/L_2=20$  and  $I_{IN}=1\text{mA}$ .



**Problem 10** Express the output current for the bipolar circuit in terms of the input current and the emitter areas for the circuit of Problem 9. Assume  $\beta$  is very large. Also express the output current for the MOS circuit in terms of the input current and the “W/L” ratios for the circuit of Problem 9. What conclusion can be drawn about the relative performance between these two circuits?

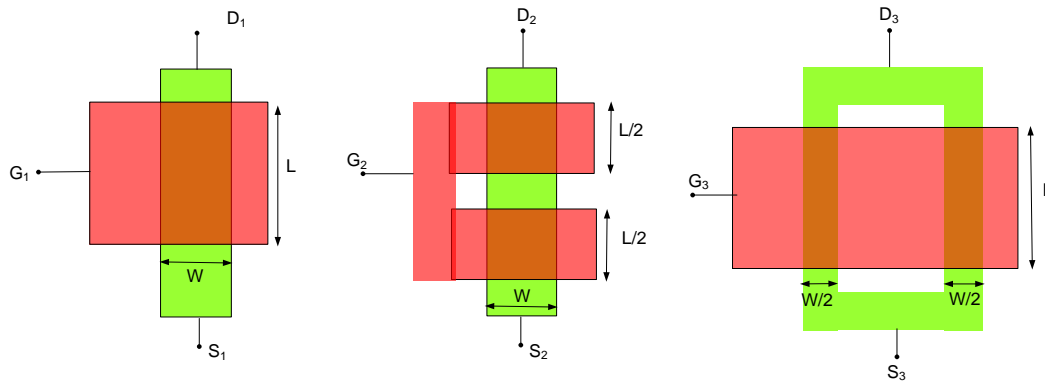**Problem 11** Three devices are shown. The color green is used to denote n-active and the red denotes polysilicon. Relative device dimensions are as indicated. Make a comparison of the performance of these structures.



**Problem 12** (Counts as 2 problems) Using the adders, gates, flip-flops, etc. from past homework assignments to create the following consisting of three registers, two holding the inputs A and B, and one holding the output S. When the select bit for the MUX is high send  $\text{ADD}(A, B)$  to the output, when the select bit is low send  $\text{AND}(A, B)$  to the output.

