

EE 230 Lab

Lab 4 report

Report: **Non-ideal effects in op-amps**

Lab work done by _____ Sean Gordon _____

and _____ Tejas Agarwal _____

Lab work date: 3-6-2019

Report submission date: 3-13-2019

Lab Section: E

Graded by _____


Score _____

Introduction

This lab focuses entirely on the limitations of operational amplifiers. The lab contains several scenarios designed to draw attention to specific limitations, going through each in turn.

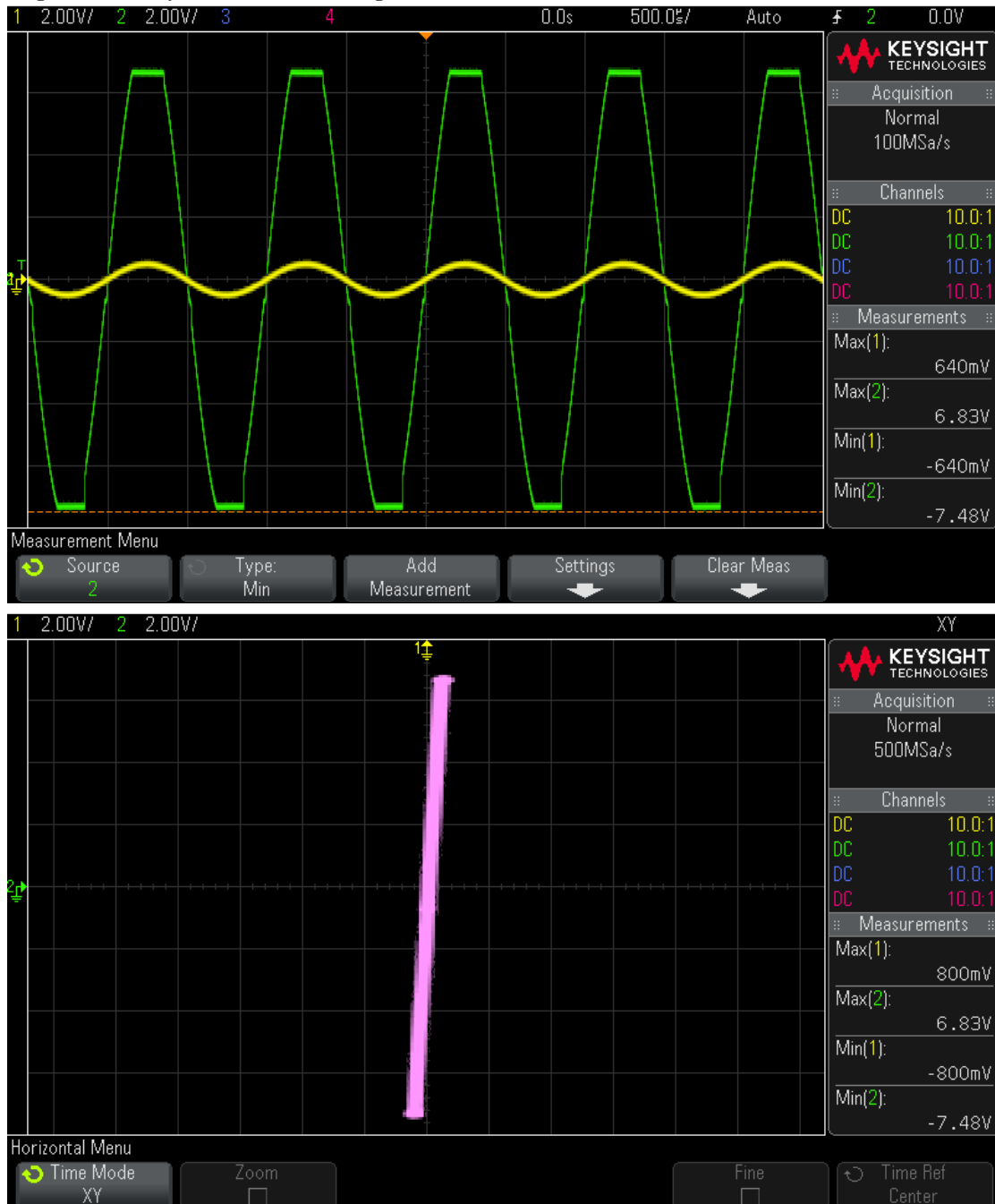A. Power supplies and output voltage limits**324 op amp**

Figures: Insert images of the oscilloscope trace of the clipped v_o from the 324 non-inverting amp and the x-y transfer function plot.




Measured positive output limit: V_{L+} 6.83v

Measured negative output limit: V_{L-} -7.48v

660 amp


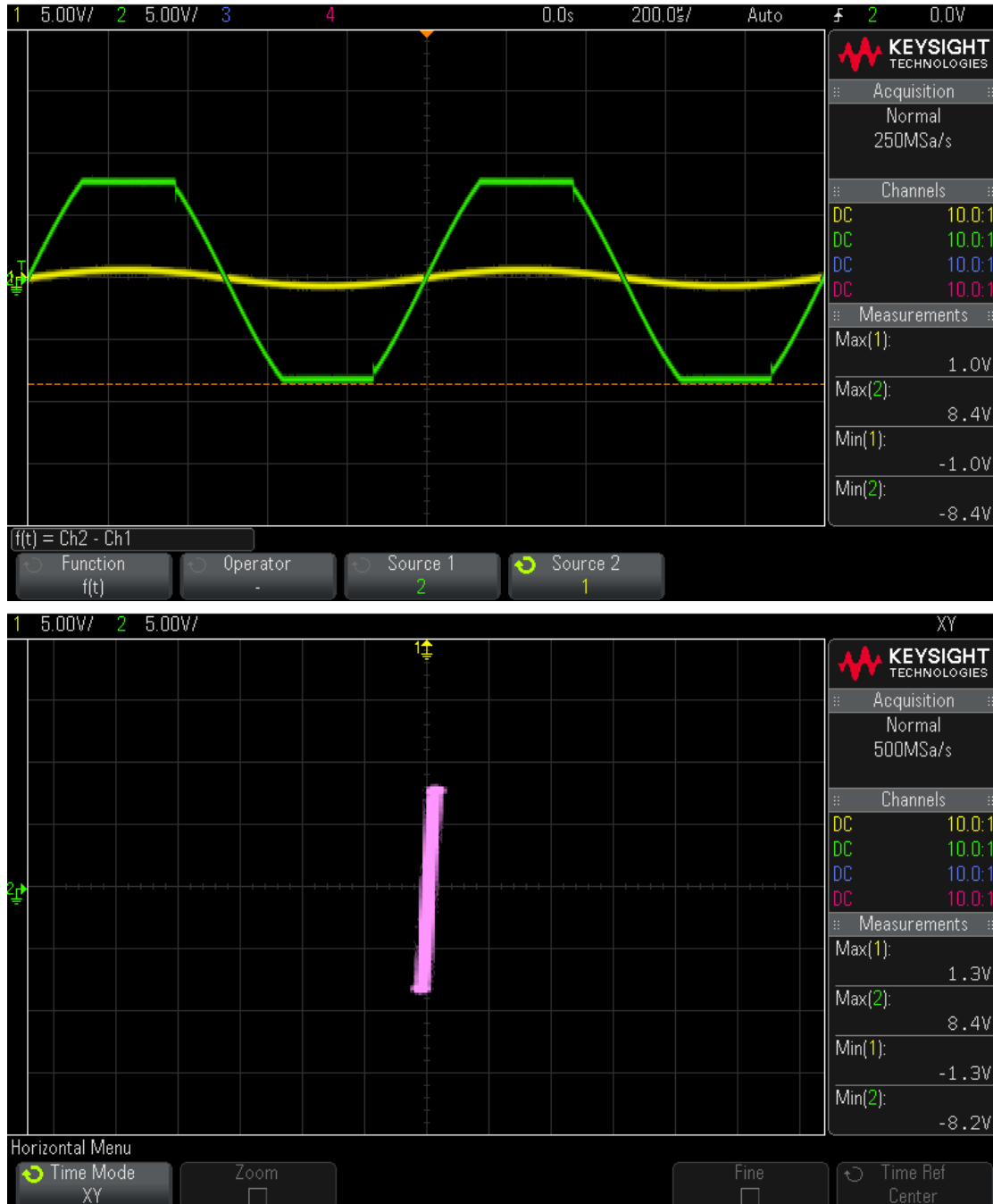
Figures: Insert images of the oscilloscope trace of the clipped v_o from the 660 non-inverting amp and the x-y transfer function plot.



Measured positive output limit: V_{L+} 8.4v

Measured negative output limit: V_{L-} -8.4v

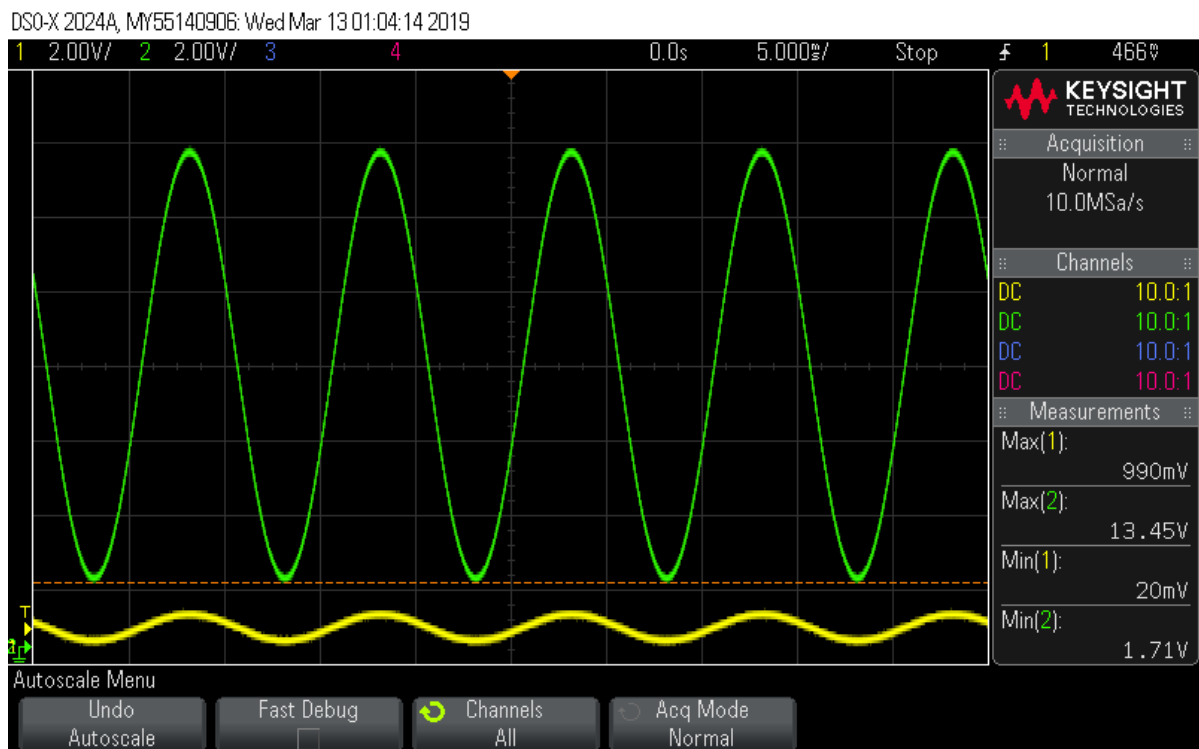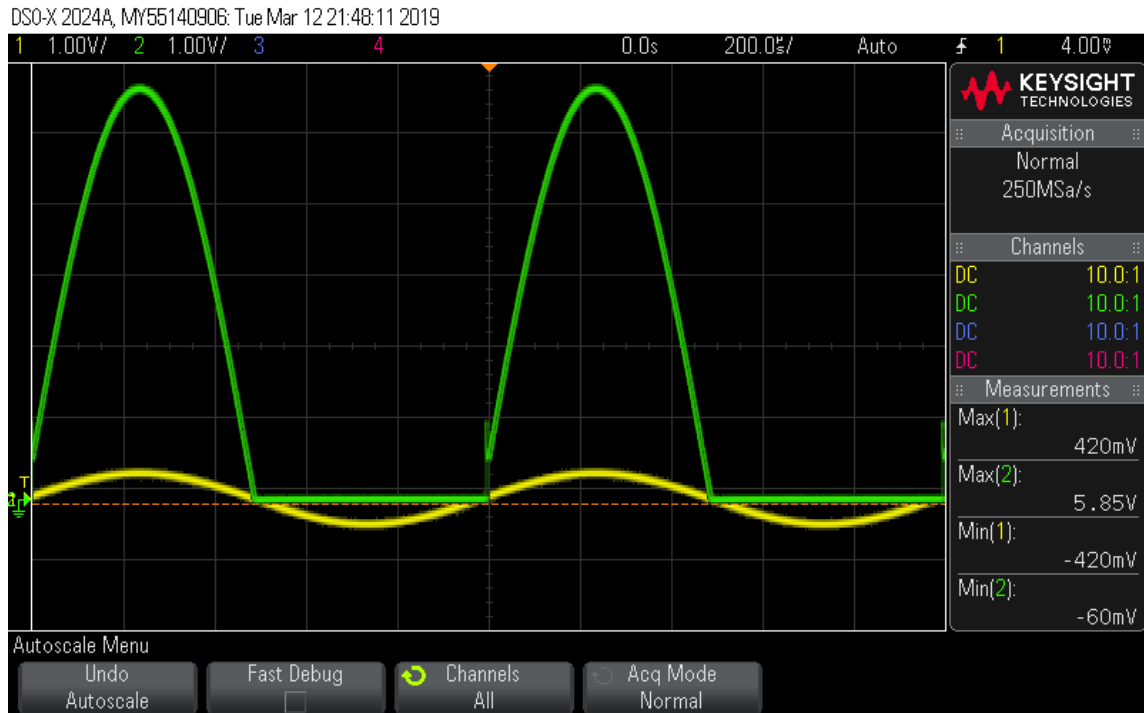
Figures: Insert an image of the oscilloscope trace of the clipped and unclipped v_o from the 660 amp using a single power supply.



B. Output current limits


324: Measured maximum output current: 48mA

Figure: Insert an image of the output voltage when the output current is at its limit.

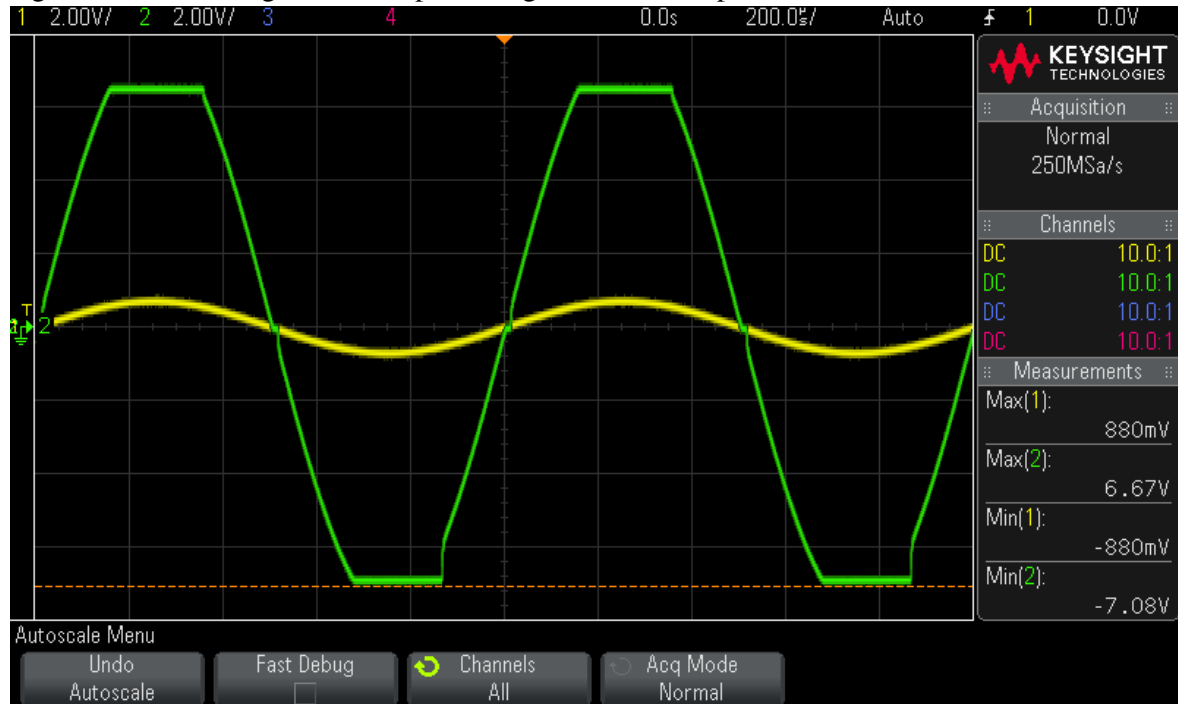

660: Measured maximum output current: 37mA

Figure: Insert an image of the output voltage when the output current is at its limit.

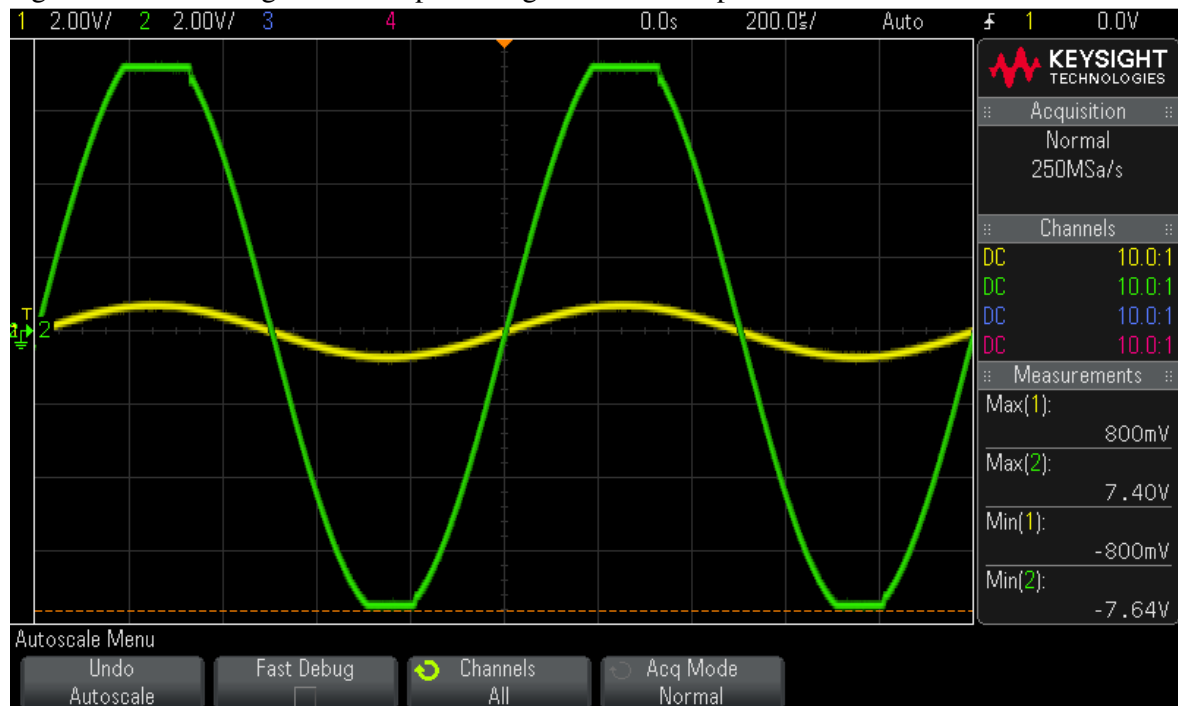


C. Gain-bandwidth limitations



660: Measured gain-bandwidth product: 2.055mHz



(List the three measured values and also the average of those.)

FreqA = 20.5kHz FreqB = 9.3kHz FreqC = 4.4kHz
 Freq_Avg = 11.4kHz

Figure: Insert the plot showing the three low-pass responses for the three different gains.

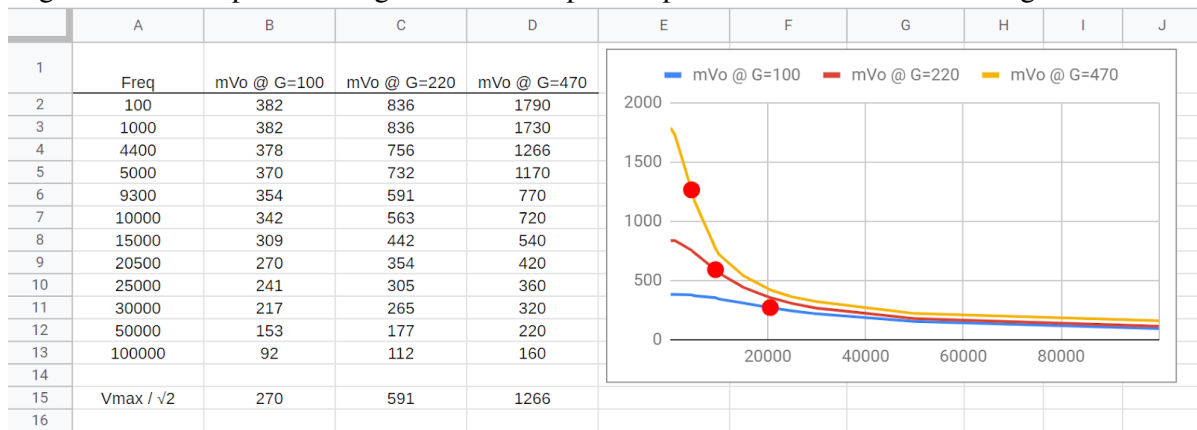


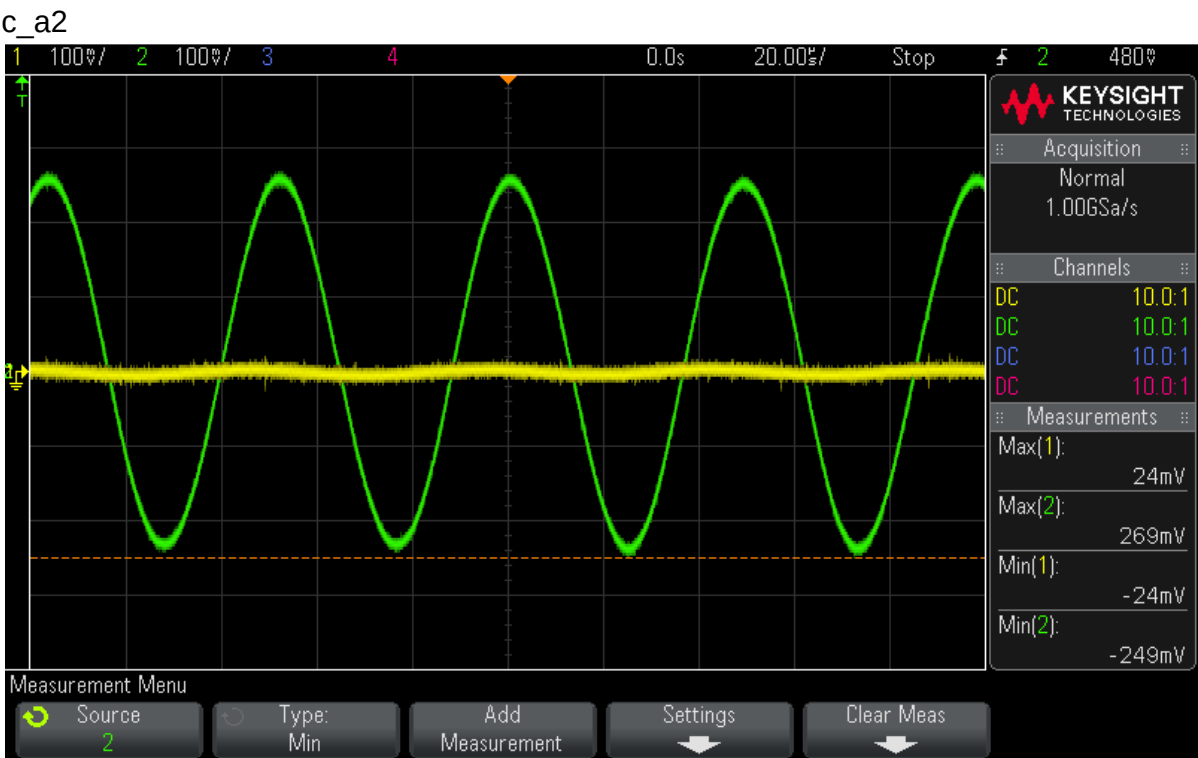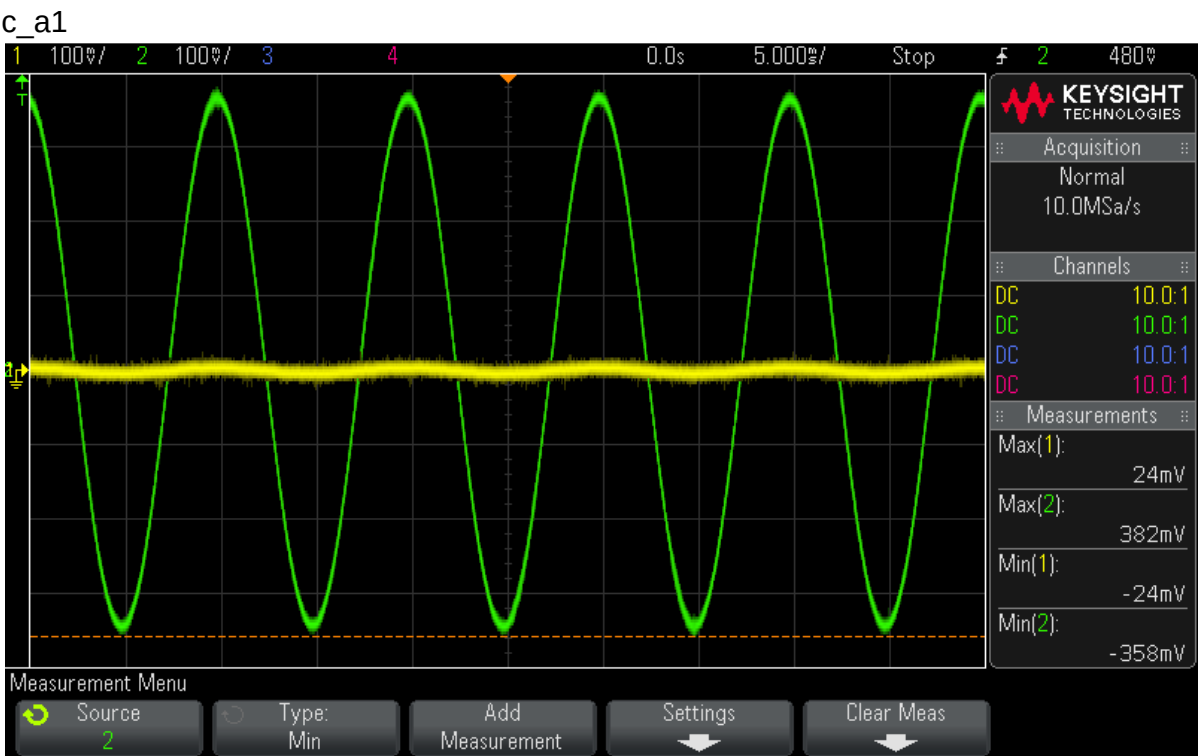

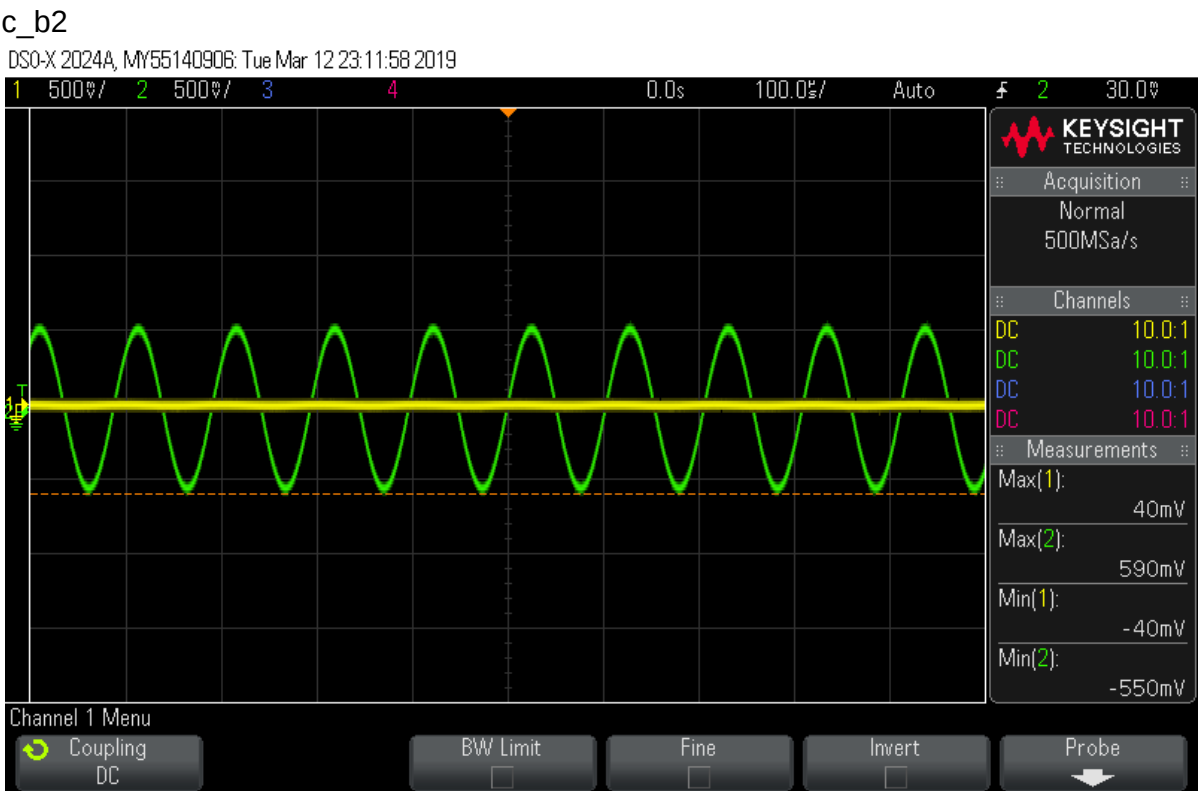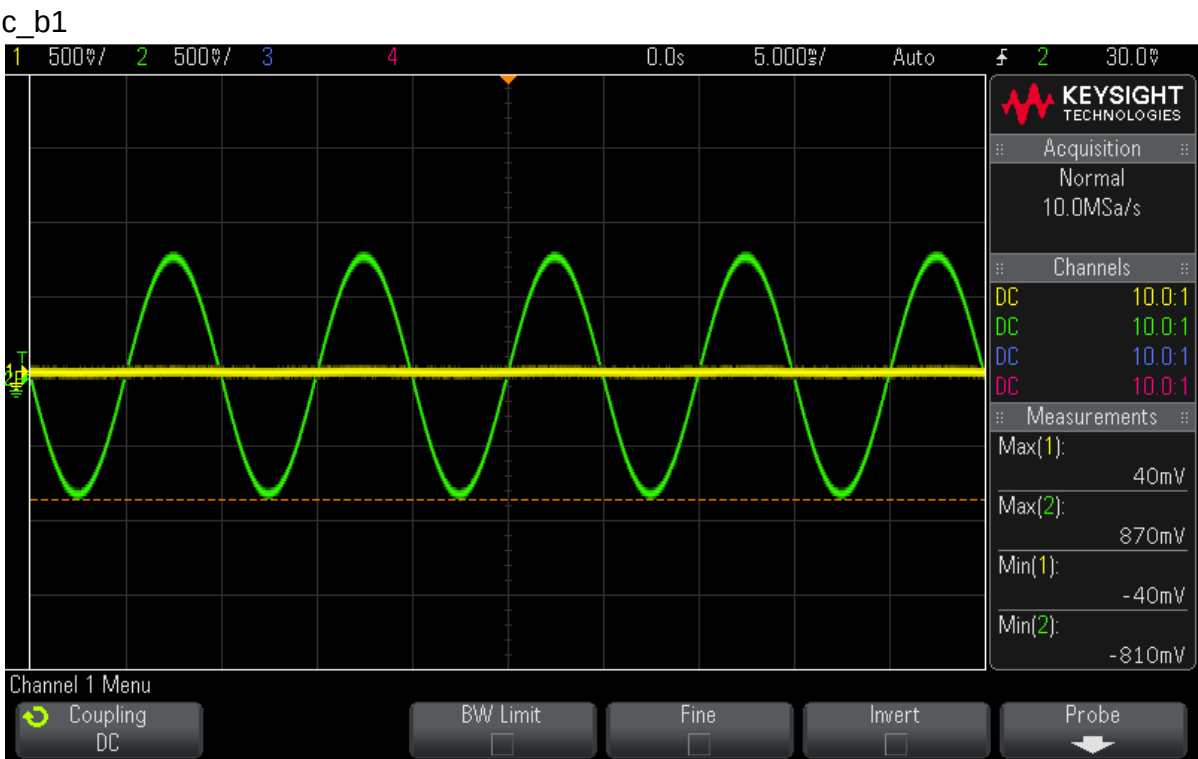


c_c1

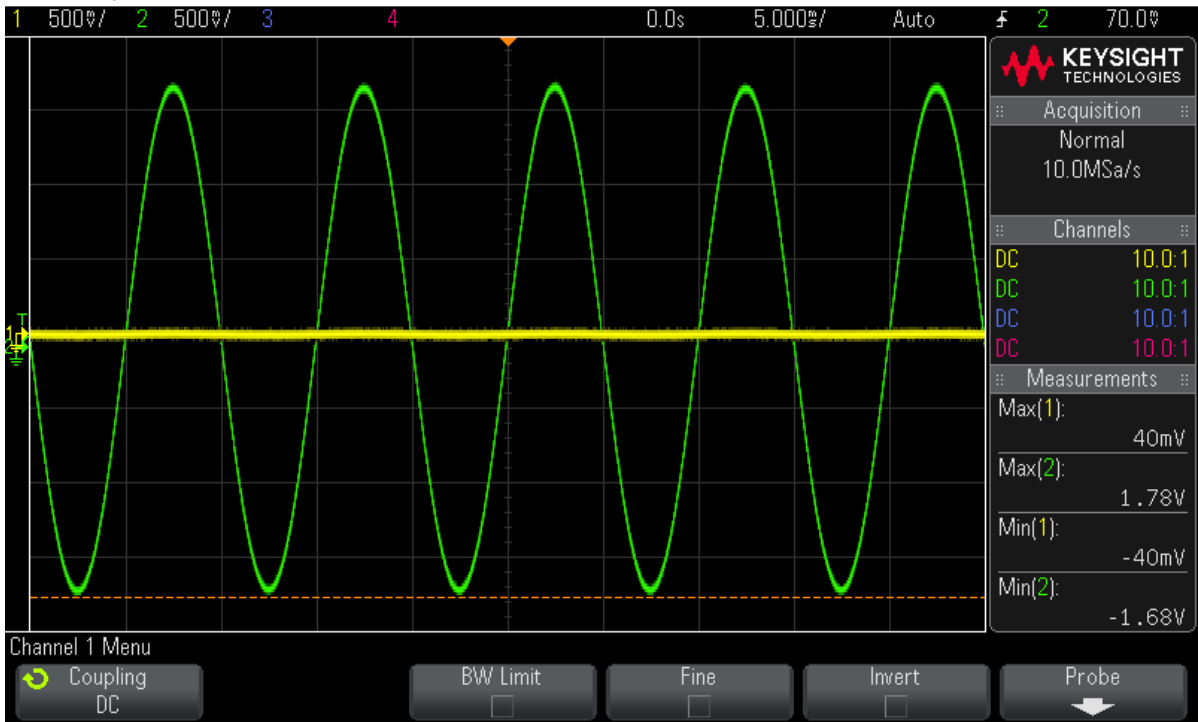DSO-X 2024A, MY55140906: Tue Mar 12 23:15:30 2019



c_c2

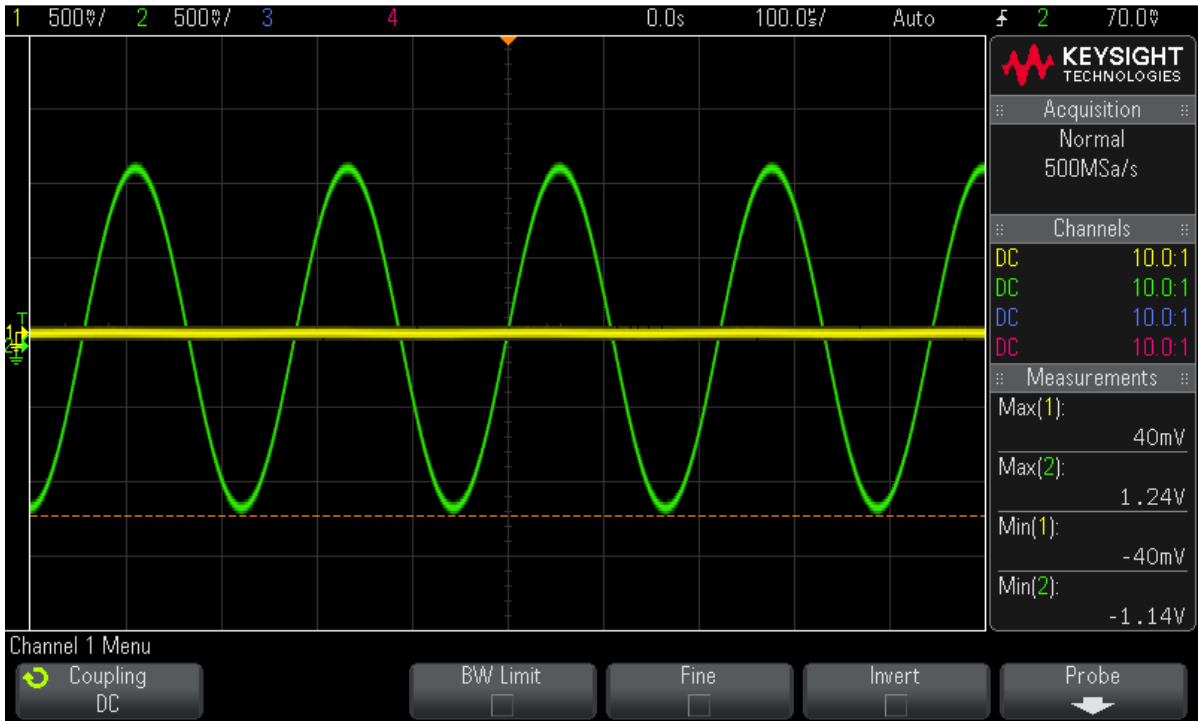DSO-X 2024A, MY55140906: Tue Mar 12 23:17:01 2019



D. Slew-rate limitations


324: Measured slew rate: .4v/us

Figure: Insert an image of slew-rate limited output for the 324 amp.



660: Measured slew rate: 2v/us


Figure: Insert an image of slew-rate limited output for the 660 amp.

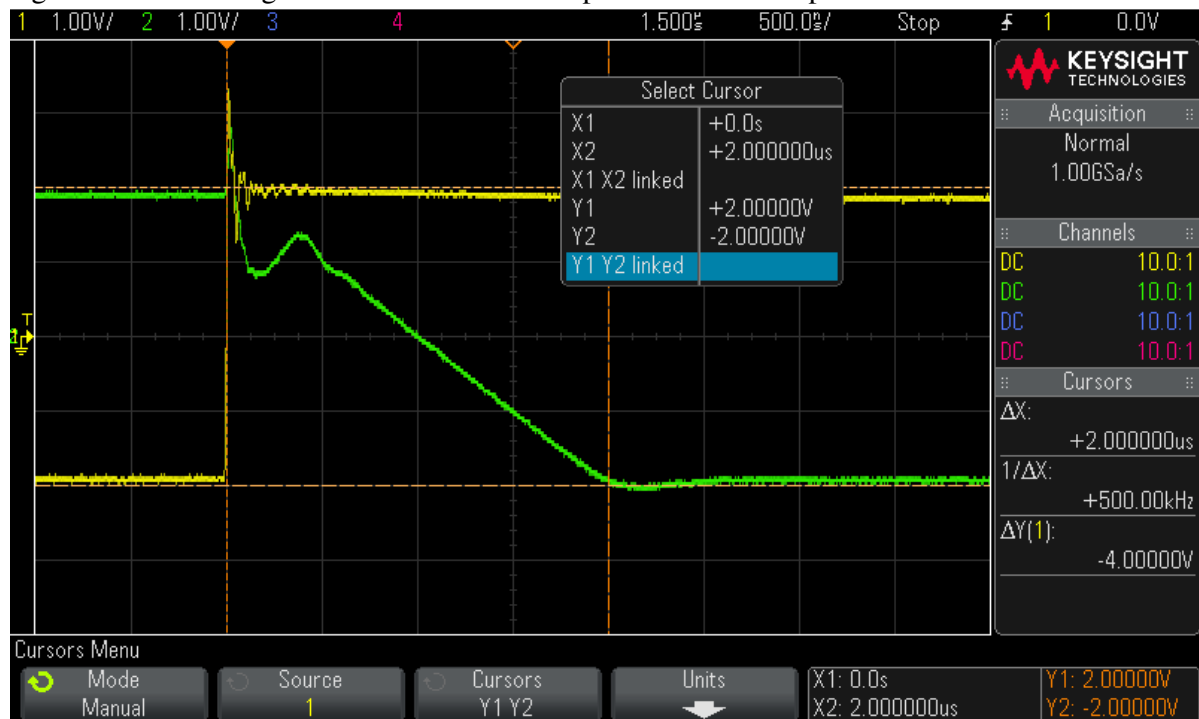


082: Measured slew rate: _____ 10.6v/us _____

Figure: Insert an image of slew-rate limited output for the TL082 amp.

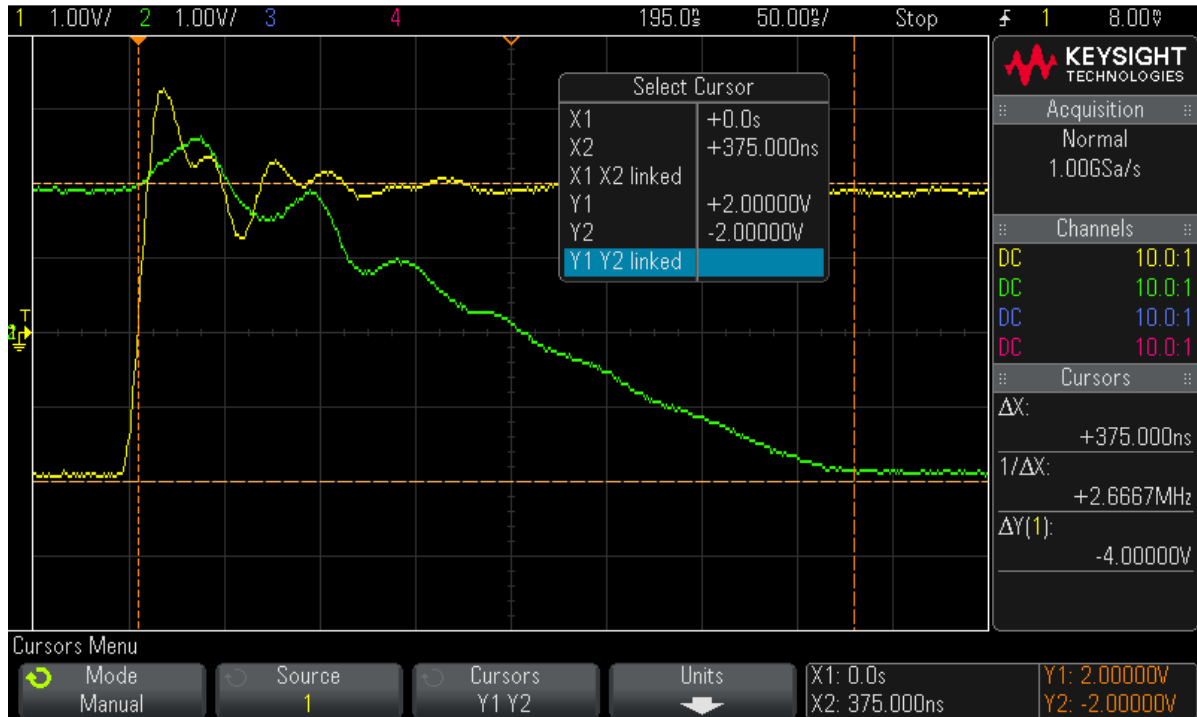DSO-X 2024A, MY55140906: Wed Mar 13 00:10:43 2019



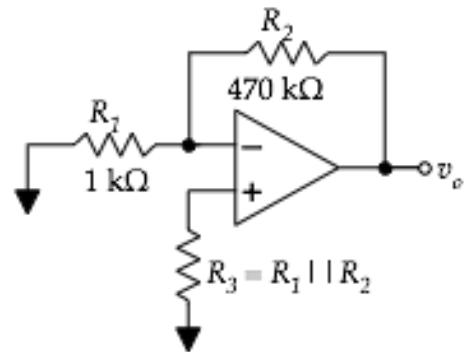E. Offset voltage and bias currents**324:**Measured v_o with R_3 in place = _____ -7.9v _____Offset voltage: V_{OS} = _____ .016v _____Measured v_o with R_3 shorted = _____ .28v _____Difference in v_o measurements = _____ 8.18v _____Bias current: I_B = _____ .0005A _____**660:**Measured v_o with R_3 in place = _____ .50mv _____Offset voltage: V_{OS} = _____ .0001v _____Measured v_o with R_3 shorted = _____ -20mv _____Difference in v_o measurements = _____ 70mv _____Bias current: I_B = _____ .00004A _____

082:Measured v_o with R_3 in place = _____ 8v _____Offset voltage: $V_{os} =$ _____ .017v _____Measured v_o with R_3 shorted = _____ 8v _____Difference in v_o measurements = _____ 0v _____Bias current: $I_B =$ _____ 0A _____**Conclusion**

This lab focuses on specific limitations of operational amplifiers, and throughout the course of the lab runs the op-amps in question through a series of tests designed to highlight those limitations. This lab went largely without hitches, however the supplied potentiometers suck and break all the time so part B was very delayed.