

Instructions: This is a 50-minute exam. Students may bring 2 pages of notes (front and back) to this exam. There are 6 short question is worth 2 points each, two short questions worth 4 points each, and 5 problems worth 16 points each. Please solve problems in the space provided on this exam and attach extra sheets only if you run out of space in solving a specific problem.

If references to semiconductor processes are needed beyond what is given in a specific problem or question, assume all n-channel MOS transistors have model parameters $\mu_n C_{OX} = 350 \mu A/V^2$ and $V_{Tn} = 0.5V$, all p-channel transistors have model parameters $\mu_p C_{OX} = 70 \mu A/V^2$ and $V_{Tp} = -0.5V$. Correspondingly, assume all npn BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 100$ and all pnp BJT transistors have model parameters $J_S = 10^{-14} A/\mu^2$ and $\beta = 25$. If the emitter area of a transistor is not given, assume it is $100 \mu^2$. If parameters are needed for CMOS process characterization beyond what is given, use the measured parameters from the TSMC 0.18 μ process given below as model parameters. Assume all diodes are characterized by the model parameters $J_{SX} = 0.5 A/\mu m^2$, $V_{G0} = 1.17V$, and $m = 2.3$.

1. (2 pts) How many small-signal parameters are required for the small-signal model of a nonlinear one-port circuit?
2. (2 pts) The diode equation is much more difficult to work with than the simpler piecewise-linear diode model (open circuit when not conducting and a dc voltage source of 0.6V when conducting). What is a quick way to check and see if the simpler piecewise-linear model can be used when analyzing a diode circuit?
3. (2pts) The parameters $\{\mu, C_{OX}, V_{TH}, \lambda, \gamma, \text{ and } \phi\}$ were used to characterize the operation of a MOSFET. Which of these parameters corresponds to the Early Voltage parameter, V_{AF} , in the bipolar transistor?
4. (2 pts) In a CMOS process that has a single polysilicon layer, it can be observed that after processing, polysilicon appears either on top of thin oxide or on top of thick oxide. What must the designer do to place polysilicon on top of thin oxide?

5. (2 pts) The base in a vertical npn transistor is very thin. What is the major reason that the based region is intentionally made very thin?


6. (2pts) The isolation diffusion is used to provide electrical separation of devices in a bipolar process. What is the counterpart method in a bulk CMOS process for providing electrical separation of devices?

7. (4 pts) An inexperienced designer was told that if Metal and Polysilicon in a CMOS process overlap, the metal will always appear on top of polysilicon. He also observed that during layout it was common to first layout the polysilicon and then do the interconnects with metal thus placing metal on top of the polysilicon. This inexperienced designer figured out a clever way to place metal under polysilicon that he thought others had overlooked and that this could be done during layout without any changes in the process flow. What he proposed was to first layout the metal and then layout the polysilicon this placing polysilicon on top of metal. He indicated that this process was more tedious because more planning needed to go into the layout process to be sure that the metal was in the right place when polysilicon was added later. After spending a lot of time following this method of layout where all metal was placed before any polysilicon was placed, a design was completed. After fabrication, will the circuit have metal under polysilicon as planned by the clever but inexperienced designer? If not, what will be observed?

8 (4 pts) If a BJT is operating in the Forward Active region and it is observed that the emitter current is 5mA and the base current is 1mA, what is the “ β ” for the transistor?

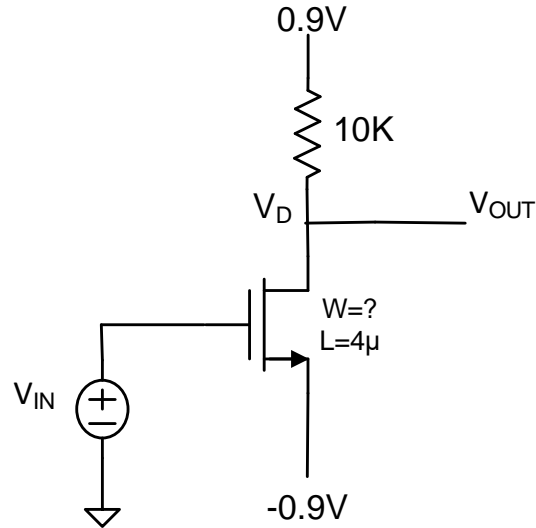Problem 1 (16 pt) Consider the following circuit.

- Draw the small signal equivalent circuit assuming the MOS transistor is operating in the saturation region
- Give the small-signal voltage gain in terms of the small-signal model parameters assuming the MOS transistor is operating in the saturation region
- Determine W so that the quiescent output voltage is $0V$
- Determine the small-signal voltage gain with the value of W determined in part c)




Problem 2 Consider the circuit shown below. Assume the capacitors are large and also assume that V_{IN} is a small-signal input. Assume further that the nonlinear device (depicted in the box below) that is characterized by the equations

$$I_1 = 10^{-3} V_1$$

$$I_2 = \begin{cases} 10^{-2} V_1 & \text{for } V_1 < 1V \text{ (termed region1)} \\ 10^{-2} V_1^3 \left(1 + \frac{V_2}{10}\right) & \text{for } V_1 > 1V \text{ (termed region2)} \end{cases}$$



(the numerical coefficients in the model have dimensions to make the expressions shown consistent but are not shown for notational convenience)

- Develop a small-signal model of this nonlinear device in terms of the “y” parameters when operating in region 2 in terms of the quiescent values for V_1 and V_2 .
- Give an equivalent circuit for the small-signal model
- Determine V_{1Q} and V_{OUTQ}
- Determine the small-signal voltage gain in terms of the circuit components and the y parameters of the nonlinear device
- (extra credit) Determine the numerical value of the voltage gain.

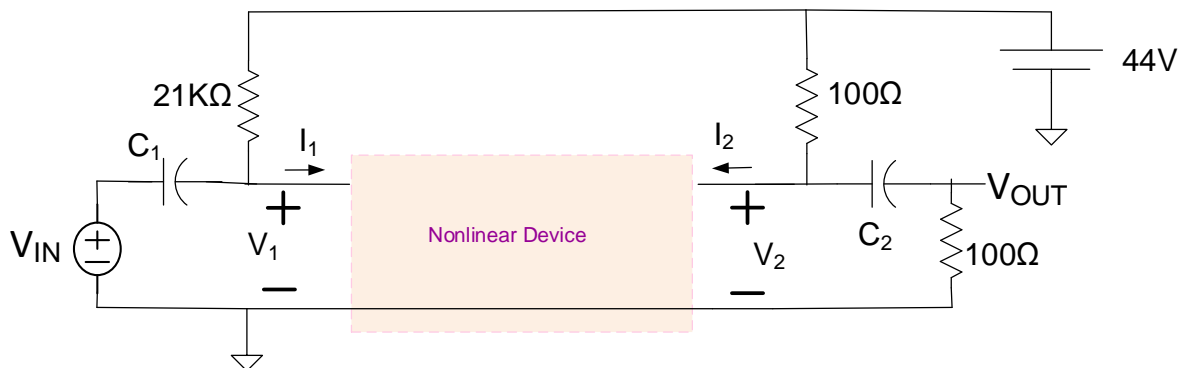



Continue solution to Problem 2 here if additional space is needed

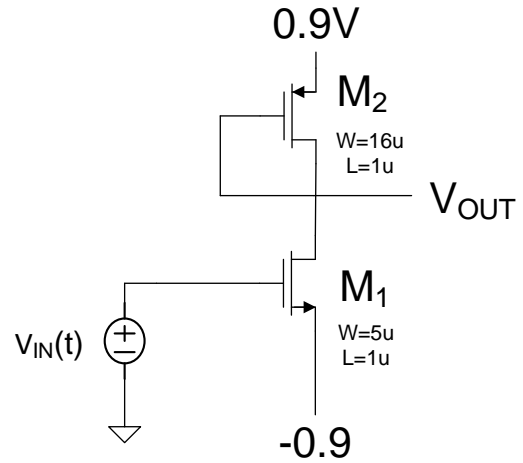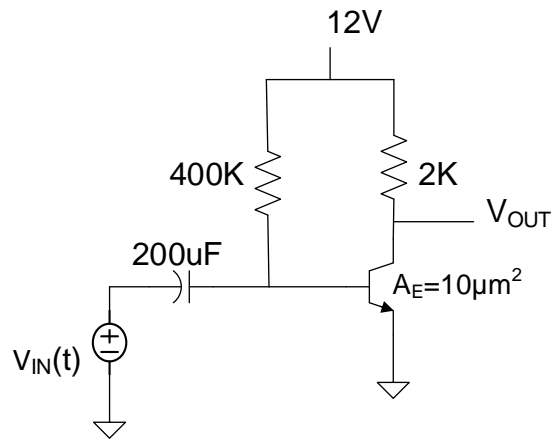Problem 3 (16 pts) Determine the quiescent output voltage for the following two circuits. Assume the small-signal inputs are very small. Use the model parameters for the devices given at the top of this exam.



Problem 4 (16 pts) Design a circuit using only MOS transistors that has an output voltage of 2V. You have available any number of MOS transistors and a single DC 5V dc power supply. Be sure to give the sizes of all transistors. Assume the MOS transistors are from a 5V process and have model parameters $\mu_n C_{OX} = 100\mu A/V^2$ and $V_{Tn} = 0.75V$, and all p-channel transistors have model parameters $\mu_p C_{OX} = 30\mu A/V^2$ and $V_{Tp} = -0.75V$.

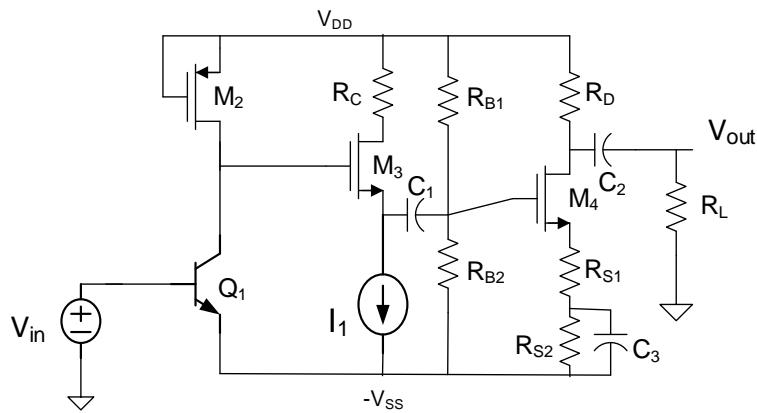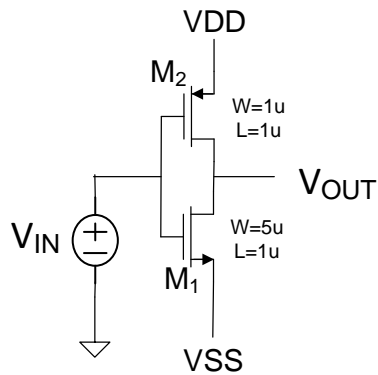Problem 5 (16 pts) Draw the small-signal equivalent circuit for the following two amplifier structures. Assume the capacitors are large, all MOS transistors are operating in the Saturation region, and all bipolar transistors are operating in the Forward Active region. Do not solve.




```

RUN: T68B (MM_NON-EPI)                                VENDOR:
TSMC                                                        FEATURE SIZE: 0.18
TECHNOLOGY: SCN018 microns
Run type: SKD
```

COMMENTS: DSCN6M018 TSMC

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM Vth	0.27/0.18	0.50	-0.51	volts
SHORT Idss	20.0/0.18	547	-250	uA/um
Vth		0.51	-0.51	volts
Vpt		4.8	-5.6	volts
WIDE Ids0	20.0/0.18	14.4	-4.7	pA/um
LARGE Vth	50/50	0.43	-0.42	volts
Vjblk		3.1	-4.3	volts
Ijlk		<50.0	<50.0	pA
K' (Uo*Cox/2)		175.4	-35.6	uA/V^2
Low-field Mobility		416.52	84.54	cm^2/V*s

Design Technology	XL (um)	XW um)
SCN6M_DEEP (lambda=0.09)	0.00	-0.01
thick oxide	0.00	-0.01
SCN6M_SUBM (lambda=0.10)	-0.02	0.00
thick oxide	-0.02	0.00

FOX TRANSISTORS	GATE	N+ACTIVE	P+ACTIVE	UNITS
Vth	Poly	>6.6	<-6.6	volts

PROCESS PARAMETERS	N+	P+	POLY	N+BLK	PLY+BLK	M1	M2	UNITS
Sheet Resistance	6.7	7.8	8.0	59.7	313.6	0.08	0.08	ohms/sq
Contact Resistance	10.6	11.0	10.0				4.79	ohms
Gate Oxide Thickness	41							angstrom














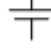














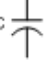
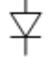




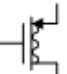

PROCESS PARAMETERS	M3	POLY_HRI	M4	M5	M6	N_W	UNITS
Sheet Resistance	0.08		0.08	0.08	0.03	930	ohms/sq
Contact Resistance	9.24		14.05	18.39	20.69		ohms







COMMENTS: BLK is silicide block.

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS	
Area (substrate)	942	1163	106	34	14	9	6	5	3				123	125	aF/um^2
Area (N+active)			8484	55	20	13	11	9	8						aF/um^2
Area (P+active)			8232												aF/um^2
Area (poly)				66	17	10	7	5	4						aF/um^2
Area (metal1)					37	14	9	6	5						aF/um^2
Area (metal2)						35	14	9	6						aF/um^2
Area (metal3)							37	14	9						aF/um^2
Area (metal4)								36	14						aF/um^2
Area (metal5)									34				984		aF/um^2
Area (r well)	920														aF/um^2
Area (d well)										582					aF/um^2
Area (no well)	137														aF/um^2
Fringe (substrate)	212	235		41	35	29	21	14							aF/um
Fringe (poly)				70	39	29	23	20	17						aF/um
Fringe (metal1)					52	34		22	19						aF/um
Fringe (metal2)						48	35	27	22						aF/um
Fringe (metal3)							53	34	27						aF/um
Fringe (metal4)								58	35						aF/um
Fringe (metal5)									55						aF/um
Overlap (N+active)			895												aF/um
Overlap (P+active)			737												aF/um

CIRCUIT PARAMETERS		UNITS
Inverters	K	
Vinv	1.0	0.74 volts
Vinv	1.5	0.78 volts
Vol (100 uA)	2.0	0.08 volts
Voh (100 uA)	2.0	1.63 volts
Vinv	2.0	0.82 volts
Gain	2.0	-23.72
Ring Oscillator Freq.		
D1024_THK (31-stg, 3.3V)	300.36	MHz
DIV1024 (31-stg, 1.8V)	363.77	MHz
Ring Oscillator Power		
D1024_THK (31-stg, 3.3V)	0.07	uW/MHz/gate
DIV1024 (31-stg, 1.8V)	0.02	uW/MHz/gate

Dc and small-signal equivalent elements

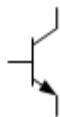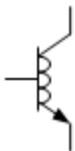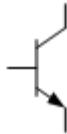	Element	ss equivalent	dc equivalent
dc Voltage Source	V_{DC} 		V_{DC} 
ac Voltage Source	V_{AC} 	V_{AC} 	
dc Current Source	I_{DC} 		I_{DC} 
ac Current Source	I_{AC} 	I_{AC} 	
Resistor	R 	R 	R 
Capacitors	Element	ss equivalent	dc equivalent
	C Large 		
Inductors	C Small 	C 	
	L Large 		
Diodes	L Small 	L 	
			 Simplified
MOS transistors			 Simplified
			 Simplified

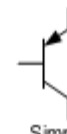	Element	ss equivalent	dc equivalent
Bipolar Transistors			 Simplified
			 Simplified
Dependent Sources	