

CprE 381: Computer Organization and Assembly Level Programming, Spring 2019

Report – Project Part 3


Lab Partners _____ Sean Gordon _____

Section /Lab Time _____ C/10:00 _____

Canvas Group ID _____ Team-8 _____


Refer to the highlighted language in the Project 3 instruction for the context of the following questions.

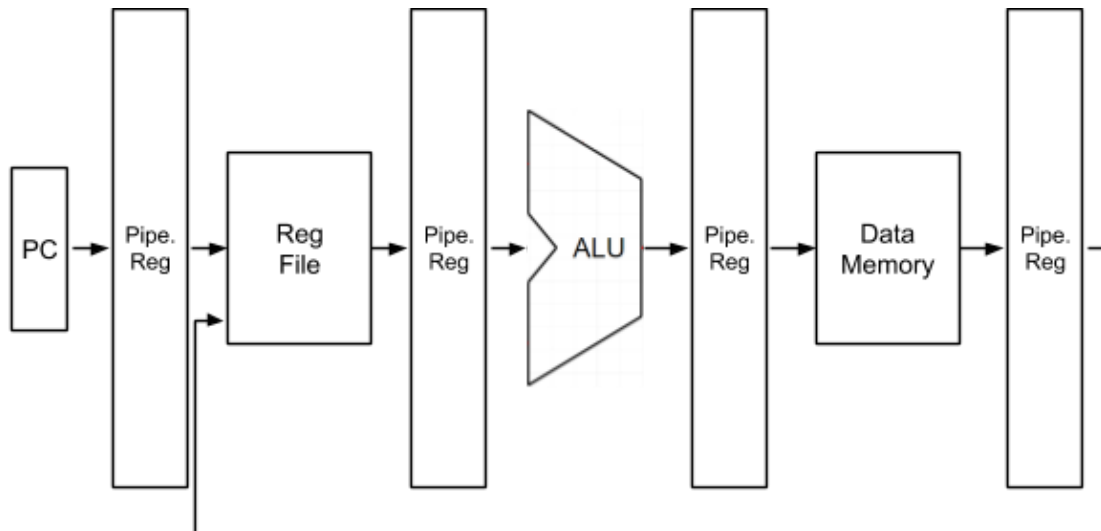- a. [Part (a.2)] Provide a high-level schematic drawing of the interconnection between components.



 - b. [Part (a.3), Testing Program #1] Include an annotated waveform in your writeup and provide a short discussion of result correctness.

The file run here is "TestAllInstrNops.s"



As, throughout the running of the test, every instruction deposited the correct value into the correct register and every instruction that did not write to the RegFile performed its required function, I decree this test successful and the processor functional.

- c. [Part (a.3), Testing Program #2-Bubble Sort] Include an annotated waveform in your writeup of two iterations or recursions of these programs executing correctly and provide a short discussion of result correctness.

The file run here is “BubbleSortFancyNops.s”



Every loop annotated above is one run of the inner section of code in BubbleSortFancyNops.s. As when the final array was printed into registers 16-25 at the end of the program the numbers were in correct order, I decree this test successful and the processor functional.

- d. [Part (a.3), not to be graded] How did you modify the bubble and merge sort so that they avoid all control and data hazard? By inserting NOPs? Or, by rearranging some instruction?

Inserted nops, it requires less movement.

- e. [Part (a.4)] Report the maximum frequency your software-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

The maximum frequency the 3a processor can run on is 38.79 mHz. The critical path is the 'branch detection → IF/ID reset' path, as the branch detection logic can only run after the falling edge of the clock due to the register file. The output is as follows:


Data Arrival Path:

Total (ns)	Incr (ns)	Type	Element	
10.000	10.000		launch edge time	
19.731	9.731	F	clock network delay	
19.963	0.232	uTco	RegFile:regs NBitReg:\G1:25:regs o_Q[10]	Register File
19.963	0.000	FF	CELL regs \G1:25:regs o_Q[10] q	and register
20.308	0.345	FF	IC regs multiplexor2 Mux21~2 datac	multiplexor,
20.589	0.281	FF	CELL regs multiplexor2 Mux21~2 combout	using the output
20.954	0.365	FF	IC regs multiplexor2 Mux21~3 datad	of the regFile
21.104	0.150	FR	CELL regs multiplexor2 Mux21~3 combout	decoder
22.161	1.057	RR	IC regs multiplexor2 Mux21~6 datac	
22.448	0.287	RR	CELL regs multiplexor2 Mux21~6 combout	
22.653	0.205	RR	IC regs multiplexor2 Mux21~9 datad	
22.808	0.155	RR	CELL regs multiplexor2 Mux21~9 combout	
23.012	0.204	RR	IC regs multiplexor2 Mux21~19 datad	
23.167	0.155	RR	CELL regs multiplexor2 Mux21~19 combout	
24.232	1.065	RR	IC Equal0~6 dataa	Comparing
24.661	0.429	RF	CELL Equal0~6 combout	outputs from
25.099	0.438	FF	IC Equal0~9 dataa	register file
25.452	0.353	FF	CELL Equal0~9 combout	for branch
25.820	0.368	FF	IC Equal0~20 datac	logic
26.101	0.281	FF	CELL Equal0~20 combout	
26.339	0.238	FF	IC IF_ID_Rst~0 datad	IF/ID reset
26.464	0.125	FF	CELL IF_ID_Rst~0 combout	combination
28.950	2.486	FF	IC IF_IDReg InstrReg o_Q~14 datad	logic
29.100	0.150	FR	CELL IF_IDReg InstrReg o_Q~14 combout	
29.100	0.000	RR	IC IF_IDReg InstrReg o_Q[28] d	
29.187	0.087	RR	CELL PipRegIF_ID:IF_IDReg Reg32BitIF_ID:InstrReg o_Q[28]	^^ Final reset
				signal, delayed
				with a reg to
				avoid issues with
				delta cycle delay

- f. [Part (b.5)] Update your global list of the datapath values and control signals that are required during each pipeline stage.

Incoming Signals per Section				
IF	ID	EXE	MEM	WB
JumpD	PC+4	ALUCtrl	MemWrite	RegWrite
JumpAddrD	Instr	ALUSrc	ALUOut	MemToReg
BranchCalcD	RegAddrWB	ReadData1	WriteData	ALUOut
BranchAddrD	WriteValWB	ReadData2	RegAddr	InstrRead
		SextImm	Lui	Lui
		Rs	Imm	RegAddr
		Rt		Imm
		Rd		
		RegDst		
		Imm		

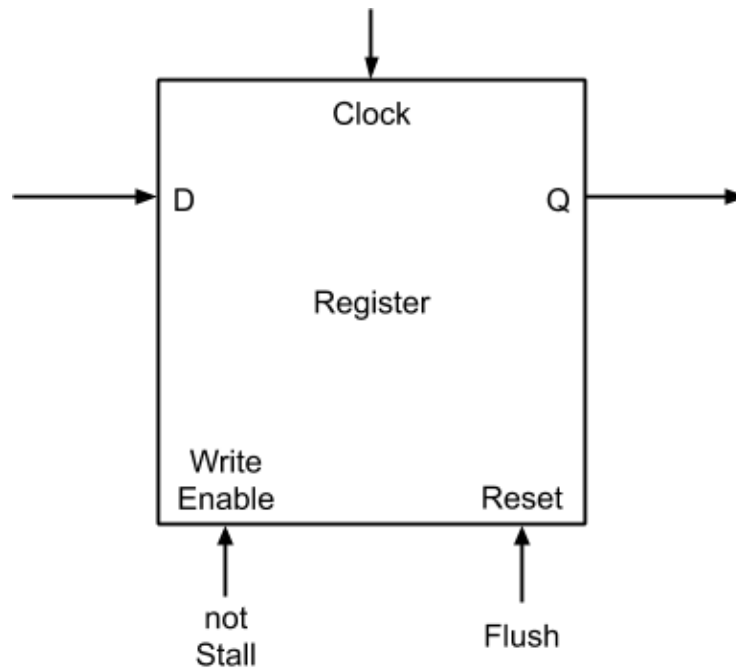- g. [Part (b.6.a)] Draw a simple schematic showing how you could implement stalling and flushing operations given an ideal N-bit register.



- h. [Part (b.6.b)] Create a testbench that instantiates all four of the registers in a single design. Show that values that are stored in the initial IF/ID register are available as expected four cycles later, and that new values can be inserted into the pipeline every single cycle. Most importantly, this testbench should also test that each pipeline register can be individually stalled or flushed.

Will probably do later. For now, the correct output of a fully functional pipelined processor below should suffice.

- i. [Part (b.7.a)] List which instructions produce values, and what signals in the pipeline these correspond to.

Instr	Produce		Consumes		Consumes	
add	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
addi	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
addu	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
addiu	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
sub	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
subu	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
and	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
andi	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
or	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
ori	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
nor	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
xor	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
sll	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rt)	<input type="checkbox"/>	
srl	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rt)	<input type="checkbox"/>	
sra	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rt)	<input type="checkbox"/>	
slt	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
sltu	<input checked="" type="checkbox"/>	(Rd)	<input checked="" type="checkbox"/>	(Rs)	<input checked="" type="checkbox"/>	(Rt)
slti	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
sltiu	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
lw	<input checked="" type="checkbox"/>	(Rt)	<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
lui	<input checked="" type="checkbox"/>	(Rt)	<input type="checkbox"/>		<input type="checkbox"/>	
sw	<input type="checkbox"/>		<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
beq	<input type="checkbox"/>		<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
bne	<input type="checkbox"/>		<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	
j	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>	
jal	<input checked="" type="checkbox"/>	(\$31)	<input type="checkbox"/>		<input type="checkbox"/>	
jr	<input type="checkbox"/>		<input checked="" type="checkbox"/>	(Rs)	<input type="checkbox"/>	

- j. [Part (b.7.b)] List which of these same instructions consume values, and what signals in the pipeline these correspond to
All immediates are sent to “Imm”, others are passed through Rs and Rt.
- k. [Part (b.7.c)] Come up with a generalized list of potential data dependencies. From this generalized list, select those dependencies that will require forwarding (write down the corresponding pipeline stages that will be forwarding and receiving the data), and those dependencies that will require hazard stalls.
Any instruction that consumes a value produced by an instruction one or two prior will have a data dependency.

1. [Part (b.8)] Write a more generalized series of data forwarding and hazard detection logic equations based on the result from the previous part. These should be of the format of those found in P&H 4.7, but there will be several more types of dependencies to consider.

Pulled from my main schematic, the numbers refer to hazard signal superscripts:

Hazard Reference List:

1. These signals are used to forward ALU output, detected by:

```
ID_Rs == MEM_RegAddr    <-- A (Same order for below)
ID_Rt == MEM_RegAddr    <-- B (Same order for below)
Operates iff MEM_RegWrite == 1 and MEM_RegAddr != $0
```

2. These signals are used to forward ALU output, detected by:

```
EXE_Rs == MEM_RegAddr
EXE_Rt == MEM_RegAddr
Operates iff MEM_RegWrite == 1 and MEM_RegAddr != $0
```

3. These signals are used to forward DMem output, detected by:

```
EXE_Rs == WB_RegAddr
EXE_Rt == WB_RegAddr
Operates iff WB_RegWrite == 1 and WB_RegAddr != $0
```

4. These signals are used to stall the pipeline. Used together, this holds current instr. in ID and lets EXE, MEM, & WB propagate. There are many situations where this is used, logic listed below:

Branch/Jump needs ALU or DMem of prev instr. or

```
ID_Rs == EXE_RegAddr
ID_Rt == EXE_RegAddr
Operates iff EXE_RegWrite == 1 and EXE_RegAddr != $0
                (Checking EXE_MemtoReg == 1 is redundant here)
```

Branch/Jump needs DMem of instr. 2 prev

```
ID_Rs == MEM_RegAddr
ID_Rt == MEM_Reg Addr
Operates iff MEM_RegWrite == 1 and MEM_RegAddr != $0
                and MEM_MemtoReg == 1
                and (not (ForwardA or ForwardB)) (1)
```

ALU needs DMem of prev instr.

(ALU <- DMem calculation must be done w/ ID, early enough to stall)

```
ID_Rs == EXE_RegAddr
ID_Rt == EXE_RegAddr
Operates iff EXE_RegWrite == 1 and EXE_RegAddr != $0
                and EXE_MemtoReg == 1
                and (not (ForwardA2 or ForwardB2)) (2)
```

5. Beware, if stalling to forward for a branch or jump, PC will be stalled, so the new address will not take unless PC stall is changed:
PCStall = (Stall) or (Jump/Branch IF/ID reset signal)

- m. [Part (b.9)] Provide a high-level schematic drawing of the interconnection between components.
Refer to main schematic below.
- n. [Part (b.10)] In your writeup, show the ModelSim output for each of the following tests, and provide a discussion of results correctness. It may be helpful to also annotate the waveform directly
 - a. Verify that your three test applications from Project Part 2 work on this processor without being modified.


Each of the files for part a was run directly from the Proj2 MARsWork testing directory.

The wlf form corresponding to this test is “Proj2_a3.wlf”

```
Please provide the assembly file to run.
Use unix style paths like: MARsWork/Examples/addiSeq.asm
>U:\cpre381\Proj2\cpre381-toolflow-release\MARsWork\Proj2Testing\a3.s
starting compilation...
Successfully compiled vhd1

Starting VHDL Simulation...
Successfully simulated program!

 Victory!! Your processes matches MARS expected output with no mismatches!!
Press any key to close . . .
```




For every instruction, register 24 was updated with the correct value, so I would assume the processor was functioning correctly.

The wlf form corresponding to this test is “Proj2_b5.wlf”

```
Please provide the assembly file to run.
Use unix style paths like: MARsWork/Examples/addiSeq.asm
>U:\cpre381\Proj2\cpre381-toolflow-release\MARsWork\Proj2Testing\b5.s
starting compilation...
Successfully compiled vhd1

Starting VHDL Simulation...
Successfully simulated program!

 Victory!! Your processes matches MARS expected output with no mismatches!!
Press any key to close . . .
```




Every branch/jump cleared the IF/ID pipeline register as intended, and skipped the 'got you' instructions inserted after the branches in the code, while every other instruction executed as intended, so I presume the processor was operating correctly.

The wlf form corresponding to this test is “Proj2_b6.wlf”

```
Please provide the assembly file to run.
Use unix style paths like: MARsWork/Examples/addiSeq.asm
>U:\cpre381\Proj2\cpre381-toolflow-release\MARsWork\Proj2Testing\b6.s
starting compilation...
Successfully compiled vhd1

Starting VHDL Simulation...
Successfully simulated program!

 Victory!! Your processes matches MARS expected output with no mismatches!!
Press any key to close . . .
```



Every instruction that was meant to run deposited the correct value into the correct register, while the jumps and branches ran at the correct times and reset the IF/ID register correctly, so I deem this test successful and this processor functional.

- b. Create an application that tries to exhaustively test the forwarding and hazard detection capabilities of your pipeline.

Creating the extra tests for this writeup takes longer than it would take to physically run from the sun to the moon, and I have other things I need to do, so I just used fibonacci.asm for this section as that should *mostly* cover this requirement.

***Note:** MARS starts the program at instruction memory location `0x0040_0000`, while this processor starts the program at instruction memory location `0x0000_0000`, so when the processor performs 'jal', different values are written to register \$31, causing the error below.

```
Please provide the assembly file to run.
Use unix style paths like: MARsWork/Examples/addiSeq.asm
>U:\cpre381\Proj3\cpre381-toolflow-release\MARsWork\Examples\fibonacci.asm
starting compilation...
Successfully compiled vhd1


Starting VHDL Simulation...
Successfully simulated program!

Oh no...

Cycle: 208
Incorrect Write to Register File
MARS instruction number: 132      Instruction: jal 4194396
MARS: Register Write to Reg: 0x1F Val: 0x00400050
Student: Register Write to Reg: 0x1F Val: 0x00000050

Almost! your processor completed the program with 1/3 allowed mismatches
```

 Final section of “fibonacci.asm” displayed below:



The program completed with no real errors, meaning every jump, branch, register write, and otherwise was completed successfully, I deem this processor fully functional.


- o. [Part (b.12)] Report the maximum frequency your hardware-scheduled pipelined processor can run at and determine what your critical path is (specify each module/entity/component that this path goes through).

The maximum frequency the 3b processor can run on is 39.40 mHz. The critical path is the 'branch detection → PC enable' path, as the branch detection logic can only run after the falling edge of the clock due to the register file. This PC logic is necessary so as not to stall the PC register during a forward if a branch or a jump needs to update its value (number 5 in hazard logic described above). The output is as follows:

Data Arrival Path:

Total (ns)	Incr (ns)	Type	Element	
10.000	10.000		launch edge time	
19.315	9.315	F	clock network delay	
19.547	0.232	uTco	RegFile:regs[NBitReg:\G1:23:regs[o_Q[23]	Register File
19.547	0.000	FF	CELL regs[\G1:23:regs[o_Q[23]]q	and register
20.070	0.523	FF	IC regs[multiplexor1 Mux8~9 datad	multiplexor,
20.195	0.125	FF	CELL regs[multiplexor1 Mux8~9 combout	using the output
20.427	0.232	FF	IC regs[multiplexor1 Mux8~10 datad	of the RegFile
20.708	0.281	FF	CELL regs[multiplexor1 Mux8~10 combout	decoder
22.018	1.310	FF	IC regs[multiplexor1 Mux8~11 datad	
22.299	0.281	FF	CELL regs[multiplexor1 Mux8~11 combout	
22.527	0.228	FF	IC regs[multiplexor1 Mux8~16 datad	
22.652	0.125	FF	CELL regs[multiplexor1 Mux8~16 combout	
22.882	0.230	FF	IC regs[multiplexor1 Mux8~19 datad	
23.032	0.150	FR	CELL regs[multiplexor1 Mux8~19 combout	
23.260	0.228	RR	IC ForA_MuxD[o_F[23]~22 datad	Forwarding mux
23.415	0.155	RR	CELL ForA_MuxD[o_F[23]~22 combout	for branch logic
23.641	0.226	RR	IC Equal0~31 datad	Comparing
23.928	0.287	RR	CELL Equal0~31 combout	outputs from
24.627	0.699	RR	IC Equal0~32 datad	register file
24.894	0.267	RF	CELL Equal0~32 combout	for branch
25.165	0.271	FF	IC Equal0~38 datad	logic
25.515	0.350	FF	CELL Equal0~38 combout	
25.761	0.246	FF	IC s_BranchOrD~0 datad	Branch OR
26.042	0.281	FF	CELL s_BranchOrD~0 combout	logic
27.070	1.028	FF	IC IF_ID_Rst~0 datad	IF/ID reset
27.350	0.280	FF	CELL IF_ID_Rst~0 combout	logic
27.620	0.270	FF	IC PCReg[o_Q[0]]ena	PC register
28.299	0.679	FF	CELL NBitReg:PCReg[o_Q[0]	enable logic

Main Schematic:

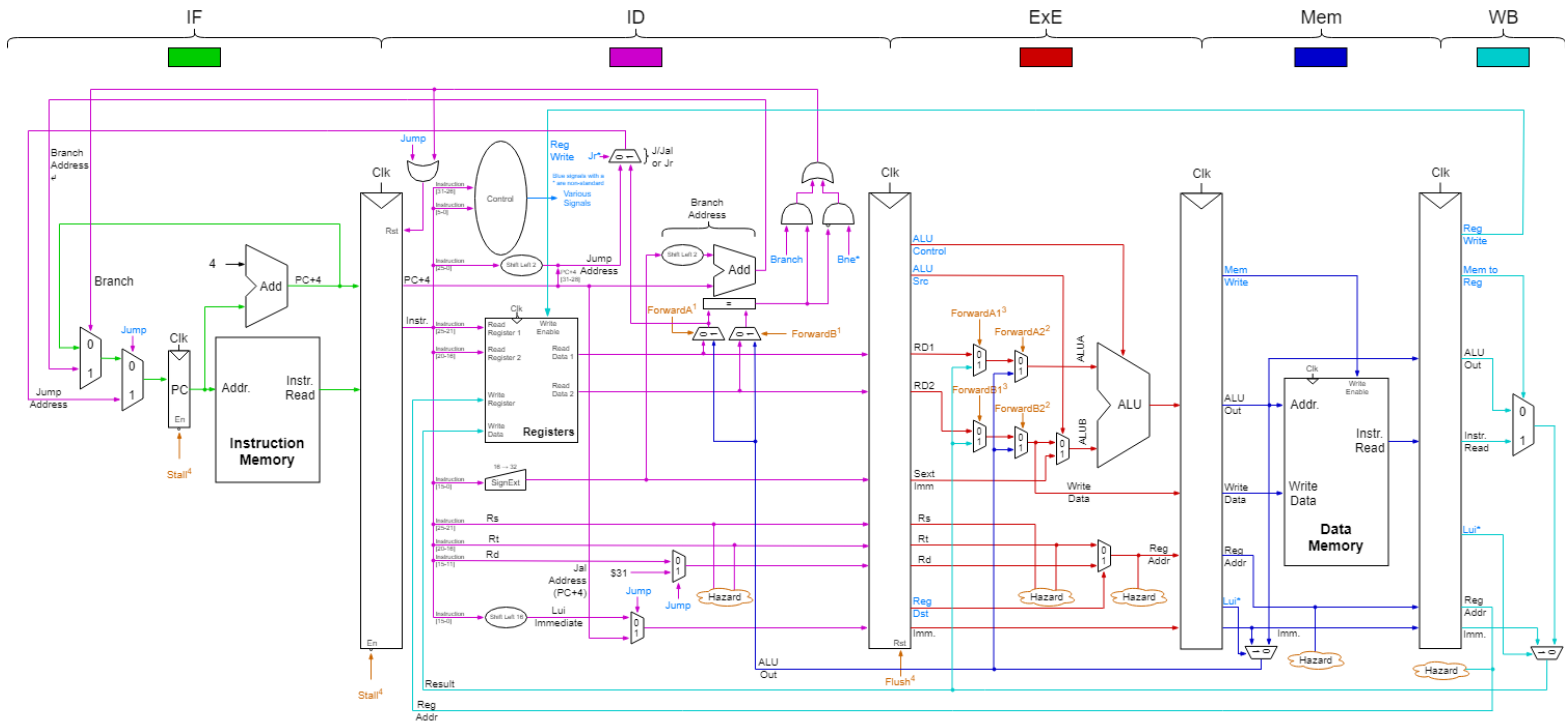

*Note: In the above schematic, I display the pipeline registers as updating on the falling edge of the clock, when in fact they update on the rising edge. This was simply something I forgot to change.

Link to schematic in draw.io:

<https://drive.google.com/file/d/19Vn-4LoZGcJRO0gRVSQViPrvZdb4JGhl/view?usp=sharing>