

Counters


- Asynchronous / Synchronous
 - Up / Down
 - Using T / D FF
 - Other features: Enable, Parallel load, Modulo
-
- Remark: *Synchronous counters can be designed as finite state machines*

Timing Analysis of Sequential Circuit (1)

- Key constraints
 - Input to each FF should have been stable for setup time before each clock edge
 - Impact max. clock frequency
 - Input to each FF shall not change before the end of hold-time period
 - Determines whether there is hold-time violation
- Principles
 - Need to consider *signal-delay along all the paths that start and stop at some flip-flops*
 - Starting and ending flip-flops can be different
 - The path with the longest delay, including setup time of ending FF, determines the *highest clock frequency*
 - The path with the shortest delay, not including setup time of ending FF, determines whether there is *any hold-time violation*

Timing Analysis of Sequential Circuit (2)

- Clock frequency, Clock period (clock cycle time)
- For next state logic,
 - Next state logic propagation delay (worst case delay)
 $\leq \text{Clock period} - \text{FF C-to-Q prop delay} - \text{FF set-up time}$
 - Next state logic contamination delay (best case delay)
 $\geq \text{FF hold time}$

 


[Figure 6.1 from the textbook]

Sequential Circuit / Finite State Machine


- Output: Moore / Mealy
 - State is different from output
 - For some Moore machine, output logic is trivial (i.e., use state directly as output)
- Input: with / without
 - No difference between Moore and Mealy machines if no input
- FF: D / T / JK

Overall structure of a Sequential Circuit

 Moore machine (outputs depend on current state, but not current inputs)



Mealy machine (outputs depend on both current state and current inputs)

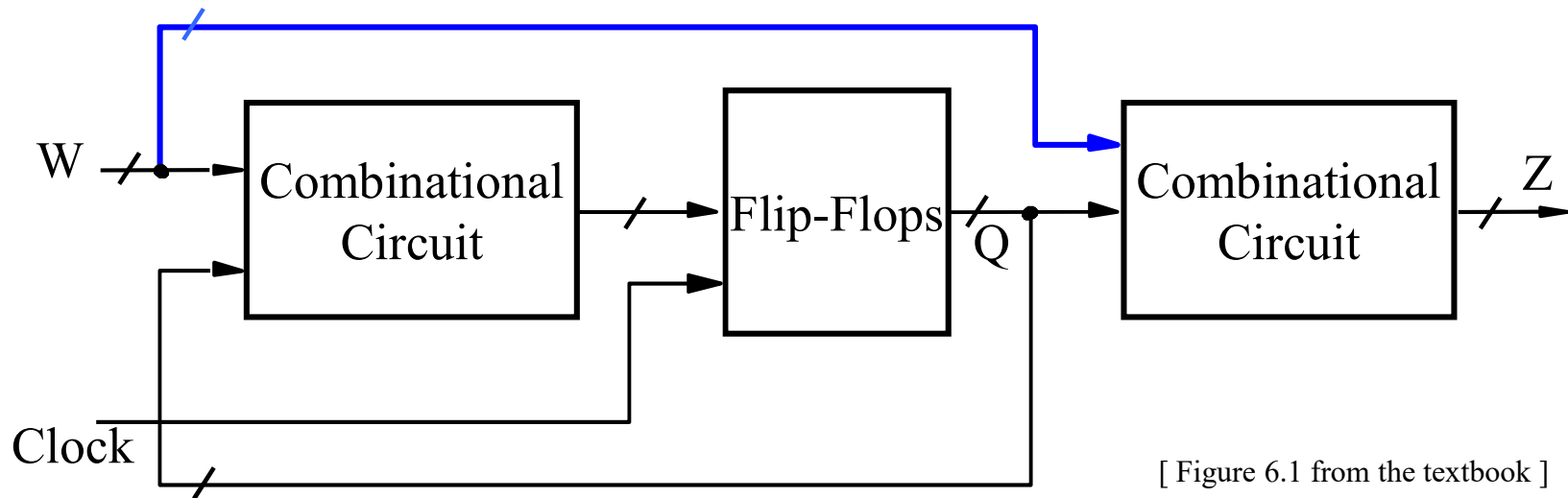

[Figure 6.1 from the textbook]

Designing a Sequential Circuit


1. Determine number of states you need and what each state represents
2. Draw a state diagram
 - It has an initial state
 - It has other states to keep track of various activities
 - It has some transitions
3. Generate a state table
4. Write state-assigned table
 - Needs state assignment, i.e., the code used for each state
 - State assignment is a complex process
 - For the time being assume straightforward combinations
5. Derive logic expressions for next state variables and for outputs
 - You should simplify the expressions
6. Implement the circuit

Specialized FSM


- Examples:
 - Pattern detector
 - Serial adder
 - Counter
 - Arbiter
 - Controller
 - Divisible by N detector
 - Vending machine

ASM Chart

- Moore machine

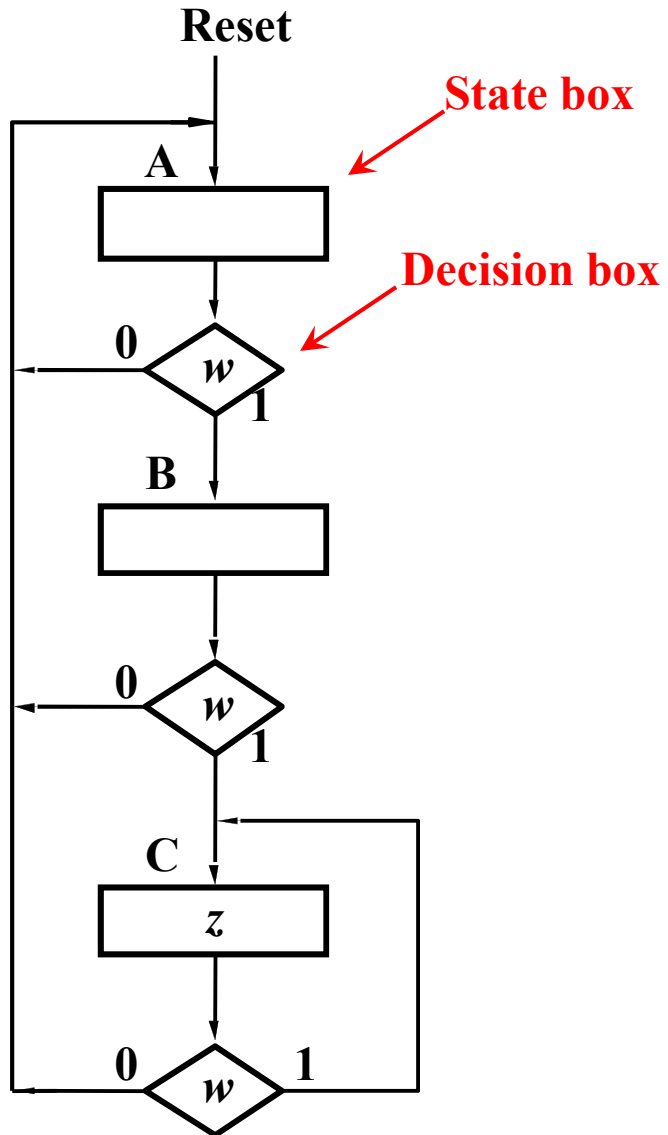

Mealy machine

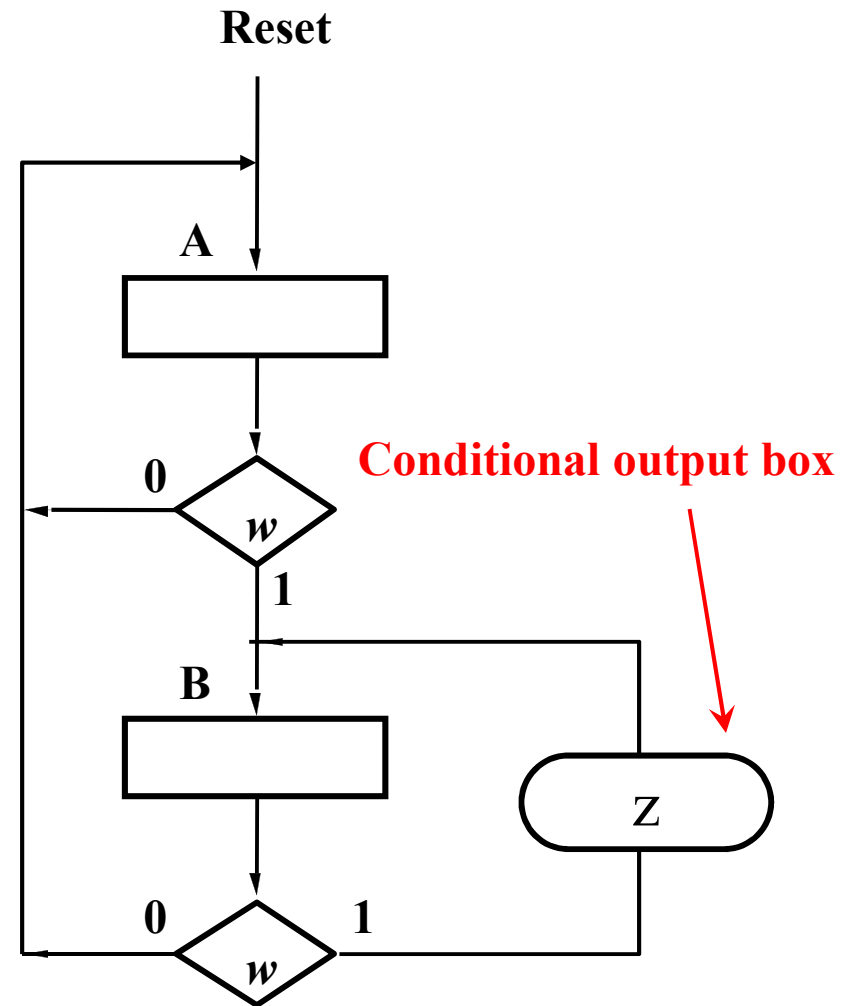

Digital System Design

- Datapath
 - Store, manipulate and transfer data
 - Register file
 - ALU
 - Bus: Implementation using tri-state buffer or MUX
 - Memory
 - ...
- Control
 - Finite state machine
 - For a given datapath, how to design a control to perform a certain operation?