

# **CprE 381: Computer Organization and Assembly Level Programming**

Processor Design

Henry Duwe  
Electrical and Computer Engineering  
Iowa State University

# Administrative

- Exam 1 will be returned on Canvas by tomorrow morning
- HW4
  - Redo your worst exam problem
  - Make it perfect (limited partial credit)
    - Sometimes you (or your classmates) get points for parts not 100% correct
    - Ask questions in OH or on Canvas (I'm fine discussing specific solutions)

# Administrative – Course Workload

- Qualitative Feedback:
  - Too much work
  - Liked “putting it together”
  - Liked and disliked seeing different ways to implement
  - Disliked amount of testing
- Going forward:
  - Reducing the number of instructions needed to support → reduce work on lower-value content
  - Reduce # of test programs individual teams are responsible for → common test pool created by class
  - Testing framework and processor interface/memory instantiation provided

# Administrative – Course Workload

- Lab 2
  - Median reporting student: 8.2hrs outside
  - Median grade (all students): 100%
- Lab 3
  - Median reporting student: 9.8hrs outside
  - Most students had 0hrs in lab two weeks ago
- 4 week average from reporting students
  - ~5hrs on labs outside of class
  - Will keep updated throughout semester

# Processor Design Approach


- Break operation down to steps even logic gates can understand
- Generally decompose into two kinds of operations:
  - Things that deal with the real data (datapath)
  - Things that control the stuff operating on the real data (control)
- Find a decomposition that is simple and efficient
- We will start simple
  - Later (in lecture and lab), we'll add features to improve performance

# The Processor: Datapath & Control

- Textbook MIPS implementation: simplified to contain only:
  - Memory-reference instructions: `lw, sw`
  - Arithmetic-logical instructions: `add, addu, sub, subu, and, or, xor, nor, slt, sltu`
  - Arithmetic-logical immediate instructions: `addi, addiu, andi, ori, xori, slti, sltiu`
  - Control flow instructions: `beq, j`
- Your lab version will require more instructions and thus modifications to this base design!
  - More info in Lec07,1
- Generic implementation:
  - Use the program counter (**PC**) to supply the instruction address and **fetch** the instruction from memory (and update the PC)
  - **Decode** the instruction (and read registers)
  - **Execute** the instruction (already built in lab)
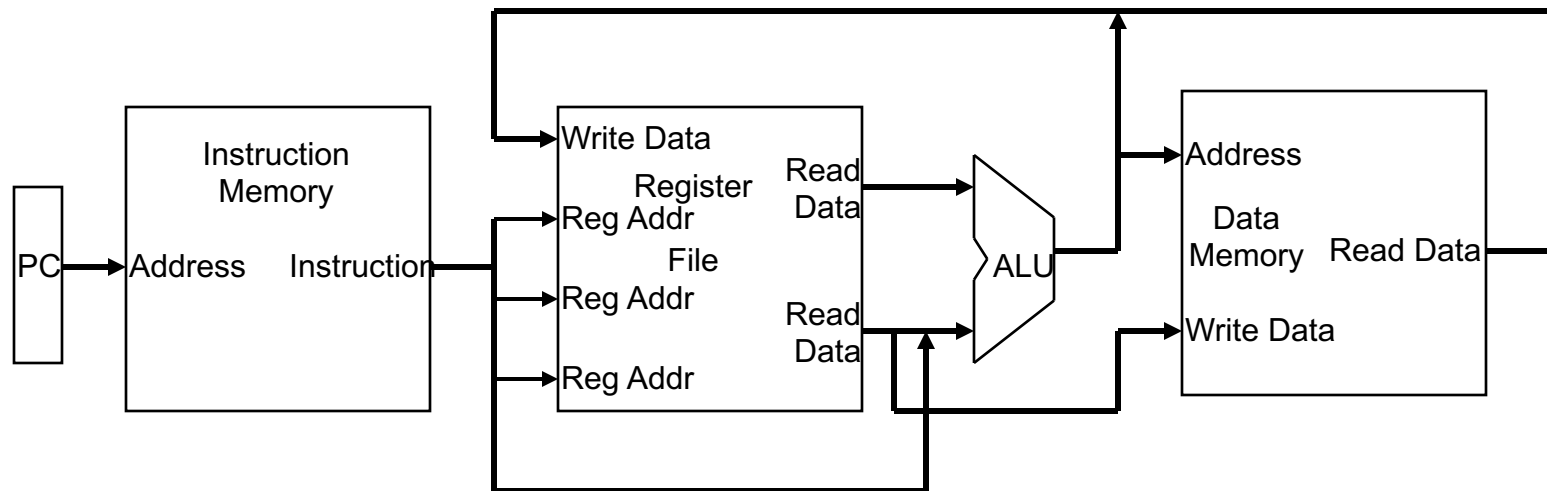
# Abstract Implementation View


- Two types of blocks:
  - Elements that operate on data values (combinational)
  - Elements that contain state (sequential)



- **Single cycle** operation
- Split memory (**Harvard**) model - one memory for instructions and one for data
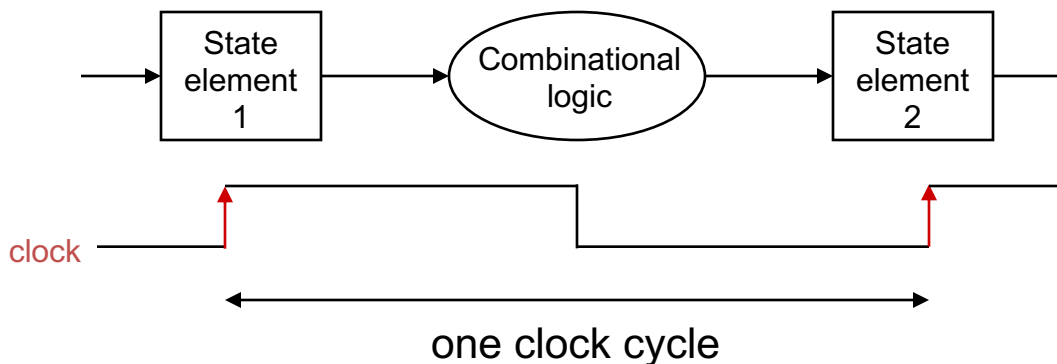
# Edge-triggered Implementation

- An edge-triggered methodology, typical execution
  - Read contents of some state elements (combinational activity, so no clock control signal needed)
  - Send values through some combinational logic
  - Write results to one or more state elements on clock edge





- Assumes state elements are written on every clock cycle; if not, need explicit write control signal
  - Write occurs only when **both** the write control is asserted and the clock edge occurs


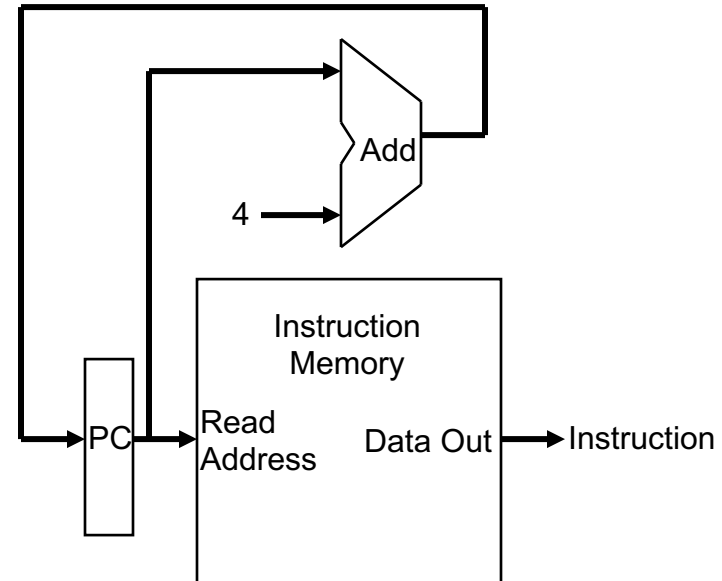 
# Fetching Instructions

- Fetching instructions involves
  - reading the instruction from the Instruction Memory
  - updating the PC value to be the address of the next (sequential) instruction



- PC is updated every clock cycle, so it does not need an explicit write control signal – just a clock signal
- Reading from the Instruction Memory is a combinational activity

# Fetching Instructions

- Fetching instructions involves
  - reading the instruction from the Instruction Memory
  - updating the PC value to be the address of the next (sequential) instruction

## **In-class Assessment!**

### **Access Code: Exams--**

**Note: sharing access code to those outside of classroom or using access while outside of classroom is considered cheating**

- PC is updated every clock cycle, so it does not need an explicit write control signal – just a clock signal
- Reading from the Instruction Memory is a combinational activity

# PC Assessment

- Consider the following instruction sequence located at (0x00400000):

begin:

**addi** \$t5, \$zero, 1195

**j** cond

loop:

**sra** \$t5, \$t5, 1

**andi** \$t6, \$t5, 0x003C

**add** \$t9, \$a0, \$t6

**sw** \$t5, 4(\$t9)

cond:


**bne** \$t5, \$zero, loop

**jr** \$s7

- What PC value fetches the `sra $t5, $t5, 1` instruction (use 0XXXXXXXXX format)?
 
# Decoding Instructions

- Decoding instructions involves
  - Sending the fetched instruction's **opcode** and **function** field bits to the control unit



- Reading two values from the Register File
  - Register File addresses are contained in the instruction

# Reading Registers “Just in Case”

- Note that both RegFile read ports are active for **all** instructions during the Decode cycle using the  $r_s$  and  $r_t$  instruction field addresses
  - Since we haven’t decoded the instruction yet, we don’t know what the instruction is!
  - *Just in case* the instruction uses values from the RegFile do “work ahead” by reading the two source operands

Which instructions *do* make use of the RegFile values?

# Reading Registers “Just in Case”

- Note that both RegFile read ports are active for **all** instructions during the Decode cycle using the  $r_s$  and  $r_t$  instruction field addresses
  - Since we haven’t decoded the instruction yet, we don’t know what the instruction is!
  - *Just in case* the instruction uses values from the RegFile do “work ahead” by reading the two source operands


Which instructions *do* make use of the RegFile values?

- Also, all instructions (except **j**) use the ALU **after** reading the registers


For what purpose? arithmetic? memory? control flow?
 
# Review: Executing R Format Operations

- R format operations (**add**, **sub**, **slt**, **and**, **or**)



 - Perform operation (**op** and **funct**) on values in **rs** and **rt**
- Store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g. **sw** or **jr**), so we need an explicit write control signal for the Register File

# Consider the `slt` Instruction

- Remember the R format instruction `slt`

```
slt $t0, $s0, $s1    # if $s0 < $s1  
                      # then $t0 = 1  
                      # else $t0 = 0
```

 - Where does the 1 (or 0) come from to store into `$t0` in the Register File at the end of the execute cycle?





# Acknowledgments

- These slides contain material developed and copyright by:
  - Joe Zambreno (Iowa State)
  - David Patterson (UC Berkeley)
  - Mary Jane Irwin (Penn State)
  - Christos Kozyrakis (Stanford)
  - Onur Mutlu (Carnegie Mellon)
  - Krste Asanović (UC Berkeley)