

# EE 330

## Lecture 27


### Small-Signal Analysis

- Examples
- Graphical Analysis

### Bipolar Processes


- Device Sizes
- Parasitic Devices
  - JFET
  - Thyristors

# Small-Signal Model of MOSFET

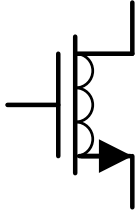

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$

$$g_o \cong \lambda I_{\text{DQ}}$$

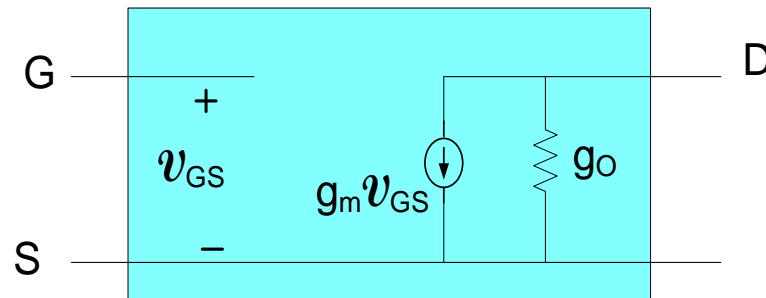

*Alternate equivalent expressions for  $g_m$ :*

$$I_{\text{DQ}} = \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2 (1 + \lambda V_{\text{DSQ}}) \cong \mu C_{\text{ox}} \frac{W}{2L} (V_{\text{GSQ}} - V_T)^2$$

$$g_m = \mu C_{\text{ox}} \frac{W}{L} (V_{\text{GSQ}} - V_T)$$


$$g_m = \sqrt{2\mu C_{\text{ox}} \frac{W}{L}} \cdot \sqrt{I_{\text{DQ}}}$$

$$g_m = \frac{2I_{\text{DQ}}}{V_{\text{GSQ}} - V_T}$$

Consider again:


Review from last lecture

## Small-signal analysis example

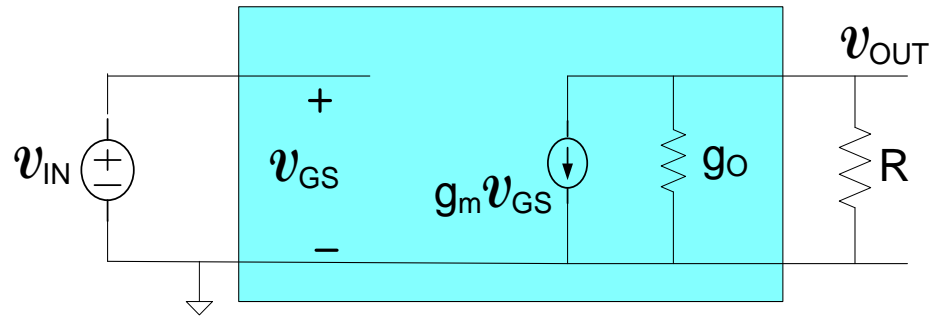

$$A_v = \frac{V_{OUT}}{V_{IN}} = -\frac{g_m}{g_o + 1/R}$$

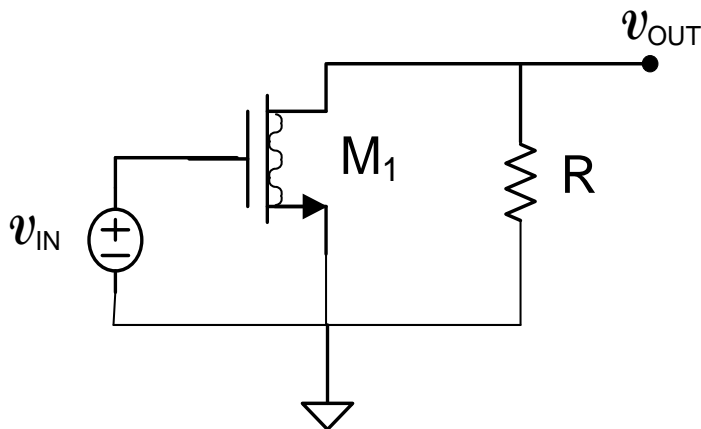For  $\lambda=0$ ,  $g_o = \lambda I_{DQ} = 0$




$$A_v = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$

- Same expression as derived before !
- More accurate gain can be obtained if  $\lambda$  effects are included and does not significantly increase complexity of small-signal analysis

Review from last lecture

# Small Signal Model of BJT

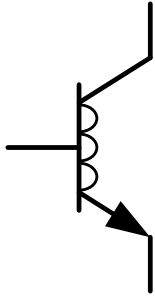

$$\begin{aligned} i_B &= y_{11} v_{BE} + y_{12} v_{CE} \\ i_C &= y_{21} v_{BE} + y_{22} v_{CE} \end{aligned}$$




$$\begin{aligned} i_B &= g_\pi v_{BE} \\ i_C &= g_m v_{BE} + g_o v_{CE} \end{aligned}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_m = \frac{I_{CQ}}{V_t}$$


$$g_o = \frac{I_{CQ}}{V_{AF}}$$

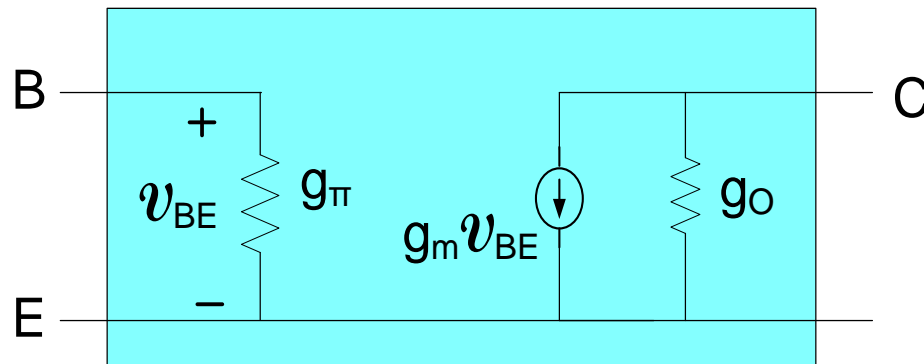

An equivalent circuit


y-parameter model using “g” parameter notation

## Review from last lecture

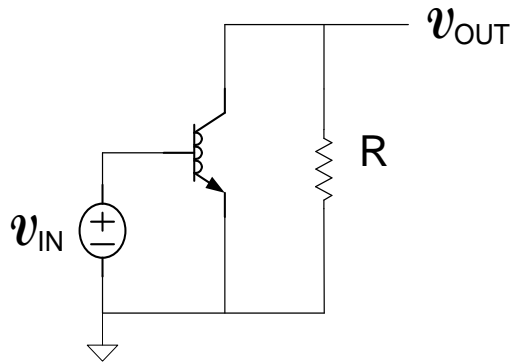

Neglect  $V_{AF}$  effects (i.e.  $V_{AF} = \infty$ ) to be consistent with earlier analysis

$$g_o = \frac{I_{CQ}}{V_{AF}} \Big|_{V_{AF} = \infty} = 0$$

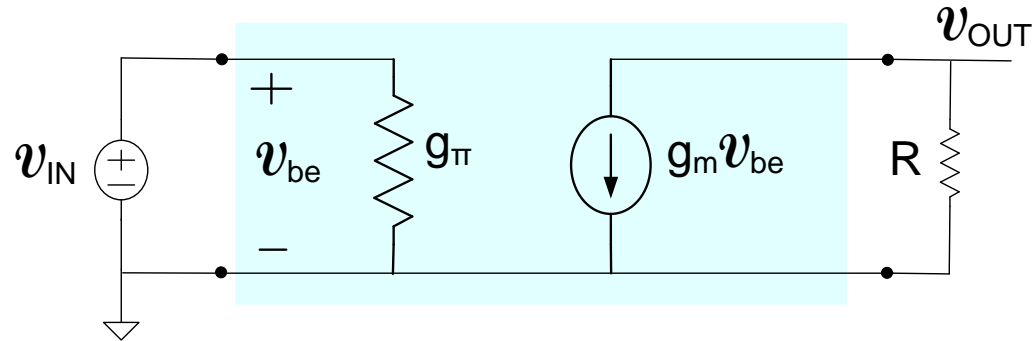

$$\left. \begin{aligned} v_{OUT} &= -g_m R v_{BE} \\ v_{IN} &= v_{BE} \end{aligned} \right\}$$


$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_m R$$

$$g_m = \frac{I_{CQ}}{V_t}$$

$$A_V = -\frac{I_{CQ} R}{V_t}$$

Note this is identical to what was obtained with the direct nonlinear analysis

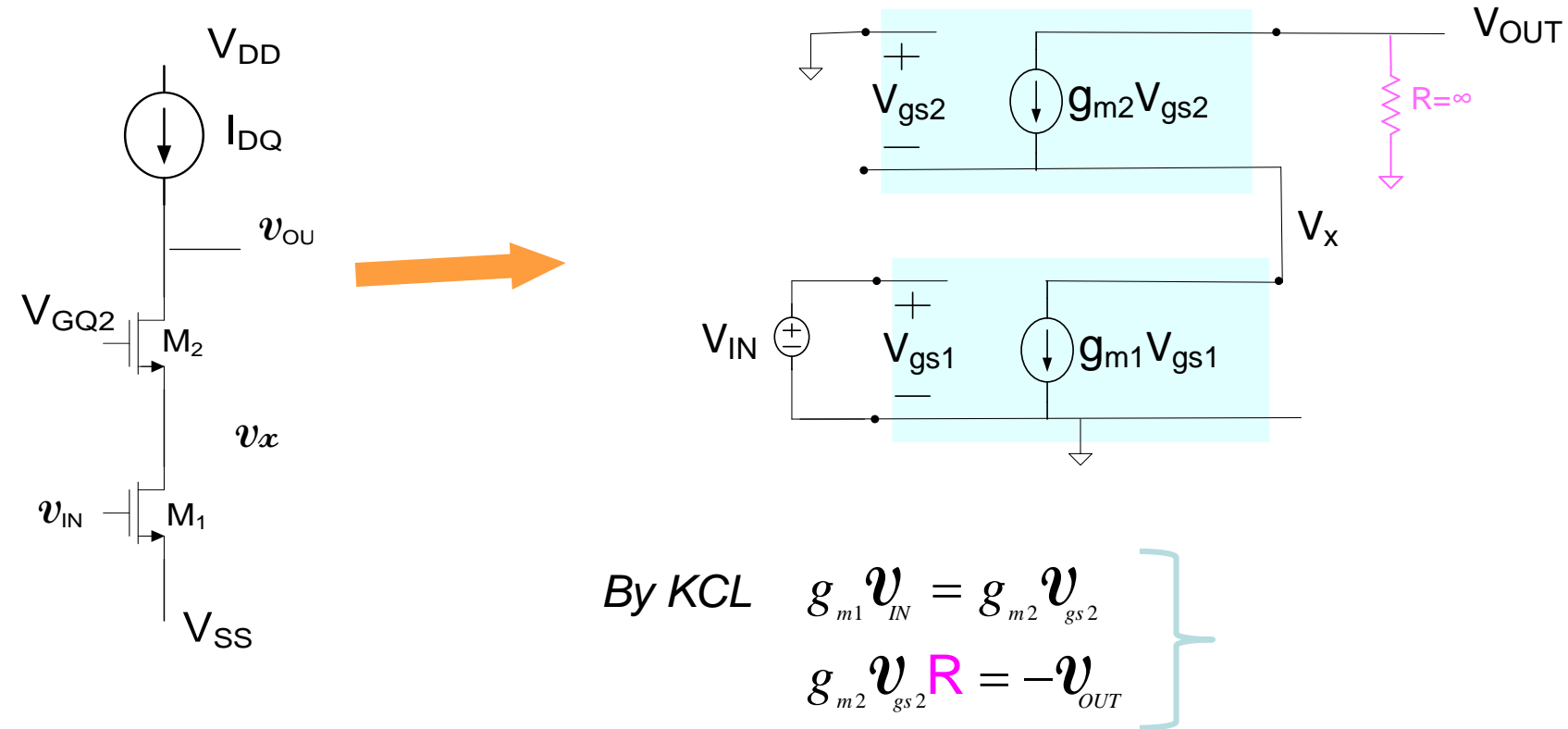
Example: Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda=0$



Solving obtain:  $A_V = \frac{v_{OUT}}{v_{IN}} = -g_{m1} R \xrightarrow{R=\infty} \infty$

Unexpectedly large, need better device models!

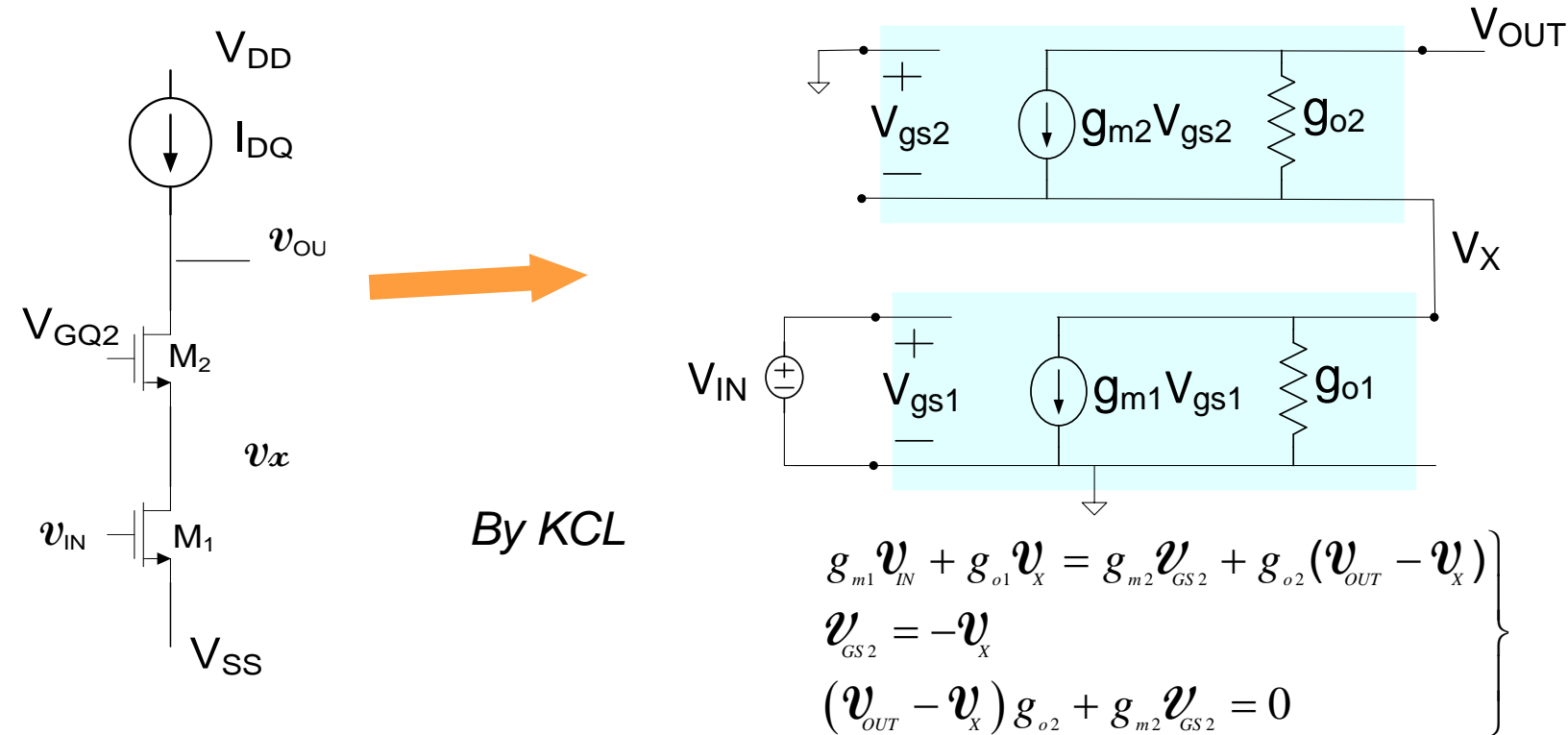Example: Determine the small signal voltage gain  $A_V = v_{OUT}/v_{IN}$ . Assume  $M_1$  and  $M_2$  are operating in the saturation region and that  $\lambda \neq 0$



$$\left. \begin{aligned} g_{m1}v_{IN} + g_{o1}v_X &= g_{m2}v_X + g_{o2}(v_{OUT} - v_X) \\ v_X &= -v_X \\ (v_{OUT} - v_X)g_{o2} + g_{m2}v_X &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} g_{m1}v_{IN} + (g_{m2} + g_{o1} + g_{o2})v_X &= g_{o2}v_{OUT} \\ v_{OUT}g_{o2} &= (g_{m2} + g_{o2})v_X \end{aligned} \right\}$$


thus:

$$A_V = \frac{v_{OUT}}{v_{IN}} = -\frac{g_{m1}g_{m2} + g_{m1}g_{o2}}{g_{o1}g_{o2}} \cong -\frac{g_{m1}}{g_{o1}} \frac{g_{m2}}{g_{o2}}$$

- Analysis is straightforward but a bit tedious
- $A_V$  is very large and would go to  $\infty$  if  $g_{o1}$  and  $g_{o2}$  were both 0
- Will look at how big this gain really is later

# Graphical Analysis and Interpretation

Consider Again

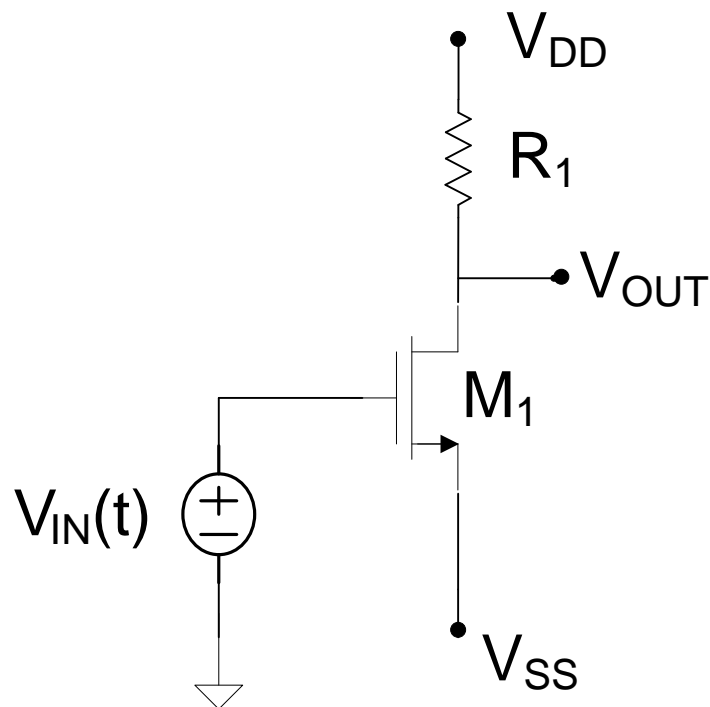

$$V_{OUT} = V_{DD} - I_D R$$



$$I_D = \frac{\mu C_{OX} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$

$$I_{DQ} = \frac{\mu C_{OX} W}{2L} (V_{SS} + V_T)^2$$


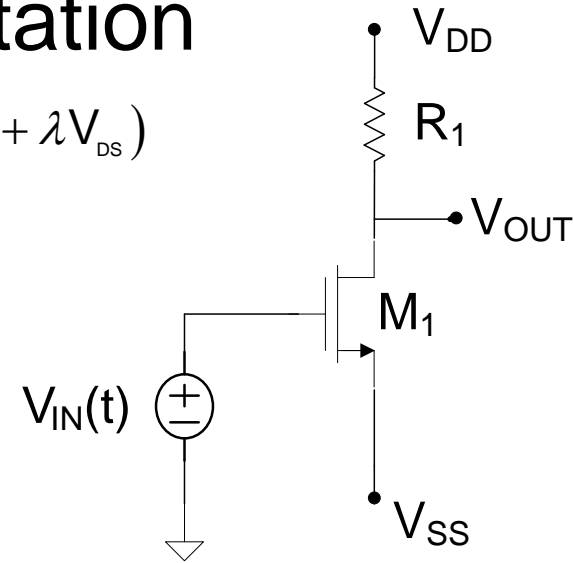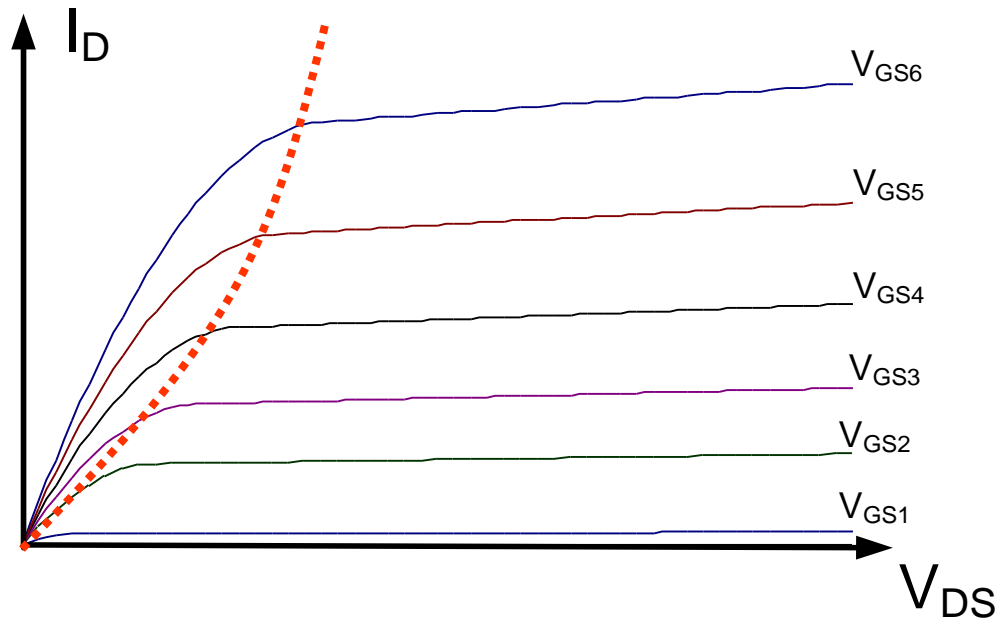
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



Load Line



Device Model




Device Model at Operating Point



$$V_{OUT} = V_{DD} - I_D R$$



$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2$$
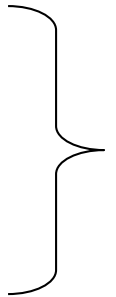
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$


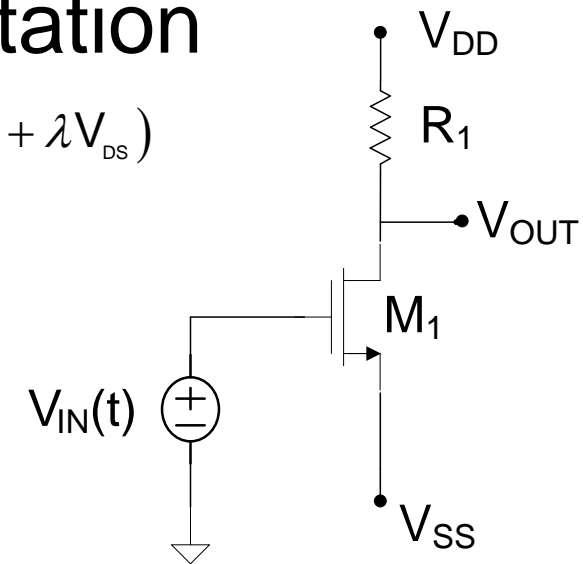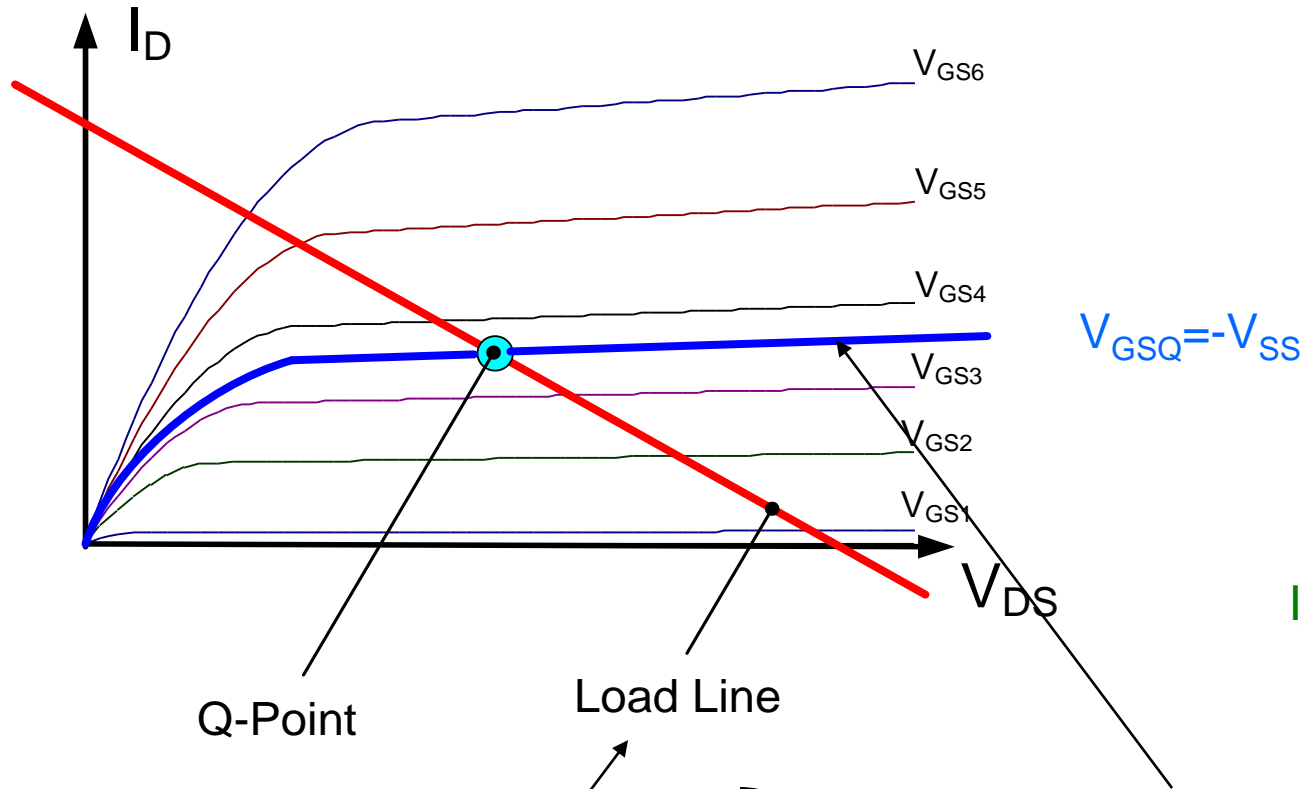
# Graphical Analysis and Interpretation

Device Model (family of curves)  $I_D = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$




$$V_{OUT} = V_{DD} - I_D R$$

$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 \quad ?$$

Must satisfy both equations  
all of the time !
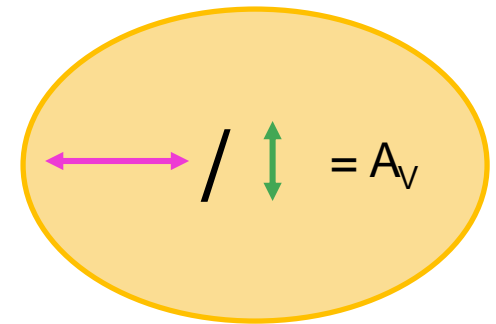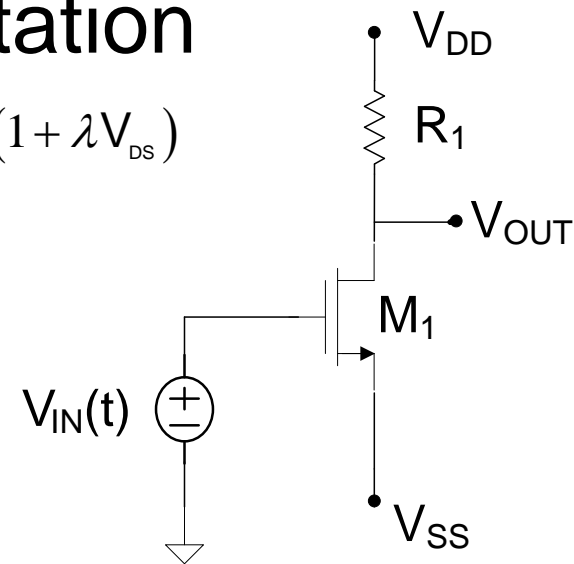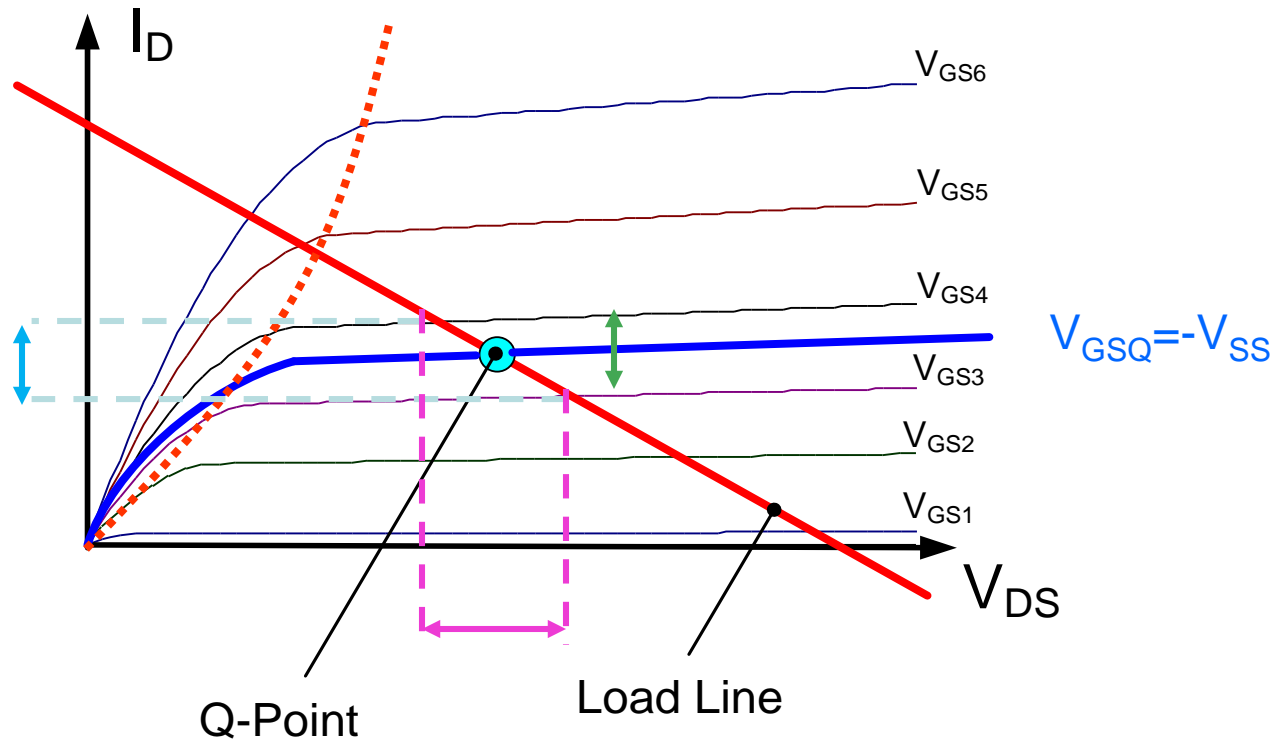
# Graphical Analysis and Interpretation



Device Model (family of curves) 
$$I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 (1 + \lambda V_{DS})$$



- As  $V_{IN}$  changes around Q-point,  $V_{IN}$  induces changes in  $V_{GS}$ . The operating point must remain on the load line!
- Small sinusoidal changes of  $V_{IN}$  will be nearly symmetric around the  $V_{GSQ}$  line
- This will cause nearly symmetric changes in both  $I_D$  and  $V_{DS}$ !
- Since  $V_{SS}$  is constant, change in  $V_{DS}$  is equal to change in  $V_{OUT}$
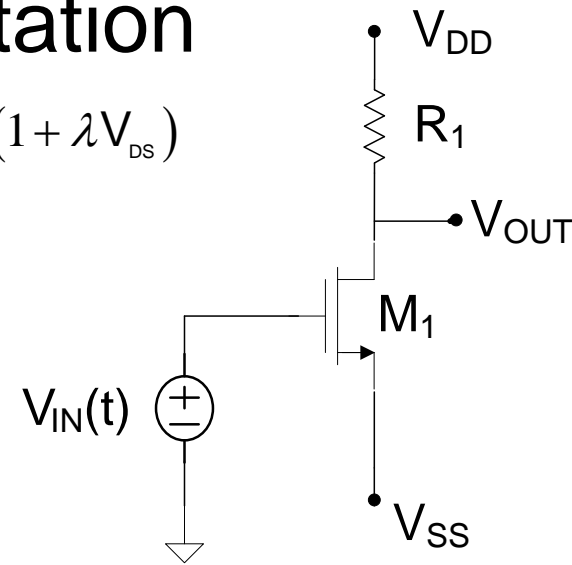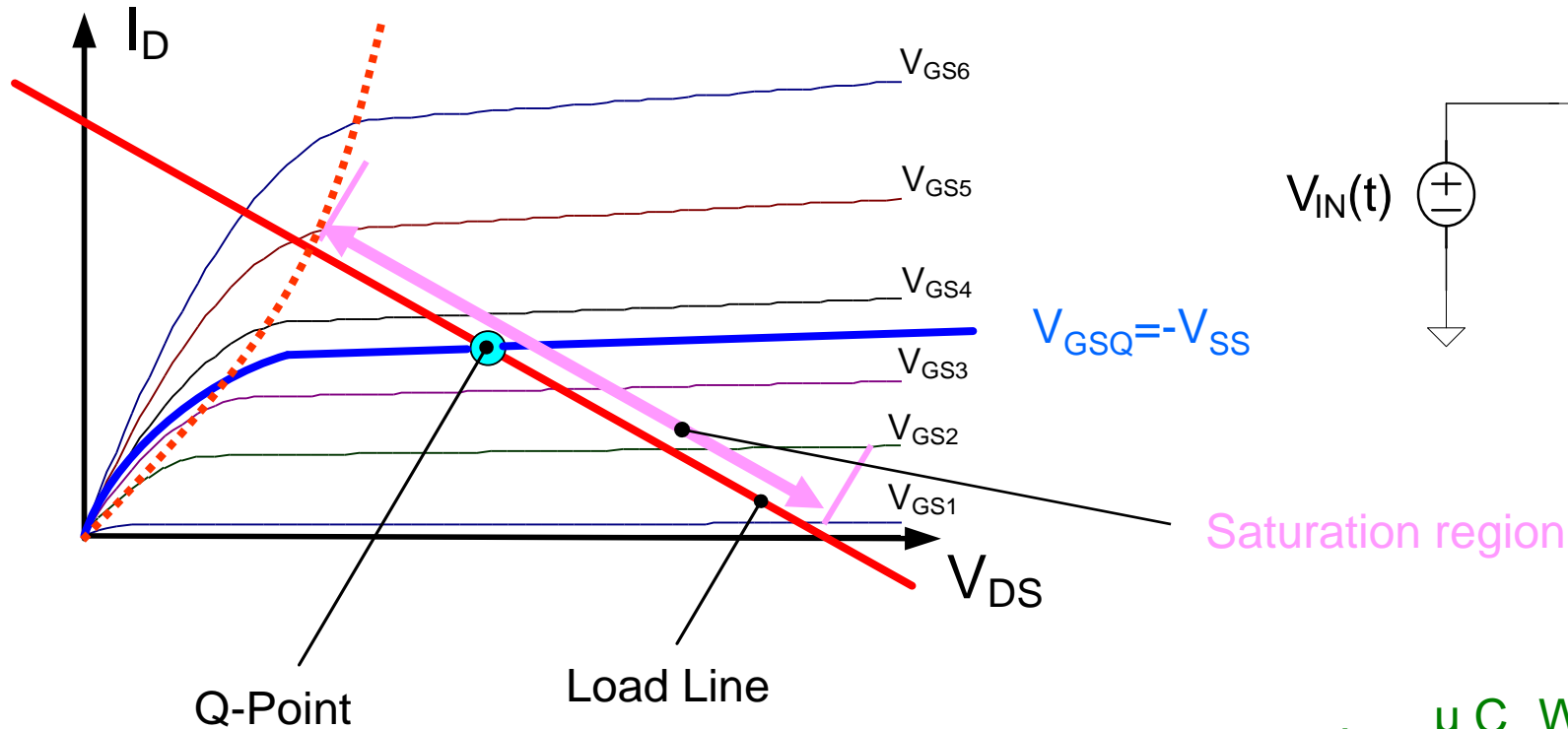
# Graphical Analysis and Interpretation

Device Model (family of curves)  $I_D = \frac{\mu C_{ox} W}{2L} (V_{IN} - V_{SS} - V_T)^2 (1 + \lambda V_{DS})$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

As  $V_{IN}$  changes around Q-point, due to changes  $V_{IN}$  induces in  $V_{GS}$ , the operating point must remain on the load line!
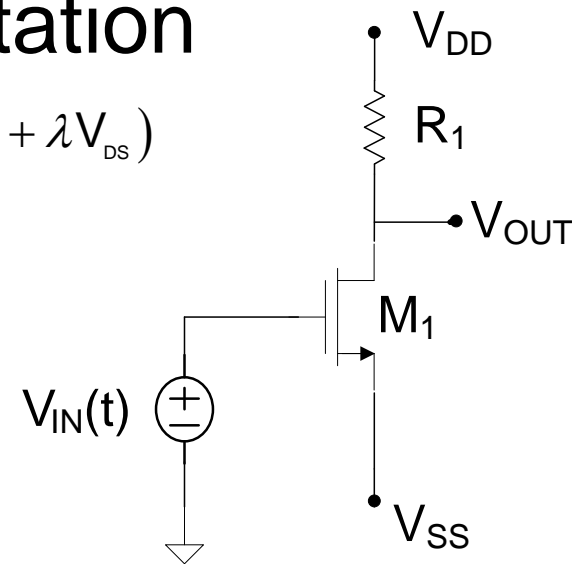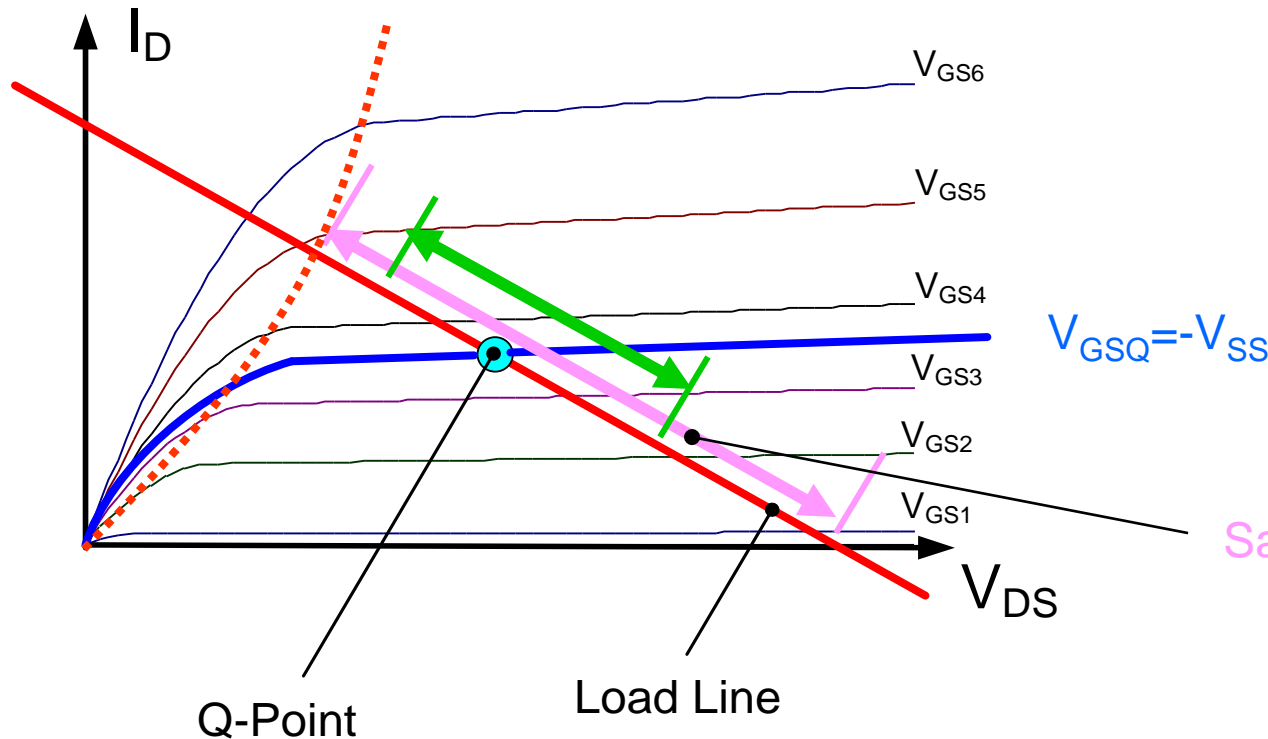
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

- Linear signal swing region smaller than saturation region
- Modest nonlinear distortion provided saturation region operation maintained
- Symmetric swing about Q-point
- Signal swing can be maximized by judicious location of Q-point
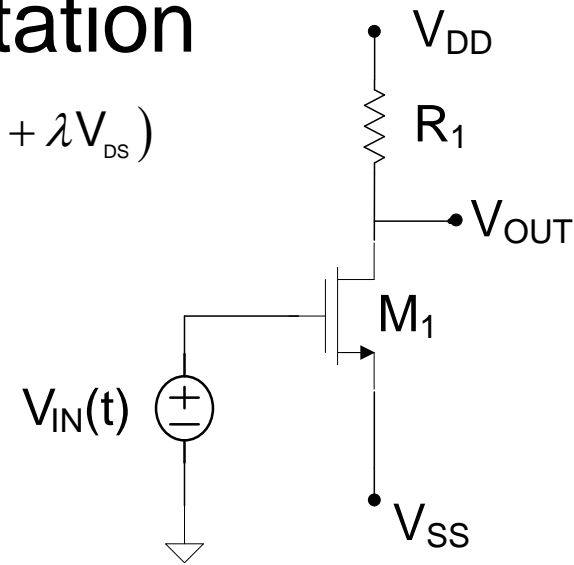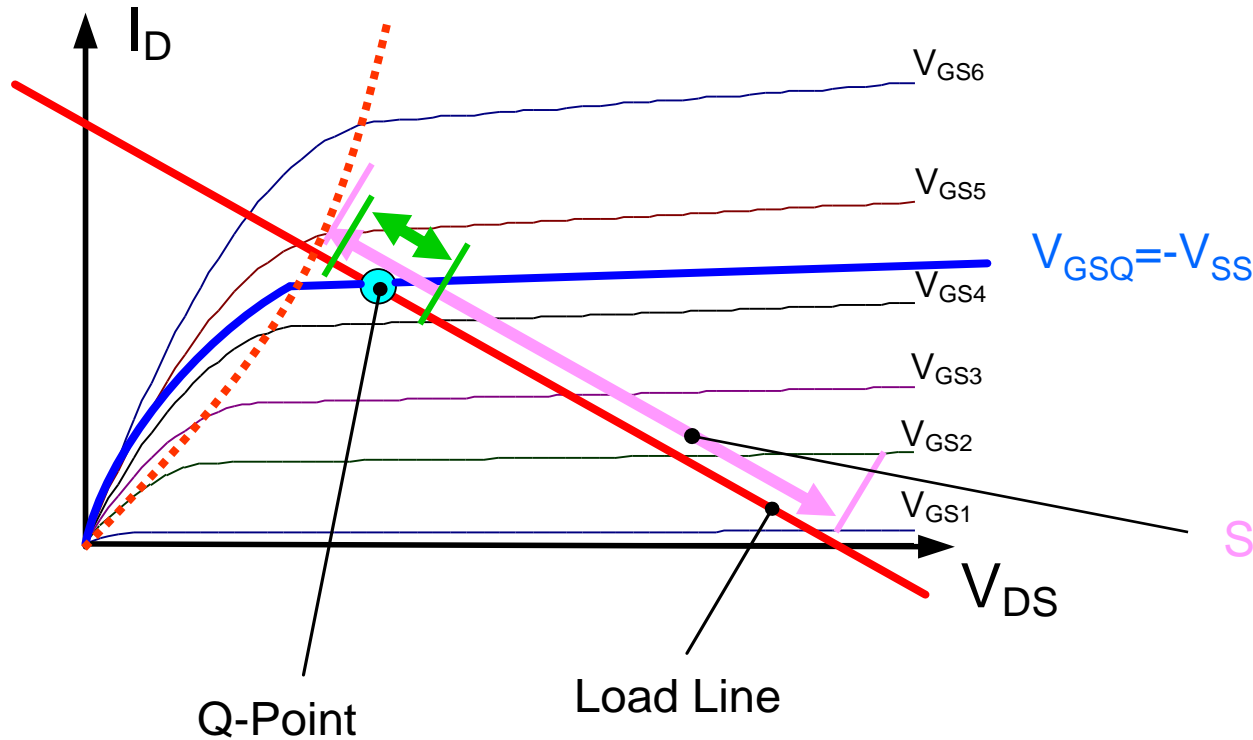
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$





$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$

Very limited signal swing with non-optimal Q-point location
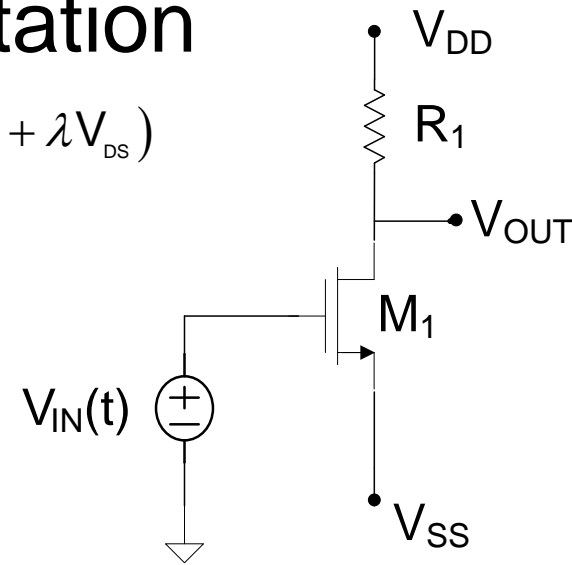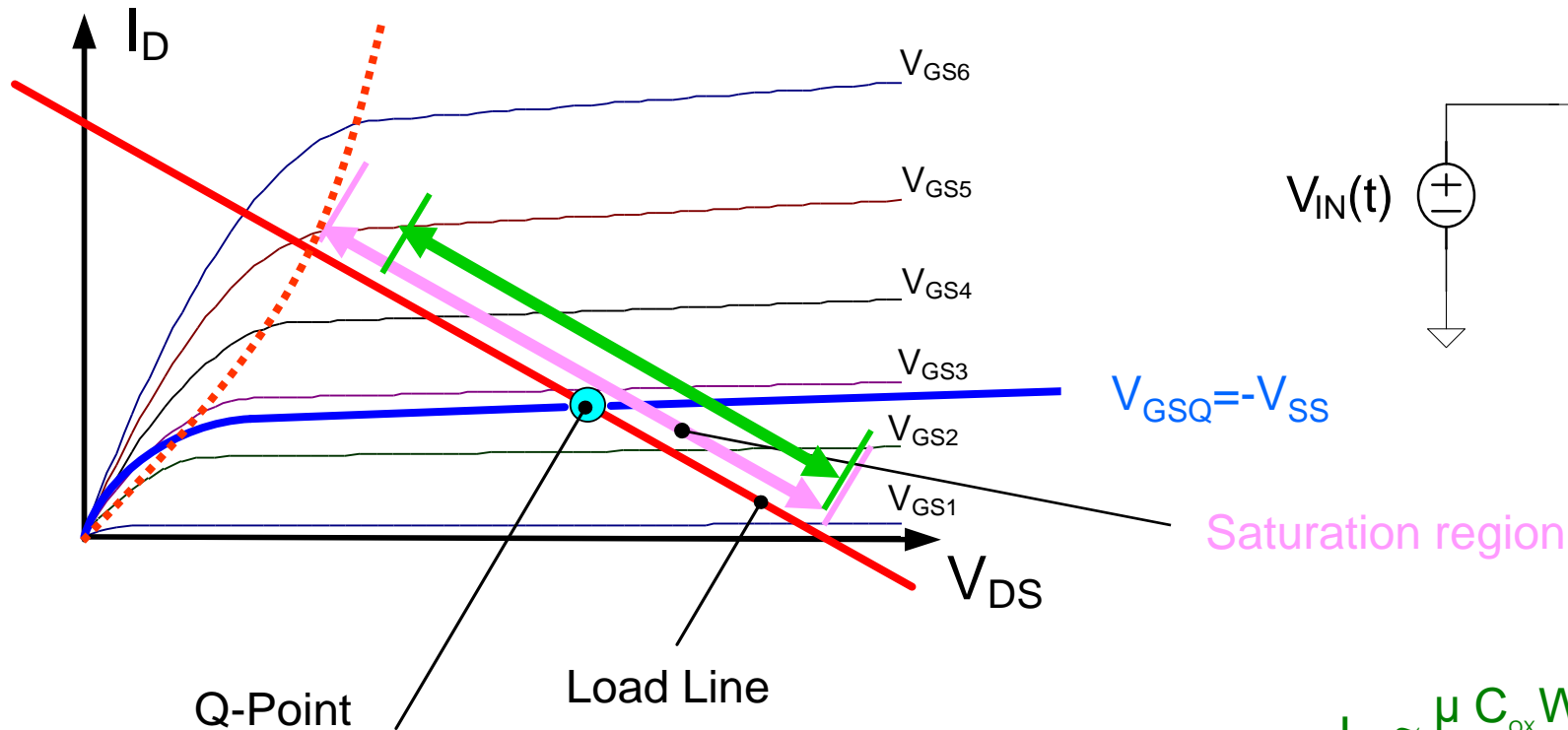
# Graphical Analysis and Interpretation

Device Model (family of curves) 
$$I_{DQ} = \frac{\mu C_{ox} W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$



$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} (V_{SS} + V_T)^2$$


- Signal swing can be maximized by judicious location of Q-point
- Often selected to be at middle of load line in saturation region
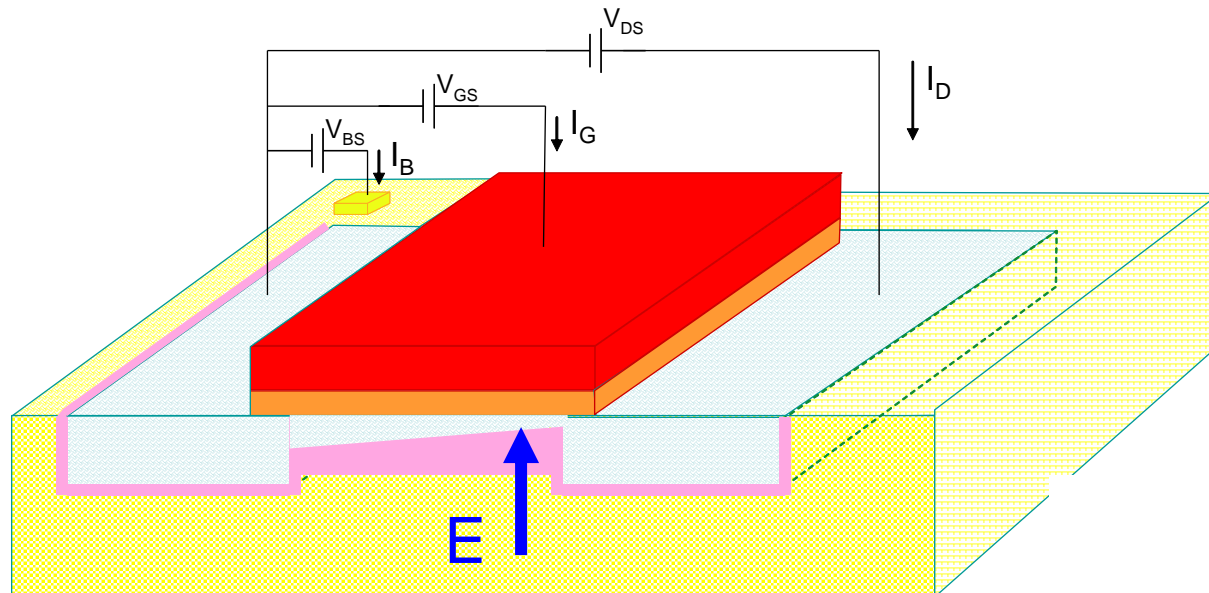
# Small-Signal MOSFET Model Extension

Existing 3-terminal small-signal model does not depend upon the bulk voltage !



**Recall** that changing the bulk voltage changes the electric field in the channel region and thus the threshold voltage!






**Recall:** Typical Effects of Bulk on Threshold Voltage for n-channel Device

$$V_T = V_{T0} + \gamma \left[ \sqrt{\phi - V_{BS}} - \sqrt{\phi} \right]$$
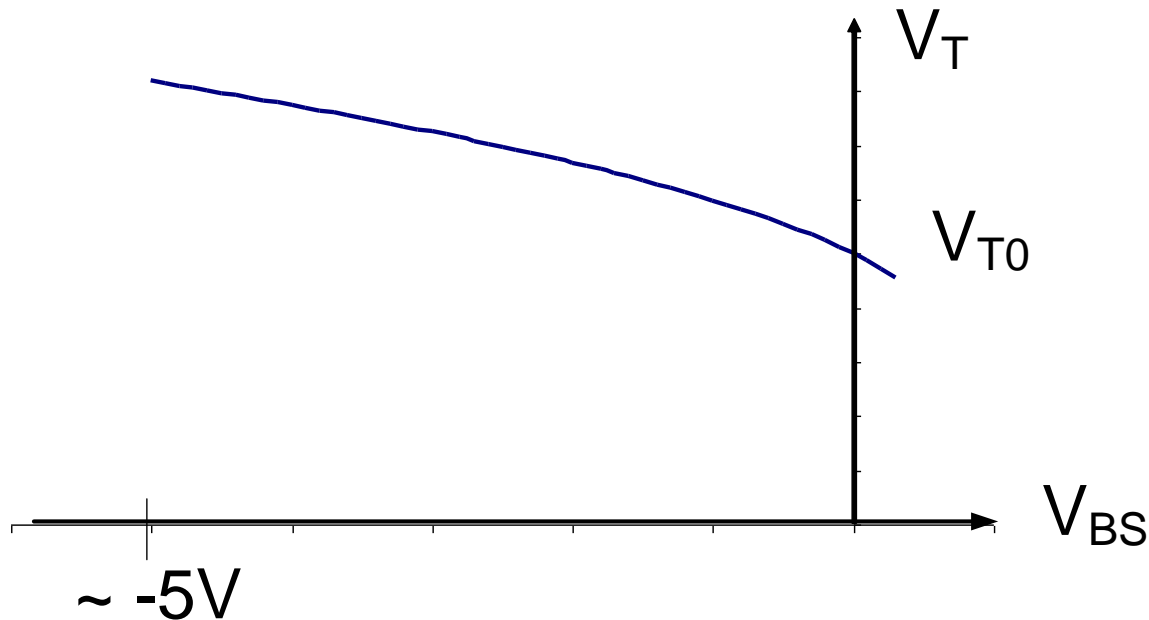
$$\gamma \cong 0.4 \text{V}^{-\frac{1}{2}} \quad \phi \cong 0.6 \text{V}$$



Bulk-Diffusion Generally Reverse Biased ( $V_{BS} < 0$  or at least less than 0.3V) for n-channel

Shift in threshold voltage with bulk voltage can be substantial


Often  $V_{BS}=0$

**Recall:** Typical Effects of Bulk on Threshold Voltage for p-channel Device

$$V_T = V_{T0} - \gamma \left[ \sqrt{\phi + V_{BS}} - \sqrt{\phi} \right]$$

$$\gamma \cong 0.4V^{-\frac{1}{2}}$$

$$\phi \cong 0.6V$$

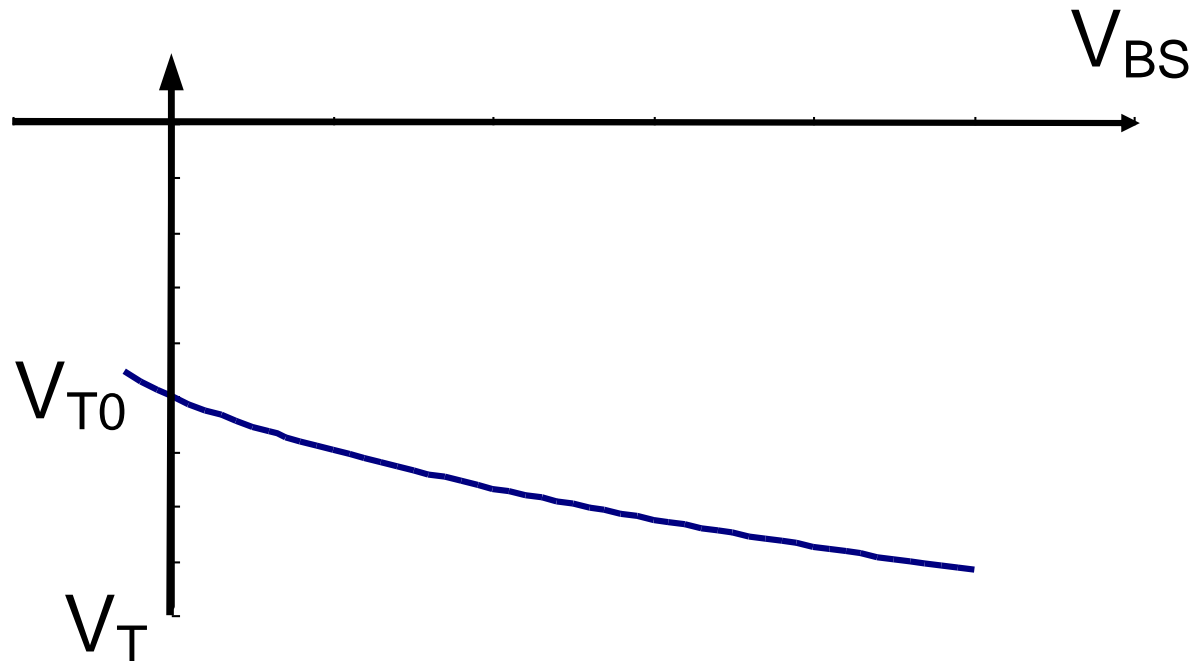

Bulk-Diffusion Generally Reverse Biased ( $V_{BS} > 0$  or at least greater than  $-0.3V$ ) for n-channel


Same functional form as for n-channel devices but  $V_{T0}$  is now negative and the magnitude of  $V_T$  still increases with the magnitude of the reverse bias

Recall:

# 4-terminal model extension

$$I_G = 0$$

$$I_B = 0$$

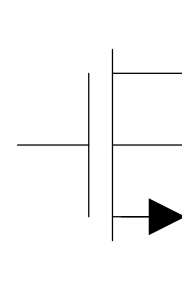

$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{ox} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T \\ \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS}) & V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T \end{cases}$$

$$V_T = V_{T0} + \gamma \left( \sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Model Parameters :  $\{\mu, C_{ox}, V_{T0}, \phi, \gamma, \lambda\}$

Design Parameters :  $\{W, L\}$  but only one degree of freedom W/L  
biasing or quiescent point

# Small-Signal 4-terminal Model Extension

$$I_G = 0$$

$$I_B = 0$$

$$I_D = \begin{cases} 0 \\ \mu C_{ox} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} \\ \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS}) \end{cases}$$

$$V_{GS} \leq V_T$$

$$V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T$$

$$V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T$$

$$V_T = V_{T0} + \gamma \left( \sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

$$y_{11} = \left. \frac{\partial I_G}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{12} = \left. \frac{\partial I_G}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{13} = \left. \frac{\partial I_G}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

$$y_{21} = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = g_m \quad y_{22} = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = g_o \quad y_{23} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = g_{mb}$$

$$y_{31} = \left. \frac{\partial I_B}{\partial V_{GS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{32} = \left. \frac{\partial I_B}{\partial V_{DS}} \right|_{\bar{V}=\bar{V}_Q} = 0 \quad y_{33} = \left. \frac{\partial I_B}{\partial V_{BS}} \right|_{\bar{V}=\bar{V}_Q} = 0$$

# Small-Signal 4-terminal Model Extension

$$I_D = \mu C_{ox} \frac{W}{2L} (V_{GS} - V_T)^2 \cdot (1 + \lambda V_{DS})$$

Definition:

$$V_{EB} = V_{GS} - V_T$$

$$V_{EBQ} = V_{GSQ} - V_{TQ}$$

$$V_T = V_{T0} + \gamma \left( \sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^1 \cdot (1 + \lambda V_{DS}) \Big|_{\vec{V}=\vec{V}_Q} \cong \mu C_{ox} \frac{W}{L} V_{EBQ}$$

Same as 3-term

$$g_o = \left. \frac{\partial I_D}{\partial V_{DS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^2 \cdot \lambda \Big|_{\vec{V}=\vec{V}_Q} \cong \lambda I_{DQ}$$


Same as 3-term

$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} = \mu C_{ox} \frac{W}{2L} 2(V_{GS} - V_T)^1 \cdot \left( -\frac{\partial V_T}{\partial V_{BS}} \right) \cdot (1 + \lambda V_{DS}) \Big|_{\vec{V}=\vec{V}_Q}$$

$$g_{mb} = \left. \frac{\partial I_D}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} \cong \mu C_{ox} \frac{W}{L} V_{EBQ} \cdot \left. \frac{\partial V_T}{\partial V_{BS}} \right|_{\vec{V}=\vec{V}_Q} = \left( \mu C_{ox} \frac{W}{L} V_{EBQ} \right) (-1) \gamma \frac{1}{2} (\phi - V_{BS})^{-\frac{1}{2}} \Big|_{\vec{V}=\vec{V}_Q} (-1)$$

$$g_{mb} \cong g_m \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}}$$

# Small Signal Model Summary

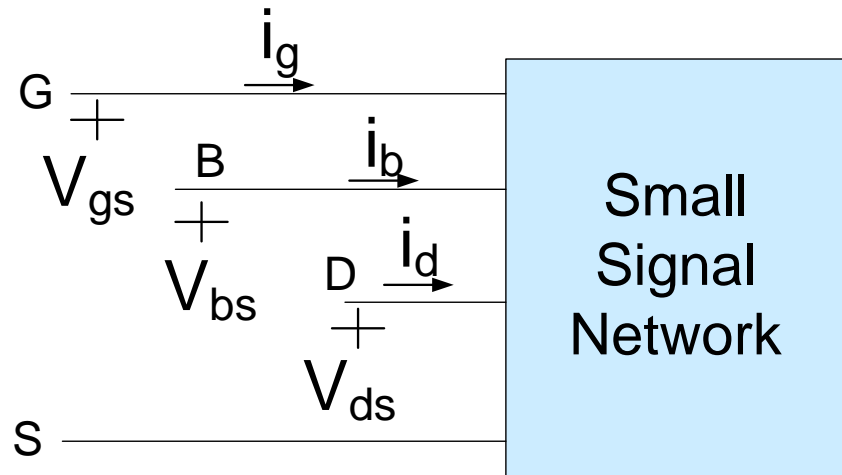

$$i_g = 0$$

$$i_b = 0$$

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

$$g_m = \frac{\mu C_{ox} W}{L} v_{EBQ}$$

$$g_o = \lambda I_{DQ}$$

$$g_{mb} = g_m \left( \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

# Relative Magnitude of Small Signal MOS Parameters

Consider:

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

3 alternate equivalent expressions for  $g_m$

$$g_m = \frac{\mu C_{ox} W}{L} V_{EBQ} \quad g_m = \sqrt{\frac{2\mu C_{ox} W}{L}} \sqrt{I_{DQ}} \quad g_m = \frac{2I_{DQ}}{V_{EBQ}}$$

If  $\mu C_{ox}=100\mu A/V^2$ ,  $\lambda=.01V^{-1}$ ,  $\gamma = 0.4V^{0.5}$ ,  $V_{EBQ}=1V$ ,  $W/L=1$ ,  $V_{BSQ}=0V$

$$I_{DQ} \cong \frac{\mu C_{ox} W}{2L} V_{EBQ}^2 = \frac{10^{-4} W}{2L} (1V)^2 = 5E-5$$

$$g_m = \frac{\mu C_{ox} W}{L} V_{EBQ} = 1E-4$$

$$g_o = \lambda I_{DQ} = 5E-7$$

$$g_{mb} = g_m \left( \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right) = .26g_m$$

In this example

$$g_o \ll g_m, g_{mb}$$

$$g_{mb} < g_m$$


This relationship is common

In many circuits,  $v_{BS}=0$  as well

- Often the  $g_o$  term can be neglected in the small signal model because it is so small
- Be careful about neglecting  $g_o$  prior to obtaining a final expression

# Large and Small Signal Model Summary

Large Signal Model

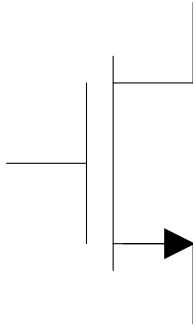


$$I_D = \begin{cases} 0 & V_{GS} \leq V_T \\ \mu C_{OX} \frac{W}{L} \left( V_{GS} - V_T - \frac{V_{DS}}{2} \right) V_{DS} & V_{GS} \geq V_T \quad V_{DS} < V_{GS} - V_T \\ \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2 \bullet (1 + \lambda V_{DS}) & V_{GS} \geq V_T \quad V_{DS} \geq V_{GS} - V_T \end{cases}$$

saturation

$$V_T = V_{T0} + \gamma \left( \sqrt{\phi - V_{BS}} - \sqrt{\phi} \right)$$

Small Signal Model

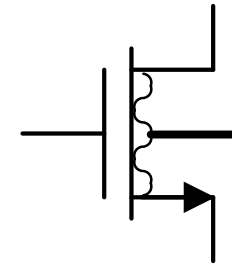

saturation

$$i_g = 0$$

$$i_b = 0$$

$$i_d = g_m v_{gs} + g_{mb} v_{bs} + g_o v_{ds}$$

where

$$g_m = \frac{\mu C_{OX} W}{L} V_{EBQ}$$


$$g_{mb} = g_m \left( \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

$$g_o = \lambda I_{DQ}$$



# Large and Small Signal Model Summary

## Large Signal Model

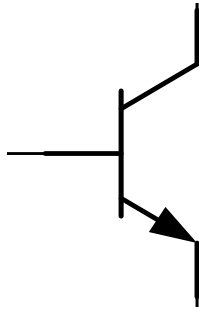

$$I_C = \beta I_B \left( 1 + \frac{V_{CE}}{V_{AF}} \right)$$

$$I_B = \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}}$$

$$V_{BE} > 0.4V$$

$$V_{BC} < 0$$

Forward Active

$$V_{BE} = 0.7V$$

$$V_{CE} = 0.2V$$


$$I_C < \beta I_B$$

$$I_C = I_B = 0$$

$$V_{BE} < 0$$

$$V_{BC} < 0$$

## Small Signal Model

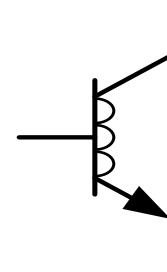

Forward Active

$$i_b = g_\pi v_{be}$$

$$i_c = g_m v_{be} + g_o v_{ce}$$

where

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$


$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

# Relative Magnitude of Small Signal BJT Parameters

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

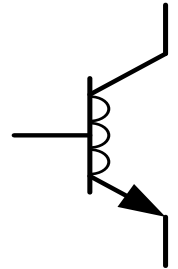

$$\frac{g_m}{g_\pi} = \frac{\left[ \frac{I_Q}{V_t} \right]}{\left[ \frac{I_Q}{\beta V_t} \right]}$$

$$\frac{g_\pi}{g_o} = \frac{\left[ \frac{I_Q}{\beta V_t} \right]}{\left[ \frac{I_Q}{V_{AF}} \right]}$$

$$g_m \gg g_\pi \gg g_o$$


Often the  $g_o$  term can be neglected in the small signal model because it is so small

# Relative Magnitude of Small Signal Parameters

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$

$$g_o \approx \frac{I_{CQ}}{V_{AF}}$$

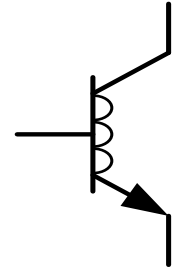


$$\frac{g_m}{g_\pi} = \frac{\left[ \frac{I_Q}{V_t} \right]}{\left[ \frac{I_Q}{\beta V_t} \right]} = \beta$$

$$\frac{g_\pi}{g_o} = \frac{\left[ \frac{I_Q}{\beta V_t} \right]}{\left[ \frac{I_Q}{V_{AF}} \right]} = \frac{V_{AF}}{\beta V_t} \approx \frac{200V}{100 \cdot 26mV} = 77$$



$$g_m \gg g_\pi \gg g_o$$

- Often the  $g_o$  term can be neglected in the small signal model because it is so small
- Be careful about neglecting  $g_o$  prior to obtaining a final expression
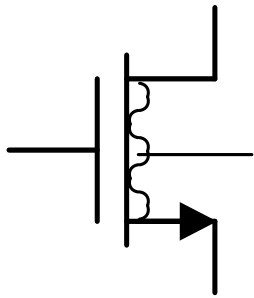
# Small Signal Model Simplifications for the MOSFET and BJT



MOSFET

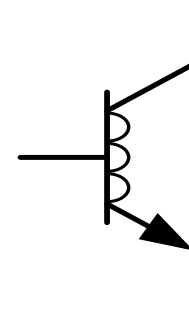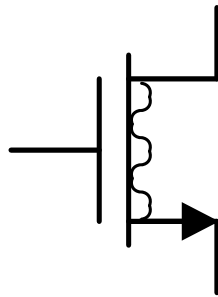


BJT


Often simplifications of the small signal model are adequate for a given application

These simplifications will be discussed next

# Small Signal MOSFET Model Summary

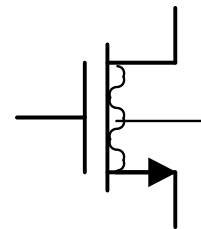

An equivalent Circuit:

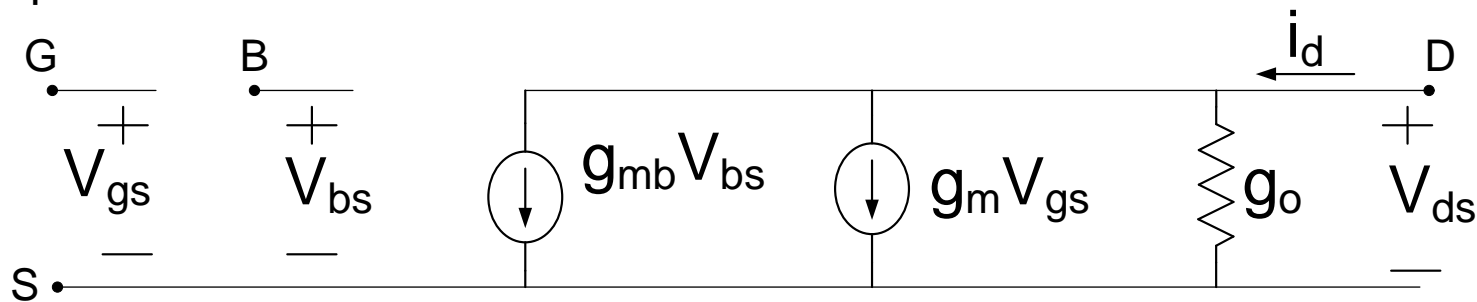

$$g_m = \frac{\mu C_{OX} W}{L} (V_{GSQ} - V_T)$$

$$g_o = \lambda I_{DQ}$$

$$g_{mb} = g_m \left( \frac{\gamma}{2\sqrt{\phi - V_{BSQ}}} \right)$$

**Alternate equivalent representations for  $g_m$**  from  $I_D \cong \mu C_{OX} \frac{W}{2L} (V_{GS} - V_T)^2$



$$g_m = \sqrt{\frac{2\mu C_{OX} W}{L}} \sqrt{I_{DQ}}$$

$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} = \frac{2I_{DQ}}{V_{EBQ}}$$


$$g_{mb} < g_m$$

$$g_o \ll g_m, g_{mb}$$



# Small Signal Model Simplifications

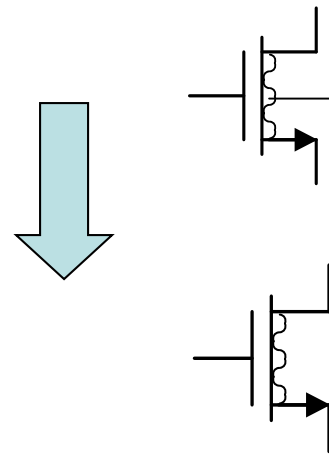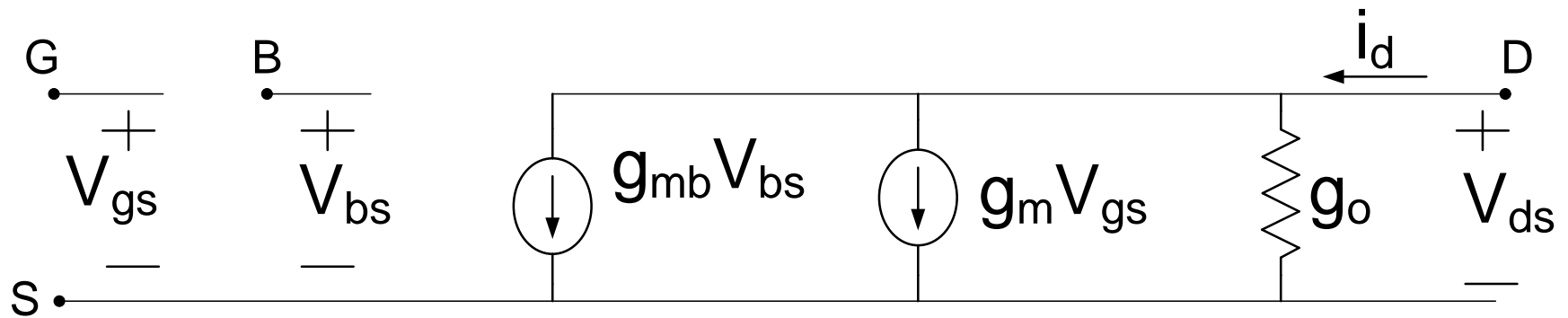

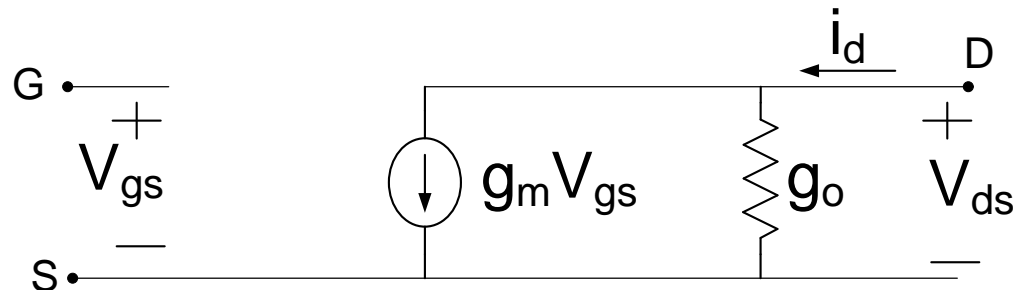
**Simplification that is often adequate**



# Small Signal Model Simplifications

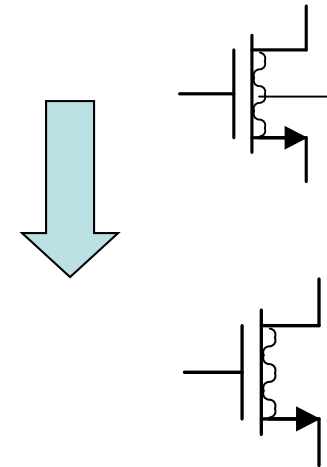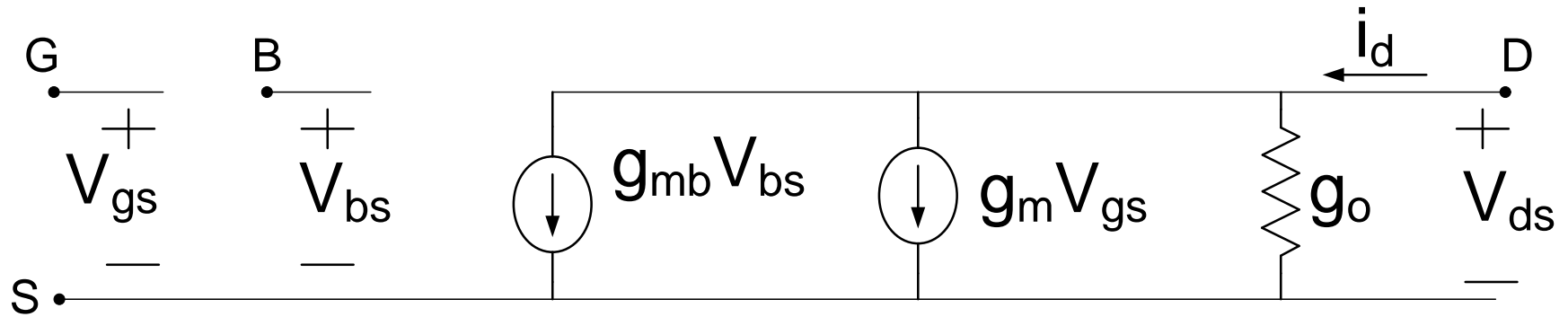


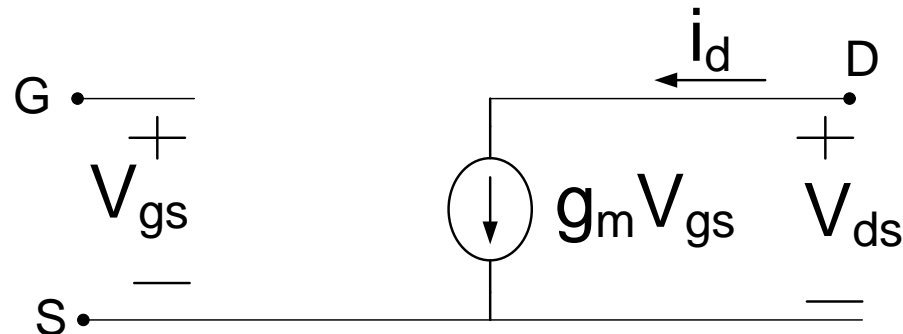Even further simplification that is often adequate



# Small Signal BJT Model Summary

An equivalent circuit

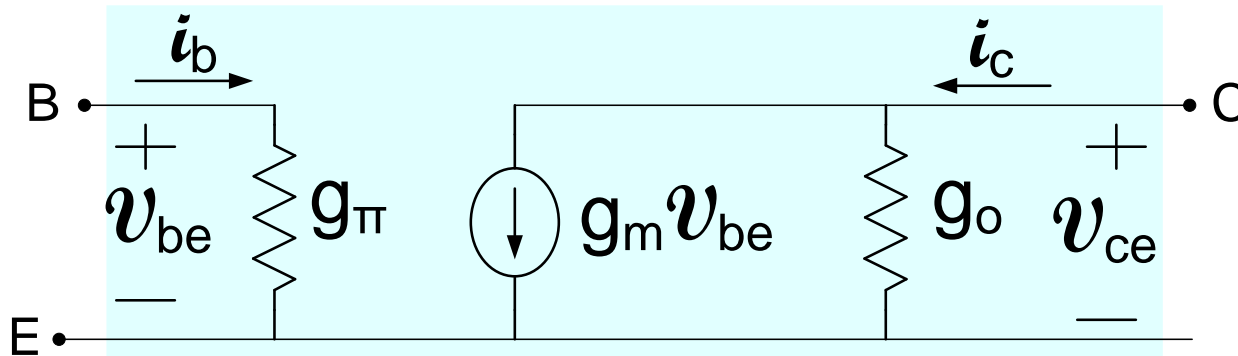

$$g_m = \frac{I_{CQ}}{V_t}$$

$$g_\pi = \frac{I_{CQ}}{\beta V_t}$$




$$g_o \cong \frac{I_{CQ}}{V_{AF}}$$

$$g_m \gg g_\pi \gg g_o$$


This contains absolutely no more information than the set of small-signal model equations



# Small Signal BJT Model Simplifications

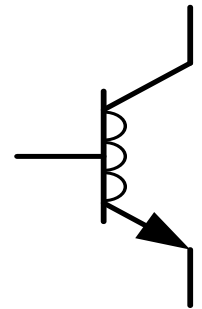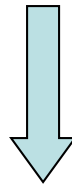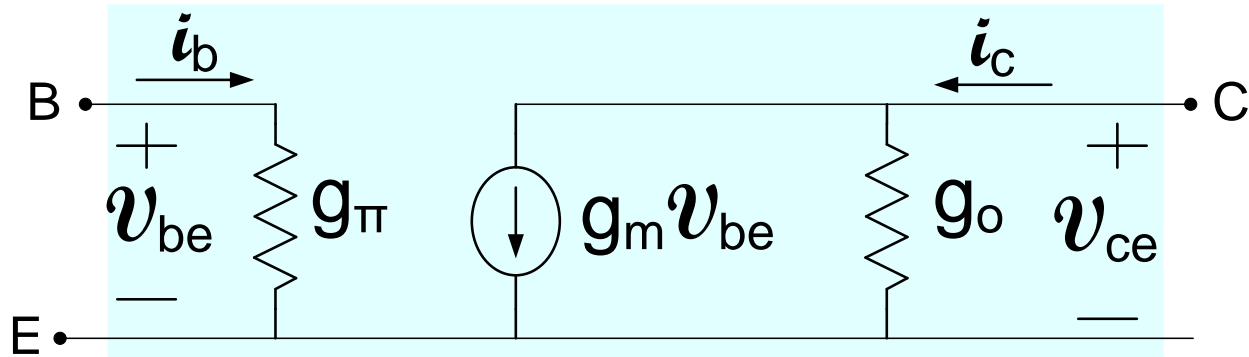


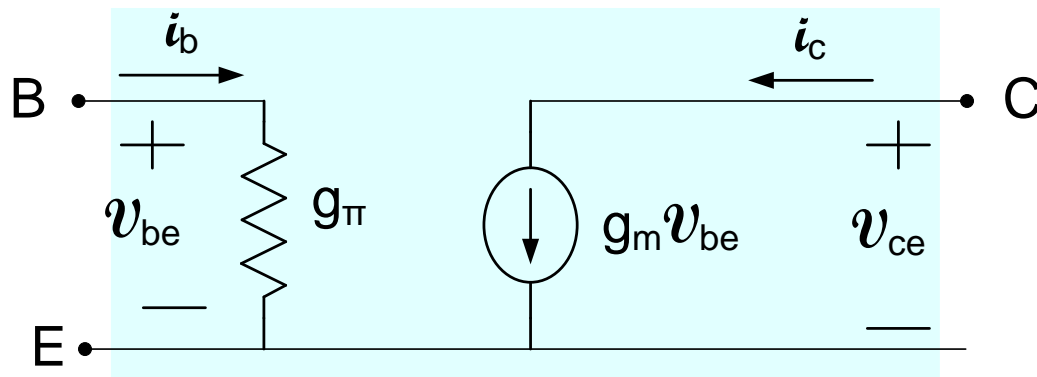**Simplification that is often adequate**




# Gains for MOSFET and BJT Circuits


## BJT

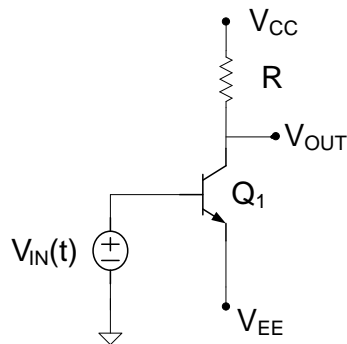


$$A_{VB} = -\frac{I_{CQ} R_1}{V_t}$$

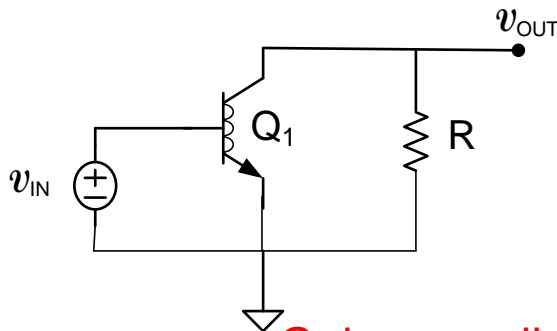

## MOSFET

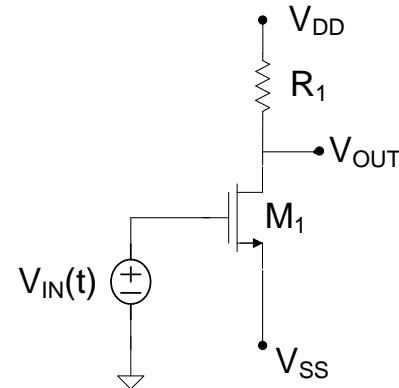
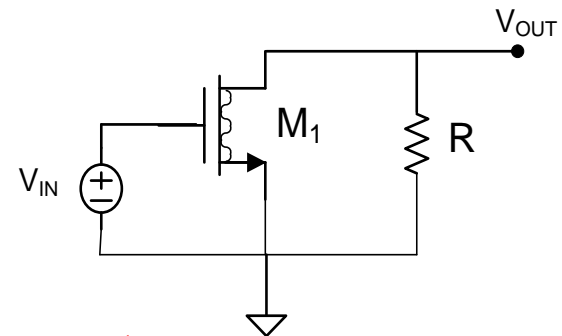
$$A_{VM} = \frac{2I_{DQ} R}{[V_{SS} + V_T]}$$



For both circuits


$$A_v = -g_m R$$

Gains vary linearly with small signal parameter  $g_m$

Power is often a key resource in the design of an integrated circuit

In both circuits, power is proportional to  $I_{CQ}$ ,  $I_{DQ}$

# How does $g_m$ vary with $I_{DQ}$ ?

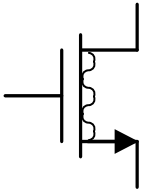

$$g_m = \sqrt{\frac{2\mu C_{ox} W}{L}} \sqrt{I_{DQ}}$$

Varies with the square root of  $I_{DQ}$

$$g_m = \frac{2I_{DQ}}{V_{GSQ} - V_T} = \frac{2I_{DQ}}{V_{EBQ}}$$

Varies linearly with  $I_{DQ}$

$$g_m = \frac{\mu C_{ox} W}{L} (V_{GSQ} - V_T)$$


Doesn't vary with  $I_{DQ}$

# How does $g_m$ vary with $I_{DQ}$ ?


All of the above are true – but with qualification

$g_m$  is a function of more than one variable ( $I_{DQ}$ ) and how it varies depends upon how the remaining variables are constrained

# Amplifier Biasing (precursor)

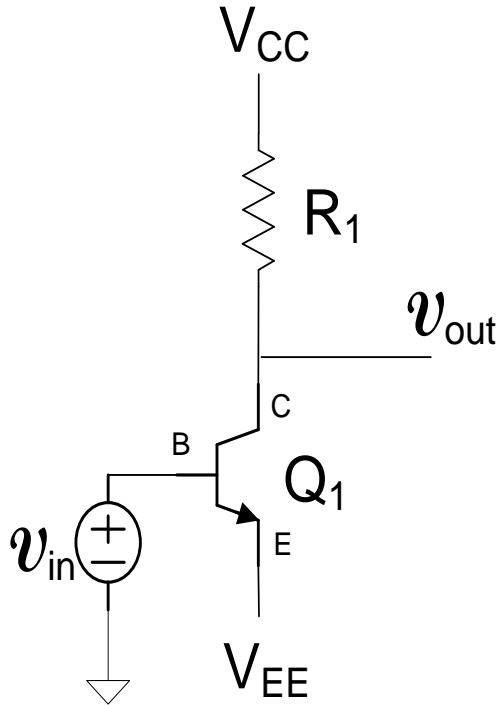

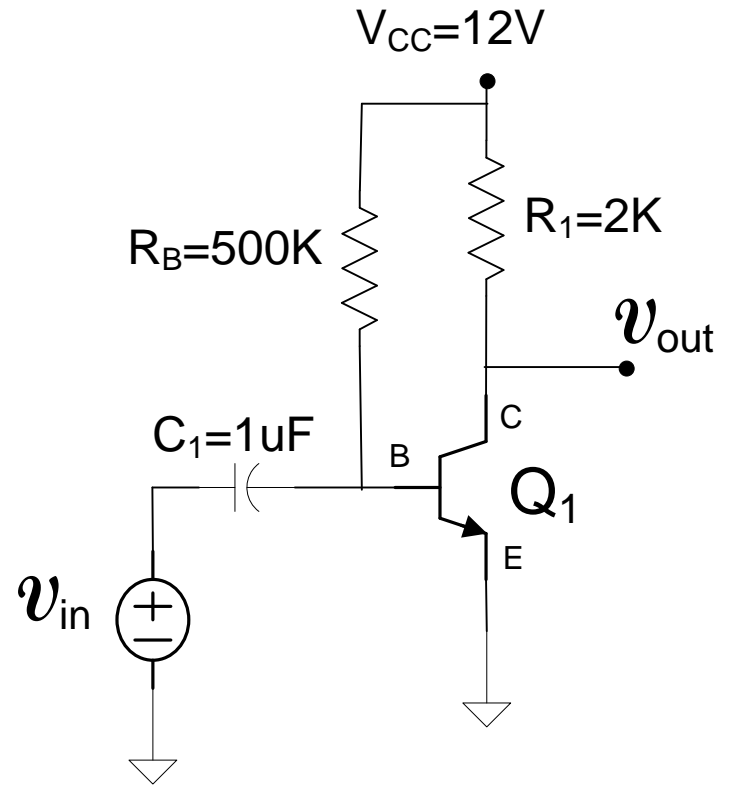Not convenient to have multiple dc power supplies  
 $V_{OUTQ}$  very sensitive to  $V_{EE}$





Single power supply  
Additional resistor and capacitor



Compare the small-signal equivalent circuits of these two structures

Compare the small-signal voltage gain of these two structures

# Amplifier Biasing (precursor)

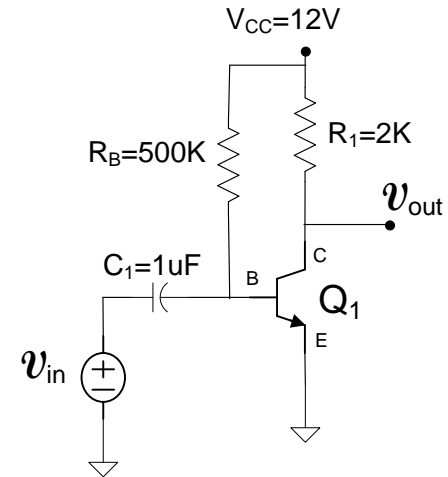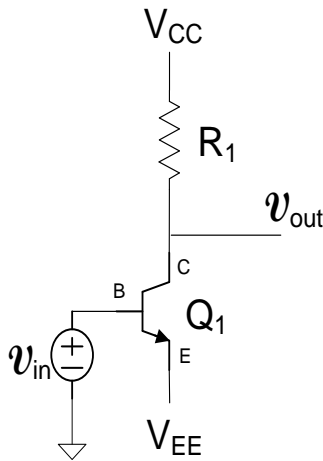

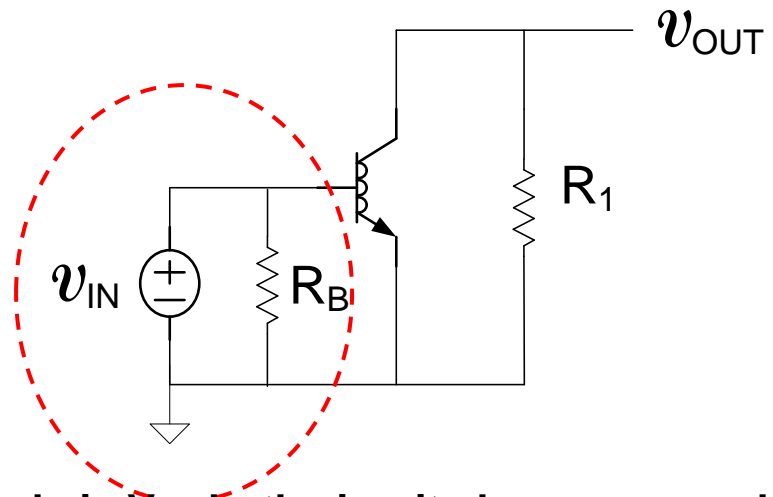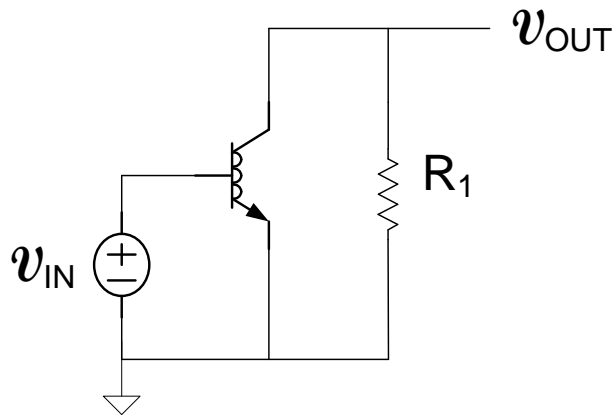Compare the small-signal equivalent circuits of these two structures



Since Thevenin equivalent circuit in red circle is  $V_{IN}$ , both circuits have same voltage gain


But the load placed on  $V_{IN}$  is different

**Method of characterizing the amplifiers is needed to assess impact of difference**
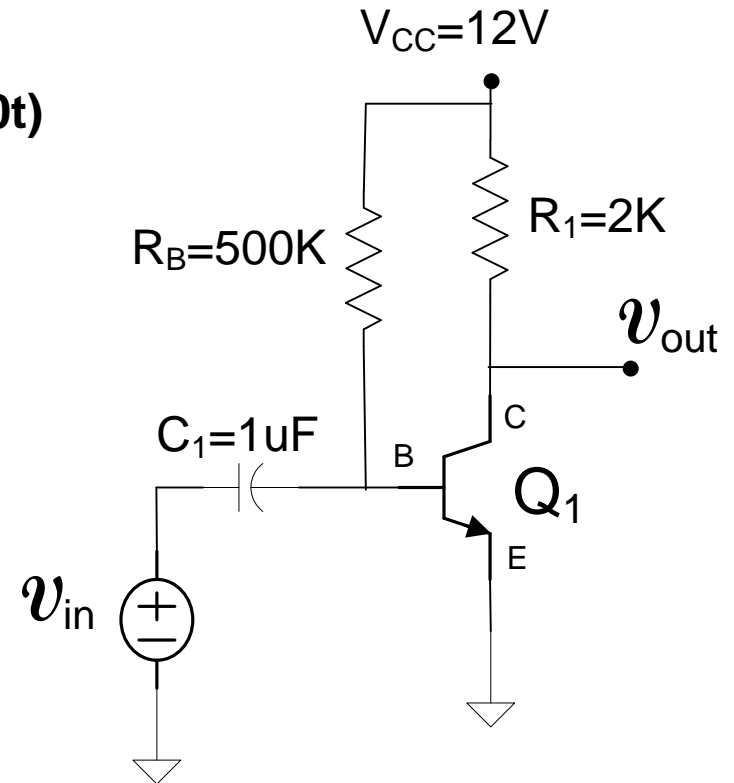
# Amplifier Characterization (an example)

Determine  $V_{OUTQ}$ ,  $A_V$ ,  $R_{IN}$

Determine  $v_{OUT}$  and  $V_{OUT}(t)$  if  $v_{IN}=.002\sin(400t)$



In the following slides we will analyze this circuit

End of Lecture 27