

# EE 330

## Lecture 19

Bipolar Device Operation and Modeling

Exam 2 Friday Oct 25

Exam 3 Friday Nov 22


**TABLE 2B.1**

**Process scenario of major process steps in typical n-well CMOS process<sup>a</sup>**

---


1.	Clean wafer	
2.	GROW THIN OXIDE	
3.	Apply photoresist	
4.	PATTERN n-well	(MASK #1)
5.	Develop photoresist	
6.	Deposit and diffus n-type impurities	
7.	Strip photoresist	
8.	Strip thin oxide	
9.	Grow thin oxide	
10.	Apply layer of Si <sub>3</sub> N <sub>4</sub>	
11.	Apply photoresist	
12.	PATTERN Si <sub>3</sub> N <sub>4</sub> (active area definition)	(MASK #2)
13.	Develop photoresist	
14.	Etch Si <sub>3</sub> N <sub>4</sub>	
15.	Strip photoresist	
	<i>Optional field threshold voltage adjust</i>	
	A.1 Apply photoresist	
	A.2 PATTERN ANTIMOAT IN SUBSTRATE	(MASK #A1)
	A.3 Develop photoresist	
	A.4 FIELD IMPLANT p-type)	
	A.5 Strip photoresist	
16.	GROW FIELD OXIDE	
17.	Strip Si <sub>3</sub> N <sub>4</sub>	
18.	Strip thin oxide	
19.	GROW GATE OXIDE	
20.	POLYSILICON DEPOSITION (POLY I)	
21.	Apply photoresist	
22.	PATTERN POLYSILICON	(MASK #3)
23.	Develop photoresist	
24.	ETCH POLYSILICON	

Review from last lecture

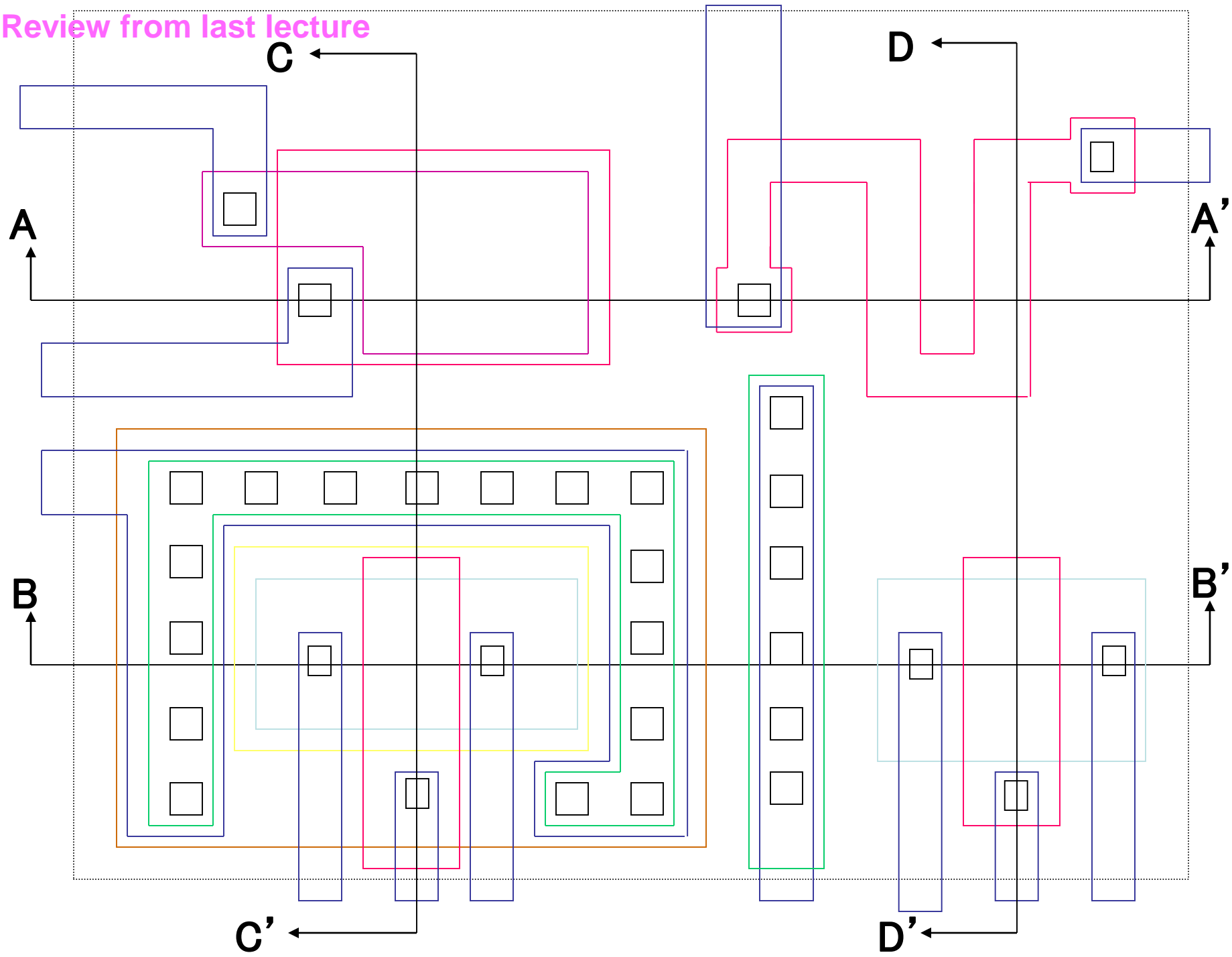


Review from last lecture

## Metal Mask

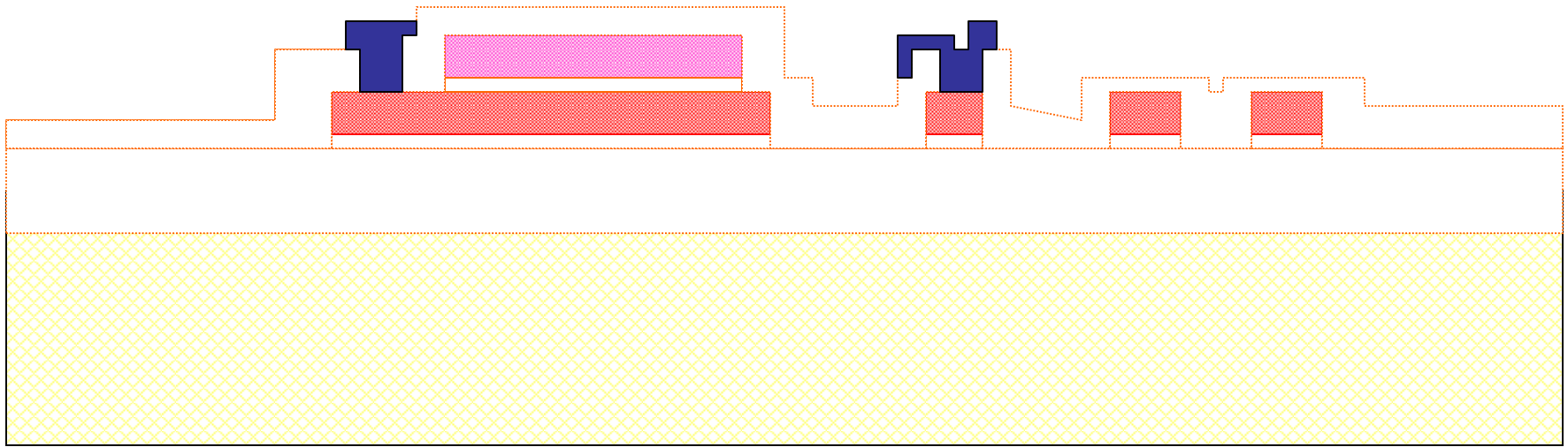

A-A' Section

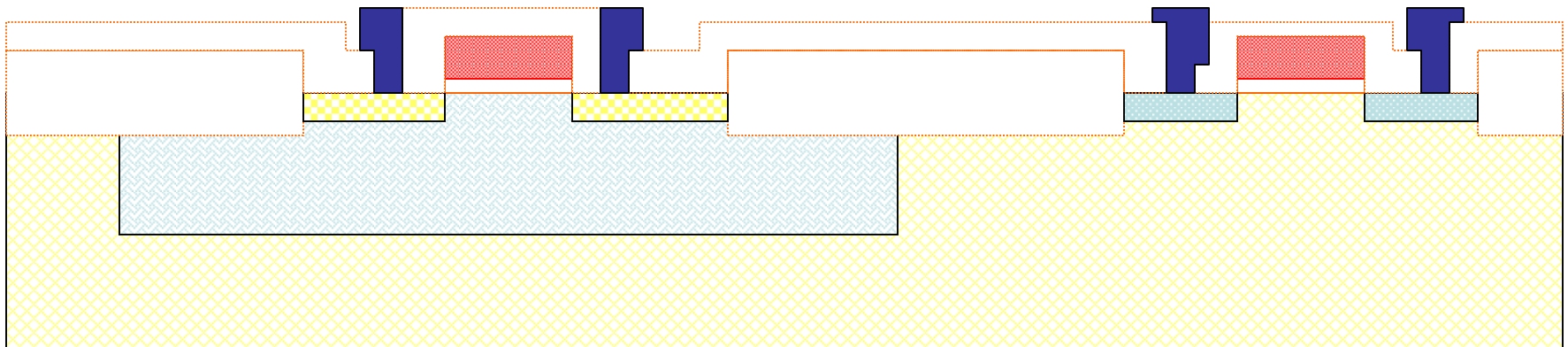

B-B' Section

# Should now know what you can do in this process !!

Can metal connect to active?

Can metal connect to substrate when on top of field oxide?

How can metal be connected to substrate?

Can poly be connected to active under gate?

Can poly be connected to active any place?

Can metal be placed under poly to isolate it from bulk?





Can metal 2 be connected directly to active?

Can metal 2 be connected to metal 1?

Can metal 2 pass under metal 1?

Could a process be created that will result in an answer of YES to most of above?

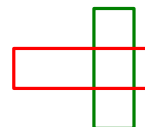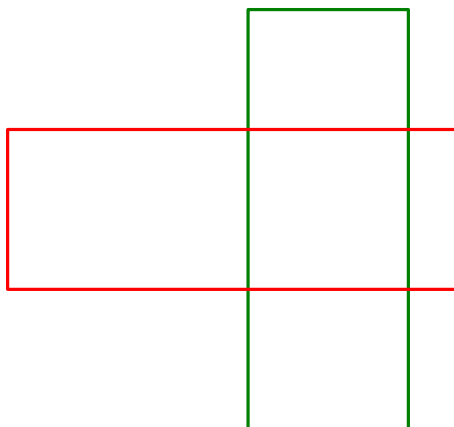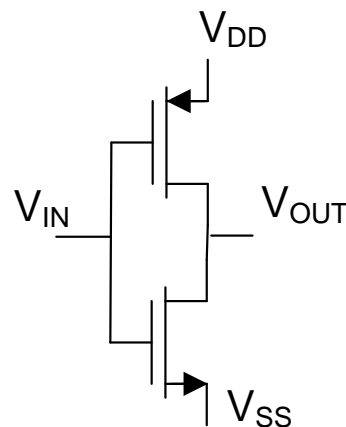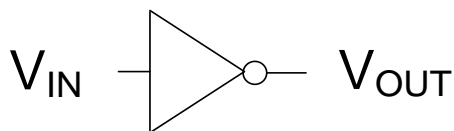How does the inverter delay compare between a 0.5u process and a 0.18u process?



RUN: T91T  
TECHNOLOGY: SCN05

VENDOR: AMIS  
FEATURE SIZE: 0.5 microns

Run type: SKD

INTRODUCTION: This report contains the lot average results obtained by MOSIS from measurements of MOSIS test structures on each wafer of this fabrication lot. SPICE parameters obtained from similar measurements on a selected wafer are also attached.

COMMENTS: American Microsystems, Inc. C5

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM Vth	3.0/0.6	0.81	-0.92	volts
SHORT Idss	20.0/0.6	466	-250	uA/um
Vth		0.69	-0.89	volts
Vpt		12.7	-11.7	volts
WIDE Ids0	20.0/0.6	< 2.5	< 2.5	pA/um
LARGE Vth	20.0/20.0	0.71	-0.94	volts
Vjbkd		8.8	-11.7	volts
Ijlk		<50.0	<50.0	pA
Gamma		0.44	0.57	V^0.5
K' (Uo*Cox/2)		54.8	-19.7	uA/V^2
Low-field Mobility		434.84	156.32	cm^2/V*s



PROCESS PARAMETERS	N+	P+	POLY	PLY2 HR	M1	UNITS
Sheet Resistance	85.3	111.2	22.4	1033	0.09	ohms/sq
Contact Resistance	59.6	145.4	17.9			ohms
Gate Oxide Thickness	137					angstroms

CAPACITANCE PARAMETERS	N+	P+	POLY	POLY2	M1	UNITS
Area (substrate)	443	745	102			aF/um <sup>2</sup>
Area (N+active)			2518			aF/um <sup>2</sup>
Area (P+active)			2441			aF/um <sup>2</sup>
Area (poly)				896	61	aF/um <sup>2</sup>

CIRCUIT PARAMETERS	UNITS
Ring Oscillator Freq.	
DIV256 (31-stg, 5.0V)	94.47 MHz
Ring Oscillator Power	
DIV256 (31-stg, 5.0V)	0.48 uW/MHz/gate

# MOSIS WAFER ACCEPTANCE TESTS

RUN: T4BK (MM\_NON-EPI\_THK-MTL)  
TECHNOLOGY: SCN018

VENDOR: TSMC  
FEATURE SIZE: 0.18 microns

INTRODUCTION: This report contains the lot average results obtained by MOSIS from measurements of MOSIS test structures on each wafer of this fabrication lot. SPICE parameters obtained from similar measurements on a selected wafer are also attached.

COMMENTS: DSCN6M018\_TSMC

TRANSISTOR PARAMETERS	W/L	N-CHANNEL	P-CHANNEL	UNITS
MINIMUM Vth	0.27/0.18	0.50	-0.53	volts
SHORT Idss	20.0/0.18	571	-266	uA/um
Vth		0.51	-0.53	volts
Vpt		4.7	-5.5	volts
WIDE Ids0	20.0/0.18	22.0	-5.6	pA/um
LARGE Vth	50/50	0.42	-0.41	volts
Vjbkd		3.1	-4.1	volts
Ijlk		<50.0	<50.0	pA
K' (Uo*Cox/2)		171.8	-36.3	uA/V^2
Low-field Mobility		398.02	84.10	cm^2/V*s


CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	R_W	D_N_W	M5P	N_W	UNITS
Area (substrate)	998	1152	103	39	19	13	9	8	3		129		127	aF/um^2
Area (N+active)			8566	54	21	14	11	10	9					aF/um^2
Area (P+active)			8324											aF/um^2
Area (poly)				64	18	10	7	6	5					aF/um^2
Area (metal1)					44	16	10	7	5					aF/um^2
Area (metal2)						38	15	9	7					aF/um^2
Area (metal3)							40	15	9					aF/um^2
Area (metal4)								37	14					aF/um^2
Area (metal5)									36			1003		aF/um^2
Area (r well)	987													aF/um^2
Area (d well)										574				aF/um^2
Area (no well)	139													aF/um^2
Fringe (substrate)	244	201		18	61	55	43	25						aF/um
Fringe (poly)				69	39	29	24	21	19					aF/um
Fringe (metal1)					61	35		23	21					aF/um
Fringe (metal2)						54	37	27	24					aF/um
Fringe (metal3)							56	34	31					aF/um
Fringe (metal4)								58	40					aF/um
Fringe (metal5)									61					aF/um
Overlap (P+active)			652											aF/um

CIRCUIT PARAMETERS			UNITS
Inverters	K		
Vinv	1.0	0.74	volts
Vinv	1.5	0.78	volts
Vol (100 uA)	2.0	0.08	volts
Voh (100 uA)	2.0	1.63	volts
Vinv	2.0	0.82	volts
Gain	2.0	-23.33	
Ring Oscillator Freq.			
D1024_THK (31-stg, 3.3V)		338.22	MHz
DIV1024 (31-stg, 1.8V)		402.84	MHz
Ring Oscillator Power			
D1024_THK (31-stg, 3.3V)		0.07	uW/MHz/gate
DIV1024 (31-stg, 1.8V)		0.02	uW/MHz/gate

How does the inverter delay compare between a 0.5u process and a 0.18u process?

Feature	0.5	0.18		Units
Vtn	0.81	0.5		V
Vtp	-0.92	-0.53		V
uCoxn	109.6	344		uA/V^2
uCoxp	39.4	72.6		uA/V^2
Cox	2.51	8.5		fF
Vdd	5	1.8		V
fosc-31	94.5	402.8		MHz

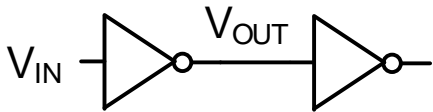Assume n-channel and p-channel devices with  $L=L_{min}$ ,  $W=1.5L_{min}$



$$t_{HL} = R_{pd} C_L$$

$$t_{LH} = R_{pu} C_L$$

$$R_{pd} = \frac{L_n}{\mu_n C_{OX} W_n (V_{DD} - V_{TN})}$$

$$R_{pu} = \frac{L_p}{\mu_p C_{OX} W_p (V_{DD} + V_{TP})}$$

$$C_L = C_{OX} (W_n L_n + W_p L_p)$$

Feature	0.5	0.18		Units
CL	1.88	0.83		fF
Rpd	1452	1491		ohms
Rpu	2858	3941		ohms
THL	2.73	1.23		psec
TLH	5.38	3.26		psec
f	123	223		GHz

Note 0.18u process is much faster than 0.5u process

# Basic Devices and Device Models

- Resistor
- Diode
- Capacitor
- MOSFET
- BJT




Lets pick up a discussion of  
Technology Files before moving to BJT

**Return to basic devices !**

# Basic Devices and Device Models

- Resistor
- Diode
- Capacitor
- MOSFET

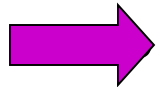

BJT


# Bipolar Junction Transistors

- Operation
- Modeling

# Carriers in Doped Semiconductors




n-type

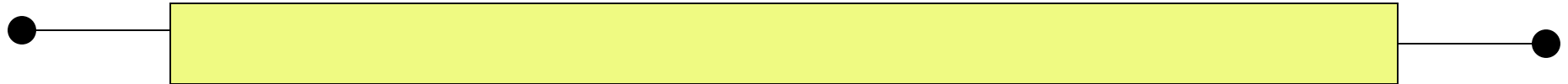

p-type




# Carriers in Doped Semiconductors

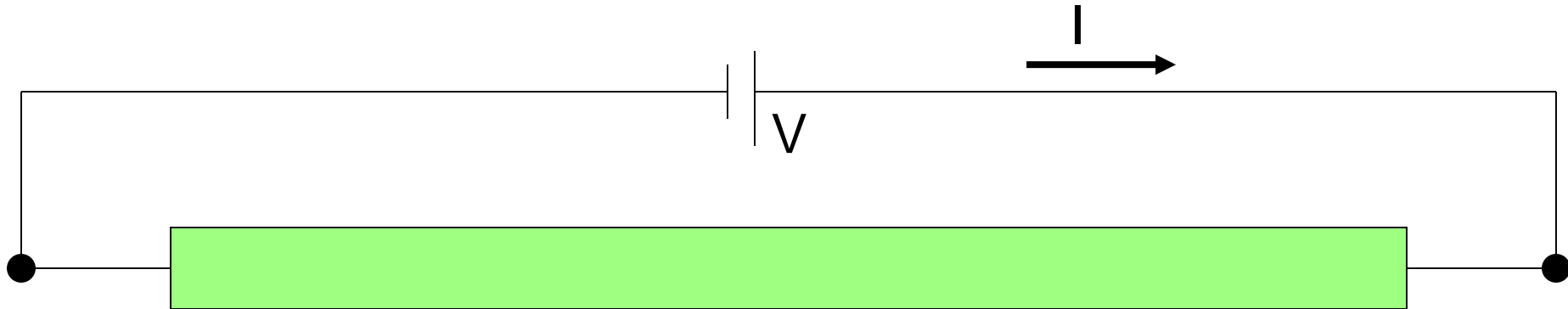

Current carriers are dominantly electrons

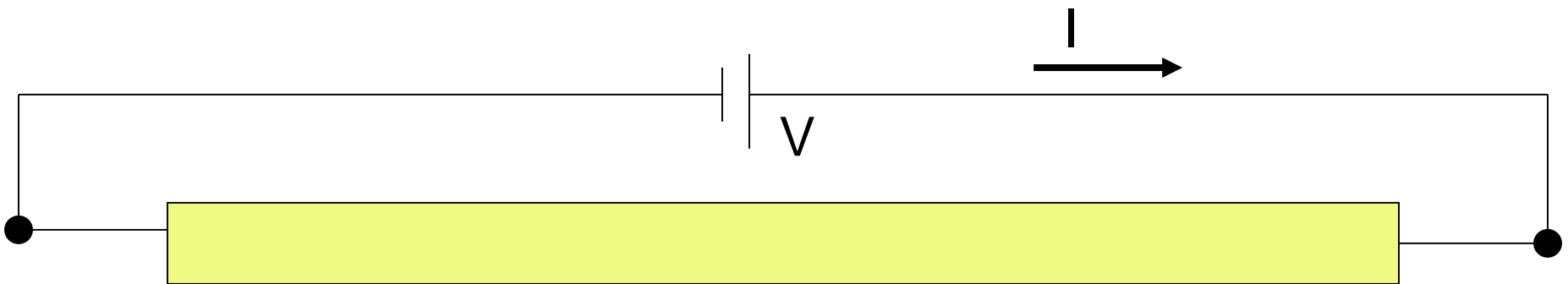Small number of holes are short-term carriers



Current carriers are dominantly holes


Small number of electrons are short-term carriers

# Carriers in Doped Semiconductors

	Majority Carriers	Minority Carriers
n-type	electrons	holes
p-type	holes	electrons


# Carriers in MOS Transistors

Consider n-channel MOSFET

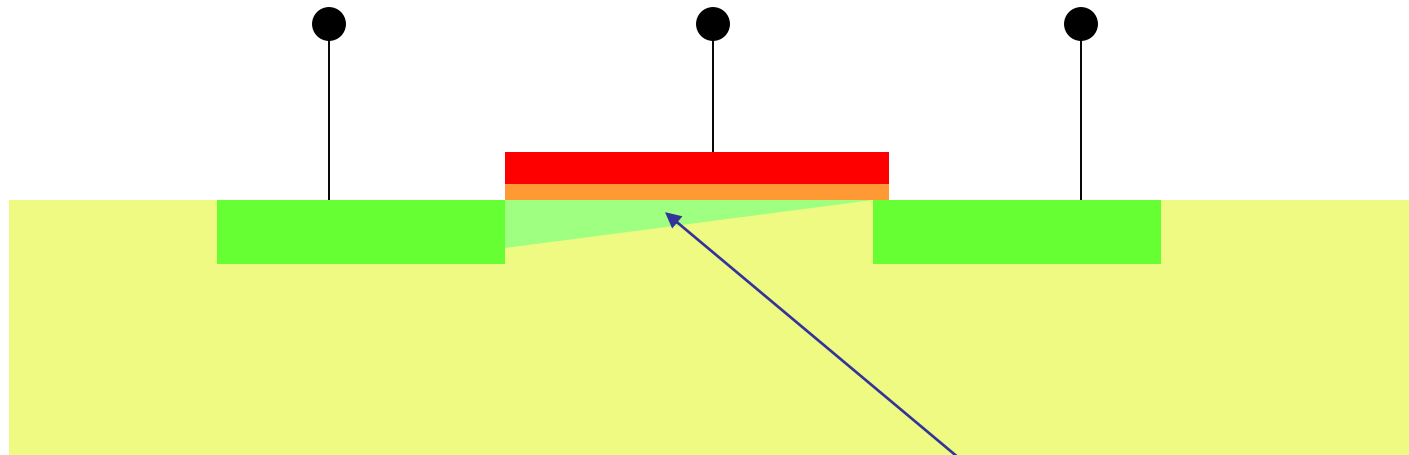

Saturation Region


Channel

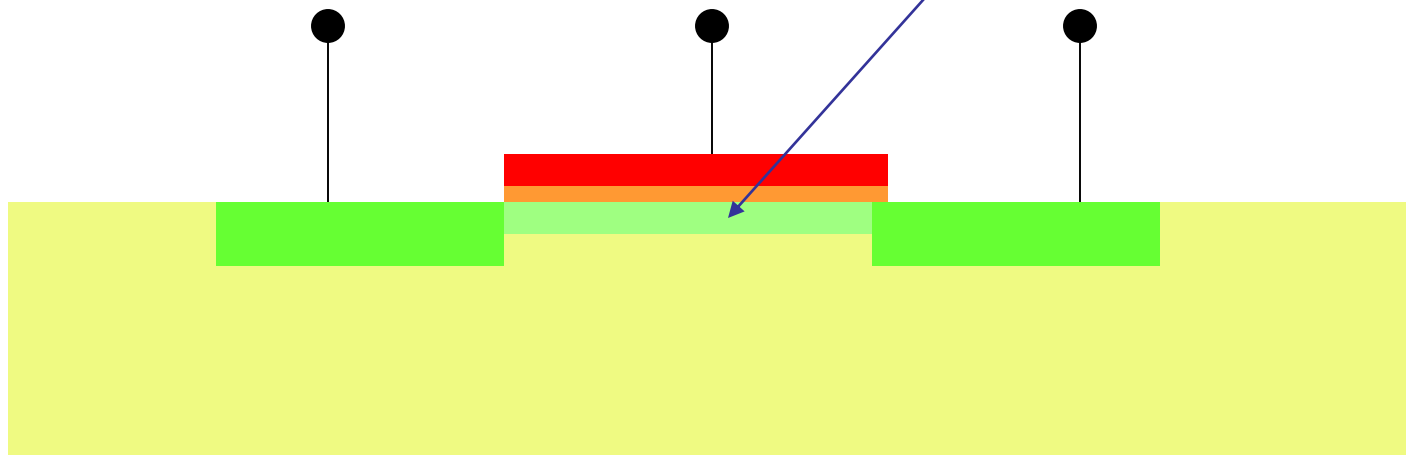


Triode Region

# Carriers in MOS Transistors

Consider n-channel MOSFET

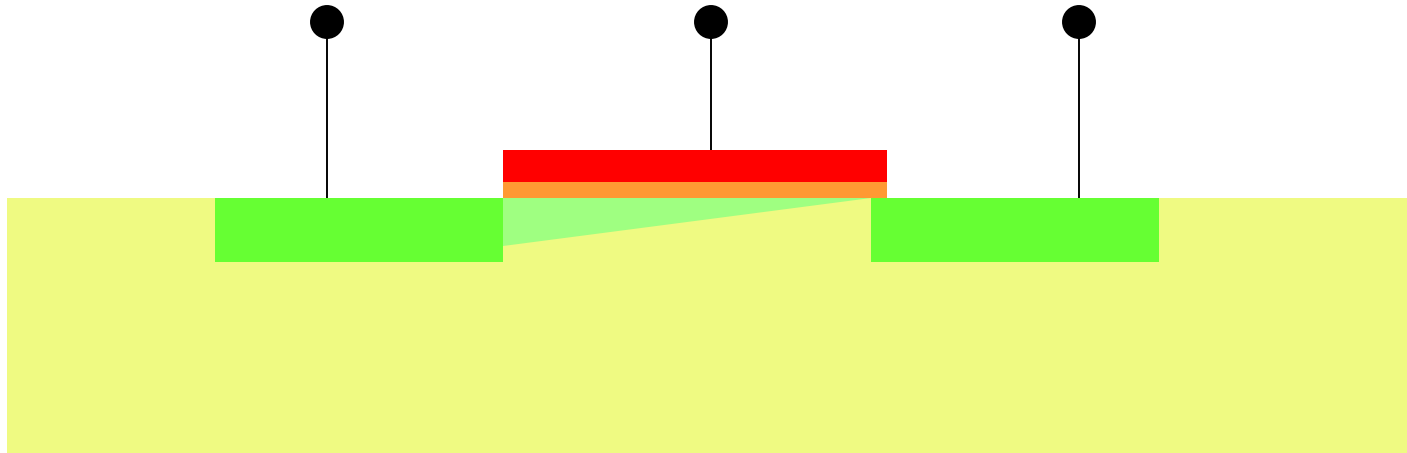

Saturation Region

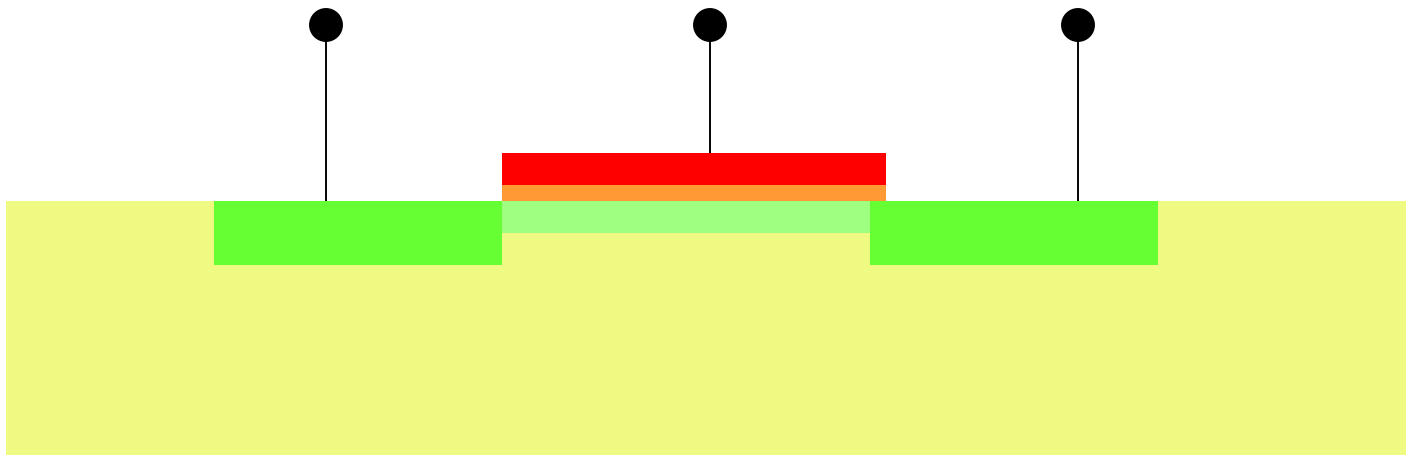


Triode Region

**Carriers in electrically induced n-channel are electrons**


# Carriers in MOS Transistors

Consider p-channel MOSFET

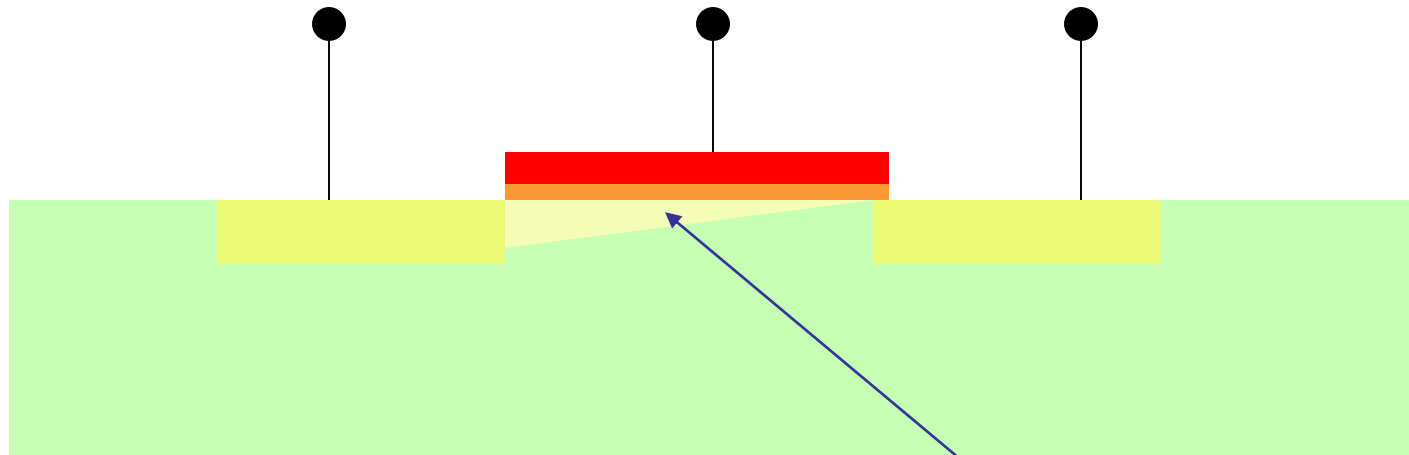

Saturation Region


Channel

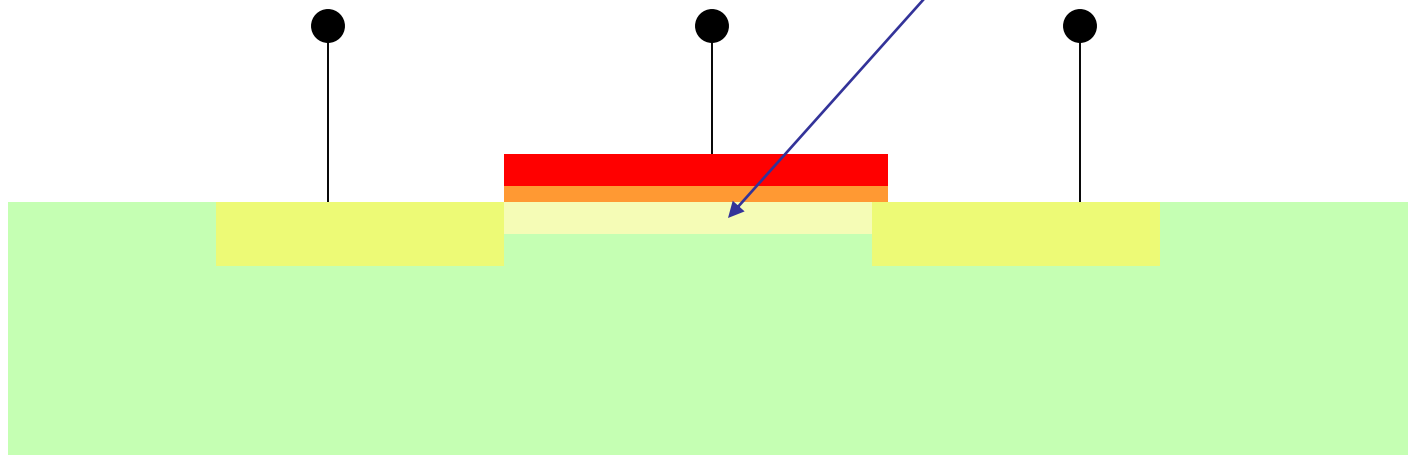


Triode Region

# Carriers in MOS Transistors

Consider p-channel MOSFET

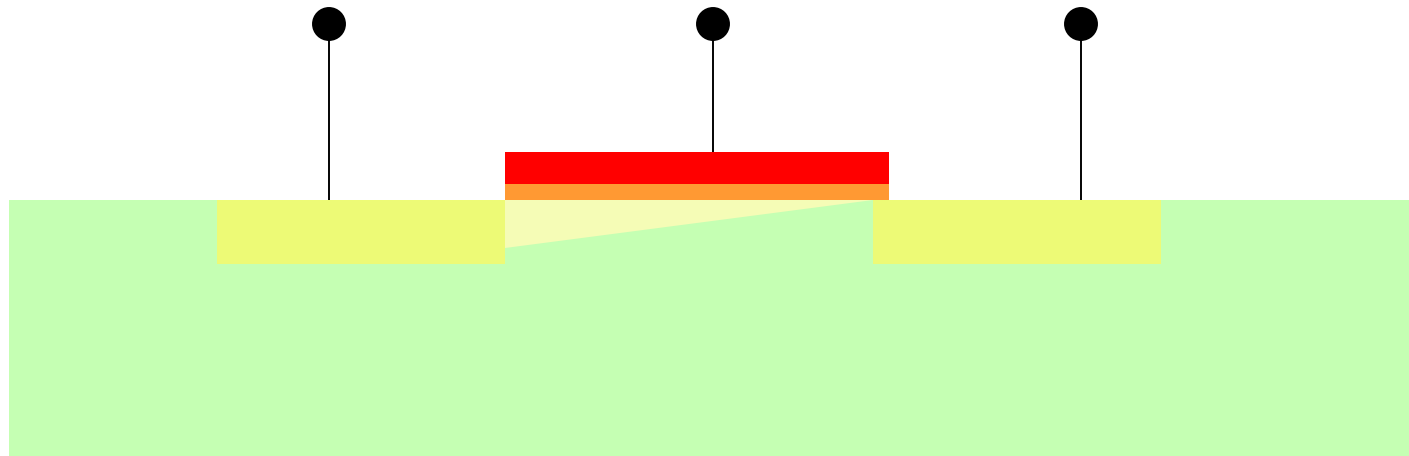





Saturation Region

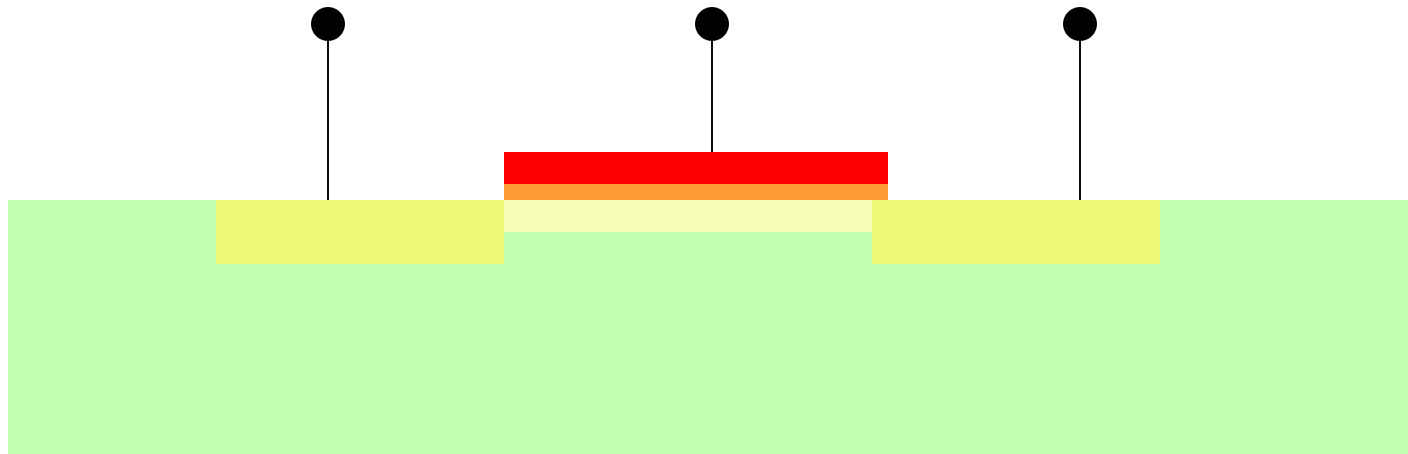

Triode Region



**Carriers in electrically induced p-channel are holes**

# Carriers in MOS Transistors

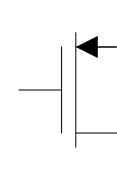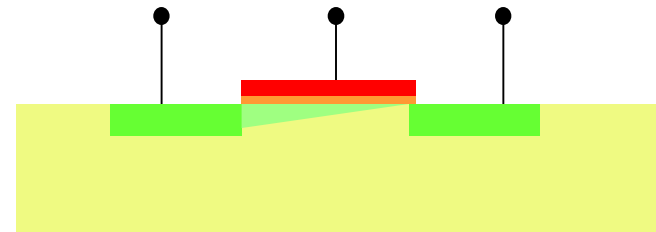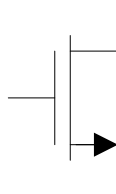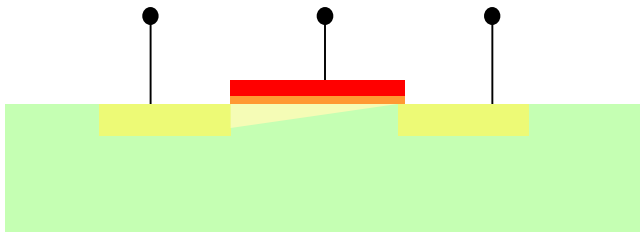


**Carriers in channel of MOS transistors are Majority carriers**


# Bipolar Transistors

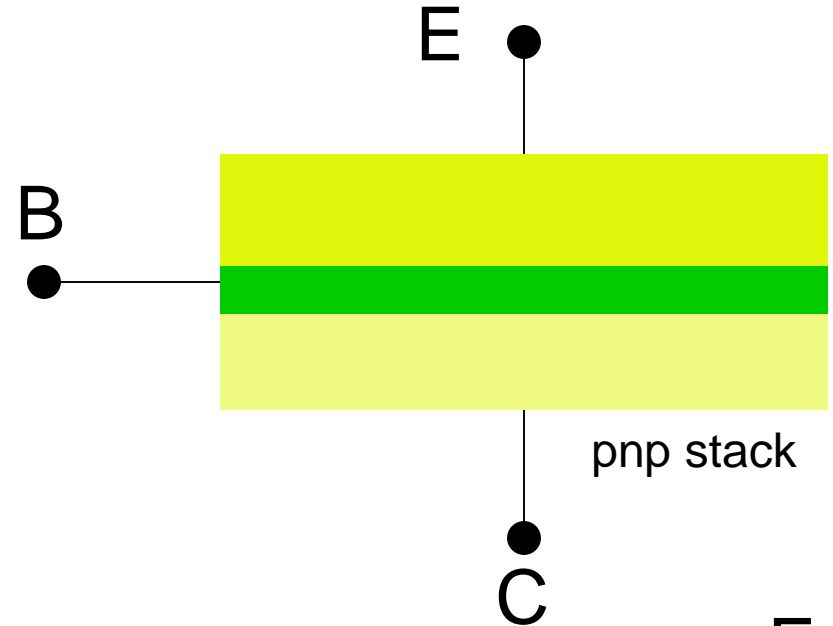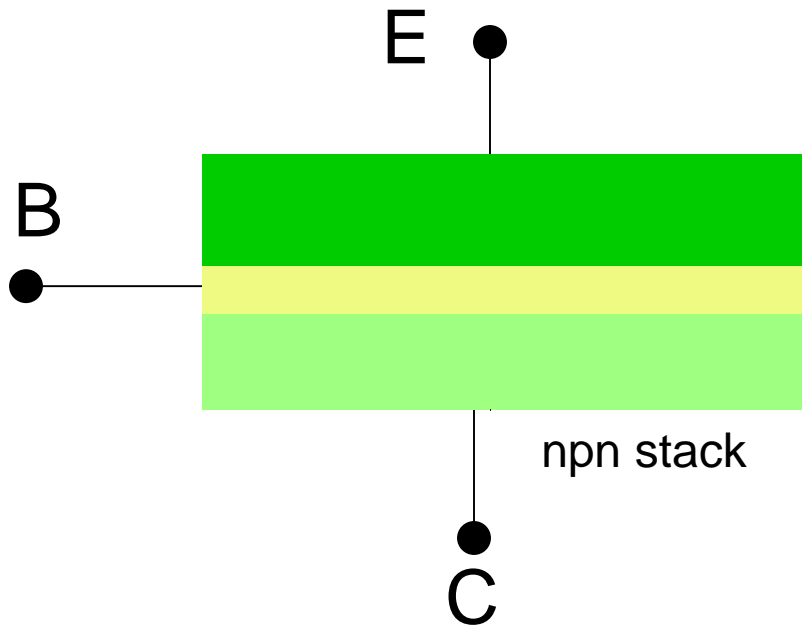

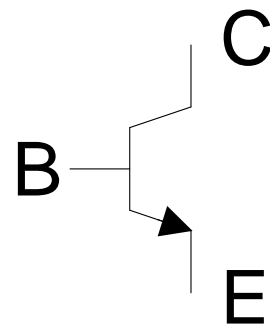- Bipolar Devices Show Basic Symmetry
- Electrical Properties not Symmetric
- Designation of C and E critical



**npn transistor**




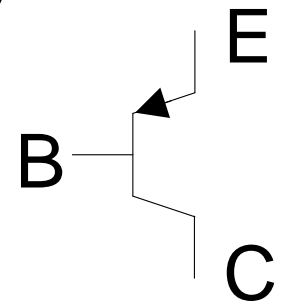


**pnp transistor**

With proper doping and device sizing these form Bipolar Transistors




# Bipolar Transistors

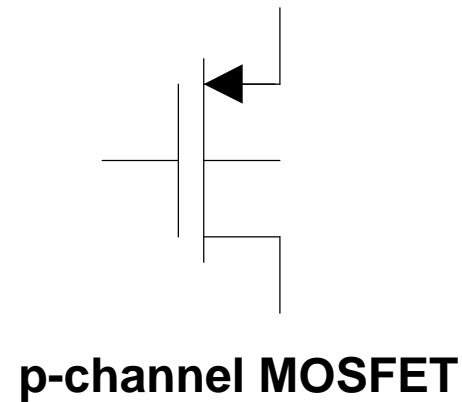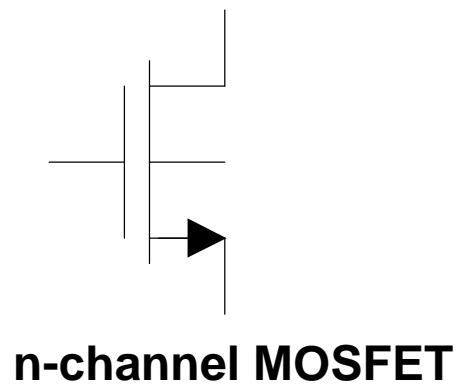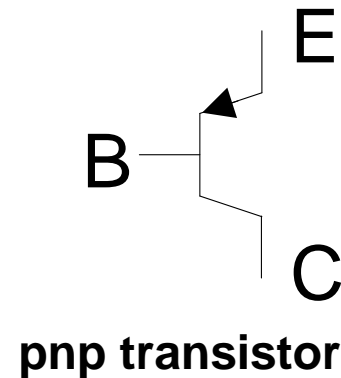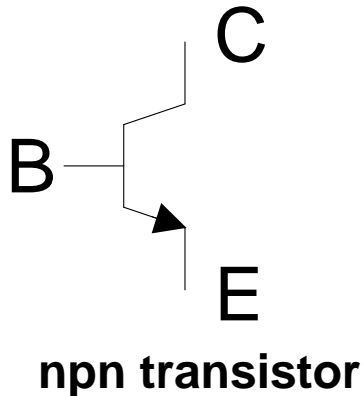

**In contrast to a MOSFET which has 4 terminals, a BJT only has 3 terminals**
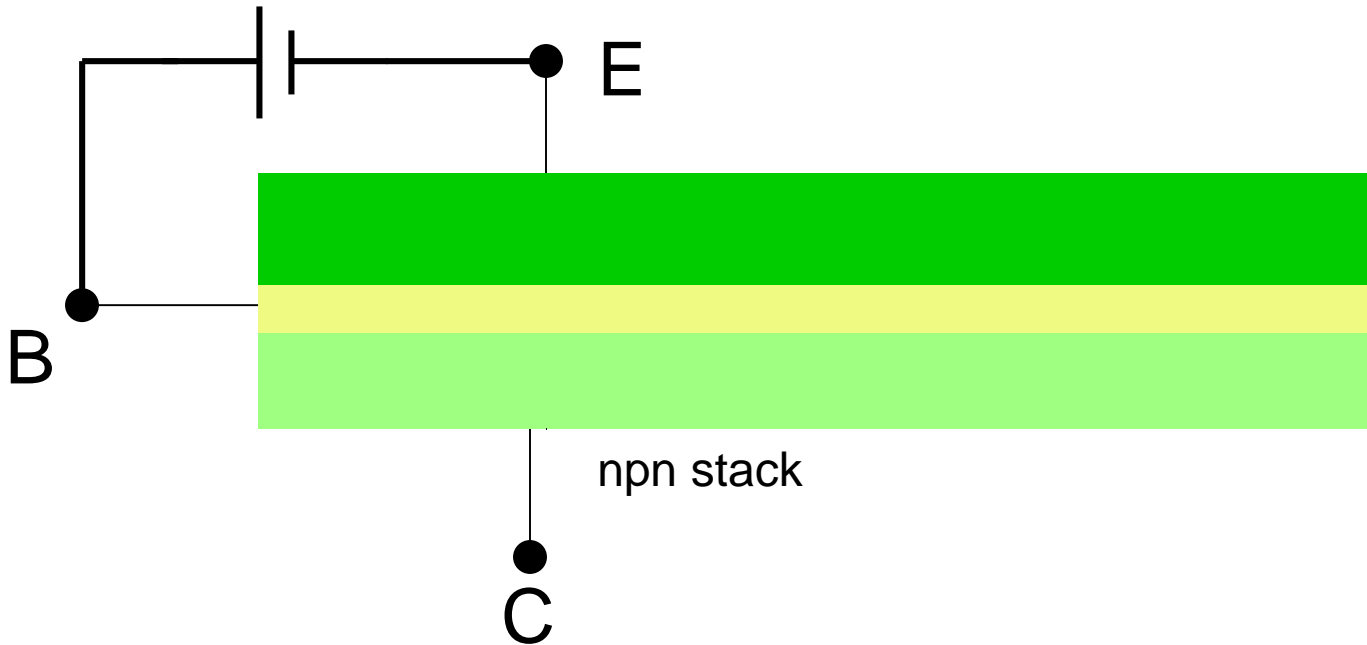
# Bipolar Operation

Consider npn transistor – Forward Active Operation



Under **forward BE bias** current flow into base and out of emitter

Current flow is governed by the diode equation

Carriers in emitter are electrons (majority carriers)


When electrons pass into the base they become minority carriers

Quickly recombine with holes to create holes base region

Dominant current flow in base is holes (majority carriers)
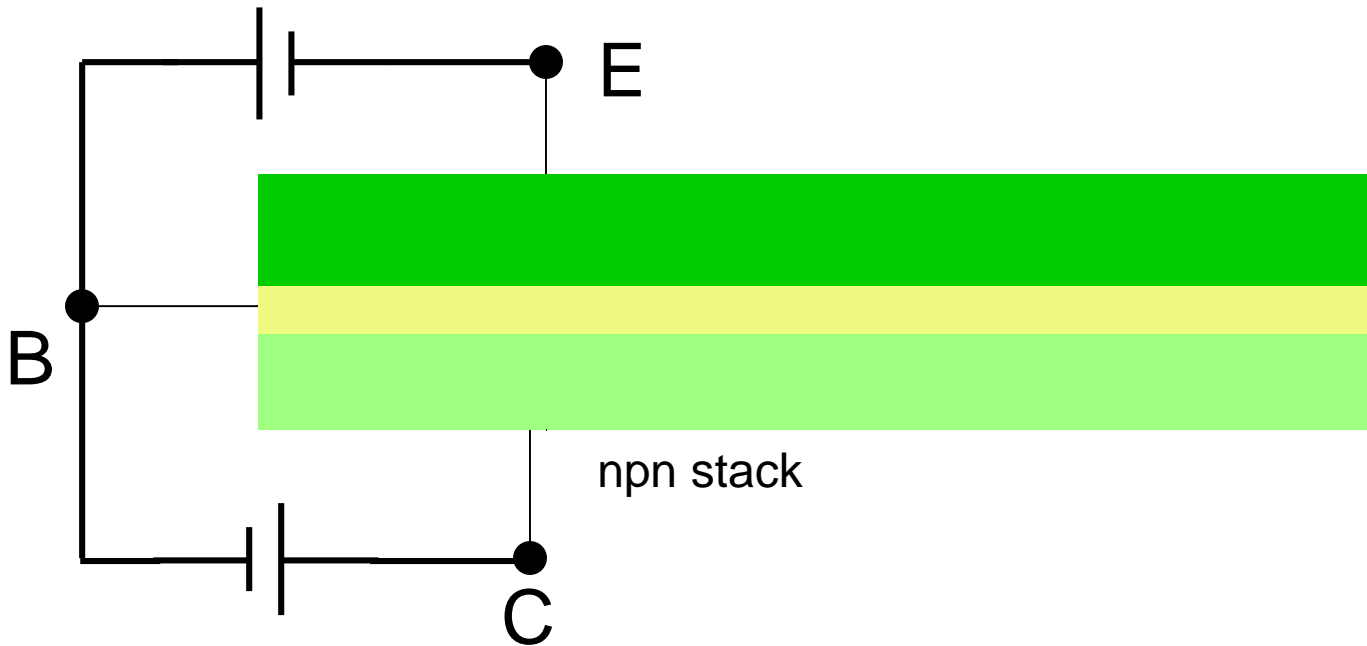
# Bipolar Operation

Consider npn transistor – Forward Active Operation



Under forward BE bias and reverse BC bias current flows into base region


Carriers in emitter are electrons (majority carriers)

When electrons pass into the base they become minority carriers

When minority carriers are present in the base they can be attracted to collector
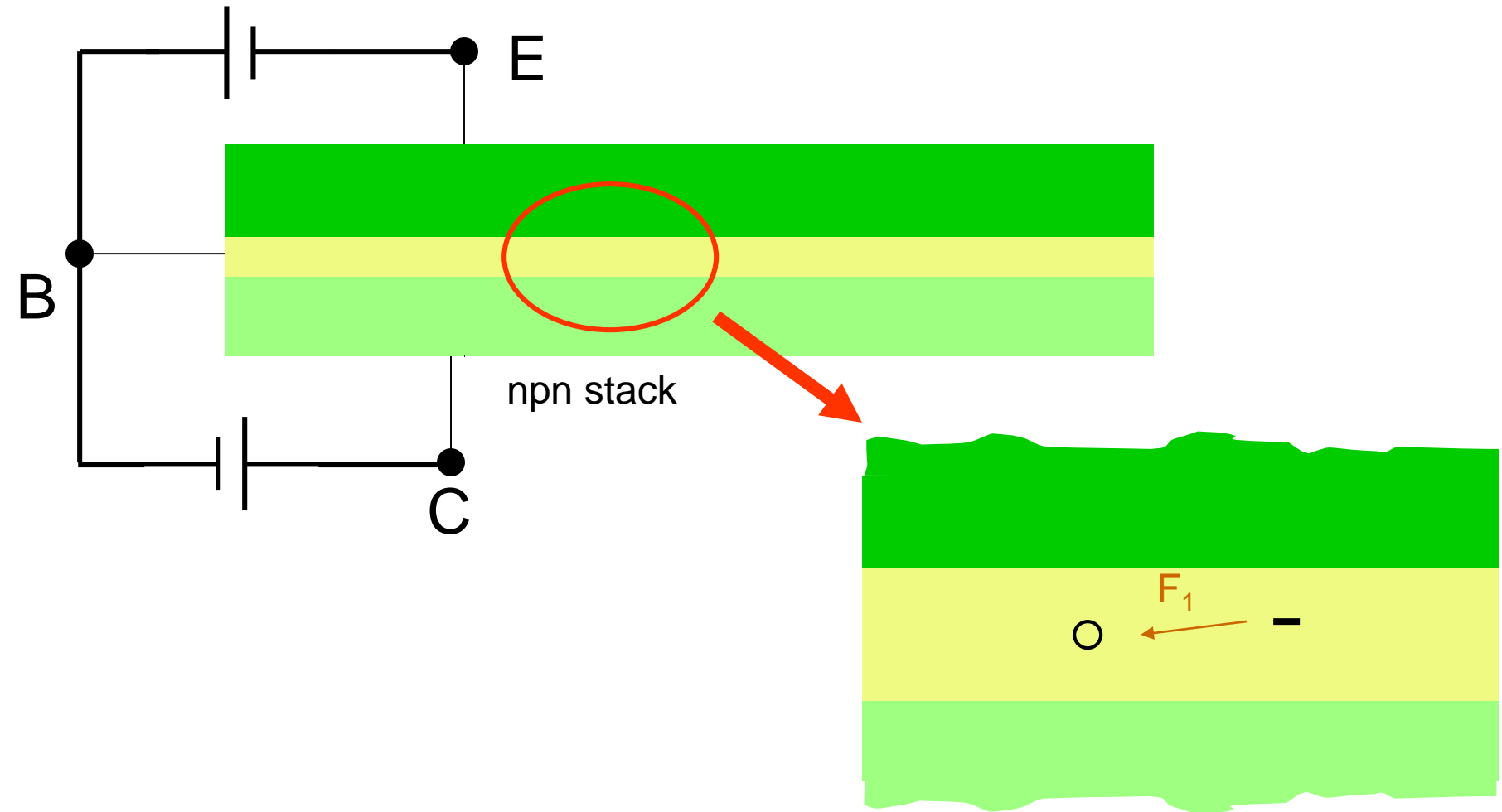
# Bipolar Operation


Consider npn transistor – Forward Active Operation



If no force on electron is applied by collector, electron will contribute to base current
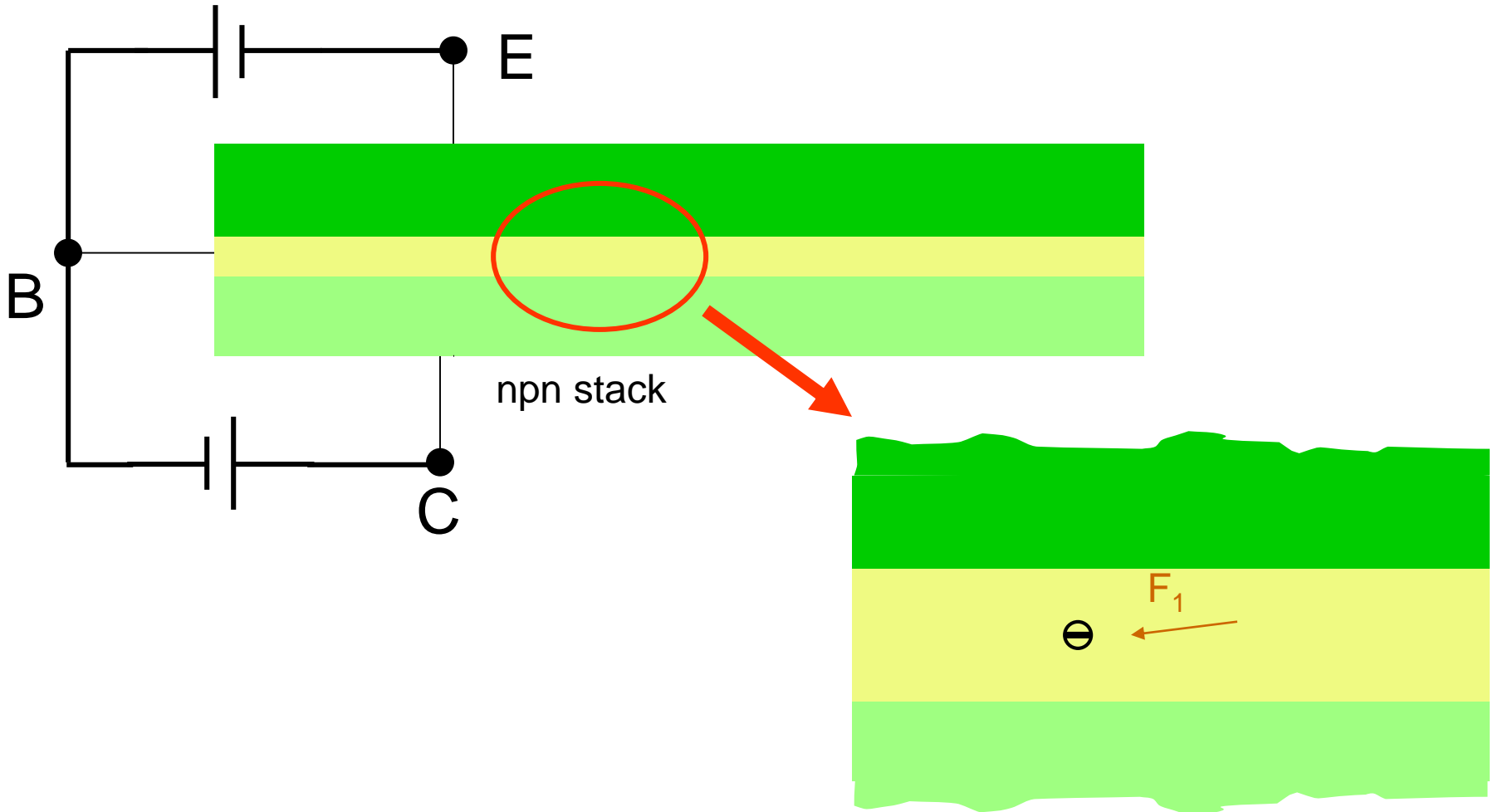
# Bipolar Operation


Consider npn transistor – Forward Active Operation



If no force on electron is applied by collector, electron will contribute to base current  
Electron will recombine with a hole so dominant current flow in base will be by majority carriers
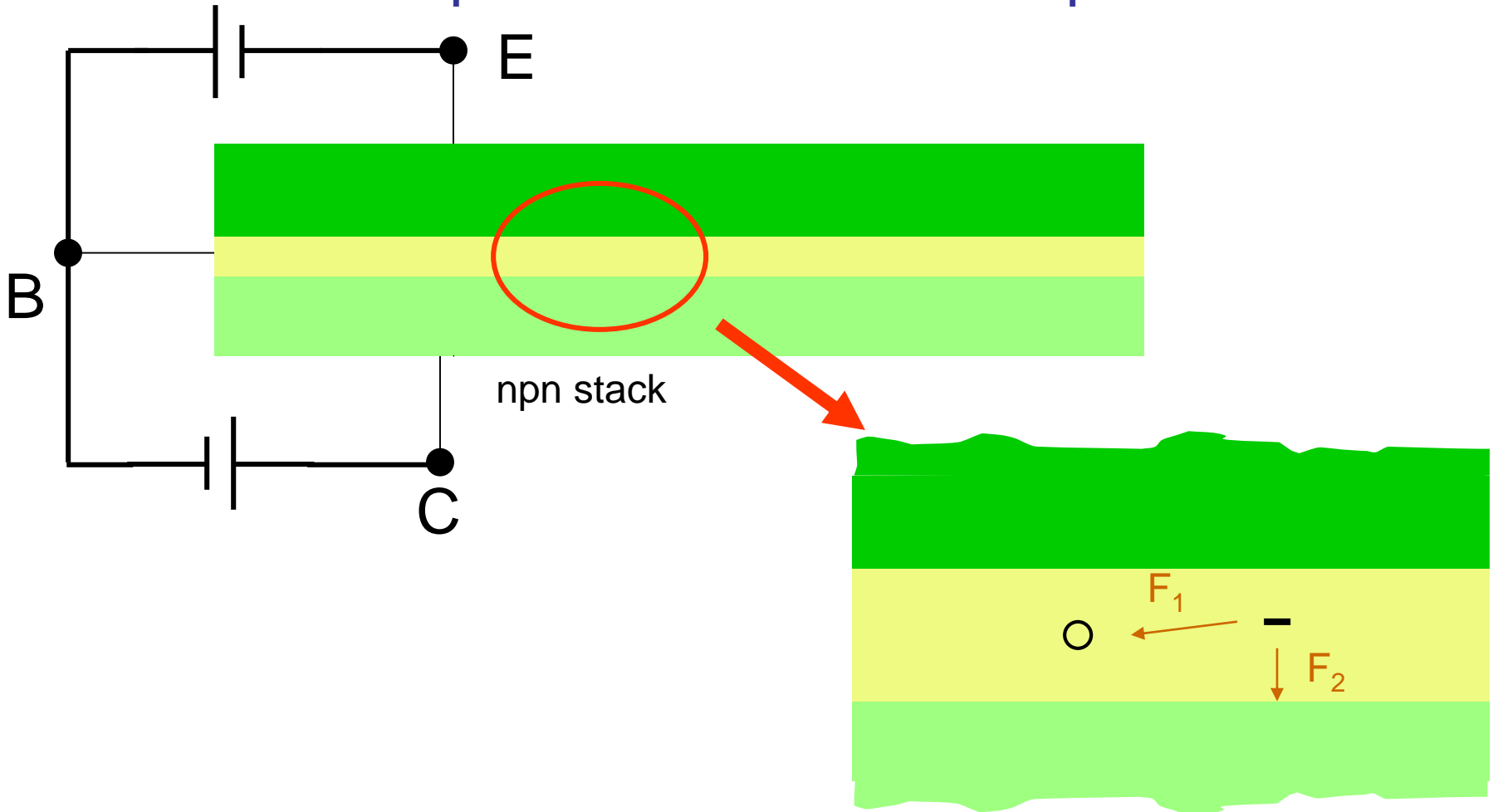
# Bipolar Operation


Consider npn transistor – Forward Active Operation



When minority carriers are present in the base they can be attracted to collector with reverse-bias of BC junction and can move across BC junction
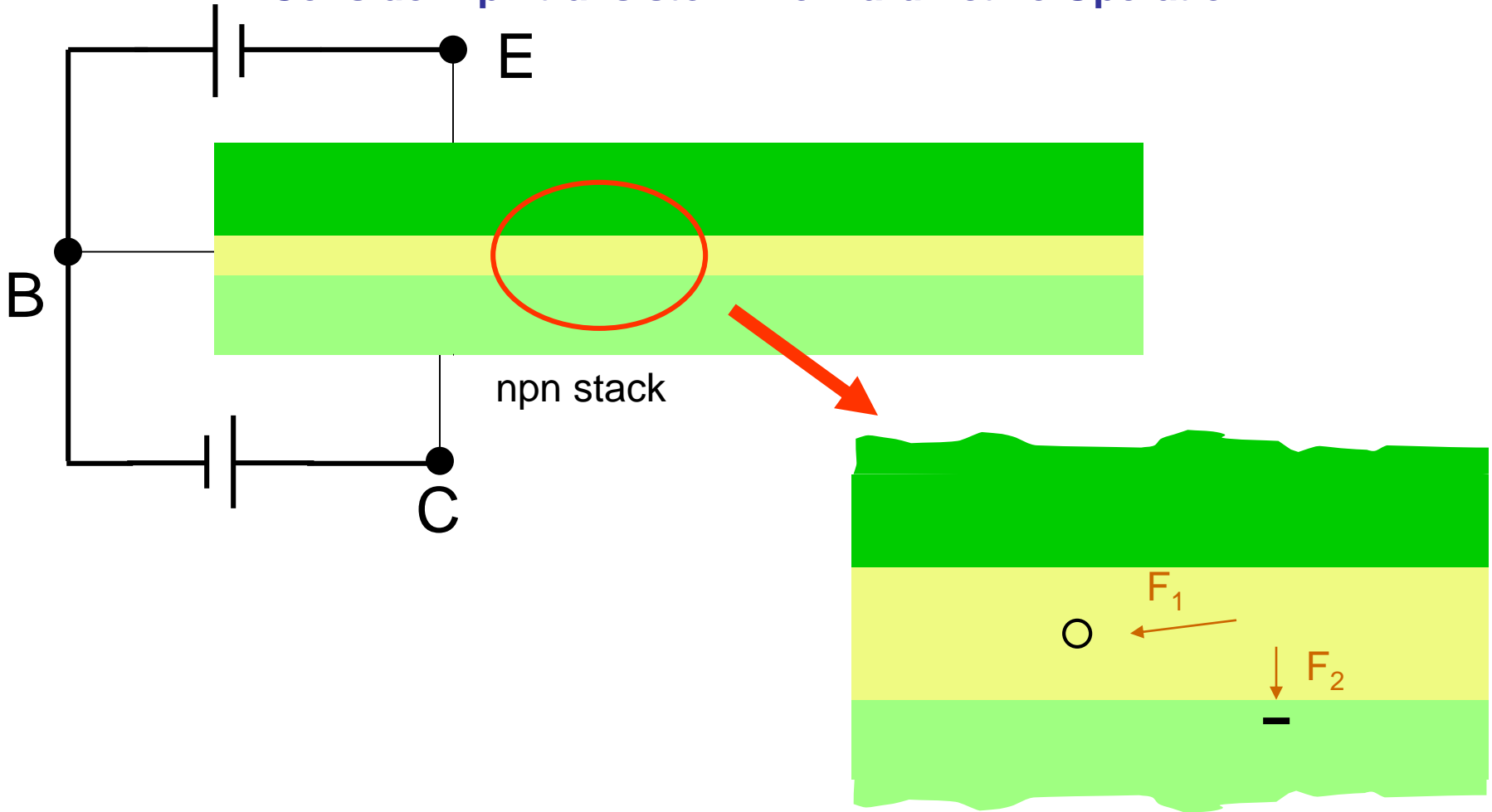
# Bipolar Operation

Consider npn transistor – Forward Active Operation




When minority carriers are present in the base they can be attracted to collector with reverse-bias of BC junction and can move across BC junction

Will contribute to collector current flow as majority carriers
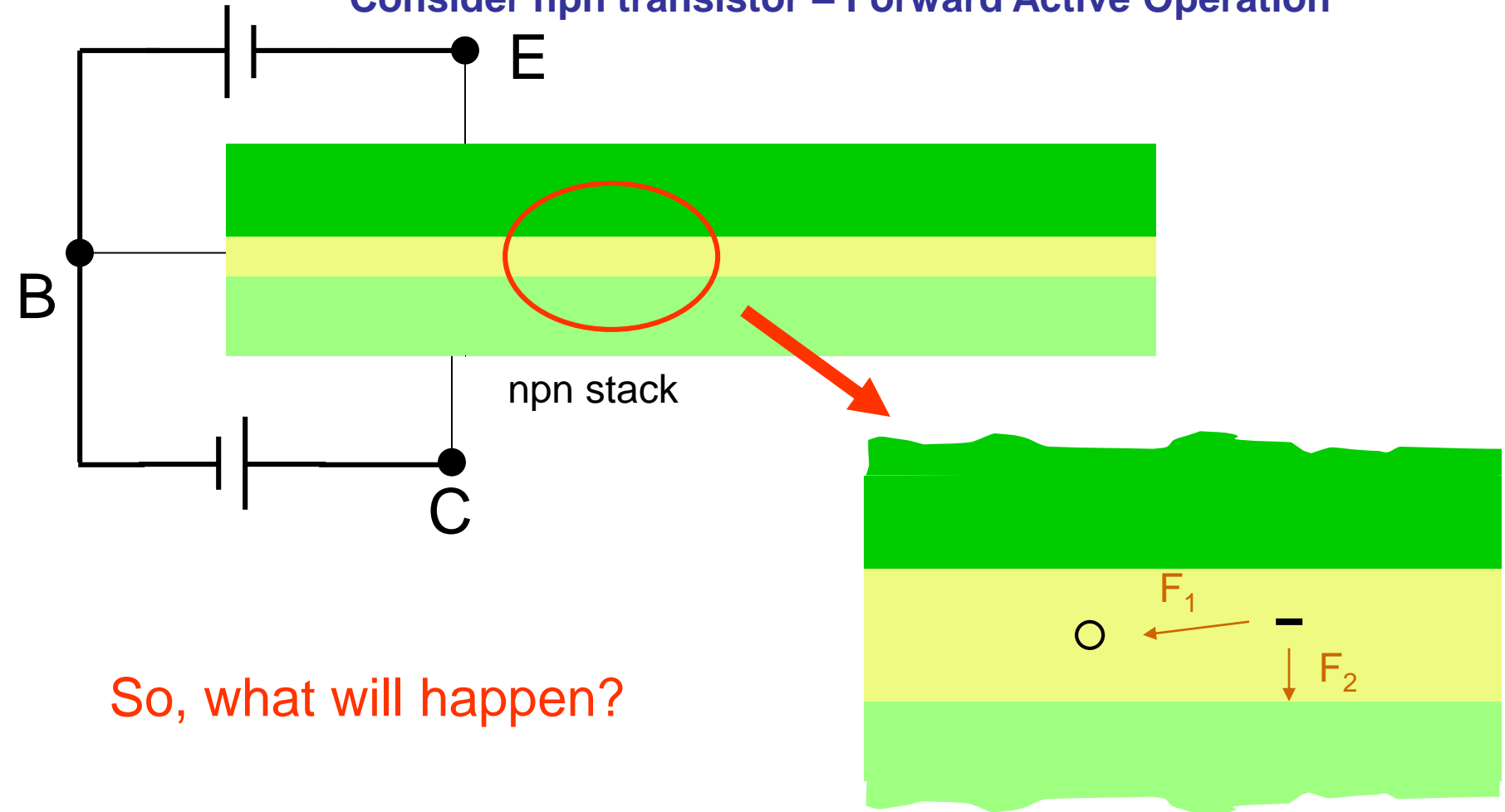
# Bipolar Operation

Consider npn transistor – Forward Active Operation




So, what will happen?


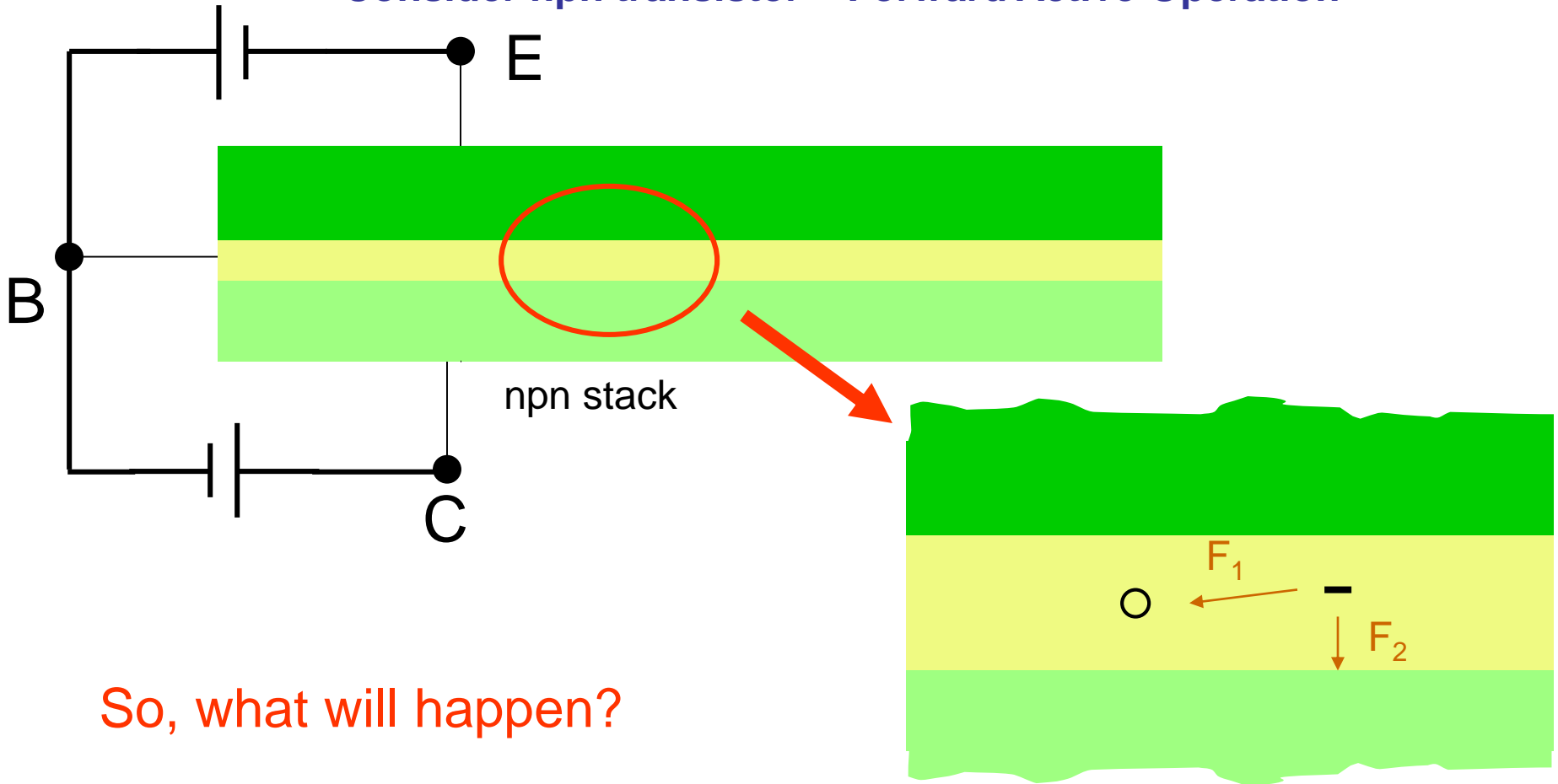
# Bipolar Operation

Consider npn transistor – Forward Active Operation




So, what will happen?

Some will recombine with holes and contribute to base current and some will be attracted across BC junction and contribute to collector

Size and thickness of base region and relative doping levels will play key role in percent of minority carriers injected into base contributing to collector current
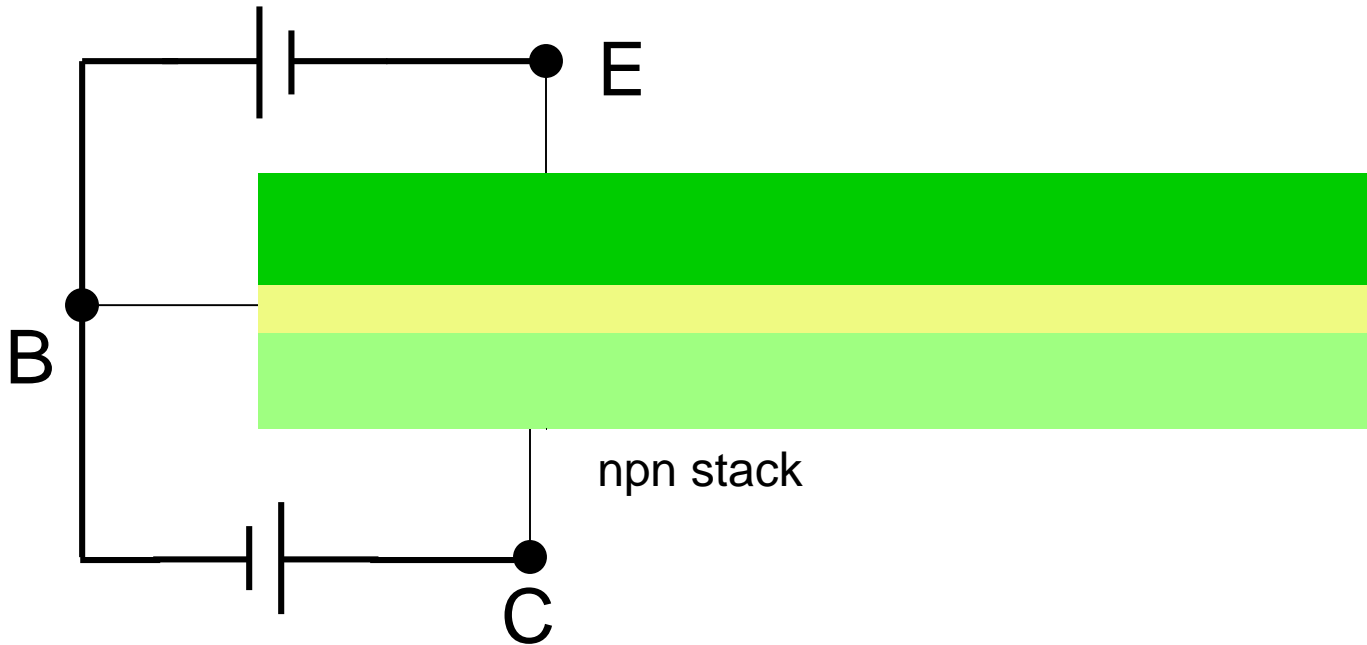
# Bipolar Operation

Consider npn transistor – Forward Active operation



Under forward BE bias and reverse BC bias current flows into base region

Carriers in emitter are electrons (majority carriers)


When electrons pass into the base they become minority carriers

When minority carriers are present in the base they can be attracted to collector

**Minority carriers either recombine with holes and contribute to base current or are attracted into collector region and contribute to collector current**
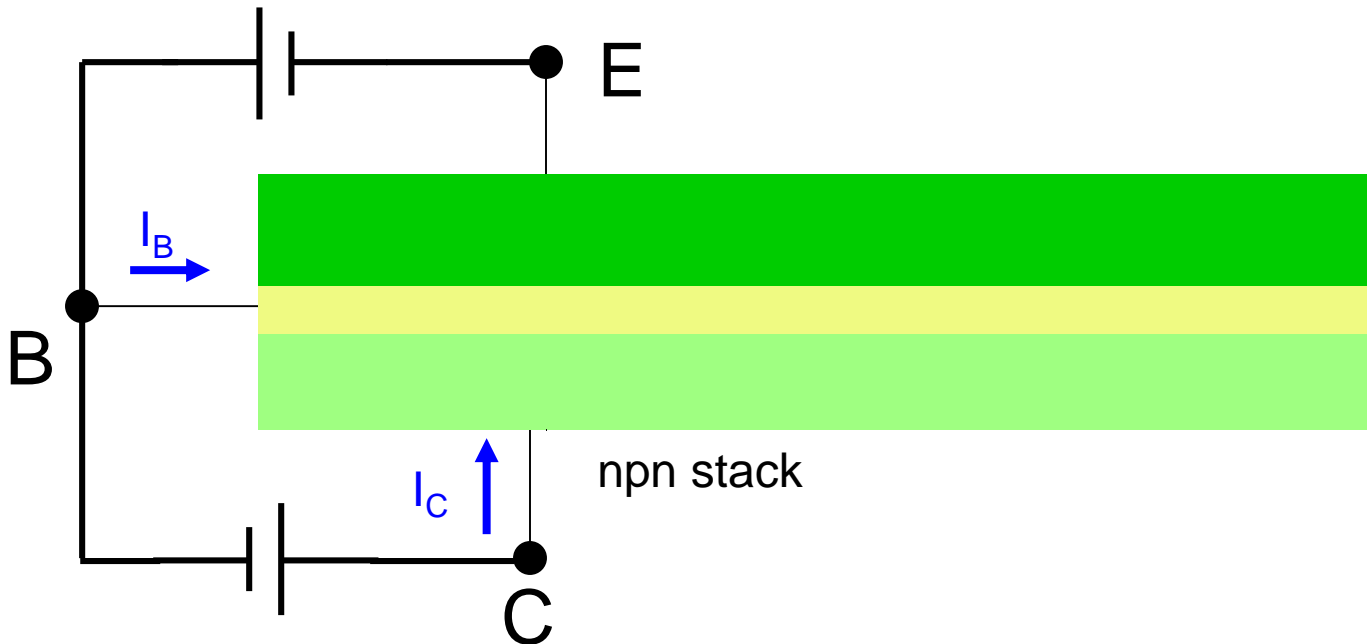
# Bipolar Operation

Consider npn transistor – Forward Active operation



**Minority carriers either recombine with holes and contribute to base current or are attracted into collector region and contribute to collector current**

If most of the minority carriers are attracted to collector,  $I_C \simeq I_E$


Thus  $I_B \ll I_C$

Implications of this observation?

If input to device is  $I_B$  and output is  $I_C$ , the BJT will behave as a current amplifier with large current gain !! This was the key observation by Bell Labs in 1948 !!
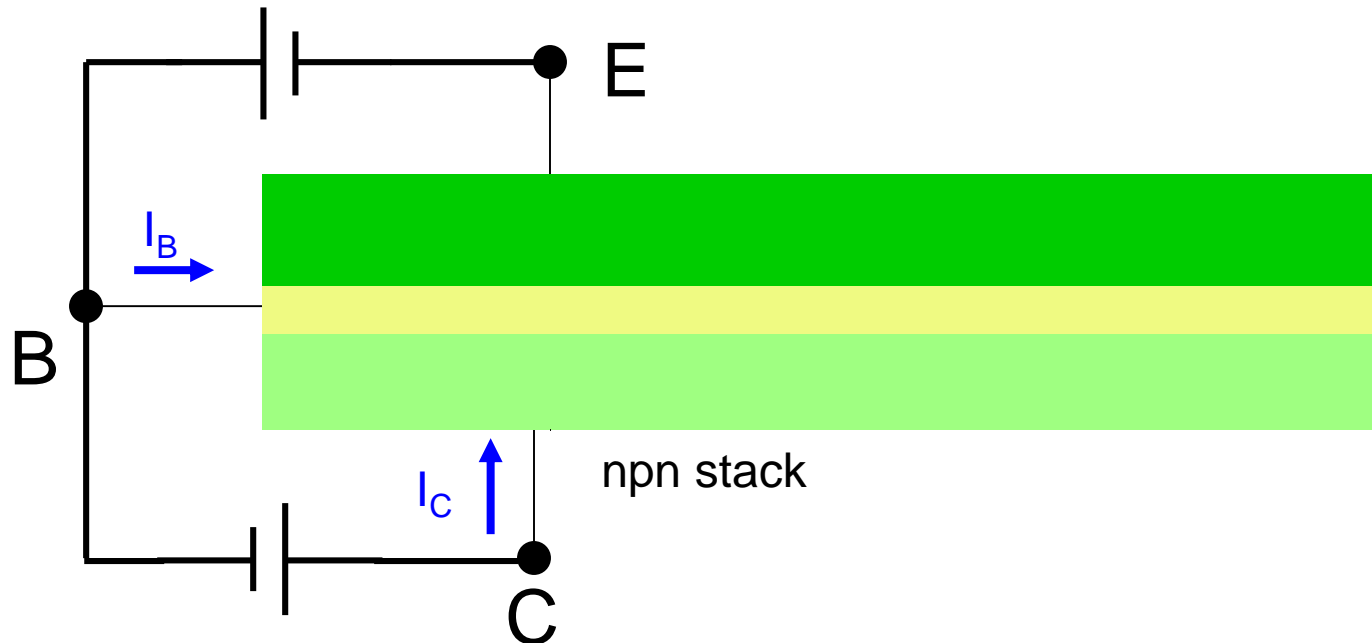
# Bipolar Operation



Consider npn transistor - Forward Active Operation



Under forward BE bias and reverse BC bias current flows into base region

- Efficiency at which minority carriers injected into base region and contribute to collector current is termed  $\alpha$
- $\alpha$  is always less than 1 but for a good transistor, it is very close to 1
- For good transistors  $.99 < \alpha < .999$
- Making the base region very thin makes  $\alpha$  large


# Bipolar Transistors

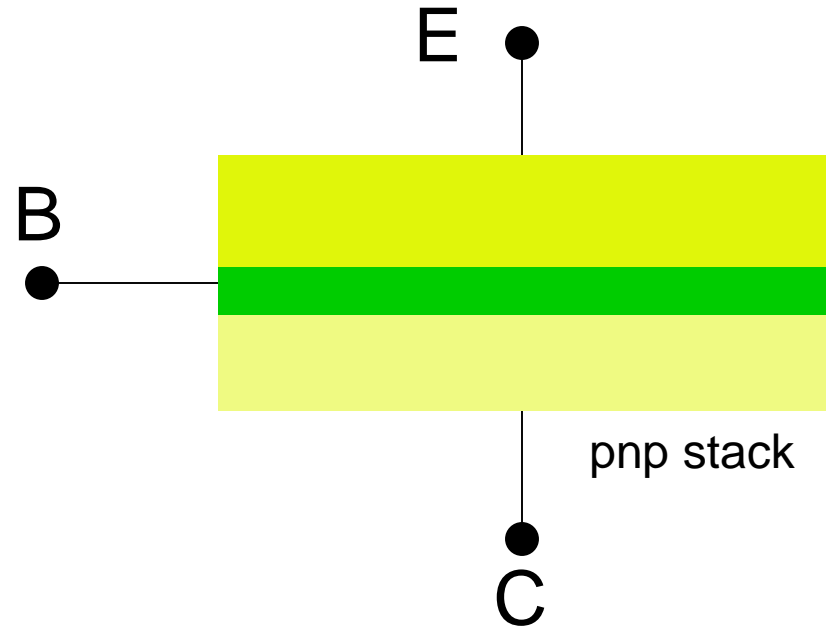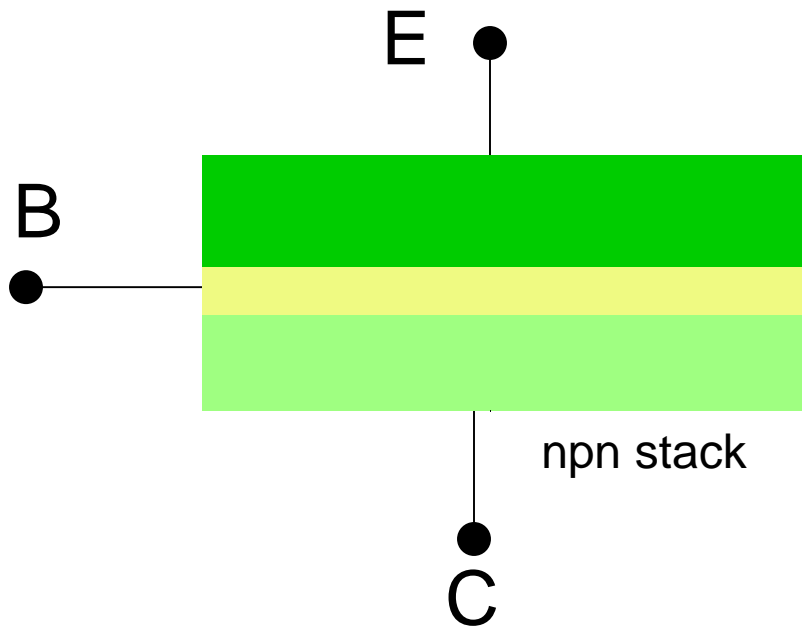

- principle of operation of pnp and npn transistors are the same
- minority carriers in base of pnp are holes
- npn usually have modestly superior properties because mobility of electrons is larger than mobility of holes
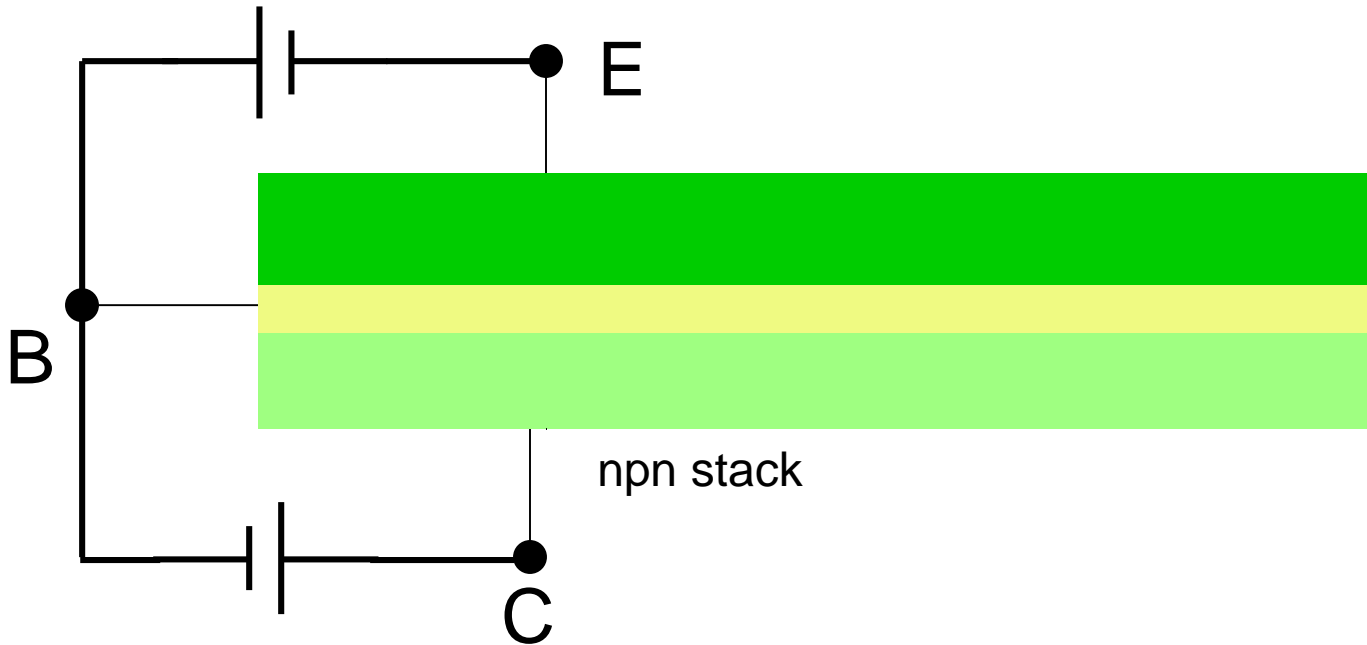
# Bipolar Operation



Consider npn transistor – Forward Active Operation



In contrast to MOS devices where current flow in channel is by majority carriers, current flow in the critical base region of bipolar transistors is by minority carriers

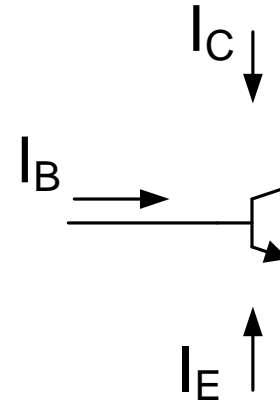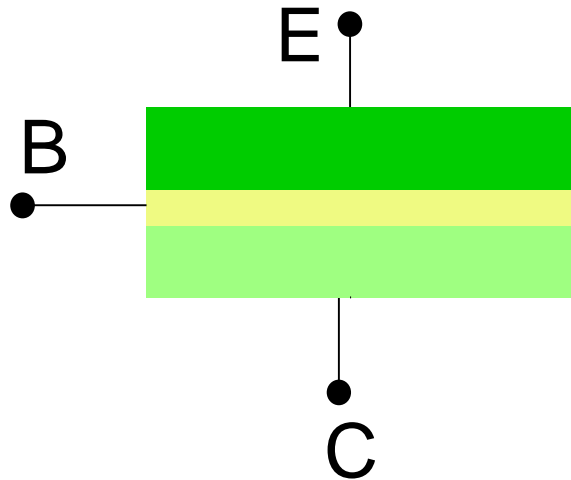
# Bipolar Operation

Consider npn transistor – Forward Active Operation



$$I_C + I_B = -I_E$$

$$I_C = -\alpha I_E$$

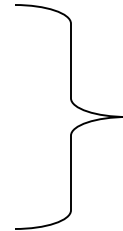

$$I_C = \frac{\alpha}{1-\alpha} I_B$$

$$\beta \stackrel{\text{defn}}{=} \frac{\alpha}{1-\alpha}$$



$$I_C = \beta I_B$$

$\beta$  is typically very large

often  $50 < \beta < 999$
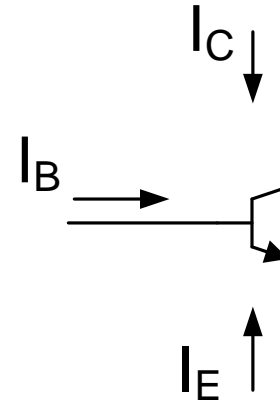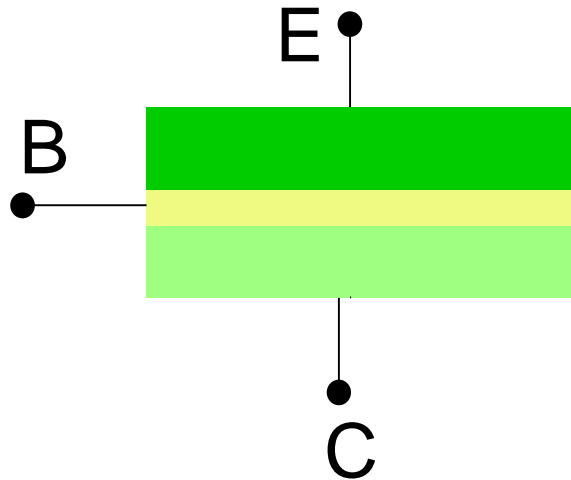
# Bipolar Operation

Consider npn transistor – Forward Active Operation



$$I_C = \beta I_B$$

$\beta$  is typically very large

Bipolar transistor can be thought of a current amplifier with a large current gain

In contrast, MOS transistor is inherently a transconductance amplifier



Current flow in base is governed by the diode equation  $I_B = \tilde{I}_s e^{\frac{V_{BE}}{V_t}}$

Collector current thus varies exponentially with  $V_{BE}$   $I_C = \beta \tilde{I}_s e^{\frac{V_{BE}}{V_t}}$





# Preliminary Comparison of MOSFET and BJT

(Saturation vs Forward Active)

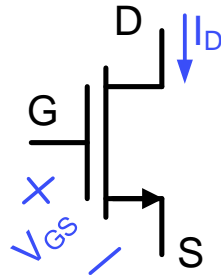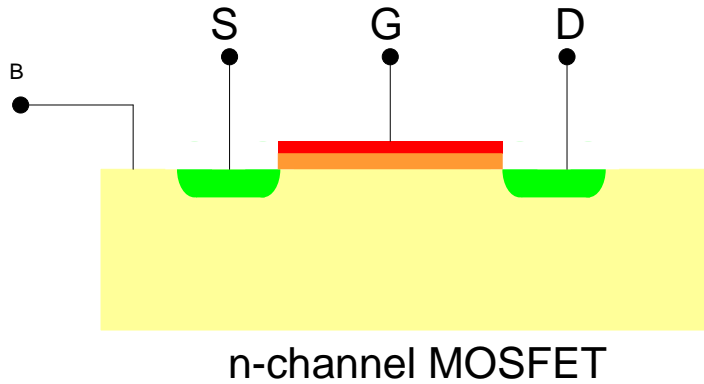

$$I_D = \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{TH})^2$$

$I_D$  independent of  $V_{DS}$

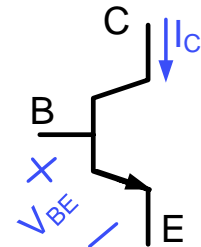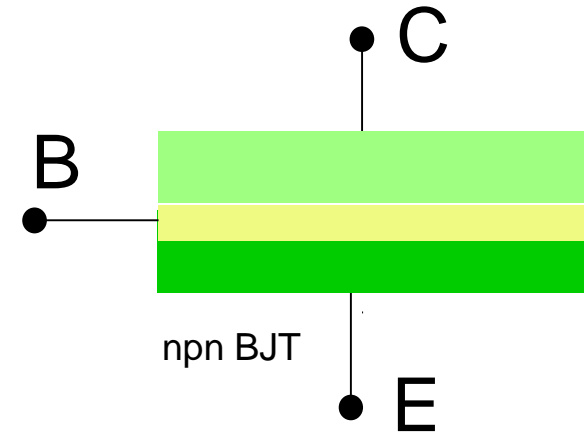

$$I_C = \beta \tilde{I}_s e^{\frac{V_{BE}}{V_t}}$$


$I_C$  independent of  $V_{CE}$



- The BJT I/O relationship is exponential in contrast to square-law for MOSFET
- Provides a very large “gain” for the BJT (assuming input is voltage and output is current)
- This property is very useful for many applications

# Bipolar Models

## Simple dc Model

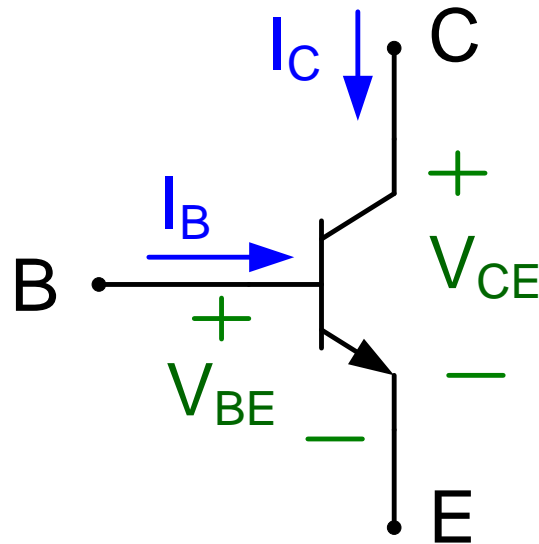


Following convention, pick  $I_C$  and  $I_B$  as dependent variables and  $V_{BE}$  and  $V_{CE}$  as independent variables

# Simple dc model

Consider npn transistor – Forward Active Operation

Summary:
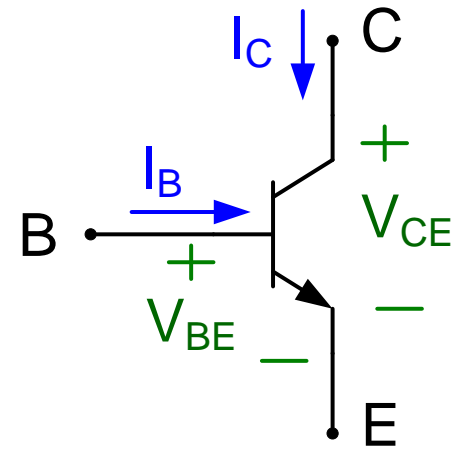
$$\left. \begin{aligned} I_B &= \tilde{I}_S e^{\frac{V_{BE}}{V_t}} \\ I_C &= \beta \tilde{I}_S e^{\frac{V_{BE}}{V_t}} \\ V_t &= \frac{kT}{q} \end{aligned} \right\}$$



This has the properties we are looking for but the variables we used in introducing these relationships are not standard

It can be shown that  $\tilde{I}_S$  is proportional to the emitter area  $A_E$

Define  $J_S$  by  $\tilde{I}_S = \beta^{-1} J_S A_E$  and substitute this into the above equations

# Simple dc model

## npn transistor – Forward Active Operation

$$\left. \begin{aligned} I_B &= \tilde{I}_S e^{\frac{V_{BE}}{V_t}} \\ I_C &= \beta \tilde{I}_S e^{\frac{V_{BE}}{V_t}} \\ V_t &= \frac{kT}{q} \end{aligned} \right\} \longrightarrow \left. \begin{aligned} I_B &= \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}} \\ I_C &= J_S A_E e^{\frac{V_{BE}}{V_t}} \\ V_t &= \frac{kT}{q} \end{aligned} \right\}$$

$k/q = 8.62 \times 10^{-5}$

$J_S$  is termed the saturation current density

Process Parameters :  $J_S, \beta$

Design Parameters:  $A_E$

Environmental parameters and physical constants:  $k, T, q$

At room temperature,  $V_t$  is around 26mV

$J_S$  very small – around .25fA/ $\mu^2$  at room temperature

# Simple dc model

## npn transistor – Forward Active Operation

$$\left. \begin{aligned} I_B &= \frac{J_S A_E}{\beta} e^{\frac{V_{BE}}{V_t}} \\ I_C &= J_S A_E e^{\frac{V_{BE}}{V_t}} \end{aligned} \right\}$$
$$V_t = \frac{kT}{q}$$

As with the diode, the parameter  $J_S$  is highly temperature dependent

$$J_S = J_{SX} \left[ T^m e^{\frac{-V_{G0}}{V_t}} \right]$$


Typical values for parameters:  $J_{SX}=20\text{mA}/\mu^2$ ,  $V_{G0}=1.17\text{V}$ ,  $m=2.3$

The parameter  $\beta$  is also somewhat temperature dependent but much weaker temperature dependence than  $J_{SX}$ .
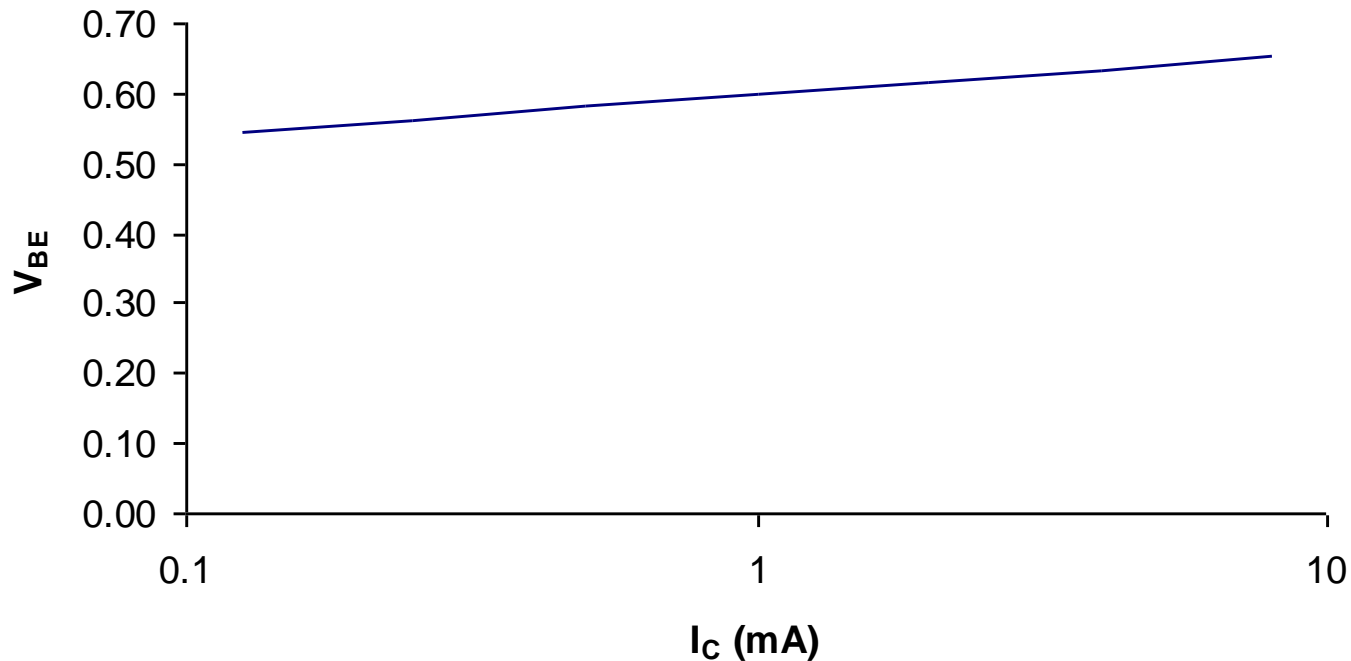
# Transfer Characteristics

npn transistor – Forward Active Operation

$$J_S = .25 \text{ fA}/\mu^2$$
$$A_E = 400 \mu^2$$




$V_{BE}$  close to 0.6V for a two decade change in  $I_C$  around 1mA

# Transfer Characteristics

## npn transistor – Forward Active Operation

$$J_S = .25 \text{ fA}/\mu^2$$

$$A_E = 400 \mu^2$$

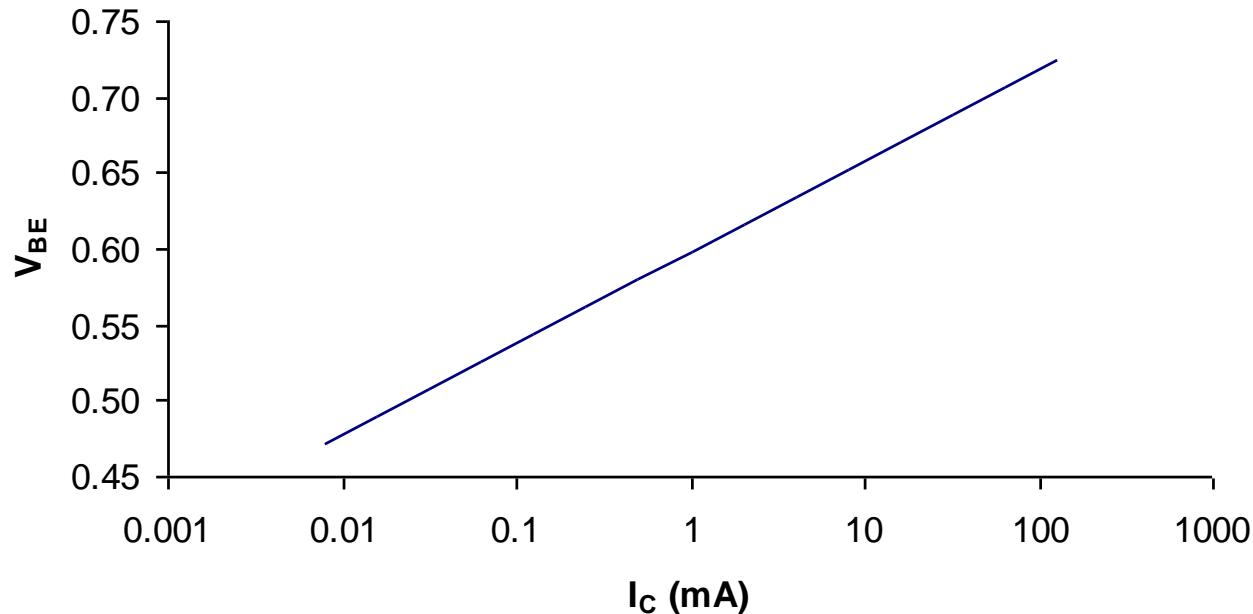


$V_{BE}$  close to 0.6V for a four decade change in  $I_C$  around 1mA

# Simple dc model

## npn transistor – Forward Active Operation

Output Characteristics

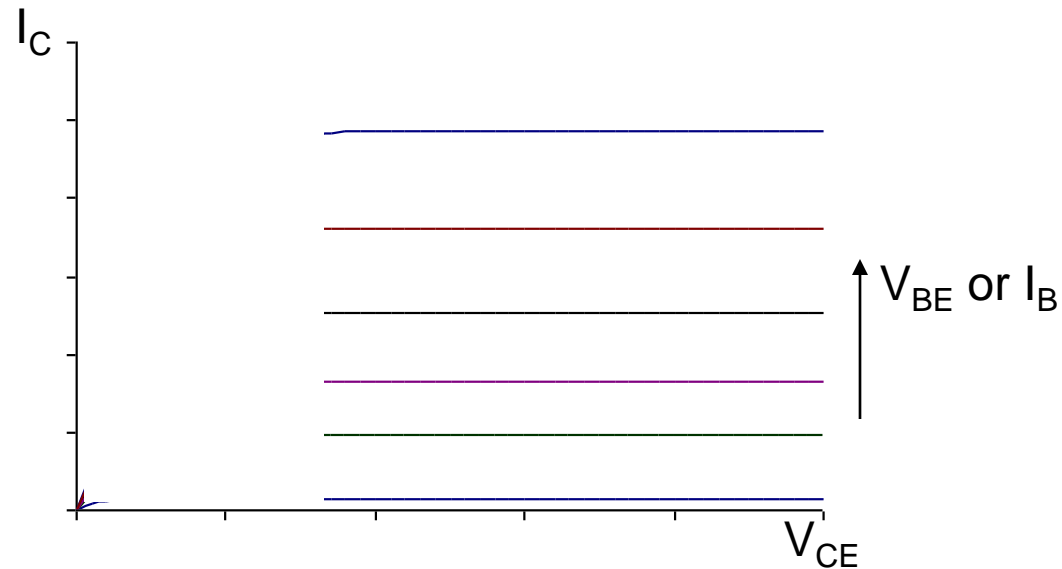


$$I_C = J_S A_E e^{\frac{V_{BE}}{V_t}}$$




# Simple dc model

Better Model of Output Characteristics

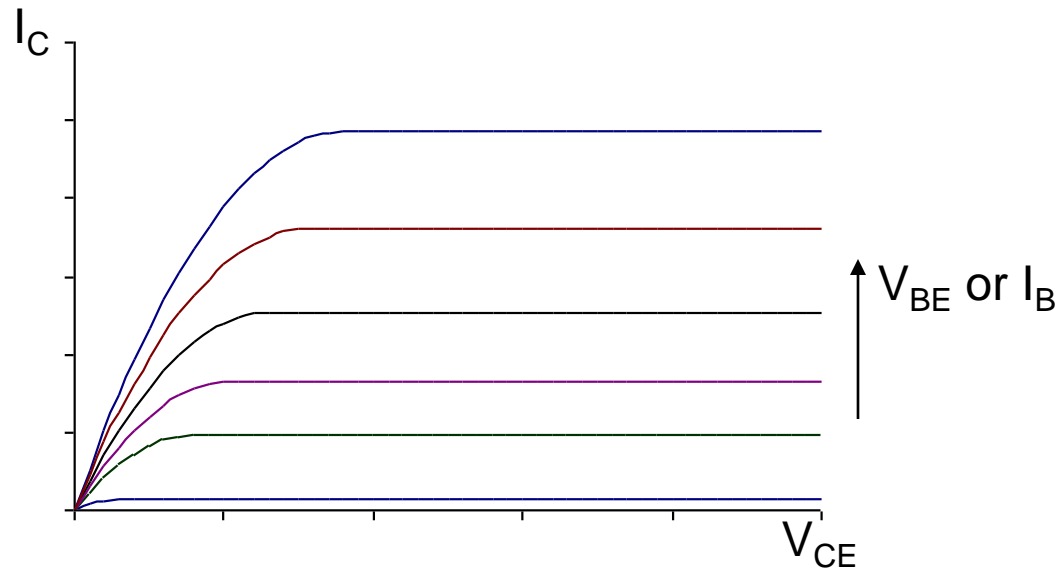

# Simple dc model

Typical Output Characteristics

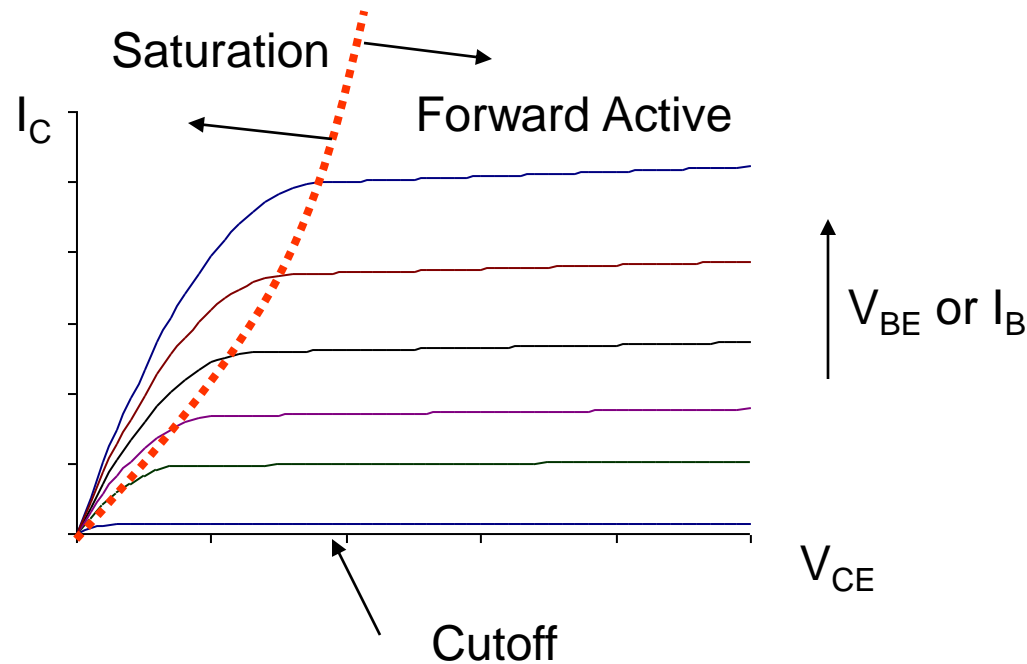

Forward Active region of BJT is analogous to Saturation region of MOSFET

Saturation region of BJT is analogous to Triode region of MOSFET

End of Lecture 19