CprE 288 Fall 2018 – Homework 4 Due: Not collected, or graded.

Notes:

- Homework must be typed and submitted as a PDF or Word Document (i.e. .doc or .docx) only.
- If collaborating with others, you must document who you collaborate with, and specify in what way you collaborated (see last page of homework assignment), review the homework policy section of the syllabus: http://class.ece.iastate.edu/cpre288/syllabus.asp for further details.
- Review University policy relating to the integrity of scholarship. See ("Academic Dishonesty"): http://catalog.iastate.edu/academic_conduct/#academicdishonestytext
- Late homework is accepted within two days from the due date. Late penalty is 10% per day. Except on Exam weeks.
- Note: Code that will not compile is a typo. Answering a question as "will not compile" will be marked incorrect. Contact the Professor if you think you have found a typo.

Note: Unless otherwise specified, all problems assume the TM4C123 is being used

Question 1 (10 pts): I/O Ports


a. Complete the function init_ports based on the comments and figure below to configure Port B and Port C, while preserving the other Ports' configuration. (5pts)

```
void init_ports(void) {
    // Start Port B and Port C clock
SYSCTL_RCGCGPIO_R = 0b000110;    // 0x03

    // Enable Digital functionality of Port B and Port C
GPIO_PORTB_DEN_R = 0xFF;
GPIO_PORTC_DEN_R = 0xFF;

    //Set direction of Port B's pins, based on the figure
GPIO_PORTB_DIR_R = 0b1011_1110;    // 0xBE

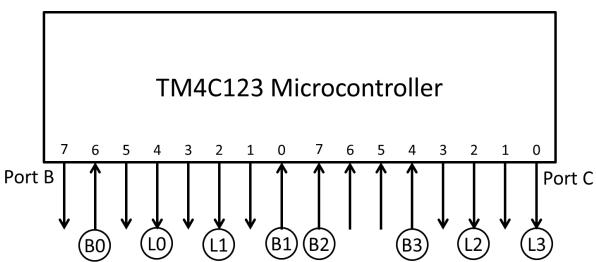    //Set direction of Port C's pins, based on the figure
GPIO_PORTC_DIR_R = 0b0000_1111;    // 0x0F
}
```



 Write C code that will read in button values, and send those values to their corresponding LEDs (i.e. B0 corresponds to L0), based on the figure in part a. Add any variables that you think you may need. (5pts)

There are 4 buttons (B0, B1, B2, B3), whose values should be stored in elements 0 to 3 of buttons (i.e. button B0 should be stored in buttons[0]). There are four LEDs (L0, L1, L2, L3) that can have a value of 1 or 0 written to them. All wires that do not have an LED or button connected should have their value persevered (i.e. your code should not change their value).

```
void main(void)
{
unsigned char buttons[4];
init ports(); // from part a
// Read in Buttons into button array
buttons[0] = (GPIO PORTB DATA R >> 6) & 0x01;
buttons[1] = (GPIO PORTB DATA R >> 0) & 0 \times 01;
buttons[2] = (GPIO PORTC DATA R >> 7) & 0x01;
buttons[3] = (GPIO PORTC DATA R >> 4) & 0x01;
// Give button values to LEDs
  // LED 0: Port B, bit 4
  if (button[0] == 1) // check if B0 is a 0 or 1
  { // B0 == 1, so write a 1 to L0 }
   GPIO PORTB DATA R = (GPIO PORTB DATA R | 0b00010000);
  }
 else
  \{ // B0 == 0, so write a 0 to L0
    GPIO PORTB DATA R = (GPIO PORTB DATA R & 0b11101111);
  // LED 1: Port B, bit 2
  if (button[1] == 1) // check if B1 is a 0 or 1
  \{ // B1 == 1, so write a 1 to L1
   GPIO PORTB DATA R = (GPIO PORTB DATA R | 0b0000100);
  }
  \{ // B1 == 0, so write a 0 to L1
   GPIO PORTB DATA R = (GPIO PORTB DATA R & 0b11111011);
```

```
// LED 2: Port C, bit 2
 if(button[2] == 1) // check if B2 is a 0 or 1
 \{ // B2 == 1, so write a 1 to L2
   GPIO PORTC DATA R = (GPIO PORTC DATA R | 0b0000100);
 }
 else
 { // B2 == 0, so write a 0 to L2
   GPIO PORTC DATA R = (GPIO PORTC DATA R & 0b11111011);
 // LED 3: Port C, bit 0
 if (button[3] == 1) // check if B3 is a 0 or 1
 { // B3 == 1, so write a 1 to L3 }
   GPIO_PORTC_DATA_R = (GPIO_PORTC_DATA_R | 0b00000001);
 else
 \{ // B3 == 0, so write a 0 to L3
   GPIO PORTC DATA R = (GPIO PORTC DATA R & 0b111111110);
}
```

}

Question 2: Memory-Mapped Registers (10 pts)

Based on the information and figure given, provide C code that will perform a 512-point FFT (Fast Fourier Transform) of the musical sound stored in Music[]. And transmit the transformed version of the musical sound out of Port B.

Some Background:


Fast Fourier Transform (FFT): The FFT is the most widely used algorithm for converting a signal represented in the time domain (i.e. amplitude vs. time) in to its frequency spectrum representation (i.e. amplitude vs. frequency).

Applications of FFT: The Fourier transform is commonly used to analysis what frequency components compose a signal. It can be useful for a wide range of tasks. A typical example would be identifying frequency components that one may want to remove from a system. Two specific examples of this usage would be a) identifying a frequency component causing a vehicle to vibrate to damping that frequency by means of mechanical modifications, and b) post processing of music to remove unwanted noise from a recording (a free app: http://www.free-audio-editor.com/index.php)

Problem Information:

- 1) Music[], an array that contains 512 8-bit sound samples
- 2) A 512-point FFT takes as input 512 time-domain 8-bit samples one-by-one, and outputs one-by-one 512 8-bit values in the frequency domain. The box labeled FFT Unit in the figure performs the FFT, where each sample is given to **Data In**, and the transformed values are output one-by-one to **Data Out**.
- 3) The box labeled Gray Conversion takes as input 8-bit color encoded pixels and outputs Gray encoded pixels.

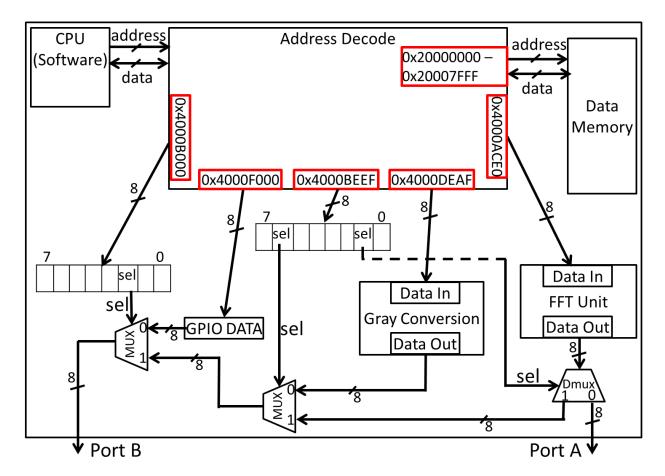Problem Figure: Internal architecture for which your C code will be run.



```
// Convert 512 music samples to the frequency domain, and output the
// converted samples out of Port B
// Note: Add any variables you wish
main()
// Variable Declarations
char Music[512]; // Holds music samples
int i; // loop variable
// Location of register that selects if GPIO data or
// an alternative type of functionality is sent to Port B
char *SEL GPIO ALT = 0x4000B000;
// Location of register that selects if Gray Conversion or FFT
// Unit is sent to Port B, and if FFT output is sent to Port A
// or Port B
char *SEL GRAY FFT PORTA PORTB = 0x4000BEEF;
// Location of register for sending data to the FFT Unit
char *FFT DATA IN = 0x4000ACE0;
  Initialize Music(Music); // Assume this function fills Music[]
                            // with 512 samples for you.
  // Initialize the Hardware
  // Send data from alternative function to Port B
  *SEL GPIO ALT = 0b00000100; // 0x04
  // Send FFT Unit data to Port B instead of Gray Conversion
  // and Send FFT Unit data to Port B instead of Port A
  *SEL GRAY FFT PORTA PORTB = 0b01000010; // 0x42
  // Send Music Samples to the FFT Unit
  for (i=0; i<512; i++)
    *FFT DATA IN = Music[i];
}
```

Question 3: GPIO Architecture (A CPRE 281, Digital Logic, view) (10 pts)


All the devices (also called on-chip peripherals) on our Microcontroller must have their signals routed through the GPIO module if they want to interact with the outside world, via the package pins (i.e. chip's external wires). The hardware structure of the GPIO module that allows a physical path from a device to a package pin (wire) can be illustrated using basic Digital Logic (i.e. CPRE 281) components.

For Port A, using only registers and multiplexers (MUXs), provide a detailed diagram that shows:

- The connection between multiplexers associated with Port A's Alternative Function Select (AFSEL), Port Control (PCTL) registers, and Port A GPIO_DATA.
- For each Device associate with <u>Port A</u>, show how they connect to the multiplexers of your diagram. <u>For simplicity</u>, assume all devices are used for output (i.e. no demultiplexers needed)
- For every input of the multiplexers in your diagram, provide the value that the select line must have to allow a given input to be selected.
- Show in detail how the AFSEL and PCTRL registers connect to the MUXs in your design.
- Note: Port A has 8 package pins (wires), thus your diagram needs to show i) all 8 of these wires, and ii) for each of the 8 wires (package pins) how all the devices associated has data routed from the device to the package pin (wire).
- Fill in specific values of your AFSEL, and PCTRL registers that will configure your diagram so that.
 - Port A wire 0: Connects to CAN1RX
 - Port A wire 1: Connects to U0TX
 - o Port A wire 2 4: Connected as GPIO DATA
 - Port A wire 5: Connected as SSIOTX
 - Port A wire 6: Connected as I2C1SCL
 - Port A wire 7: Connected as M1PWM3

See Next Page for Figure

- Fill in specific values of your AFSEL, and PCTRL registers that will configure your diagram so that.
 - o Port A wire 0: Connects to CAN1RX
 - Port A wire 1: Connects to U0TX
 - o Port A wire 2 4: Connected as GPIO DATA
 - Port A wire 5: Connected as SSIOTX
 - Port A wire 6: Connected as I2C1SCL
 - o Port A wire 7: Connected as M1PWM3

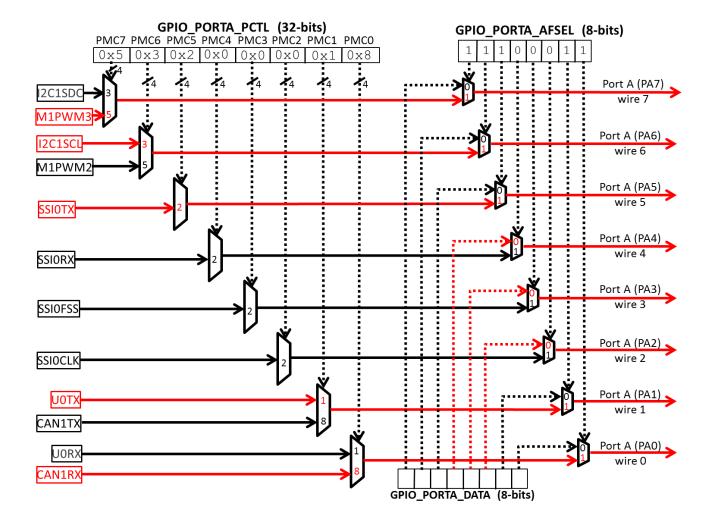

Question 4: Pointers (10 pts)

Complete the table below (i.e. fill in the memory map) to show the state of memory after the following C fragment has been executed. Assume the TM4C123 platform, and all the variables are in the stack (and thus the storage is allocated from high address to low address). Remember the TM4C123 is a little endian architecture (i.e. least significant byte of a variable is stored in the lowest address)

Be very careful with this question.

(-.5pts for each incorrect value)

```
typedef struct coord
 char x;
 char y;
} coord t;
coord t *coord ptr;
int *num ptr;
int **p ptr = &num ptr;
char a = 0x07;
coord t my coord[2];
int num array[2]=\{1,4\};
int main()
 coord ptr = my_coord;
 num ptr = num_array;
 my coord[1].x = 0x33;
 coord ptr++;
  coord ptr->y = 0x44;
 num ptr = num ptr + 2;
  *num ptr = 0x5040;
 p ptr++;
  *p_ptr = 0xFEC0;
```

Address	Variable Name	Value
0xFFFF_FFFF	coord_ptr	0xFF -00
0xFFFF_FFFE		0xFF -00
0xFFFF_FFFD		0xFF FE
0xFFFF_FFFC		0xEF F1-C0
0xFFFF_FFFB	num_ptr	0xFF
0xFFFF_FFFA		0xFF
0xFFFF_FFF9		0xFF
0xFFFF_FFF8		0xE7 EF
0xFFFF_FFF7	p_ptr	0xFF
0xFFFF_FFF6		0xFF
0xFFFF_FFF5		0xFF
0xFFFF_FFF4		0xF8 -FC
0xFFFF_FFF3	a	0x07
0xFFFF_FFF2	my_coord[1].y	0x44 -00
0xFFFF_FFF1	my_coord[1].x	0x33- 00
0xFFFF_FFF0	my_coord[0].y	0x50
0xFFFF_FFEF	my_coord[0].x	0x40
0xFFFF_FFEE	num_array[1]	0x00
0xFFFF_FFED		0x00
0xFFFF_FFEC		0x00
0xFFFF_FFEB		0x04
0xFFFF_FFEA	num_array[0]	0x00
0xFFFF_FFE9		0x00
0xFFFF_FFE8		0x00
0xFFFF_FFE7		0x01

Name:	Lab Section:	
<u>Collabora</u>	ation Documentation	
List the people (First and Last name) you collaborated with:		
For each collaborator, describe the manne	r in which you collaborated:	
1)		

2)